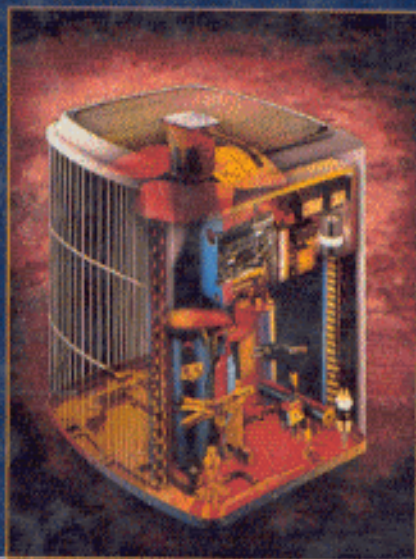


Electricity, Electronics, and Control Systems for HVAC

Second Edition


Thomas E. Kissell



Summaree University of Technology



31051000607578

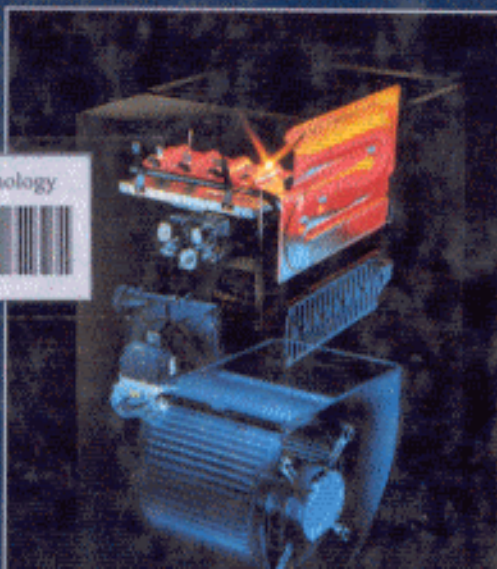

Contents

1 SAFETY 1

- 1.0 Overview of Safety and Shop Practices 1
- 1.1 Safety Glasses, Protective Clothing, and Protective Equipment 1
- 1.2 Safety Mats and Equipment to Prevent Fatigue 3
- 1.3 Safety Light Curtains and Two-Hand Start Buttons 4
- 1.4 Safety Shields 4
- 1.5 Checking Guards and Active Safety Devices 5
- 1.6 Cleanliness and Shop Housekeeping 5
- 1.7 Leaks 6
- 1.8 Material Safety Data Sheets 6
- 1.9 First Aid and CPR 6
- 1.10 Fire Safety 7
- 1.11 Electrical Safety 9
- 1.12 Working Safely with Hand Tools and Power Tools 10
- 1.13 Safety Briefings and Safety Meetings 11
- 1.14 Review 11
 - Questions 12
 - True or False 12
 - Multiple Choice 12
 - Problems 13

2 FUNDAMENTALS OF ELECTRICITY AND ELECTRICAL METERS 15

- Objectives 15
- 2.0 Overview of Electricity 15
- 2.1 Example of a Simple Electrical Circuit in a Heating System 16

2.2	Example of Voltage in a Circuit	19
2.3	Example of Current in a Circuit	19
2.4	Example of Resistance in a Circuit	20
2.5	Identifying the Basic Parts of a Circuit	21
2.6	Comparing Electricity with a Water System	22
2.7	Using Ohm's Law to Calculate Volts, Amps, and Ohms	23
2.8	Ohm's Law Formulas	23
2.9	Using Ohm's Law to Calculate Voltage	24
2.10	Using Ohm's Law to Calculate Current	24
2.11	Using Ohm's Law to Calculate Resistance	24
2.12	Using Ohm's Law Wheel to Remember Ohm's Law Formulas	24
2.13	Calculating Electrical Power	25
2.14	Presenting All the Formulas	26
2.15	Measuring Volts, Amps, and Ohms	27
2.16	Measuring Voltage	27
2.17	Measuring Electrical Current	30
2.18	Measuring Milliamps	32
2.19	Creating a Multiplier with a Clamp-On Ammeter	33
2.20	Measuring Electrical Resistance	33
2.21	Reading the Scales of the VOM Meter	35
2.22	Measuring DC Volts and Reading the VOM Scales	36
2.23	Measuring and Reading the Milliamp Scales on the VOM	38
2.24	Measuring and Reading Resistance Scales on the VOM	39
2.25	Making Measurements with Digital VOM Meters	40
2.26	Review	41
	Questions	42
	True or False	43
	Multiple Choice	43
	Problems	45

3 SERIES CIRCUITS 47

	Objectives	47
3.0	Introduction	47
3.1	Examples of Series Circuits	48
3.2	Adding Loads in Series	49
3.3	Using Resistors as Loads	52
3.4	Resistor Color Codes	52

- 3.5 Decoding a Resistor 54
- 3.6 Calculating the Resistor Tolerance 54
- 3.7 Using Ohm's Law to Calculate Ohms, Volts, and Amps for Resistors in Series 55
- 3.8 Solving for Current in a Series Circuit 56
- 3.9 Calculating the Voltage Drop Across Each Resistor 57
- 3.10 Calculating the Power Consumption of Each Resistor 58
- 3.11 Calculating the Power Consumption of an Electrical Heating Element 59
- 3.12 Review 59
 - Questions 60
 - True or False 60
 - Multiple Choice 61
 - Problems 61

4 PARALLEL AND SERIES-PARALLEL CIRCUITS 63

- Objectives 63
- 4.0 Introduction 63
- 4.1 Calculating Voltage, Current, and Resistance in a Parallel Circuit 64
- 4.2 Calculating Resistance in a Parallel Circuit 66
- 4.3 Calculating Power in a Parallel Circuit 69
- 4.4 Reviewing the Principles of Parallel Circuits 69
- 4.5 Using Prefixes with Units of Measure 70
- 4.6 Series-Parallel Circuits 72
- 4.7 Series-Parallel Circuits in Air-Conditioning and Refrigeration Systems 78
- 4.8 Troubleshooting Series-Parallel Circuits 79
- 4.9 Review 80
 - Questions 80
 - True or False 81
 - Multiple Choice 81
 - Problems 82

5 MAGNETIC THEORY 83

- Objectives 83
- 5.0 Magnetic Theory 83

- 5.1 A Typical Bar Magnet and Flux Lines 85
- 5.2 Electromagnets 86
- 5.3 Adding Coils of Wire to Increase the Strength of an Electromagnet 89
- 5.4 Using a Core to Increase the Strength of the Magnetic Field of a Coil 90
- 5.5 Reversing the Polarity of a Magnetic Field in an Electromagnet 90
- 5.6 An Overview of AC Voltage 92
- 5.7 Electromagnetic Induction 93
- 5.8 Review of Magnetic Principles 94
 - Questions 95
 - True or False 95
 - Multiple Choice 95
 - Problems 96

6 FUNDAMENTALS OF AC ELECTRICITY 97

- Objectives 97
- 6.0 What Is Alternating Current? 97
- 6.1 Where Does AC Voltage Originate? 98
- 6.2 Frequency of AC Voltage 98
- 6.3 Peak Voltage and rms Voltage 100
- 6.4 The Source of AC Voltage for Heating, Ventilating, and Air-Conditioning Systems 101
- 6.5 Measuring AC Voltage in a Disconnect 103
- 6.6 Voltage and Current in AC Circuits 104
- 6.7 Resistance and Capacitance in an AC Circuit 105
- 6.8 Calculating Capacitive Reactance 106
- 6.9 Calculating the Total Opposition for a Capacitive and Resistive Circuit 107
- 6.10 Resistance and Inductance in an AC Circuit 107
- 6.11 Calculating Inductive Resistance 108
- 6.12 Calculating the Total Opposition for an Inductive and Resistive Circuit 109
- 6.13 True Power and Apparent Power in an AC Circuit 109
- 6.14 Calculating Power Factor 110
- 6.15 Review 110
 - Questions 111

True or False	112
Multiple Choice	112
Problems	113

7 TRANSFORMERS, THREE-PHASE, AND SINGLE-PHASE VOLTAGE 115

Objectives	115
7.0 Overview of Transformers	115
7.1 Operation of a Transformer and Basic Magnetic Theory	117
7.2 Connecting a Transformer to a Disconnect for Testing	118
7.3 Transformer Rated for 230 Volts and 208 Volts Primary	120
7.4 Transformer Voltage, Current, and Turns Ratios	120
7.5 Step-up and Step-down Transformers	123
7.6 VA Ratings for Transformers	123
7.7 The 110 VAC Control Transformer	124
7.8 Wiring the Control Transformer for 480 VAC Primary Volts	125
7.9 Wiring the Control Transformer for 240 VAC Primary Volts	126
7.10 Troubleshooting a Transformer	127
7.11 Nature of Three-Phase Voltage	128
7.12 Why Three-Phase Voltage Is Generated	128
7.13 Three-Phase Transformers	129
7.14 The Wye-Connected Three-Phase Transformer	131
7.15 The Delta-Connected Three-Phase Transformer	131
7.16 Delta- and Wye-Connected Transformers with a Neutral Terminal	132
7.17 The High Leg Delta System	135
7.18 Three-Phase Voltage on Site	137
7.19 Installing Wiring in a Three-Phase Disconnect	139
7.20 Testing for a Bad Fuse in a Disconnect	139
7.21 Single-Phase Voltage from a Three-Phase Supply	141
7.22 Wiring a Duplex Receptacle as a Utility Outlet	141
7.23 Review	142
Questions	143
True or False	143
Multiple Choice	144
Problems	145

8 SYMBOLS AND DIAGRAMS FOR HVAC AND REFRIGERATION SYSTEMS 147

- Objectives 147
- 8.0 Overview of Electrical Systems 147
- 8.1 Simple Air-Conditioning Electrical Systems 148
- 8.2 Electrical Symbols 148
- 8.3 Electrical Diagram of an Air-Conditioning System 150
- 8.4 Loads for the Air-Conditioning System 154
- 8.5 Controls for the Air-Conditioning System 156
- 8.6 Electrical Diagrams of a Simple Heating System 157
- 8.7 Loads in the Heating System 159
- 8.8 Electrical Diagram of a Simple Refrigeration System 162
- 8.9 Loads for the Refrigeration System 164
- 8.10 Controls for the Refrigeration System 167
- 8.11 Review 168
- Questions 169
- True or False 169
- Multiple Choice 169
- Problems 170

9 RELAYS, CONTACTORS, AND SOLENOIDS 171

- Objectives 171
- 9.0 Overview of Relays and Contactors in the Control Circuit 171
- 9.1 The Control Transformer 172
- 9.2 The Theory and Operation of a Relay 172
- 9.3 Types of Armature Assemblies for Relays 174
- 9.4 Pull-in and Hold-in Current 178
- 9.5 Normally Open and Normally Closed Contacts 178
- 9.6 Ratings for Relay Contacts and Relay Coils 180
- 9.7 Identifying Relays by the Arrangement of Their Contacts 181
- 9.8 Examples of Relays Used in Air-Conditioning, Heating, and Refrigeration Systems 183
- 9.9 Current Relays and Potential Relays for Starting Single-Phase Compressors 183
- 9.10 The Difference Between a Relay and a Contactor 185
- 9.11 NEMA Ratings for Contactors 187

- 9.12 Using a Relay to Control the Furnace Fan 189
- 9.13 Using a Contactor to Control a Compressor Motor 189
- 9.14 The Function of the Control Circuit 192
- 9.15 Solenoids Used in HVAC and Refrigeration Systems 192
- 9.16 Basic Parts of a Solenoid Valve 193
- 9.17 Troubleshooting a Solenoid Valve 194
- 9.18 Reversing Valve for Heat Pumps 195
- 9.19 The Internal Operation of the Reversing Valve 196
- 9.20 Troubleshooting Relays, Contactors, and Solenoids 199
- 9.21 Review 200
 - Questions 200
 - True or False 201
 - Multiple Choice 201
 - Problems 202

10 SINGLE-PHASE OPEN MOTORS 203

- Objectives 203
- 10.0 Overview of AC Single-Phase Induction Motors 203
- 10.1 AC Split-Phase Motor Theory 204
- 10.2 The Rotor 206
- 10.3 Locked-Rotor Amperage and Full-Load Amperage 207
- 10.4 Rotor Slip and Torque in an AC Induction Motor 208
- 10.5 End Plates 209
- 10.6 The Stator 211
- 10.7 The Start Winding 212
- 10.8 The Operation of the Centrifugal Switch 214
- 10.9 The Run Winding 217
- 10.10 Multiple-Speed Motors 218
- 10.11 Motor Data Plates 219
- 10.12 Wiring Split-Phase Motors for a Change of Rotation and Change of Voltage 224
- 10.13 Overview of Capacitor-Start, Induction-Run Open-Type Motors 224
- 10.14 Theory of Operation of a Capacitor-Start, Induction-Run Motor 225
- 10.15 Applying Voltage to the Start Winding and Capacitor 228
- 10.16 Wiring Split-Phase and Capacitor-Start, Induction-Run Motors for 115 Volts 229

- 10.17 Wiring a Capacitor-Start, Induction-Run, Motor for 230 Volts 229
- 10.18 Wiring Split-Phase and Capacitor-Start, Induction-Run Motors for a Change of Rotation 230
- 10.19 Changing Speeds with a Capacitor-Start, Induction-Run Motor 231
- 10.20 Overview of Permanent Split-Capacitor Open-Type Motors 231
- 10.21 Basic Parts and Theory of Operation of a PSC Motor 233
- 10.22 Applying Voltage to the Start Winding and Capacitor of a Permanent Split-Capacitor Motor 234
- 10.23 Installation and Servicing Practices: Changing Rotation, Changing Voltages, and Changing Speeds of a Permanent Split-Capacitor Motor 236
- 10.24 Wiring a Permanent Split-Capacitor Motor for a Change of Rotation 236
- 10.25 Changing Speeds of a Permanent Split-Capacitor Motor 238
- 10.26 Overview of Shaded-Pole Open-Type Motors 239
- 10.27 Basic Parts and Electrical Diagram of the Shaded-Pole Open Motor 241
- 10.28 Theory of Operation of a Shaded-Pole Motor 243
- 10.29 Installation and Servicing Practices: Changing Rotation, Changing Voltages, and Changing Speeds of a Shaded-Pole Motor 244
- 10.30 Changing Speeds of a Shaded-Pole Motor 244
- 10.31 Wiring a Shaded-Pole Motor for a Change of Rotation 245
- 10.32 Troubleshooting Single-Phase Motors 246
- 10.33 Review 248
 - Questions 248
 - True or False 249
 - Multiple Choice 249
 - Problems 250

11 SINGLE-PHASE HERMETIC COMPRESSORS 251

- Objectives 251
- 11.0 The Split-Phase Hermetic Compressor 251
- 11.1 Basic Parts of a Split-Phase Hermetic Compressor 252

- 11.2** The Split-Phase Motor inside the Compressor 256
- 11.3** The Current Relay 257
- 11.4** Theory of Operation of the Split-Phase Compressor 258
- 11.5** Theory of Operation of the Current Relay 259
- 11.6** Starting the Split-Phase Compressor with the Current Relay 260
- 11.7** Using the Wiring Diagram to Install the Permanent Split-Capacitor Compressor 262
- 11.8** The Capacitor-Start, Induction-Run Hermetic Compressor 263
- 11.9** Basic Parts of a Capacitor-Start, Induction-Run Hermetic Compressor 263
- 11.10** The Operation of the Current Relay 265
- 11.11** Thermal Overload Device 266
- 11.12** The Hot Wire Relay 268
- 11.13** The Solid-State Starting Relay 270
- 11.14** Overview of the Permanent Split-Capacitor Compressor 271
- 11.15** Basic Parts of the Permanent Split-Capacitor Compressor 273
- 11.16** Theory of Operation of the PSC Compressor 274
- 11.17** Using the Wiring Diagram to Install a Permanent Split-Capacitor Compressor 275
- 11.18** Capacitor-Start, Capacitor-Run Compressor 277
- 11.19** Components of the CSCR Compressor 278
- 11.20** Theory of Operation of the CSCR Compressor 281
- 11.21** Hard Start Kits for Compressors 281
- 11.22** Using a Current Relay and Start Capacitor as a Hard Start Kit 283
- 11.23** Adding a Potential Relay and Start Capacitor as a Hard Start Kit 283
- 11.24** Using the Wiring Diagram to Install the Capacitor-Start, Capacitor-Run Compressor 284
- 11.25** Controlling the CSCR Compressor 284
- 11.26** Troubleshooting the Split-Phase Compressor 286
- 11.27** Troubleshooting Procedure 1 286
- 11.28** Troubleshooting Procedure 2 288
- 11.29** Testing the Current Relay 289
- 11.30** Troubleshooting Procedure 3 292
- 11.31** Troubleshooting the CSCR Compressor 292
- 11.32** Testing the CSCR Compressor Circuit for Current 293

- 11.33 Testing the Potential Relay Out of the Circuit 295
- 11.34 Testing the Potential Relay While It Is in the Circuit 295
- 11.35 Troubleshooting the PSC Compressor 296
- 11.36 Review 296
 - Questions 297
 - True or False 298
 - Multiple Choice 298
 - Problems 299

12 THREE-PHASE OPEN MOTORS AND THREE-PHASE HERMETIC COMPRESSORS 301

- Objectives 301
- 12.0 Three-Phase Motor Theory 301
- 12.1 The Three-Phase Hermetic Compressor 302
- 12.2 Basic Parts of a Three-Phase Compressor Motor 303
- 12.3 Theory of Operation of the Three-Phase Compressor 303
- 12.4 Wiring a Three-Phase Hermetic Compressor 306
- 12.5 Changing Connections in Open Three-Phase Motors to Change Torque, Speed, or Voltage Requirements 306
- 12.6 Wiring a Three-Phase Motor in a Wye Configuration 307
- 12.7 Wiring a Three-Phase Motor in a Delta Configuration 307
- 12.8 Rewiring a Nine-Lead Three-Phase Wye-Connected Motor for a Change of Voltage 309
- 12.9 Rewiring a Nine-Lead Three-Phase Delta-Connected Motor for a Change of Voltage 311
- 12.10 The 12-Lead Three-Phase Open-Type Motor 312
- 12.11 Wiring a Three-Phase Open-Type Motor for a Change of Rotation 313
- 12.12 Controlling a Three-Phase Compressor 313
- 12.13 Controlling the Speed of a Three-Phase Motor 315
- 12.14 Troubleshooting the Three-Phase Compressor 316
- 12.15 Testing the Three-Phase Motor for Continuity 317
- 12.16 Testing a Three-Phase Motor for Current 319
- 12.17 Review 320
 - Questions 320
 - True or False 321

Multiple Choice	321
Problems	322

13 MOTOR STARTERS AND OVERCURRENT CONTROLS 323

Objectives	323
13.0 Overview of Motor Starters	323
13.1 Why Motor Starters Are Used in HVAC and Refrigeration Systems	324
13.2 The Basic Parts of a Motor Starter	324
13.3 The Operation of the Overload	327
13.4 Exploded View of a Motor Starter	329
13.5 Sizing Motor Starters	329
13.6 Solid-State Motor Protectors	329
13.7 Overcurrent Controls	333
13.8 Thermal Overloads	333
13.9 Fuses	334
13.10 Fused Disconnect Panels	336
13.11 Circuit Breakers and Load Centers	337
13.12 Conductors	328
13.13 Troubleshooting Motor Starters and Overcurrent Controls	339
13.14 Review	341
Questions	342
True or False	342
Multiple Choice	342
Problems	343

14 THERMOSTATS AND HEATING CONTROLS 345

Objectives	345
14.0 Overview of Thermostats and Heating Controls	345
14.1 Sensing Temperature	346
14.2 Using the Bimetal Element to Sense Temperature	346
14.3 Amplifying the Movement of the Bimetal Element	347
14.4 The Heating Thermostat	348
14.5 The Heat Anticipator	350
14.6 The Thermostat Subbase	352

14.7	Cooling Thermostat	352
14.8	Heating and Cooling Thermostats	354
14.9	The Fan Switch	355
14.10	Programmable Thermostats	355
14.11	Line-Voltage Thermostats	356
14.12	Thermocouples	356
14.13	Resistive Temperature Detectors	358
14.14	Thermistors	358
14.15	Gas Furnace Controls	359
14.16	The Pilot Assembly and Thermocouple	359
14.17	The Gas Valve	360
14.18	Direct-Spark Ignition-Type Gas Valves	361
14.19	Igniter and Flame Rod	362
14.20	Oil Burner Controls	364
14.21	The Ignition Components	365
14.22	The Primary Control and CAD Cell	365
14.23	The Operational and Safety Circuit	365
14.24	Fan and Limit Controls for Furnaces	367
14.25	The Fan Switch	370
14.26	Fan and Limit Control	371
14.27	Air Flow Switches	373
14.28	Humidistat	374
14.29	Troubleshooting Thermostats and Heating Controls	375
14.30	Review	375
	Questions	376
	True or False	376
	Multiple Choice	377
	Problems	377

15 PRESSURE CONTROLS, TIMER CONTROLS, AND OTHER CONTROLS 379

	Objectives	379
15.0	Overview of Pressure, Timer, and Overcurrent Controls	379
15.1	Pressure Controls	380
15.2	Low-Pressure Switches	382
15.3	Fixed Pressure Switches	383
15.4	Dual Pressure Switches	383

- 15.5 Electrical Diagrams for Pressure Switches 384
- 15.6 Oil Pressure Switches 385
- 15.7 Cut-in and Cut-out Pressures 387
- 15.8 Timer Controls 388
- 15.9 Defrost Timer 388
- 15.10 Electronic Defrost Controls 390
- 15.11 Compressor Time-Delay Timers 391
- 15.12 Troubleshooting Pressure Controls and Timers 392
- 15.13 Review 392
 - Questions 393
 - True or False 393
 - Multiple Choice 393
 - Problems 394

16 ELECTRONIC DEVICES FOR HVAC SYSTEMS 395

- Objectives 395
- 16.0 Overview of Electronics Used in HVAC and Refrigeration Systems 395
- 16.1 Conductors, Insulators, and Semiconductors 396
- 16.2 Combining Atoms 397
- 16.3 Combining Arsenic and Silicon to Make N-Type Material 398
- 16.4 Combining Aluminum and Silicon to Make P-Type Material 399
- 16.5 The PN Junction 400
- 16.6 Forward Biasing the PN Junction 400
- 16.7 Reverse Biasing the PN Junction 401
- 16.8 Using a Diode for Rectification 401
- 16.9 Half-Wave and Full-Wave Rectifiers 403
- 16.10 Three-Phase Rectifiers 403
- 16.11 Testing Diodes 404
- 16.12 Identifying Diode Terminals with an Ohmmeter 405
- 16.13 Light-Emitting Diodes 406
- 16.14 PNP and NPN Transistors 407
- 16.15 Operation of a Transistor 408
- 16.16 Typical Transistors 409
- 16.17 Troubleshooting Transistors 409

- 16.18 Unijunction Transistors 411
- 16.19 Operation of the UJT 412
- 16.20 Testing the UJT 413
- 16.21 The Silicon Controlled Rectifier 413
- 16.22 Operation of the Silicon Controlled Rectifier 414
- 16.23 Controlling the SCR 415
- 16.24 Testing the SCR 416
- 16.25 Typical SCRs 417
- 16.26 The Diac 418
- 16.27 Operation of the Diac 418
- 16.28 The Triac 418
- 16.29 Using the Triac as a Switch 419
- 16.30 Using the Triac for Variable Voltage Control 421
- 16.31 Testing the Triac 422
- 16.32 Operational Amplifiers 422
- 16.33 The Op Amp as an Amplifier 424
- 16.34 Controlling a Relay with an Op Amp 425
- 16.35 A Heating and Cooling Control System 426
- 16.36 Using Proportional Valves Instead of Relays 427
- 16.37 Controlling the Speed of a Three-Phase Motor with a Variable-Frequency Drive 429
- 16.38 Operation of the Variable-Frequency Drive Circuit 430
- 16.39 Solid-State Relays 432
- 16.40 Troubleshooting Solid-State Devices 434
- 16.41 Review 435
 - Questions 435
 - True or False 436
 - Multiple Choice 436
 - Problems 437

17 ELECTRICAL CONTROL OF HEATING SYSTEMS 439

- Objectives 439
- 17.0 Overview of Heating Systems 439
- 17.1 Electric Heating Systems 440
- 17.2 The Main Part of the System 440
- 17.3 Normal Operation 441

- 17.4 Troubleshooting the Electric Heating Furnace 443
- 17.5 Troubleshooting the Heating Coils 444
- 17.6 Testing the Fan Motor 445
- 17.7 The Gas Heating System 446
- 17.8 The Main Part of the Gas Furnace 447
- 17.9 Normal Operation of the Gas Furnace 447
- 17.10 Troubleshooting the Gas Furnace 448
- 17.11 Troubleshooting the Control Circuit of a Gas Furnace 448
- 17.12 Troubleshooting the Combustion Blower and Furnace Fan 452
- 17.13 The Oil Heating System 454
- 17.14 Normal Operation of the Oil Furnace 455
- 17.15 Troubleshooting the Combustion Control of an Oil
Furnace 456
- 17.16 Troubleshooting the Oil Furnace Fan 458
- 17.17 Review 459
 - Questions 460
 - True or False 460
 - Multiple Choice 460
 - Problems 461

18 ELECTRICAL CONTROL OF AIR-CONDITIONING SYSTEMS 463

- Objectives 463
- 18.0 Overview of Air-Conditioning Systems 463
- 18.1 Room Air Conditioners (Window Air Conditioners) 464
- 18.2 The Main Components of the System 465
- 18.3 Normal Operation 466
- 18.4 Troubleshooting the System 466
- 18.5 Testing the Fan Motor 467
- 18.6 Testing the Compressor 468
- 18.7 Split-System Residential Air-Conditioning Systems 469
- 18.8 The Main Components of the System 470
- 18.9 Normal Operation 472
- 18.10 Using the Wiring Diagram to Troubleshoot 472
- 18.11 Using the Ladder Diagram to Troubleshoot 473
- 18.12 Troubleshooting the System 473
- 18.13 Testing the Condenser Fan Motor 473

- 18.14 Testing the Compressor 474
- 18.15 Commercial Packaged Air-Conditioning Systems 476
- 18.16 Review 477
 - Questions 480
 - True or False 480
 - Multiple Choice 480
 - Problems 481

19 ELECTRICAL CONTROL OF HEAT PUMP SYSTEMS 483

- Objectives 483
- 19.0 Overview of Heat Pump Systems 483
- 19.1 The Main Parts of a Split-System Heat Pump 485
- 19.2 Normal Operation in Cooling 486
- 19.3 Normal Operation in the Heating Cycle 487
- 19.4 Normal Operation During the Defrost Cycle 489
- 19.5 The Heat Pump Thermostat 490
- 19.6 Troubleshooting the Heat Pump 493
- 19.7 Troubleshooting the Heat Pump in the Cooling Mode 493
- 19.8 Troubleshooting the Heat Pump in the Heating Mode 498
- 19.9 Troubleshooting the Heat Pump in the Defrost Mode 499
- 19.10 Package-Type Heat Pumps 499
- 19.11 Review 500
 - Questions 503
 - True or False 503
 - Multiple Choice 503
 - Problems 504

20 ELECTRICAL CONTROL OF REFRIGERATION SYSTEMS 505

- Objectives 505
- 20.0 Overview of Refrigeration Systems 505
- 20.1 Reach-In Coolers and Refrigeration Cases 506
- 20.2 Normal Operation for the Reach-In Cooler 508
- 20.3 Troubleshooting the Refrigeration System 508
- 20.4 Freezer Cases 511
- 20.5 Troubleshooting the Freezer Case 514

- 20.6 Troubleshooting the Defrost Cycle 521
- 20.7 Ice Makers 521
- 20.8 Normal Operation of an Ice Maker 522
- 20.9 Review 527
 - Questions 527
 - True or False 528
 - Multiple Choice 528
 - Problems 529

APPENDIX A

- Developing a Ladder Diagram from a Wiring Diagram 531

INDEX 543