

POWER ELECTRONIC SYSTEMS
Theory and Design



Jai P. Agrawal

CONTENTS

Preface vii

PART I: INTRODUCTION 1

1 BIRDS-EYE VIEW OF POWER ELECTRONICS SYSTEMS 3

- 1.1 Introduction 3
- 1.2 A Simple Voltage Converter 5
- 1.3 Systems View of Power Electronic Converters 6
- 1.4 Elements of the Converter Systems: Modeling and Assumptions 11
- 1.5 Converter Topology 24
- 1.6 Converter Operation and Desired Characteristics 28
- 1.7 Converter Performance Measures 28
- 1.8 Protection 33
- 1.9 Packaging 34
- Problems 35

PART II: POWER ELECTRONIC COMPONENTS 41

2 UNDERSTANDING COMPONENTS 43

- 2.1 Introduction 43
- 2.2 Basics of Magnetism 43
- 2.3 Magnetic Materials 45

- 2.4 Magnetic Circuits 46
- 2.5 Inductor 47
- 2.6 Nonlinearities in Magnetic Components 50
- 2.7 Losses in Magnetic Components 53
- 2.8 Windings 56
- 2.9 Types of Inductors 56
- 2.10 Transformers 61
- 2.11 Motors 65
- 2.12 Electrostatics and Dielectric Materials 69
- 2.13 Capacitors 69
- 2.14 Semiconductor Switches 71
- 2.15 Snubbing: Protection of Switching Devices 73
- 2.16 Zero-Current Switching 77
- 2.17 Zero-Voltage Switching 77
- 2.18 PSpice Simulation 77
- References 79
- Problems 79

3 POWER DIODES 85

- 3.1 Introduction 85
- 3.2 p-n Junctions 86
- 3.3 Power Diodes 92

3.4	Parallel and Series Connection of Diodes	98		
3.5	Schottky Barrier Diode	100		
3.6	New Trends in Diodes	102		
3.7	Device Specification	102		
3.8	PSPICE Simulation	104		
3.9	Summary	104		
	References	106		
	Problems	107		
4	TRANSISTORS: LEVEL TRIGGERED SWITCHING DEVICES	109		
4.1	Introduction	109		
4.2	Basic MOS Structure	110		
4.3	Power MOSFETs	114		
4.4	Insulated Gate Bipolar Transistor (IGBT)	126		
4.5	Comparison of MOSFET and IGBT	134		
4.6	Device Specifications	134		
4.7	Summary	138		
	References	138		
	Problems	138		
5	THYRISTORS: PULSE TRIGGERED DEVICES	141		
5.1	Introduction	141		
5.2	Basic Structure	142		
5.3	Static Characteristics	143		
5.4	Cathode-Shorted Structure of Thyristors	146		
5.5	Effect of Temperature	147		
5.6	Switching Characteristics	147		
5.7	Series Operation of Thyristors	151		
5.8	Parallel Operation of Thyristors	153		
5.9	Thyristor Triggering Circuits	153		
5.10	Forced Commutation of Thyristors	156		
5.11	Thyristor Snubber Circuits	159		
5.12	Gate Turn-Off Thyristors (GTO)	159		
5.13	Triacs	163		
5.14	The MOS Controlled Thyristor (MCT)	164		
5.15	Device Specification	167		
5.16	Summary	169		
	References	170		
	Problems	170		
			PART III: POWER ELECTRONIC CONVERTER CIRCUITS	173
6	DC TO CONTROLLED DC	175		
6.1	Introduction	175		
6.2	Uncontrolled and Controlled Conversion	175		
6.3	Buck Converters	178		
6.4	Boost Converters	185		
6.5	Buck-Boost Converters	192		
6.6	ĆUK Converters	196		
6.7	Two-Quadrant Converters	198		
6.8	Full-Bridge Converters	198		
6.9	Isolated DC-DC Converters	204		
6.10	Multi-Output DC-DC Converter	211		
6.11	Design Exercise: Switching Power Supply	212		
6.12	PSPICE Simulation	213		
6.13	Summary	214		
	References	214		
	Problems	215		
7	DC TO CONTROLLED AC	219		
7.1	Introduction	219		
7.2	Controlled Inversion	219		
7.3	Full-Bridge Inverter (VSI) with Square-Wave Switching	224		
7.4	Pulse-Width Modulation (PWM) Control of VSI	230		
7.5	Current-Mode Control of PWM VSI	234		
7.6	Current Source PWM Full-Bridge Inverter	234		
7.7	Pruning of Harmonic Profile	236		
7.8	Sine-PWM Inverter	242		
7.9	Control Signal Generation	247		
7.10	3-Phase Full-Bridge Inverter	248		
7.11	Rectifier Mode of Operation of Inverters	252		
7.12	Design Exercise: 2 KW, 1-Phase Inverter for Emergency Applications	252		
7.13	PSPICE Simulation	253		
7.14	Summary	255		
	References	255		
	Problems	255		

8 AC TO DC: NO CONTROL 259

- 8.1 Introduction 259
- 8.2 AC-DC Converter Topologies 260
- 8.3 1-Phase Half-Wave Rectifier 263
- 8.4 1-Phase Full-Bridge AC-DC Converter 273
- 8.5 Line Quality Issues 286
- 8.6 3-Phase 6-Pulse Full-Wave Rectifier 292
- 8.7 Transient Considerations 299
- 8.8 Design Example 300
- 8.9 Effect of Device Characteristics 300
- 8.10 PSPICE Simulation 300
- 8.11 Summary 302
 - References 303
 - Problems 303

9 AC TO DC: WITH CONTROL 307

- 9.1 Introduction 307
- 9.2 Controlled AC-DC Conversion 308
- 9.3 1-Phase AC-DC Converters 312
- 9.4 3-Phase 6-Pulse Full-Bridge Converters 336
- 9.5 Design Exercise: PWM Drive for DC Motor 346
- 9.6 PSPICE Simulation 348
- 9.7 Summary 349
 - References 351
 - Problems 351

10 AC TO CONTROLLED AC 355

- 10.1 Introduction 355
- 10.2 Modeling and Analysis 356
- 10.3 AC Controller 357
- 10.4 Cycloconverter 373
- 10.5 DC-Link AC-AC Converter 382
- 10.6 PSPICE Simulation 385
- 10.7 Summary 385
 - References 386
 - Problems 387

11 RESONANT CONVERTERS 391

- 11.1 Introduction 391
- 11.2 Resonant Converter Systems 391
- 11.3 Resonant Tank Circuits 392

- 11.4 Resonant Tank in Excitation 396
- 11.5 Series Resonant DC-DC Converter with Voltage Sink (Current Coupled Resonant Converter) 399
- 11.6 Parallel Resonant DC-DC Converter (PRC) (Voltage Coupled Resonant Converter) 414
- 11.7 High-Order Resonant DC-DC Converter 420
- 11.8 Class E Converters 423
- 11.9 Resonant Switch Converters 423
- 11.10 Resonant-Link Inverters 428
- 11.11 Bidirectional Resonant Converters 428
- 11.12 Control of Resonant Converters 429
- 11.13 PSPICE Simulation 432
- 11.14 Summary 433
 - References 434
 - Problems 434

PART IV: POWER ELECTRONIC APPLICATION SYSTEMS 437**12 ELECTRIC UTILITY INTERFACE: POWER FACTOR CORRECTION AND STATIC VAR CONTROL 439**

- 12.1 Introduction 439
- 12.2 Electric Utility Distribution System 439
- 12.3 Passive Filtering 440
- 12.4 Active Current Shaping: Power Factor Correction 441
- 12.5 Interface for Bidirectional Power Flow 447
- 12.6 3-Phase Utility Interface 449
- 12.7 Static VAR Compensators 449
- 12.8 Summary 452
 - References 453
 - Problems 453

13 CONVERTER CONTROL 455

- 13.1 Introduction 455
- 13.2 Averaged Model 455
- 13.3 Linearized Model 459
- 13.4 State-Space Averaged Model 461
- 13.5 Feedback Control 465
- 13.6 Summary 468

References 469
Problems 469

14 APPLICATIONS I: POWER SUPPLIES AND ... 471

- 14.1 Introduction 471
- 14.2 DC Power Supply System 471
- 14.3 Control of Switch-Mode DC Power Supplies 473
- 14.4 Protection of DC Power Supplies 474
- 14.5 Electrical Isolation 476
- 14.6 Equivalent Series Resistance (ESR) 476
- 14.7 Synchronous Rectifiers 477
- 14.8 Cross Regulation in Multiple Outputs 477
- 14.9 Battery Charging Systems 477
- 14.10 Uninterruptible (AC) Power Supply (UPS) 478
- 14.11 Electronic Lamp Ballast 480
- 14.12 Induction Heating 480
- 14.13 Switch-Mode Welding 481
- 14.14 Electromagnetic Interference Considerations 481
- 14.15 Summary 483
 - References 483
 - Problems 484

15 APPLICATIONS II: MOTOR DRIVES 487

- 15.1 Introduction 487
- 15.2 DC Motor Drives 487
- 15.3 Induction Motor Drives 492
- 15.4 Synchronous Motor Drives 501
- 15.5 Summary 505
 - References 505
 - Problems 505

16 TEMPERATURE CONTROL, PROTECTION, AND PACKAGING 507

- 16.1 Introduction 507
- 16.2 Temperature Control in Semiconductor Devices 507

- 16.3 Heat Transfer Basics 508
- 16.4 Heat Transfer Systems 508
- 16.5 Static Thermal Model of Heat Transfer Systems 512
- 16.6 Transient Thermal Impedance 513
- 16.7 Heat Sink 516
- 16.8 Surge Voltage Protection 516
- 16.9 Fault Current Protection 517
- 16.10 Circuit Layout Techniques 519
- 16.11 Summary 520
 - References 521
 - Problems 521

APPENDIX A 523

- A-1 Review of Basic Principles 523
- A-2 Basic Mathematical Methods 524
- A-3 Energy and Power 530
- A-4 Pspice Simulation 533

APPENDIX B 537

- B-1 Electromagnetics 537

APPENDIX C 539

- C-1 Semiconductor Basics 539
- C-2 Charge Transport in Homogenous-Structure Semiconductor Devices 541
- C-3 Heterogeneous-Structure Devices 542

APPENDIX D 547

APPENDIX E 549

APPENDIX F 551

INDEX 553