

Electronic Devices and Circuits

Discrete and Integrated

Denton J. Dailey

Sarawak University of Technology



31051000622734

CONTENTS

1 THE PN JUNCTION DIODE	1
1.1 Semiconductor Basics	2
<i>The Bohr Model of the Atom</i>	2
<i>Intrinsic Silicon</i>	2
<i>Extrinsic Silicon</i>	3
1.2 Diode Fundamentals: The p-n Junction	5
<i>The Depletion Region</i>	5
<i>Bias Conditions</i>	5
<i>Diode Transconductance</i>	7
1.3 Diode Modeling and Approximations	9
<i>Graphical Analysis of Diode Circuits</i>	13
1.4 Dynamic Resistance	14
<i>Dynamic Resistance and Nonlinearity</i>	16
1.5 Diode Specifications	18
<i>Reverse-Bias Parameters</i>	18
<i>Forward Bias Parameters</i>	19
<i>A Simple Diode Test</i>	20
<i>Multiple-Diode Connections</i>	20
1.6 Zener Diodes	21
<i>Zener Characteristics</i>	21
<i>Reverse Breakdown Mechanisms</i>	24
1.7 Other Diodes	25
<i>Light-Emitting Diodes</i>	25
<i>Photodiodes</i>	28
<i>Schottky Diodes</i>	29
<i>Varactor Diodes</i>	30
1.8 Computer-Aided Analysis Applications	33
<i>Operating-Point Analysis</i>	33
<i>Plotting a Transconductance Curve</i>	34
<i>Small-Signal Considerations</i>	35
2 DIODE APPLICATIONS	43
2.1 The Half-Wave Rectifier	44
<i>Half-Wave Rectifier Load Voltage and Current</i>	44
<i>Half-Wave Rectifier Diode Current and Voltage</i>	46
<i>Half-Wave Rectifier Average Current and Voltage</i>	46
<i>Conduction Angle</i>	47
2.2 Full-Wave Rectifiers	48
<i>Bridge Rectifier</i>	48
<i>Center-Tap Full-Wave Rectifier</i>	51
2.3 An Alternative Perspective on Rectification	52
2.4 Filtering and Power Supplies	54
<i>Capacitor Filter</i>	54
The Ripple Factor	54
Filter Effects on Diode Current and Voltage	56
Filter Capacitor Charging Current	58
2.5 Alternative Filter Techniques	59
<i>RC Filters</i>	59
<i>LC Filters</i>	60
2.6 Bipolar Power Supplies	61
2.7 Voltage Multipliers	62
<i>Half-Wave Voltage Doubler</i>	62
<i>Full-Wave Voltage Doubler</i>	63
<i>Higher-Order Voltage Multipliers</i>	63
2.8 The Clamper	64
2.9 Clipper Circuits	66
<i>Simple Diode Clippers</i>	66
<i>Transfer Characteristic Curves</i>	66
<i>Additional Clipper Variations</i>	66
<i>Biased Clipper Circuits</i>	68
2.10 Zener Regulated Power Supplies	69
<i>Regulation Fundamentals</i>	69
<i>Basic Zener Regulator Operation</i>	71
<i>Zener Impedance Effects</i>	73
2.11 Computer-Aided Analysis Applications	76
<i>Filtered Full-Wave Rectifier</i>	76
<i>The Clamper</i>	77
<i>Asymmetrical Diode Clipper</i>	78
3 THE BIPOLAR TRANSISTOR	83
3.1 BJT Structure	84
<i>Schematic Symbols</i>	85
<i>Doping Concentrations</i>	85
3.2 Basic Transistor Action	85
<i>Base-Emitter Loop</i>	86
<i>Collector-Base Loop</i>	86
<i>Injection Current</i>	86
3.3 Transistor Current Relationships	86
<i>More on β_{dc}</i>	88
<i>Thermal Runaway</i>	88
<i>More on α_{dc}</i>	89
<i>Transconductance</i>	90
3.4 Regions of Operation	91
<i>Active Region</i>	91
<i>Cutoff Region</i>	92
<i>Saturation Region</i>	93
3.5 Basic Transistor Biasing Configurations	93
<i>Common-Base Biasing</i>	93
<i>Common-Emitter Biasing</i>	93

3.6	<i>Common-Collector Biasing</i>	95	<i>Current Gain</i>	160	
	Transistor Leakage Currents	96	<i>Relationships between Power, Voltage and Current Gain</i>	160	
3.7	<i>Collector Leakage Current</i>	96	5.2	Basic BJT Amplifier Configurations	161
	Additional Transistor Parameters	97	5.3	Common-Emitter Configuration	161
	<i>Early Voltage</i>	98		<i>Common-Emitter Voltage Gain</i>	162
	<i>Base-Spreading Effects</i>	100		<i>Common-Emitter Input Resistance</i>	163
	<i>Breakdown Voltage</i>	101		<i>Common-Emitter Phase Relationships</i>	163
3.8	Signal-Related Parameters	103		<i>Common-Emitter Current and Power Gain</i>	164
	<i>AC Beta and Alpha</i>	103		<i>Common-Emitter Amplifier Voltages</i>	164
	<i>Dynamic Emitter Resistance</i>	105	5.4	Effects of Emitter-Feedback on the CE Amplifier	165
3.9	Hybrid Parameters	107		<i>Voltage Gain</i>	166
3.10	Transistor Packages and Classification Schemes	107		<i>Input Resistance</i>	167
	<i>Package Types</i>	107		<i>Power Gain and Current Gain</i>	167
	<i>General-Purpose Transistors</i>	108		<i>Output Resistance</i>	167
3.11	Computer-Aided Analysis Applications	109		<i>Common-Emitter Amplifier Variations</i>	167
	<i>Generating Collector Characteristic Curves: Nested Sweep</i>	110		<i>Emitter Bypassing</i>	169
	<i>About Transistor Models</i>	112		<i>Collector Feedback</i>	172
4	BIPOLAR TRANSISTOR BIASING	117	5.5	<i>Emitter-Follower</i>	174
4.1	Base Biasing	118		<i>Voltage Gain</i>	174
	<i>DC Load-Line</i>	119		<i>Input Resistance</i>	175
	<i>Base-Biasing Disadvantages</i>	121		<i>Output Resistance</i>	175
	<i>Base-Biasing Variations</i>	122		<i>Uses of the Emitter Follower</i>	177
	<i>Saturated Switching Applications</i>	124		<i>Emitter-Follower Stability</i>	177
	<i>Forced Beta</i>	126	5.6	The Common-Base Amplifier	177
4.2	Emitter Feedback	127		<i>Voltage Gain</i>	177
	<i>Effects of Emitter Feedback on Q-Point Stability</i>	129		<i>Base Bypassing</i>	178
4.3	Collector Feedback	131		<i>Input and Output Resistance</i>	178
	<i>Collector Feedback versus Emitter Feedback</i>	133		<i>Current Gain</i>	179
4.4	Voltage-Divider Biasing	134	5.7	Darlington Pair	180
	<i>Voltage-Divider Biasing Stability</i>	136		<i>Darlington Pair DC Analysis</i>	180
	<i>Some Voltage Divider Bias Design Guidelines</i>	137		<i>Darlington Pair AC Analysis</i>	182
4.5	Emitter Bias	139	5.8	Overview of Small-Signal Amplifiers	184
	<i>Memorization and Formulas</i>	141		<i>Amplifier Configuration Summary</i>	184
4.6	Additional Biasing Variations	141		<i>Distortion</i>	184
	<i>PNP Load-Line</i>	146	5.9	The AC Load-Line and Output Voltage Compliance	186
4.7	Integrated-Circuit Biasing Techniques	147		<i>Common-Emitter AC Load Line Construction</i>	186
	<i>Monolithic ICs</i>	147		<i>Output Voltage Compliance</i>	188
	<i>Current Mirror</i>	147	5.10	Computer-Aided Analysis Applications	191
	<i>Widlar Current Source</i>	150		<i>Voltage-Gain and Distortion</i>	191
4.8	Computer-Aided Analysis Applications	152		<i>Emitter Feedback</i>	192
	<i>Operating-Point Analysis</i>	152		<i>Frequency Response and Input Resistance</i>	194
5	SMALL-SIGNAL BJT AMPLIFIERS	158	6	FIELD EFFECT TRANSISTORS	201
5.1	Fundamental Amplifier Characteristics	159	6.1	The Junction FET	202
	<i>Power Gain</i>	159		<i>Physical Structure of the JFET</i>	202
	<i>Voltage Gain</i>	159		<i>JFET Operation</i>	202
				<i>Additional JFET DC Characteristics</i>	206
			6.2	JFET Biasing Techniques	208
				<i>Fixed-Bias</i>	208
				<i>Self-Bias</i>	208

<i>Voltage-Divider Bias</i>	212	<i>Single-Ended-Input, Differential-Output Configuration</i>	288		
<i>Current-Source Biasing</i>	215	<i>Differential-Input, Differential-Output Configuration</i>	290		
<i>A Few JFET Applications</i>	216	<i>Differential-Input, Single-Ended-Output Configuration</i>	293		
6.2	The Depletion-Mode MOSFET	219	8.4	Differential Amplifier Variations	296
	<i>DMOS Structure and Operation</i>	220		<i>Swamped Differential Amplifier</i>	296
	<i>Dual-Gate MOSFETs</i>	225		<i>Darlington- and FET-Based Differential Pairs</i>	298
	<i>MOSFET Handling Precautions</i>	225		<i>Active Loading</i>	299
6.3	The Enhancement-Mode MOSFET	225	8.5	Differential-Pair Error Sources	300
	<i>EMOS FET Structure and Operation</i>	225		<i>Common-Mode Response</i>	300
	<i>EMOS FET Biasing</i>	227		<i>Bias Current, Offset Current, and Offset Voltage</i>	302
	<i>Vertical MOSFET</i>	228	8.6	Practical Differential Amplifier Implementation	304
6.4	Computer-Aided Analysis Applications	229	8.7	Computer-Aided Analysis Applications	305
	<i>Basic Listings</i>	229		<i>Manual Analysis Results</i>	305
	<i>PSpice Applications</i>	229		<i>PSpice Q-Point Analysis Results</i>	306
7	FET SMALL-SIGNAL AMPLIFIERS	238		<i>Small-Signal Analysis</i>	308
7.1	Basic Amplifier Configurations	239	9	INTRODUCTION TO MULTIPLE-STAGE AMPLIFIERS	319
7.2	Small-Signal Transconductance	239	9.1	Basic Gain Relationships	320
7.3	JFET Small-Signal Amplifiers	240	9.2	Capacitively Coupled Amplifiers	323
	<i>Common-Source Amplifier</i>	240	9.3	Direct Coupling	330
	<i>Source-Follower</i>	245	9.4	Multiple-Stage Differential Amplifiers	333
	<i>Common-Gate Amplifier</i>	246	9.5	Level-Translating Stages	337
7.4	DMOSFET Small-Signal Amplifiers	248	9.6	Decibels	340
7.5	EMOS FET Small-Signal Amplifiers	249		<i>Decibel Power Gain</i>	340
7.6	Active Loads	252		<i>Decibel Voltage Gain</i>	341
	<i>Enhancement Loads</i>	252	9.7	Computer-Aided Analysis Applications	343
	<i>Depletion Load</i>	252		<i>Direct-Coupled CE Amplifier: Q-Point Analysis</i>	344
7.7	Alternative FET Parameter Notation	253		<i>Diff-Amp with Level Translator: DC Analysis</i>	346
7.8	The BJT versus the FET	254		<i>Diff-Amp with Level Translator: Signal Analysis</i>	346
	<i>Voltage-Gain Characteristics</i>	254	10	POWER AMPLIFIER FUNDAMENTALS	357
	<i>Saturation Characteristics</i>	254	10.1	Amplifier Classifications	358
	<i>Temperature Characteristics</i>	254		<i>Conduction Angle</i>	358
	<i>Distortion Characteristics</i>	256	10.2	Class A Amplifiers	359
7.9	Computer-Aided Analysis Applications	256		<i>Amplifier Power Dissipation</i>	360
	<i>JFET Amplifier</i>	256		<i>Load Power Dissipation</i>	361
	<i>Defining Your Own Device Model</i>	258		<i>Efficiency of the Capacitively-Coupled Class A Amplifier</i>	363
	<i>EMOS FET Amplifiers</i>	260		<i>Transformer Coupled Class A Amplifier</i>	364
8	DIFFERENTIAL AMPLIFIERS	269	10.3	Class B and Class AB Amplifiers: Biasing Considerations	368
8.1	DC Analysis of the Differential Amplifier	270		<i>Complementary-Symmetry Amplifiers</i>	369
	<i>Differential-Pair Current Relationships</i>	270		<i>Class AB Amplifiers</i>	374
	<i>Differential Amplifier Voltage Relationships</i>	273			
8.2	Active Current Sources	275			
	<i>Voltage-Divider-Biased Current Source</i>	275			
	<i>Current-Mirror</i>	278			
	<i>Widlar Current-Source</i>	280			
	<i>Supply-Voltage-Independent Current Source</i>	281			
	<i>Additional Active Current-Source Variations</i>	285			
8.3	AC Analysis of the Differential Amplifier	285			
	<i>Single-Ended-Input, Single-Ended-Output Configuration</i>	285			

10.4	Class B and AB Amplifiers: Large-Signal Considerations	378	11.5	Computer-Aided Analysis Applications	445
	<i>Average Emitter Resistance</i>	378		<i>Open-Loop Analysis</i>	445
	<i>AC Analysis of the Basic Push-Pull Amplifier</i>	378		<i>Closed-Loop Analysis: $R_F = 10 \text{ k}\Omega$, $R_A = 10 \text{ k}\Omega$</i>	449
	<i>Emitter Swamping</i>	384			
	<i>Class B and AB Efficiency</i>	386			
10.5	Alternative Biasing and Driver Circuits	386	12	OPERATIONAL AMPLIFIERS	455
	<i>Direct-Coupled Drivers</i>	387	12.1	What Is an Operational Amplifier?	456
	<i>The V_{BE} Multiplier</i>	389	12.2	Ideal Voltage Amplifiers	456
	<i>Overcurrent Protection</i>	392	12.3	Sampling of Commercial Op Amps	456
	<i>Increasing Output Current Drive Capability</i>	394	12.4	Op Amp Feedback Analysis	457
10.6	FET Power Amplifiers	394		<i>The Noninverting Configuration</i>	458
10.7	Amplifier Thermal Considerations	395		<i>The Inverting Configuration</i>	462
	<i>Transistor Current Voltage and Power Limitations</i>	395	12.5	Small-Signal Bandwidth	464
	<i>Thermal Resistance and Heat Sinks</i>	396		<i>Noise Gain</i>	465
	<i>Derating Curves</i>	399		<i>Gain-Bandwidth Product</i>	465
10.8	Class C Amplifiers	400		<i>Bandwidth of Cascaded Amplifiers</i>	467
	<i>Efficiency of the Class C Amplifier</i>	400	12.6	Slew Rate and Power Bandwidth	469
	<i>Class C Distortion</i>	402		<i>Slew Rate and Sine Waves</i>	470
	<i>Base-Emitter Junction Protection</i>	402		<i>Power Bandwidth</i>	471
	<i>Tuned Class C Amplifiers</i>	403		<i>Distortion and Frequency Limitations</i>	473
	<i>Where Are Class C Amplifiers Used?</i>	404	12.7	Bias Currents and Other Nonideal Characteristics	474
	<i>Frequency Multipliers</i>	404		<i>Bias Current</i>	474
10.9	Computer-Aided Analysis			<i>Input Offset Current</i>	476
	Applications	406		<i>Input Offset Voltage</i>	476
	<i>Simulation of the Basic Class AB Amplifier</i>	406		<i>Offset Compensation</i>	477
	<i>Tuned Class C Amplifier</i>	411	12.8	CMRR and PSRR	480
				<i>Common-Mode Rejection Ratio</i>	480
				<i>Power Supply Rejection Ratio</i>	482
11	NEGATIVE FEEDBACK AND FREQUENCY RESPONSE	421	12.9	Computer-Aided Analysis Applications	482
11.1	Frequency Response Terms and Definitions	422		<i>Designating Supply Voltages</i>	483
	<i>Bode Plots</i>	422		<i>Closed-Loop Frequency Response</i>	483
	<i>Corner Frequency</i>	422		<i>Phase Response</i>	484
	<i>Bandwidth, Passband, and Stopband</i>	423		<i>Real and Imaginary Response</i>	484
	<i>Center Frequency</i>	423		<i>Input Resistance as a Function of Frequency</i>	485
	<i>Rolloff Rate</i>	424		<i>Slew Rate</i>	486
	<i>Response Order</i>	424			
11.2	Amplifier Low-Frequency Response	428	13	LINEAR OP AMP APPLICATIONS	490
	<i>A Word About Coupling Capacitors and Approximations</i>	431	13.1	The Summing Amplifier	491
11.3	Negative Feedback	431		<i>Summing Amplifier Output Voltage Equation</i>	491
	<i>Real-World Amplifiers, Negative Feedback, and Voltage Gain</i>	435		<i>Bandwidth of the Summing Amplifier</i>	492
	<i>Negative Feedback and Distortion</i>	437		<i>Averagers</i>	495
11.4	Amplifier High-Frequency Response	438		<i>Summing Amplifier Variations</i>	496
	<i>Transistor Junction Capacitances</i>	438	13.2	Differential and Instrumentation Amplifiers	498
	<i>The Miller Effect</i>	438		<i>Basic Differential Amplifier Analysis</i>	498
	<i>Beta and Alpha Cutoff and Transition Frequencies</i>	441		<i>Common-Mode Response</i>	499
	<i>The Cascode Amplifier</i>	442		<i>Instrumentation Amplifiers</i>	500

13.3	Voltage-to-Current and Current-to-Voltage Conversion	506	15	NONLINEAR OP AMP APPLICATIONS	586
	<i>The VCIS</i>	506	15.1	Comparators	586
	<i>The ICVS</i>	508		<i>Op Amp Comparators</i>	587
	<i>The ICIS</i>	509		<i>Zero Crossing Detector</i>	591
13.4	Differentiators and Integrators	509		<i>Bounding Circuits</i>	591
	<i>Differentiation</i>	509		<i>Input Bounding</i>	592
	<i>The Differentiator</i>	514		<i>Schmitt Triggers</i>	593
	<i>Integration</i>	518		<i>Window Comparators</i>	595
	<i>The Integrator</i>	521	15.2	<i>The LM311 Comparator</i>	597
13.5	Miscellaneous Linear Op Amp Applications	529		Logarithmic and Antilogarithmic Amplifiers	599
	<i>Adders and Subtractors</i>	529		<i>The Logarithmic Amplifier</i>	599
	<i>Bridged Amplifiers</i>	532		<i>Antilog Amplifiers</i>	604
	<i>Increasing Op Amp Drive Capability</i>	533		<i>Log and Antilog Amplifier Applications</i>	605
13.6	Computer-Aided Analysis Applications	534	15.3	Precision Rectifiers	609
	<i>Summing Amplifier Simulation</i>	535		<i>Precision Half-Wave Rectifier</i>	610
	<i>Integrator and Differentiator Simulation</i>	536		<i>Precision Full-Wave Rectifier</i>	612
	<i>Waveform Visualization</i>	538	15.4	Computer-Aided Analysis Applications	614
14	ACTIVE FILTERS	545		<i>Zero-Crossing Detector Simulation</i>	614
14.1	Some Filter Fundamentals	546		<i>Logarithmic Amplifier Simulation</i>	616
	<i>Filter Order</i>	546		<i>Analog Behavioral Modeling: The Analog Multiplier</i>	616
	<i>Damping and Response Shapes</i>	546		<i>Precision Rectifier Simulation</i>	619
	<i>Filter Response Equations</i>	548	16	DATA CONVERSION DEVICES	625
14.2	Equal-Component Sallen-Key LP and HP Active Filters	552	16.1	Some Basic Concepts	626
	<i>LP-HP and HP-LP Transformations</i>	554		<i>Continuous and Discrete Signals and Systems</i>	626
14.3	Higher Order HP and LP Filters	555	16.2	Digital-to-Analog Conversion	626
14.4	Bandpass Filters	557		<i>DAC Transfer Characteristics</i>	627
	<i>Wide-Bandwidth Filters</i>	557		<i>Resolution and Accuracy</i>	627
	<i>The Infinite-Gain Multiple-Feedback BP Filter</i>	559		<i>Determination of Output Voltage</i>	629
14.5	Notch Filters	560		<i>Other DAC Specifications</i>	629
	<i>IGMF-Based Notch Filter</i>	561		<i>Coding Schemes</i>	630
14.6	State-Variable Filters	562		<i>DAC Circuits</i>	632
14.7	The Biquadratic Filter	564		<i>The Weighted-Resistor DAC</i>	632
14.8	All-Pass Filters	566		<i>The R-2R Ladder DAC</i>	633
	<i>Derivation of the All-Pass Filter Response</i>	566		<i>Monolithic Digital-to-Analog Converters</i>	635
	<i>Lagging-Phase All-Pass Filter</i>	568		<i>A Few DAC Applications</i>	637
	<i>Phase Equalization</i>	568	16.3	Analog-to-Digital Conversion	642
	<i>Audio Phase Shifters</i>	569		<i>Sample-and-Hold and Track-and-Hold Circuits</i>	642
14.9	Switched-Capacitor Filters	570		<i>Sample Rate and Aliasing</i>	643
	<i>Switched-Capacitor Concepts</i>	571		<i>Dynamic Range</i>	645
	<i>Switched-Capacitor Integrators</i>	572		<i>ADC Circuits</i>	645
	<i>The MF4-50</i>	572		<i>Computer-Aided Analysis Applications</i>	654
	<i>The MF5 Universal Filter</i>	574		<i>The Ramp Generator</i>	654
14.10	Computer-Aided Analysis Applications	577		<i>Counting ADC</i>	655
	<i>Second-Order VCVS Response</i>	577		<i>Sampled Data Systems</i>	657
	<i>Bandpass Filter Response</i>	579			
	<i>All-Pass Filter Response</i>	580			

17 TUNED AMPLIFIERS AND OSCILLATORS	664	18.7	The Phase-Locked Loop Capture and Lock Range FM Demodulation FSK Demodulator PLL Motor Speed Control Servomechanism PLL Frequency Multipliers The LM565 PLL The LM567 Tone Decoder	734 734 734 735 735 735 735 737 739
17.1 Transformer-Coupled Tuned Amplifiers	665	18.8	Computer-Aided Analysis Applications 555 Timer Simulation Linear Regulator Simulation Balanced Modulator Simulation	741 741 742 743
<i>Transformer Review</i>	665			
<i>Resonant Circuit Review</i>	668			
<i>Transformer-Coupled Tuned Amplifier Analysis</i>	672			
17.2 Alternative Coupling Techniques	676			
17.3 Transistor Performance Considerations	679			
<i>Frequency Effects</i>	679			
<i>RF Transistors</i>	680			
<i>Noise Specifications</i>	680			
17.4 Oscillators	682			
<i>The Barkhausen Criteria</i>	682			
<i>The Hartley Oscillator</i>	682			
<i>The Colpitts Oscillator</i>	688			
<i>The Clapp Oscillator</i>	691			
<i>The Phase-Shift Oscillator</i>	692			
<i>The Wein Bridge Oscillator</i>	692			
<i>Crystal-Controlled Oscillators</i>	694			
17.5 Computer-Aided Analysis Applications	695			
<i>Transformer-Coupled Tuned Amplifier Simulation</i>	695			
<i>Hartley Oscillator Simulation</i>	698			
18 A SAMPLING OF LINEAR INTEGRATED CIRCUITS AND THEIR APPLICATIONS	703	19	THYRISTORS AND OTHER MISCELLANEOUS DEVICES	749
18.1 The 555 Timer	704	19.1	Silicon-Controlled Rectifiers and Four-Layer Diodes	750
<i>Astable Operation</i>	704		SCR Behavior	750
<i>Practical Design Considerations</i>	707		Commutation	751
<i>Monostable Operation</i>	708		Reverse Blocking	751
<i>Additional 555 Timer Applications</i>	710		Four-Layer Diodes	752
18.2 Voltage Regulators	713		SCR Phase Control	753
<i>Linear Voltage Regulators</i>	713	19.2	Triacs and Diacs	756
<i>Adjustable Regulators</i>	715		Triac Phase Control	757
<i>Overcurrent Protection</i>	716		Filters and Snubbers	758
18.3 Monolithic Voltage Regulators	719	19.3	Unijunction Transistors	759
<i>The LM317 and LM337 Regulators</i>	719	19.4	Tunnel Diodes	761
18.4 Switching Regulators	720	19.5	Computer Aided Analysis Applications	762
<i>The Step-Down Configuration</i>	720			
<i>The Step-Up Configuration</i>	721			
<i>The Inverting Configuration</i>	721			
<i>Filter Capacitors and ESR</i>	722			
18.5 Operational Transconductance Amplifiers	722			
<i>OTA Biasing and Operation</i>	722			
<i>An OTA AM Modulator</i>	725			
<i>The OTA Integrator</i>	729			
18.6 Balanced Modulators	730			
<i>Double-Sideband, Suppressed-Carrier Modulator</i>	730			
<i>Single-Sideband Modulator</i>	731			
<i>Balanced-Modulator Phase Detector</i>	732			
<i>The LM1496 Balanced Modulator</i>	733			
		APPENDIX 1: SOLUTIONS TO ODD-NUMBERED PROBLEMS		765
		APPENDIX 2: DATA SHEETS	773	
		1N4001-1N4007 Rectifier Diodes	774	
		MMBT3904 Transistor	776	
		2N3055, MJ2955 Complementary Power Transistors	782	
		MPF102 N-Channel JFET	786	
		VN2406L TMOS FET	794	
		TL071C JFET Input OpAmp	796	
		LM741C Op Amp	804	
		APPENDIX 3: DERIVATIONS	809	
		APPENDIX 4: NOTES ON OrCAD PSpice, RELEASE 9		813
		INDEX	817	