

# COMPUTER-BASED ELECTRONIC MEASUREMENT

A. BRUCE BUCKMAN



# TABLE OF CONTENTS

## Laboratory Measurements with *LabVIEW* and *Virtual Bench*

Chapter M1. Signal Generation	M1-1
Chapter M2. Waveform Capture	M2-1
Chapter M3. Measuring Waveform Spectral Content	M3-1
Chapter M4. Measuring Complex Transfer Function	M4-1
Chapter M5. Measuring Current and Impedance	M5-1
Chapter M6. Measuring Current-voltage ( <i>i-v</i> ) characteristics for Non-linear Devices	M6-1
Chapter M7. Small-signal Parameter Measurements	M7-1

## Laboratory Projects

<b>Amplifiers I: Op-amp realizations</b>	
Project 1. Non-inverting Amplifier	P1-1
Project 2. Inverting Amplifier	P2-1
<b>Impedance Transformations</b>	
Project 3. Artificial Inductor	P3-1
Project 4. Transformers and Impedance	P4-1
<b>Filters and Phase-shifters</b>	
Project 5. First- and Second-order Low Pass Filters	P5-1
Project 6. All-pass filters and Other Phase-Shifters	P6-1
<b>Non-linear Circuits I: Diode Circuits</b>	
Project 7. Rectifiers	P7-1
Project 8. Limiting Circuits	P8-1
<b>Oscillators</b>	
Project 9. RC Relaxation Oscillator	P9-1
Project 10. Phase-shift Oscillator	P10-1
<b>Amplifiers II: Single-stage discrete devices</b>	
Project 11. Amplifier Circuits with Bipolar Junction Transistors (BJT's)	P11-1
Project 12. The Source-follower FET Amplifier	P12-1
<b>Nonlinear Circuits II: Modulation</b>	
Project 13. Voltage-Controlled Gain and Amplitude Modulation	P13-1
<b>Appendix. PSPICE Essentials</b>	
	A-1