

OrCAD PSpice[®] and Circuit Analysis

FOURTH EDITION

John Keown

SOFTWARE ENCLOSED
Book not returnable if software
has been removed.
PRENTICE-HALL, INC.

Contents

Introduction

1

A Bit of Background 2

Getting Started 3

A Few Helpful Points 4

Here's How It's Done 5

 Creating the Input File 6

 Examining the Output File 7

 Changing the Input File 8

 The Current Directions 9

Further Reading 10

PSpice Overview

11

DC Circuit Analysis 11

AC Circuit Analysis 14

Probe 17

Transistor Circuit Analysis 20

1

DC Circuit Analysis

An Introductory Example	25
Using SPICE to Investigate the Circuit	26
Examining the Output File	27
Another Simple Circuit for Analysis	28
Basic Circuit Laws	30
Getting More from the Output File	32
Current Directions	32
Circuit with Two Voltage Sources	33
Thévenin's Theorem and Applications	35
SPICE and Thévenin's Theorem	36
Practical Application of Thévenin's Theorem	37
Circuit for Thévenin Replacement	38
Practical Current Source vs. Practical Voltage Source	41
SPICE Analysis of Circuit with Current Source	42
Norton's Theorem	43
Using Norton's Theorem	44
Short-Circuit Current in Missing Element	44
Circuit with Current and Voltage Sources	45
Maximum Power Transfer	46
Dependent Sources in Electric Circuits	47
Voltage-Dependent Voltage Source	47
Current-Dependent Voltage Source	50
Current-Dependent Current Source	51
Another Current-Dependent Current Source	52
Voltage-Dependent Current Source	54
Another Current-Dependent Voltage Source	55
Polynomial-Dependent Sources	56
Dependent Source as a Function of Two Other Voltages	57
Mesh Analysis and PSpice	59
DC Sweep	61
Using the .PROBE Statement	61
Nodal Analysis and PSpice	63
A Nonplanar Circuit	65
Summary of PSpice Statements Used in This Chapter	66
Dot Commands Used in This Chapter	68
Problems	69

2**AC Circuit Analysis (for Sinusoidal Steady-State Conditions)****75**

Series AC Circuit with R and L	75
Series AC Circuit with R and C	77
Parallel Branches in AC Circuit	77
Parallel Branches with Capacitive Branch	78
Maximum Power Transfer in AC Circuit	79
Resonance in Series RLC Circuit	79
Frequency Sweep for Series-Parallel AC Circuit	82
Effect of Changes in Coil Resistance	83
A Parallel-Resonant Circuit	84
Using the Probe Cursor	85
Finding the Input Impedance of an AC Circuit	86
Input Impedance of a Two-Branch Network	87
A Phase-Shift Network	89
Locus of Admittances	90
Admittance Locus for Series RLC	93
Multiple Sources in AC Networks	94
Transformers	96
Frequency Response of Tuned Circuit	97
Three-Phase AC Circuits	98
Power-Factor Improvement	101
Three-Phase Power-Factor Improvement	102
A Three-Phase Rectifier	105
Voltage Regulation in a Three-Phase System	108
A Two-Phase System	109
Summary of New PSpice Statements Used in This Chapter	111
Dot Commands Used in This Chapter	112
.Probe	113
Problems	113

3**Transistor Circuits****119**

The Bipolar-Junction Transistor	119
A Model Suitable for Bias Calculations	119
Saturation Considerations	121

Biasing Example for a Ge Transistor	121
Small-Signal h -Parameter Model of the BJT	123
Common-Emitter Transistor Analysis Using h -Parameter Model	123
Common-Collector Transistor Analysis Using h -Parameter Model	126
Common-Base Transistor Analysis Using h -Parameter Model	127
Other Configurations	128
Using a Circuit Involving Miller's Theorem	128
The Dual of Miller's Theorem	130
CC Circuit with Collector Resistor	133
High-Input-Resistance Amplifier	135
Two-Stage Amplifiers	136
Simplified h -Parameter Model	137
The CE Amplifier Using the Simplified h -Parameter Model	138
Field-Effect Transistor Amplifiers	139
Common-Drain FET with External Drain Resistor	141
Frequency Response of FET Amplifiers	142
High-Frequency Model of the BJT	143
Emitter Follower at High Frequencies	144
DC Sensitivity	147
DC Sensitivity of Biasing Circuit	149
The PSpice Parts Library	150
Sensitivity of Library BJT Circuit	151
Summary of New PSpice Statements Used in This Chapter	152
Dot Commands Used in This Chapter	154
Problems	155

4

Multistage Amplifiers, Frequency Response, and Feedback

161

Low-Pass Filter	161
Low-Frequency Response of High-Pass RC Network	163
Common-Emitter Amplifier with Bypass Capacitor	163
Two-Stage Amplifier at High Frequencies	166
Two-Stage CE Amplifier with Voltage-Series Feedback	167
Two-Pole Amplifier Model with Feedback	172
CE Amplifier with Voltage-Shunt Feedback	175
Current-Shunt Feedback Two-Stage CE Amplifier	176
Three-Stage CE Amplifier Frequency Response	178

Effects of Circuit Modifications	179
Three-Stage Amplifier with Voltage-Shunt Feedback	180
Summary of New PSpice Statements Used in This Chapter	181
Various Forms of Transient Specification	181
The Exponential Source	182
The Pulse Source	183
The <i>PWL</i> Source	184
The Frequency-Modulated Source	185
The Sine-Wave Source	186
Problems	188

5 193

The Operational Amplifier

The Ideal Op Amp	193
Noninverting Ideal Op Amp	195
Op Amp Giving Voltage Difference Output	196
Frequency Response of the Op Amp	197
Using a Subcircuit for the Op Amp	202
Op Amp Differentiator Circuit	203
Op Amp Integrator Circuit	204
Response to Unit Step Function	206
Double Op Amp Circuit	207
Active Filters	210
Second-Order Butterworth Low-Pass Filter	211
Fourth-Order Butterworth Low-Pass Filter	213
Active Resonant Band-Pass Filter	217
Active <i>RC</i> Band-Pass Filter	221
Summary of New PSpice Statements Used in This Chapter	222
Problems	223

6 227

Transients and the Time Domain

Switch Closing in an <i>RL</i> Circuit	227
Nonzero Initial Current in the Transient Analysis	228
Resistor and Capacitor in the Transient Analysis	230

A Double-Energy Circuit	232
Overdamped <i>RLC</i> Series Circuit	232
The Critically Damped <i>RLC</i> Circuit	234
The Underdamped <i>RLC</i> Circuit	235
Step Response of an Amplifier	237
Low-Frequency Response of an Amplifier	238
Circuit with Charged Capacitor	240
Switch-Opening Circuit with <i>L</i> and <i>C</i>	242
Circuit with Current Source	244
Bridge Circuit with Initial Current	247
A Ringing Circuit	249
Problems	249

7

Fourier Series and Harmonic Components

253

Fundamental and Second-Harmonic Frequency	253
Decomposition and Reconstruction of Wave	256
Second-Harmonic Distortion in a Power Amplifier	257
Intermodulation Distortion	259
Adding Sine Waves	263
Adding Fundamental and Second Harmonic	265
Amplitude Modulation	266
Summary of New Dot Command Used in This Chapter	267
Problems	268

8

Stability and Oscillators

271

The Feedback Loop	271
The Wien-Bridge Oscillator with Initial Help	272
The <i>LC</i> Oscillator with Initial Help	274
Measurements with a Test Circuit	276
The Phase-Shift Oscillator	276
The Wien-Bridge Oscillator	279
Another Wien-Bridge Example	282
The Colpitts Oscillator	284
Problems	286

9**An Introduction to PSpice Devices****289**

A Half-Wave Rectifier	289
The Built-in Model for a Diode	290
The Filtered Half-Wave Rectifier	292
The Full-Wave Rectifier	295
Full-Wave Rectifier with Filter	295
Simple Diode Clipper	297
A Double-Ended Clipper	298
Variable Load Resistor for Maximum Power	299
Built-in Model for the Bipolar-Junction Transistor	301
Output Characteristics of the Common-Emitter Transistor	302
Input Characteristics of the <i>CE</i> Transistor	303
Output Characteristics of the Junction Field-Effect Transistor	305
Other Active Semiconductor Devices	305
The Differential Amplifier	305
Difference-Mode Gain	305
Common-Mode Gain	306
Transfer Characteristics of the Differential Amplifier	306
Logic Gates	309
The 7402 NOR Gate	309
Summary of New PSpice Statements Used in This Chapter	313
New Dot Commands	314
Problems	314

10**The Bipolar-Junction Transistor and Its Model****319**

The Bipolar-Junction Transistor	319
Output Characteristics	319
Input Characteristics	321
A Common-Emitter BJT Amplifier	321
Biasing Case Study	325
The AC Analysis	326
<i>CE</i> Amplifier with Unbypassed Emitter Resistor	330
Finding the Input Resistance	334
Using Our Own Model with the <i>h</i> Parameters	334
The <i>h</i> -Parameter Analysis	334

Phase Relations in the <i>CE</i> Amplifier	335
The Amplifier without the Emitter Capacitor	336
The Amplifier with the Emitter Capacitor	338
The BJT Flip-Flop	339
The PSpice Analysis	340
The Astable Multivibrator	343
An Emitter-Coupled BJT Multivibrator	344
Problems	349

11

The Field-Effect Transistor

351

Output Characteristics for the Junction Field-Effect Transistor	351
Input Characteristics for the JFET	352
JFET Biasing Circuit	354
The JFET Amplifier	356
JFET Waveshapes	357
The Power MOSFET	357
The Output Characteristics	357
The Input Characteristics	359
The MOSFET Amplifier	361
The Waveshapes	363
The Gallium Arsenide FET	363
Problems	365

12

Two-Port Networks and Passive Filters

371

Two-Port Parameters	371
Finding the y Parameters	371
Using the y Parameters to Solve a Circuit	374
y Parameters of Network with Dependent Source	375
The Open-Circuit Impedance Parameters	377
The z Parameters for an AC Circuit	379
Using the z Parameters to Solve a Circuit	380
The $ABCD$ Parameters	380
The Hybrid Parameters	383

Another Set of Hybrid Parameters	383
Transmission Lines	384
A Long Telephone Line	385
Constant- k Filter	387
Stop-Band Behavior of the Constant- k Filter	389
Lossless Transmission Line	391
Lossless Line Composed of Several Sections	395
Input Impedance at Points along the Line	397
A Band-Pass Filter	398
Band-Elimination Filter	400
Problems	402

13

Nonlinear Devices

405

The Nonlinear Resistor	405
The Iron-Core Inductor	406
The BH Curve	407
The Iron-Core Transformer	409
Voltage-Controlled Switch for Variable Resistor	411
Current-Controlled Switch	414
Summary of New PSpice Statements Used in This Chapter	416
New Dot Command	416
Problems	416

14

Capture

419

A DC Series Circuit	420
Creating a Schematic in Capture	420
Analyzing the Circuit	423
Examining the Output File	423
Printing the Results	424
Net Aliases	426
Drawing a Tee Circuit	427
Running the Simulation	428
Dependent Sources in Schematics	429
Voltage-Dependent Voltage Source	431

Current-Dependent Current Source	432
An AC Circuit	436
Producing the AC Sweep	436
Finding More Accurate Trace Values	439
Order of the Nodes	439
Sine-Wave Representation for AC Analysis	440
Plotting Current with Voltages	442
Series Circuit with R and C	442
Maximum Power to Load Impedance	444
The Probe Voltage and Current Notation	446
Series Resonance	446
Multiple-Source AC Network	448
Sine-Wave Representation of Multisource AC	450
Sine Waves of Currents	452
Transformers	452

15

Transistor Circuits in Capture

455

Output Characteristics of $Q2N3904$	455
Input Characteristics of $Q2N3904$	458
Common-Emitter Bipolar-Junction Transistor Case Study	459
The AC Analysis	462
The Transient Analysis	462
Modifying the Transistor Parameters	465
Using the h -Parameter Model	468
Field-Effect Transistor Characteristics	471
The JFET Amplifier	472
The Transient Analysis (JFET Waveshapes)	478
Frequency Response of BJT	478
Changing the Transistor Characteristics	480

16

Operational Amplifiers in Capture

481

Noninverting Ideal Op Amp	481
Op Amp for Voltage-Difference Output	483
Frequency Response of the Op Amp	485

Active Filter	486
Active Resonant Band-Pass Filter	489
Part <i>uA741</i>	490
Frequency Response of the <i>uA741</i>	490
Subroutine-Node Designation	491
The <i>uA741</i> as a Level Detector	495
Op Amp Phase Shifter	498
Phase Shift Using an Ideal Op Amp	499

17

Other Topics in Schematics

503

The Stimulus Editor	503
A Temperature Sweep	506
Changing the Zener-Breakdown Voltage	508
Using the Breakout Zener Diode	511
Noise Analysis	512
Harmonic Content in Output Voltage	516
Using a Variable Parameter	520
Using Device Tolerances	522
Monte Carlo Analysis	524
Worst-Case Analysis	526
Effect of Resistor Tolerance on Worst-Case Analysis	527
Digital Capture	528
The NOR Gate	530
A Half-Adder Circuit	531
A Circuit for Simplification	535
The D Flip-Flop	535

Appendix A

541

Brief Summary of PSpice Statements

Appendix B

545

PSpice Devices and Statements

CONTENTS

Appendix C	561
Installing the Software, Manuals, and Tutorials	
Appendix D	573
PSpice Devices and Model Parameters	
Appendix E	579
Sample Standard Device Library	
Index	605