

**OPERATIONAL
AMPLIFIERS
WITH
LINEAR INTEGRATED
CIRCUITS**

FOURTH EDITION
WILLIAM D. STANLEY

CONTENTS

1	GENERAL AMPLIFIER CONCEPTS	1
	Objectives	1
1-1	Introduction	2
1-2	Linear Versus Digital Electronics	2
1-3	Source Models	6
1-4	Controlled-Source Models	8
1-5	Complete Amplifier Signal Model	10
1-6	Cascade of Amplifier Stages	12
1-7	Decibel Gain Computations	17
1-8	Frequency Response Considerations	22
1-9	One-Pole Low-Pass Model	27
1-10	Multisim Examples	36
	Summary	41
	Problems	41
2	IDEAL OPERATIONAL AMPLIFIER ANALYSIS AND DESIGN	47
	Objectives	47
2-1	Introduction	48
2-2	General Approach	48
2-3	Operational Amplifier (Op-Amp)	49
2-4	Ideal Operational Amplifier	53
2-5	Simplified Design of Amplifier Circuits	64
2-6	Voltage-Controlled Current Sources	71

xi | CONTENTS

2-7	Current-Controlled Sources	77
2-8	Linear Combination Circuit	81
2-9	Closed-Loop Differential Amplifier	86
2-10	Multisim Examples	89
	Summary	100
	Problems	101

3 OPERATIONAL AMPLIFIER dc EFFECTS AND LIMITATIONS 113

	Objectives	113
3-1	Introduction	114
3-2	Low-Frequency Model of Op-Amp	114
3-3	Noninverting Amplifier: Gain, Input Impedance, and Output Impedance	116
3-4	Inverting Amplifier: Gain, Input Impedance, and Output Impedance	125
3-5	Noise Gain	130
3-6	Offset Voltage and Currents	134
3-7	Multisim Examples	144
	Summary	148
	Problems	148

4 OPERATIONAL AMPLIFIER ac EFFECTS AND LIMITATIONS 157

	Objectives	157
4-1	Introduction	158
4-2	Closed-Loop Frequency Response	158
4-3	Slew Rate	167
4-4	Combination of Linear Bandwidth and Slew Rate	172
4-5	Noise in Operational Amplifiers	179
4-6	Common-Mode Rejection	183
4-7	Multisim Examples	186
	Summary	199
	Problems	199

5 LINEAR OPERATIONAL AMPLIFIER CIRCUITS 207

	Objectives	207
5-1	Introduction	208

xii | CONTENTS

5-2	Instrumentation Amplifier	208
5-3	Integrator and Differentiator Circuits	216
5-4	General Inverting Gain Circuit	223
5-5	ac Integrator	224
5-6	Low-Frequency Differentiator	233
5-7	Phase Shift Circuits	241
5-8	Single Power Supply Operation	246
5-9	Multisim Examples	252
	Summary	258
	Problems	258

6 COMPARATORS

267

	Objectives	267
6-1	Introduction	268
6-2	Input Voltage Considerations	268
6-3	Input-Output Characteristic	269
6-4	Open-Loop Comparators	270
6-5	Comparators with Positive Feedback	280
6-6	LM311 Comparator	288
6-7	Multisim Examples	290
	Summary	294
	Problems	294

7 OSCILLATORS AND WAVEFORM GENERATORS

305

	Objectives	305
7-1	Introduction	306
7-2	Classification Scheme	306
7-3	Operational Amplifier Astable Multivibrator	307
7-4	The 555 Timer	314
7-5	Square/Triangular Wave Function Generator	326
7-6	Barkhausen Criterion	330
7-7	Wien Bridge Oscillator	334
7-8	Phase Shift Oscillator	339
7-9	The 8038 Waveform Generator	342
7-10	Multisim Examples	343
	Summary	349
	Problems	350

8	ACTIVE FILTERS	361
	Objectives	361
8-1	Introduction	362
8-2	Filter Classifications	362
8-3	Frequency and Impedance Scaling	368
8-4	Butterworth Filter Responses	374
8-5	Low-Pass and High-Pass Unity-Gain Designs	381
8-6	Low-Pass and High-Pass Equal-Component Designs	389
8-7	Two-Pole Band-Pass Response	397
8-8	Multiple-Feedback Band-Pass Filter	401
8-9	State-Variable Filter	404
8-10	Multisim Examples	413
	Summary	419
	Problems	420
9	RECTIFIER, DIODE, AND POWER CIRCUITS	427
	Objectives	427
9-1	Introduction	428
9-2	Signal-Processing Rectifier Circuits	428
9-3	Holding Circuits	436
9-4	Clamping Circuits	447
9-5	Limiting Circuits	451
9-6	Power Supply Review	455
9-7	Voltage Regulators	460
9-8	LM117/LM317 Regulators	468
9-9	Multisim Examples	470
	Summary	474
	Problems	475
10	ANALOG-TO-DIGITAL AND DIGITAL-TO-ANALOG CONVERSION	487
	Objectives	487
10-1	Introduction	488
10-2	Sampling and Data Conversion	488
10-3	Digital-to-Analog Conversion	493
10-4	Analog-to-Digital Conversion	501

xiv | CONTENTS

10-5	Integrating Analog-to-Digital Converters	508
10-6	Converter Specifications	512
10-7	ADC0801-0805 A/D Converters	522
10-8	DAC0806-0808 D/A Converters	524
10-9	Analog Switches and Multiplexers	526
10-10	Voltage and Frequency Conversions	528
10-11	Multisim Example	530
	Summary	533
	Problems	533

11 MISCELLANEOUS CIRCUITS **541**

	Objectives	541
11-1	Introduction	542
11-2	Multipliers	542
11-3	Logarithmic Amplifiers	549
11-4	Phase-Locked Loops	554
11-5	NE/SE 565 Phase-Locked Loop	557
	Summary	562
	Problems	562

GENERAL REFERENCES **567**

Appendix A Resistor and Capacitor Values | **Appendix B** Linear Integrated-Circuit Manufacturers | **Appendix C** Specification Sheets | **Appendix D** Analysis of a Differential Amplifier | **Appendix E** Introduction to Multisim

GLOSSARY	641
ANSWERS TO SELECTED ODD-NUMBERED PROBLEMS	647
INDEX	655