
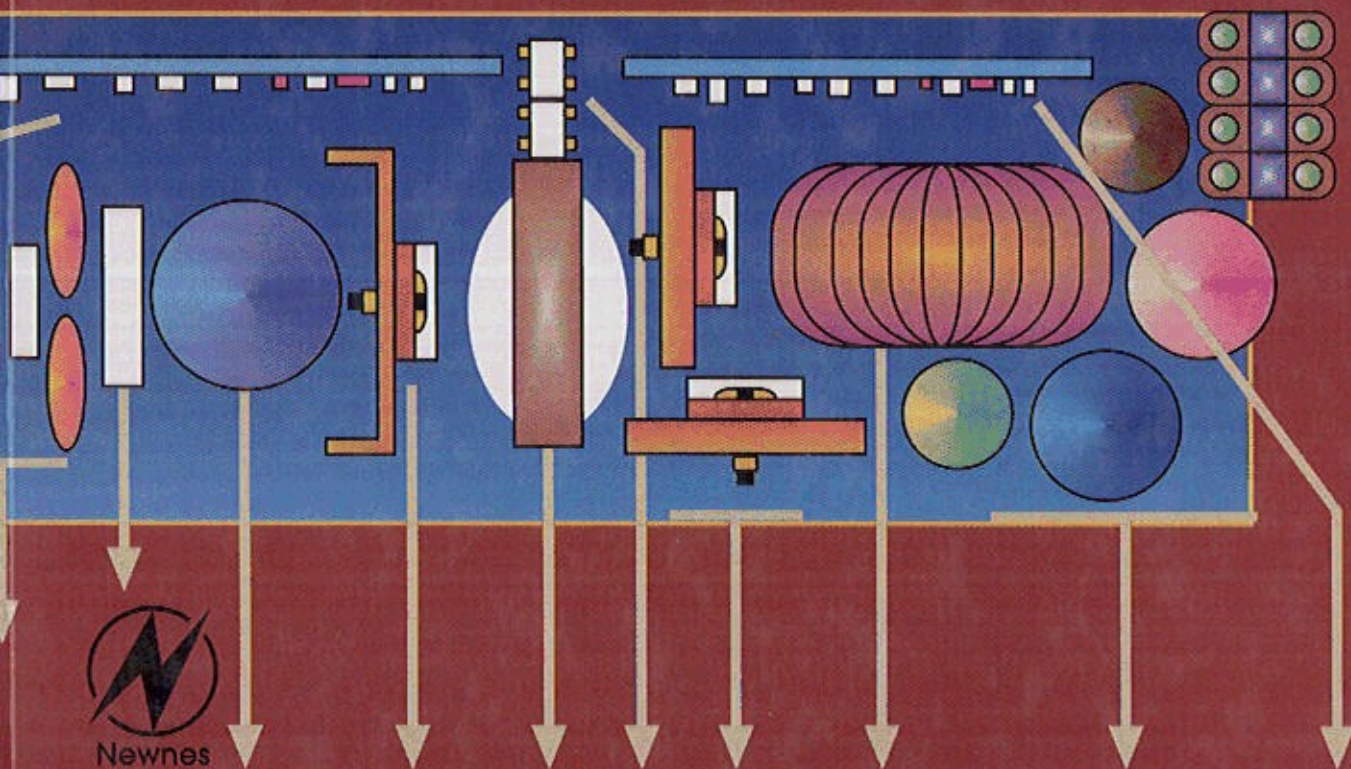


Switching Power Supplies

SANJAYA MANIKTALA

A to Z

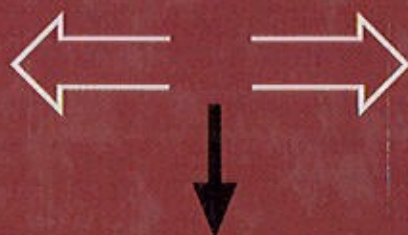

Contents

Preface	xi
Acknowledgements	xvii
Chapter 1: The Principles of Switching Power Conversion	1
Introduction	3
Overview and Basic Terminology	5
Understanding the Inductor	22
Evolution of Switching Topologies	43
Chapter 2: DC-DC Converter Design and Magnetics	61
DC Transfer Functions	64
The DC Level and the “Swing” of the Inductor Current Waveform	65
Defining the AC, DC, and Peak Currents	68
Understanding the AC, DC and Peak Currents	70
Defining the “Worst-case” Input Voltage	72
The Current Ripple Ratio ‘ r ’	75
Relating r to the Inductance	75
The Optimum Value of r	77
Do We Mean Inductor? Or Inductance?	79
How Inductance and Inductor Size Depend on Frequency	80
How Inductance and Inductor Size Depend on Load Current	80
How Vendors Specify the Current Rating of an Off-the-shelf Inductor and How to Select It	81
What Is the Inductor Current Rating We Need to Consider for a Given Application? ...	82
The Spread and Tolerance of the Current Limit	85
Worked Example (1)	88
Worked Examples (2, 3, and 4)	100
Worked Example (5) — When Not to Increase the Number of Turns	106
Worked Example (6) — Characterizing an Off-the-shelf Inductor in a Specific Application	110
Calculating the “Other” Worst-case Stresses	118

Chapter 3: Off-line Converter Design and Magnetics	127
Flyback Converter Magnetics	130
Forward Converter Magnetics	152
Chapter 4: The Topology FAQ	177
Questions and Answers	179
Chapter 5: Conduction and Switching Losses	203
Switching a Resistive Load	206
Switching an Inductive Load	210
Switching Losses and Conduction Loss	213
A Simplified Model of the Mosfet for Studying Inductive Switching Losses	215
The Parasitic Capacitances Expressed in an Alternate System	217
Gate Threshold Voltage	218
The Turn-on Transition	218
The Turn-off Transition	222
Gate Charge Factors	224
Worked Example	227
Applying the Switching Loss Analysis to Switching Topologies	231
Worst-case Input Voltage for Switching Losses	232
How Switching Losses Vary with the Parasitic Capacitances	233
Optimizing Driver Capability vis-à-vis Mosfet Characteristics	234
Chapter 6: Printed Circuit Board Layout	237
Introduction	239
Trace Section Analysis	239
Some Points to Keep in Mind During Layout	240
Thermal Management Concerns	247
Chapter 7: Feedback Loop Analysis and Stability	249
Transfer Functions, Time Constant and the Forcing Function	251
Understanding ‘e’ and Plotting Curves on Log Scales	252
Time Domain and Frequency Domain Analysis	255
Complex Representation	256
Nonrepetitive Stimuli	258
The s-plane	258
Laplace Transform	260

Disturbances and the Role of Feedback	262
Transfer Function of the RC Filter	264
The Integrator Op-amp (“pole-at-zero” Filter)	267
Mathematics in the Log Plane	269
Transfer Function of the LC Filter	270
Summary of Transfer Functions of Passive Filters	273
Poles and Zeros	274
Interaction of Poles and Zeros	276
Closed and Open Loop Gain	277
The Voltage Divider	280
Pulse Width Modulator Transfer Function (gain)	281
Voltage Feedforward	282
Power Stage Transfer Function	283
Plant Transfer Functions of All the Topologies	284
Boost Converter	286
Feedback Stage Transfer Functions	289
Closing the Loop	291
Criteria for Loop Stability	293
Plotting the Open-loop Gain and Phase with an Integrator	293
Canceling the Double Pole of the LC Filter	295
The ESR Zero	296
Designing a Type 3 Op-amp Compensation Network	297
Optimizing the Feedback Loop	301
Input Ripple Rejection	304
Load Transients	305
Type 1 and Type 2 Compensations	306
Transconductance Op-amp Compensation	308
Simpler Transconductance Op-amp Compensation	311
Compensating with Current Mode Control	313
Chapter 8: EMI from the Ground up — Maxwell to CISPR	323
The Standards	326
Maxwell to EMI	328
Susceptibility/Immunity	333
Some Cost-related Rules-of-thumb	335
EMI for Subassemblies	335
CISPR 22 for Telecom Ports — Proposed Changes	336

Chapter 9: Measurements and Limits of Conducted EMI	339
Differential Mode and Common Mode Noise	341
How Conducted EMI Is Measured	344
The Conducted Emission Limits	348
Quasi-peak, Average, and Peak Measurements	351
Chapter 10: Practical EMI Line Filters	355
Safety Issues in EMI Filter Design	357
Practical Line Filters	359
Safety Restrictions on the Total Y-capacitance	367
Equivalent DM and CM Circuits	368
Some Notable Industry Experiences in EMI	371
Chapter 11: DM and CM Noise in Switching Power Supplies	373
Main Source of DM Noise	375
The Main Source of CM Noise	377
The Ground Choke	385
Chapter 12: Fixing EMI across the Board	387
The Role of the Transformer in EMI	389
EMI from Diodes	394
Beads, and an Industry Experience — the dV/dt of Schottky Diodes	397
Basic Layout Guidelines	398
Last-ditch Troubleshooting	399
Are We Going to Fail the Radiation Test?	402
Chapter 13: Input Capacitor and Stability Considerations in EMI Filters	403
Is the DM Choke Saturating?	405
Practical Line Filters in DC-DC Converter Modules	410
Chapter 14: The Math behind the Electromagnetic Puzzle	417
Math Background — Fourier Series	419
The Rectangular Wave	420
Analysis of the Rectangular Wave	423
The Trapezoid	424
The EMI from a Trapezoid	426
The Road to Cost-effective Filter Design	427
Practical DM Filter Design	430
Practical CM Filter Design	433

<i>Appendix 1: Focusing on Some Real-world Issues</i>	437
Sounds Like Worst-case, But There’s Danger Lurking in the Middle	439
Loop Design Sometimes Compensates for Lower-quality Switchers	440
Re-inventing the Wheel... as a Square	442
The Mighty Zener	444
Better Do the Math: Ignore Transfer Functions at Your Own Peril	447
Aluminum Cap Multipliers — Why We Can’t Have Them and Eat Them Too	449
Limit Your Peak Current, Not Your Reliability	452
Reliability Is No Flash in the Pan	455
The Incredible Shrinking Core	459
Plain Lucky We Don’t Live in a PSpice World!	462
Why Does the Efficiency of My Flyback Nose-dive?	465
It’s Not a Straight Line: Computing the Correct Drain to Source Resistance from V-I Curves	468
Don’t Have a Scope? Use a DMM, Dummy!	470
Are We Making Light of Electronic Ballasts?	473
More on Designing Reliable Electronic Ballasts	476
The Organizational Side of Power Management: One Engineer’s Perspective	480
<i>Appendix 2: Reference Design Table</i>	485
<i>References</i>	489
<i>Index</i>	493