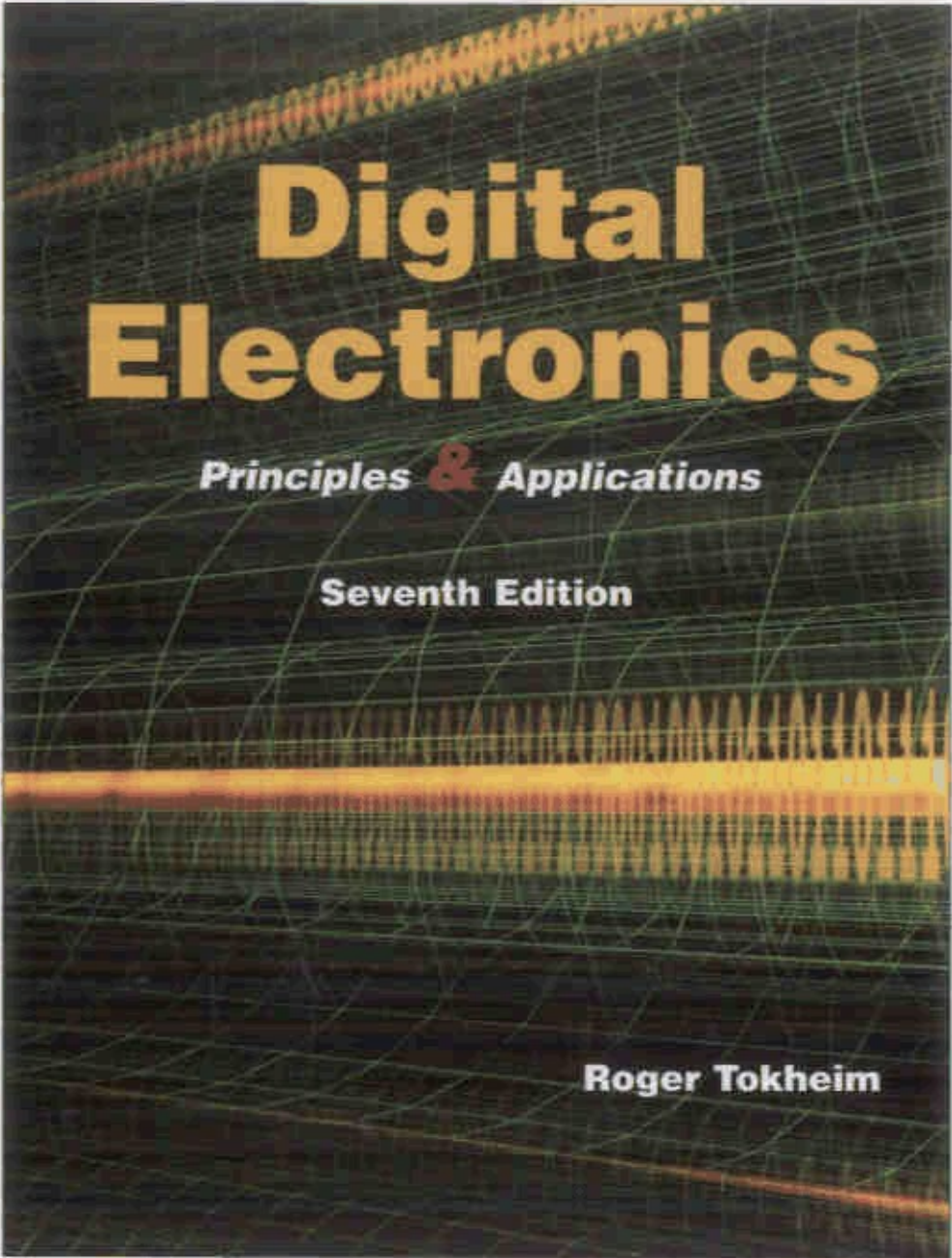




Digital Electronics

Principles & Applications

Seventh Edition

Roger Tokheim

McGraw-Hill INTERNATIONAL EDITION



Contents

Editor's Foreword	vi
Preface	vii
Acknowledgments	ix
Safety	x

Chapter 1 Digital Electronics 1

1-1 What Is a Digital Circuit?	2
1-2 Why Use Digital Circuits?	4
1-3 How Do You Generate a Digital Signal?	6
1-4 How Do You Test for a Digital Signal?	12
1-5 Simple Instruments	16

Chapter 2 Numbers We Use in Digital Electronics 25

2-1 Counting in Decimal and Binary	25
2-2 Place Value	26
2-3 Binary to Decimal Conversion	28
2-4 Decimal to Binary Conversion	28
2-5 Electronic Translators	29
2-6 Hexadecimal Numbers	30
2-7 Octal Numbers	32
2-8 Bits, Bytes, Nibbles, and Word Size	34

Chapter 3 Logic Gates 39

3-1 The AND Gate	39
3-2 The OR Gate	42
3-3 The Inverter and Buffer	43
3-4 The NAND Gate	46
3-5 The NOR Gate	47
3-6 The Exclusive OR Gate	49
3-7 The Exclusive NOR Gate	50
3-8 The NAND Gate as a Universal Gate	52
3-9 Gates with More Than Two Inputs	53
3-10 Using Inverters to Convert Gates	55
3-11 Practical TTL Logic Gates	58
3-12 Practical CMOS Logic Gates	61
3-13 Troubleshooting Simple Gate Circuits	63
3-14 IEEE Logic Symbols	66
3-15 Simple Logic Gate Applications	67
3-16 Logic Functions Using Software (BASIC Stamp Module)	71

Chapter 4 Combining Logic Gates 83

4-1 Constructing Circuits from Boolean Expressions	84
4-2 Drawing a Circuit from a Maxterm Boolean Expression	85
4-3 Truth Tables and Boolean Expressions	86
4-4 Sample Problem	89
4-5 Simplifying Boolean Expressions	92
4-6 Karnaugh Maps	93
4-7 Karnaugh Maps with Three Variables	94
4-8 Karnaugh Maps with Four Variables	95
4-9 More Karnaugh Maps	96
4-10 A Five-Variable Karnaugh Map	98
4-11 Using NAND Logic	99
4-12 Computer Simulations-Logic Converter	100
4-13 Solving Logic Problems—Data Selectors	104
4-14 More Data Selector Problems	107
4-15 Programmable Logic Devices (PLDs)	110
4-16 Using DeMorgan's Theorems	118
4-17 Solving a Logic Problem (BASIC Stamp Module)	121

Chapter 5 IC Specifications and Simple Interfacing 137

5-1 Logic Levels and Noise Margin	137
5-2 Other Digital IC Specifications	141
5-3 MOS and CMOS ICs	145
5-4 Interfacing TTL and CMOS with Switches	147
5-5 Interfacing TTL and CMOS with LEDs	152
5-6 Interfacing TTL and CMOS ICs	156
5-7 Interfacing with Buzzers, Relays, Motors, and Solenoids	160
5-8 Optoisolators	163
5-9 Interfacing with Servo- and Stepper-Motors	166
5-10 Using Hall-Effect Sensors	173
5-11 Troubleshooting Simple Logic Circuits	179
5-12 Interfacing the Servo (BASIC Stamp Module)	181

**Chapter 6 Encoding, Decoding,
and Seven-Segment Displays 191**

6-1	The 8421 BCD Code	192
6-2	The Excess-3 Code	193
6-3	The Gray Code	194
6-4	The ASCII Code	195
6-5	Encoders	197
6-6	Seven-Segment LED Displays	198
6-7	Decoders	201
6-8	BCD-to-Seven-Segment Decoder/Drivers ..	202
6-9	Liquid-Crystal Displays	206
6-10	Using CMOS to Drive an LCD Display ...	211
6-11	Vacuum Fluorescent Displays	214
6-12	Driving a VF Display	217
6-13	Troubleshooting a Decoding Circuit	220

Chapter 7 Flip-Flops 229

7-1	The R-S Flip-Flop	229
7-2	The Clocked R-S Flip-Flop	231
7-3	The D Flip-Flop	234
7-4	The J-K Flip-Flop	236
7-5	IC Latches	239
7-6	Triggering Flip-Flops	242
7-7	Schmitt Trigger	244
7-8	IEEE Logic Symbols	245

Chapter 8 Counters 251

8-1	Ripple Counters	251
8-2	Mod-10 Ripple Counters	253
8-3	Synchronous Counters	254
8-4	Down Counters	256
8-5	Self-Stopping Counters	258
8-6	Counters as Frequency Dividers	258
8-7	TTL IC Counters	260
8-8	CMOS IC Counters	265
8-9	A 3-Digit BCD Counter	269
8-10	Counting Real-World Events	272
8-11	Using a CMOS Counter in an Electronic Game	276
8-12	Using Counters—An Experimental Tachometer	278
8-13	Troubleshooting a Counter	284

Chapter 9 Shift Registers 293

9-1	Serial Load Shift Registers	294
9-2	Parallel Load Shift Registers	297
9-3	A Universal Shift Register	299
9-4	Using the 74194 IC Shift Register	301
9-5	An 8-Bit CMOS Shift Register	304

9-6	Using Shift Registers—Digital Roulette ...	306
9-7	Troubleshooting a Simple Shift Register ...	311

Chapter 10 Arithmetic Circuits 317

10-1	Binary Addition	317
10-2	Half Adders	319
10-3	Full Adders	320
10-4	Three-Bit Adders	322
10-5	Binary Subtraction	323
10-6	Parallel Subtractors	325
10-7	IC Adders	327
10-8	Binary Multiplication	330
10-9	Binary Multipliers	332
10-10	2s Complement Notation, Addition, and Subtraction	335
10-11	2s Complement Adders/Subtractors	340
10-12	Troubleshooting a Full Adder	342

Chapter 11 Memories 347

11-1	Overview of Memory	348
11-2	Random-Access Memory (RAM)	351
11-3	Static RAM ICs	353
11-4	Using a SRAM	356
11-5	Read-Only Memory (ROM)	358
11-6	Using a ROM	361
11-7	Programmable Read-Only Memory (PROM)	363
11-8	Nonvolatile Read/Write Memory	366
11-9	Memory Packaging	370
11-10	Computer Bulk Storage Devices	373
11-11	Digital Potentiometer—Using NV Memory	380

Chapter 12 Digital Systems 389

12-1	Elements of a System	389
12-2	A Digital System of an IC	390
12-3	Digital Games	391
12-4	The Digital Clock	396
12-5	The LSI Digital Clock	399
12-6	A Practical LSI Digital Clock System	403
12-7	The Frequency Counter	407
12-8	An Experimental Frequency Counter	411
12-9	LCD Timer with Alarm	414
12-10	JTAG/Boundary Scan	421

Chapter 13 Computer Systems 427

13-1	The Computer	427
13-2	The Microcomputer	429
13-3	Microcomputer Operation	432

13-4	Microcomputer Address Decoding	436
13-5	Data Transmission	439
13-6	Detecting Errors in Data Transmissions	443
13-7	Data Transmission in a Computer System . .	446
13-8	Programmable Logic Controllers (PLCs) . .	450
13-9	Microcontrollers	454
13-10	The BASIC Stamp Microcontroller Modules	459
13-11	Digital Signal Processing	464
13-12	DSP in a Digital Camera	468

Chapter 14 Connecting with Analog Devices 475

14-1	D/A Conversion	476
14-2	Operational Amplifiers	477

14-3	A Basic D/A Converter	478
14-4	Ladder-Type D/A Converters	480
14-5	An A/D Converter	482
14-6	Voltage Comparators	484
14-7	An Elementary Digital Voltmeter	486
14-8	Other A/D Converters	488
14-9	A/D Converter Specifications	492
14-10	An A/D Converter IC	493
14-11	Digital Light Meter	496
14-12	Digitizing Temperature	499
Appendix A	Solder and the Soldering Process	505
Appendix B	Formulas and Conversions	510
Glossary		511
Credits		525
Index		527