



# Introduction to **Linear Circuit Analysis and Modelling**

From DC to RF

Luis Moura • Izzat Darwazeh



# Contents

<b>Preface</b>	<b>ix</b>
<b>Acknowledgements</b>	<b>xi</b>
<b>1 Elementary electrical circuit analysis</b>	<b>1</b>
1.1 Introduction . . . . .	1
1.2 Voltage and current . . . . .	1
1.2.1 Voltage sources . . . . .	2
1.2.2 Current sources . . . . .	3
1.3 Electrical passive elements . . . . .	5
1.3.1 Resistance and conductance . . . . .	5
1.3.2 Capacitance . . . . .	8
1.3.3 Inductance . . . . .	9
1.4 Kirchhoff's laws . . . . .	10
1.4.1 Series and parallel combinations of passive elements . . . . .	11
1.4.2 Other types of circuit element connections . . . . .	17
1.4.3 Electrical network analysis – Nodal analysis . . . . .	18
1.4.4 Resistive voltage and current dividers . . . . .	20
1.4.5 Controlled sources . . . . .	21
1.5 Thévenin's theorem . . . . .	22
1.6 Norton's theorem . . . . .	23
1.7 Superposition theorem . . . . .	25
1.8 Bibliography . . . . .	26
1.9 Problems . . . . .	27
<b>2 Complex numbers: An introduction</b>	<b>32</b>
2.1 Introduction . . . . .	32
2.2 Definition . . . . .	32
2.3 Elementary algebra . . . . .	34
2.3.1 Addition . . . . .	34
2.3.2 Subtraction . . . . .	34
2.3.3 Multiplication . . . . .	35
2.3.4 Division . . . . .	37
2.3.5 Complex equations . . . . .	38
2.3.6 Quadratic equations . . . . .	38
2.4 Polar representation . . . . .	39

2.4.1	Multiplication and division . . . . .	40
2.5	The exponential form . . . . .	41
2.5.1	Trigonometric functions and the exponential form . . . . .	42
2.6	Powers and roots . . . . .	43
2.7	Bibliography . . . . .	46
2.8	Problems . . . . .	46
<b>3</b>	<b>Frequency domain electrical signal and circuit analysis</b>	<b>48</b>
3.1	Introduction . . . . .	48
3.2	Sinusoidal AC electrical analysis . . . . .	48
3.2.1	Effective electrical values . . . . .	49
3.2.2	<i>I</i> - <i>V</i> characteristics for passive elements . . . . .	50
3.2.3	Phasor analysis . . . . .	54
3.2.4	The generalised impedance . . . . .	56
3.2.5	Maximum power transfer . . . . .	64
3.3	Generalised frequency domain analysis . . . . .	65
3.3.1	The Fourier series . . . . .	65
3.3.2	Fourier coefficients, phasors and line spectra . . . . .	72
3.3.3	Electrical signal and circuit bandwidths . . . . .	73
3.3.4	Linear distortion . . . . .	79
3.3.5	Bode plots . . . . .	80
3.3.6	The Fourier transform . . . . .	88
3.3.7	Transfer function and impulse response . . . . .	98
3.3.8	The convolution operation . . . . .	100
3.4	Bibliography . . . . .	106
3.5	Problems . . . . .	106
<b>4</b>	<b>Natural and forced responses circuit analysis</b>	<b>109</b>
4.1	Introduction . . . . .	109
4.2	Time domain analysis . . . . .	109
4.3	Transient analysis using Fourier transforms . . . . .	113
4.3.1	Differentiation theorem . . . . .	113
4.3.2	Integration theorem . . . . .	114
4.3.3	<i>I</i> - <i>V</i> characteristics for passive elements . . . . .	114
4.4	The Laplace transform . . . . .	117
4.4.1	Theorems of the Laplace transform . . . . .	119
4.4.2	Partial-fraction expansion . . . . .	123
4.5	Analysis using Laplace transforms . . . . .	127
4.5.1	Solving differential equations . . . . .	127
4.5.2	<i>I</i> - <i>V</i> characteristics for passive elements . . . . .	128
4.5.3	Natural response . . . . .	130
4.5.4	Response to the step function . . . . .	136
4.6	Bibliography . . . . .	147
4.7	Problems . . . . .	147

<b>5 Electrical two-port network analysis</b>	<b>150</b>
5.1 Introduction . . . . .	150
5.2 Electrical representations . . . . .	150
5.2.1 Electrical impedance representation . . . . .	150
5.2.2 Electrical admittance representation . . . . .	153
5.2.3 Electrical chain representation . . . . .	157
5.2.4 Conversion between electrical representations . . . . .	159
5.2.5 Miller's theorem . . . . .	161
5.3 Computer-aided electrical analysis . . . . .	163
5.4 Bibliography . . . . .	167
5.5 Problems . . . . .	167
<b>6 Basic electronic amplifier building blocks</b>	<b>169</b>
6.1 Introduction . . . . .	169
6.2 Modelling the amplification process . . . . .	169
6.3 Operational amplifiers . . . . .	177
6.3.1 Open-loop and feedback concepts . . . . .	177
6.3.2 Other examples and applications . . . . .	179
6.4 Active devices . . . . .	183
6.4.1 The junction or $p$ - $n$ diode . . . . .	183
6.4.2 The bipolar junction transistor . . . . .	183
6.4.3 The insulated gate field-effect transistor . . . . .	192
6.4.4 The common-emitter amplifier . . . . .	196
6.4.5 The differential pair amplifier . . . . .	215
6.5 Bibliography . . . . .	221
6.6 Problems . . . . .	221
<b>7 RF circuit analysis techniques</b>	<b>224</b>
7.1 Introduction . . . . .	224
7.2 Lumped versus distributed . . . . .	224
7.3 Electrical model for ideal transmission lines . . . . .	227
7.3.1 Voltage Standing Wave Ratio – VSWR . . . . .	234
7.3.2 The $\lambda/4$ transformer . . . . .	239
7.3.3 Lossy transmission lines . . . . .	242
7.3.4 Microstrip transmission lines . . . . .	247
7.4 Scattering parameters . . . . .	248
7.4.1 $S$ -parameters and power waves . . . . .	254
7.4.2 Power waves and generalised $S$ -parameters . . . . .	258
7.4.3 Conversions between different two-port parameters . . . . .	263
7.5 The Smith chart . . . . .	264
7.5.1 The impedance and the reflection coefficient planes . . . . .	264
7.5.2 Representation of impedances . . . . .	266
7.5.3 Introduction to impedance matching . . . . .	272
7.6 Bibliography . . . . .	276
7.7 Problems . . . . .	276

<b>8</b>	<b>Noise in electronic circuits</b>	<b>279</b>
8.1	Introduction . . . . .	279
8.2	Random variables . . . . .	279
8.2.1	Moments of a random variable . . . . .	285
8.2.2	The characteristic function . . . . .	288
8.2.3	The central limit theorem . . . . .	290
8.2.4	Bivariate Gaussian distributions . . . . .	293
8.3	Stochastic processes . . . . .	295
8.3.1	Ensemble averages . . . . .	295
8.3.2	Stationary random processes . . . . .	296
8.3.3	Ergodic random processes . . . . .	296
8.3.4	Power spectrum . . . . .	298
8.3.5	Cross-power spectrum . . . . .	301
8.3.6	Gaussian random processes . . . . .	302
8.3.7	Filtered random signals . . . . .	303
8.4	Noise in electronic circuits . . . . .	305
8.4.1	Thermal noise . . . . .	305
8.4.2	Electronic shot-noise . . . . .	306
8.4.3	$1/f$ noise . . . . .	306
8.4.4	Noise models for passive devices . . . . .	307
8.4.5	Noise models for active devices . . . . .	308
8.4.6	The equivalent input noise sources . . . . .	310
8.4.7	The noise figure . . . . .	319
8.5	Computer-aided noise modelling and analysis . . . . .	323
8.5.1	Noise representations . . . . .	323
8.5.2	Calculation of the correlation matrices . . . . .	325
8.5.3	Elementary two-port interconnections . . . . .	327
8.5.4	Transformation matrices . . . . .	328
8.6	Bibliography . . . . .	339
8.7	Problems . . . . .	340
<b>A</b>	<b>Mathematical formulae for electrical engineering</b>	<b>342</b>
<b>B</b>	<b>Elementary matrix algebra</b>	<b>350</b>
<b>C</b>	<b>Two-port electrical parameters</b>	<b>352</b>
<b>Index</b>		<b>356</b>