

The top half of the cover features a dark, textured background with a complex, organic red pattern. The pattern consists of thick, wavy lines that form a series of interconnected loops and spirals, resembling a stylized circuit board or a biological structure. The lines are a vibrant red color, contrasting sharply with the dark background.

International Student Version

NINTH EDITION

Basic Engineering Circuit Analysis

J. DAVID IRWIN & R. MARK NELMS

CONTENTS

Preface

xiii

CHAPTER 1

BASIC ELECTRIC CIRCUIT CONCEPTS 1

- 1.1 System of Units 2
- 1.2 Basic Quantities 2
- 1.3 Circuit Elements 8
 - Summary 16
 - Problems 16

CHAPTER 2

ANALYSIS OF RESISTIVE CIRCUITS 23

- 2.1 Ohm's Law 24
- 2.2 Kirchhoff's Laws 28
- 2.3 Single-Loop Circuits 37
- 2.4 Single-Node-Pair Circuits 43
- 2.5 Series and Parallel Resistor Combinations 48
- 2.6 Circuits with Series-Parallel Combinations of Resistors 53
- 2.7 Wye \rightleftharpoons Delta Transformations 57
- 2.8 Circuits with Dependent Sources 60
- 2.9 Resistor Technologies for Electronic Manufacturing 64
- 2.10 Application Examples 67
- 2.11 Design Examples 71
 - Summary 76
 - Problems 77

CHAPTER 3

LOOP AND NODAL TECHNIQUES FOR CIRCUIT ANALYSIS 95

- 3.1 Nodal Analysis 96
- 3.2 Loop Analysis 115
- 3.3 Application Example 131
- 3.4 Design Example 133
 - Summary 133
 - Problems 134

CHAPTER 4

INTRODUCTION TO OPERATIONAL AMPLIFIERS 149

- 4.1 Introduction 150
- 4.2 Op-Amp Models 150
- 4.3 Fundamental Op-Amp Circuits 156
- 4.4 Comparators 164
- 4.5 Application Examples 165
- 4.6 Design Examples 169
 - Summary 172
 - Problems 172

CHAPTER 5

ADDITIONAL TECHNIQUES FOR CIRCUIT ANALYSIS 183

- 5.1 Introduction 184
- 5.2 Superposition 186

5.3	Thévenin's and Norton's Theorems	191
5.4	Maximum Power Transfer	208
5.5	dc SPICE Analysis Using <i>Schematic Capture</i>	212
5.6	Application Example	224
5.7	Design Examples	225
	Summary	231
	Problems	231

CHAPTER 6

ENERGY STORAGE ELEMENTS: THE CAPACITOR AND THE INDUCTOR 248

6.1	Capacitors	249
6.2	Inductors	255
6.3	Capacitor and Inductor Combinations	264
6.4	RC Operational Amplifier Circuits	271
6.5	Application Examples	274
6.6	Design Examples	278
	Summary	280
	Problems	280

CHAPTER 7

ANALYSIS OF FIRST- AND SECOND-ORDER TRANSIENT CIRCUITS 291

7.1	Introduction	292
7.2	First-Order Circuits	293
7.3	Second-Order Circuits	314
7.4	Transient PSPICE Analysis Using <i>Schematic Capture</i>	328
7.5	Application Examples	337
7.6	Design Examples	348
	Summary	356
	Problems	356

CHAPTER 8

AC CIRCUIT ANALYSIS TECHNIQUES 375

8.1	Sinusoids	376
8.2	Sinusoidal and Complex Forcing Functions	379
8.3	Phasors	383
8.4	Phasor Relationships for Circuit Elements	385
8.5	Impedance and Admittance	389
8.6	Phasor Diagrams	396

8.7	Basic Analysis Using Kirchhoff's Laws	399
8.8	Analysis Techniques	401
8.9	AC PSPICE Analysis Using <i>Schematic Capture</i>	416
8.10	Application Examples	429
8.11	Design Examples	431
	Summary	434
	Problems	435

CHAPTER 9

POWER CALCULATIONS IN AC CIRCUITS 455

9.1	Instantaneous Power	456
9.2	Average Power	457
9.3	Maximum Average Power Transfer	462
9.4	Effective or rms Values	466
9.5	The Power Factor	469
9.6	Complex Power	471
9.7	Power Factor Correction	476
9.8	Single-Phase Three-Wire Circuits	479
9.9	Safety Considerations	482
9.10	Application Examples	490
9.11	Design Example	494
	Summary	496
	Problems	496

CHAPTER 10

ANALYSIS OF MAGNETICALLY COUPLED CIRCUITS 507

10.1	Mutual Inductance	508
10.2	Energy Analysis	518
10.3	The Ideal Transformer	521
10.4	Safety Considerations	529
10.5	Application Examples	530
10.6	Design Examples	535
	Summary	539
	Problems	540

CHAPTER 11

ANALYSIS OF THREE-PHASE CIRCUITS 553

11.1	Three-Phase Circuits	554
11.2	Three-Phase Connections	559
11.3	Source/Load Connections	560

- 11.4 Power Relationships 568
- 11.5 Power Factor Correction 572
- 11.6 Application Examples 573
- 11.7 Design Examples 576
 - Summary 580
 - Problems 581

CHAPTER 12

VARIABLE-FREQUENCY CIRCUITS 587

- 12.1 Variable Frequency-Response Analysis 588
- 12.2 Sinusoidal Frequency Analysis 596
- 12.3 Resonant Circuits 608
- 12.4 Scaling 629
- 12.5 Filter Networks 631
- 12.6 Application Examples 655
- 12.7 Design Examples 659
 - Summary 665
 - Problems 666

CHAPTER 13

INTRODUCTION TO THE LAPLACE TRANSFORM 677

- 13.1 Definition 678
- 13.2 Two Important Singularity Functions 679
- 13.3 Transform Pairs 681
- 13.4 Properties of the Transform 683
- 13.5 Performing the Inverse Transform 686
- 13.6 Convolution Integral 692
- 13.7 Initial-Value and Final-Value Theorems 696
- 13.8 Application Example 697
 - Summary 699
 - Problems 699

CHAPTER 14

CIRCUIT ANALYSIS USING THE LAPLACE TRANSFORM 705

- 14.1 Laplace Circuit Solutions 706
- 14.2 Circuit Element Models 707

- 14.3 Analysis Techniques 709
- 14.4 Transfer Function 721
- 14.5 Pole-Zero Plot/Bode Plot Connection 732
- 14.6 Steady-State Response 735
- 14.7 Application Example 737
- 14.8 Design Examples 739
 - Summary 746
 - Problems 746

CHAPTER 15

USING FOURIER TECHNIQUES IN CIRCUIT ANALYSIS 758

- 15.1 Fourier Series 759
- 15.2 Fourier Transform 781
- 15.3 Application Examples 788
- 15.4 Design Examples 795
 - Summary 801
 - Problems 802

CHAPTER 16

MODELS FOR TWO-PORT NETWORKS 809

- 16.1 Admittance Parameters 810
- 16.2 Impedance Parameters 813
- 16.3 Hybrid Parameters 815
- 16.4 Transmission Parameters 817
- 16.5 Parameter Conversions 818
- 16.6 Interconnection of Two-Ports 819
- 16.7 Application Examples 822
- 16.8 Design Example 826
 - Summary 828
 - Problems 828

APPENDIX

COMPLEX NUMBERS 835

INDEX 840