

# THE ANALYSIS & DESIGN OF **LINEAR CIRCUITS**

sixth edition



ROLAND E. THOMAS ■ ALBERT J. ROSA ■ GREGORY J. TOUSSAINT



# CONTENTS

|                                                    |               |
|----------------------------------------------------|---------------|
| <b>CHAPTER 1 • INTRODUCTION</b>                    | <b>1</b>      |
| 1-1 About This Book                                | 2             |
| 1-2 Symbols and Units                              | 3             |
| 1-3 Circuit Variables                              | 5             |
| 1-4 Computational Software Introduction            | 11            |
| SUMMARY                                            | 12            |
| PROBLEMS                                           | 12            |
| INTEGRATING PROBLEMS                               | 14            |
| <br><b>CHAPTER 2 • BASIC CIRCUIT ANALYSIS</b>      | <br><b>16</b> |
| 2-1 Element Constraints                            | 17            |
| 2-2 Connection Constraints                         | 22            |
| 2-3 Combined Constraints                           | 30            |
| 2-4 Equivalent Circuits                            | 36            |
| 2-5 Voltage and Current Division                   | 42            |
| 2-6 Circuit Reduction                              | 50            |
| 2-7 Computer-Aided Circuit Analysis                | 55            |
| SUMMARY                                            | 61            |
| PROBLEMS                                           | 61            |
| INTEGRATING PROBLEMS                               | 68            |
| <br><b>CHAPTER 3 • CIRCUIT ANALYSIS TECHNIQUES</b> | <br><b>70</b> |
| 3-1 Node-Voltage Analysis                          | 71            |
| 3-2 Mesh-Current Analysis                          | 87            |
| 3-3 Linearity Properties                           | 96            |
| 3-4 Thévenin and Norton Equivalent Circuits        | 103           |
| 3-5 Maximum Signal Transfer                        | 115           |
| 3-6 Interface Circuit Design                       | 119           |
| SUMMARY                                            | 131           |
| PROBLEMS                                           | 131           |
| INTEGRATING PROBLEMS                               | 141           |

|                                                                       |                |
|-----------------------------------------------------------------------|----------------|
| <b>CHAPTER 4 • ACTIVE CIRCUITS</b>                                    | <b>143</b>     |
| 4-1 Linear Dependent Sources                                          | 144            |
| 4-2 Analysis of Circuits with Dependent Sources                       | 147            |
| 4-3 The Operational Amplifier                                         | 162            |
| 4-4 OP AMP Circuit Analysis                                           | 169            |
| 4-5 OP AMP Circuit Design                                             | 184            |
| 4-6 OP AMP Circuit Applications                                       | 191            |
| SUMMARY                                                               | 208            |
| PROBLEMS                                                              | 208            |
| INTEGRATING PROBLEMS                                                  | 217            |
| <br><b>CHAPTER 5 • SIGNAL WAVEFORMS</b>                               | <br><b>219</b> |
| 5-1 Introduction                                                      | 220            |
| 5-2 The Step Waveform                                                 | 221            |
| 5-3 The Exponential Waveform                                          | 226            |
| 5-4 The Sinusoidal Waveform                                           | 231            |
| 5-5 Composite Waveforms                                               | 238            |
| 5-6 Waveform Partial Descriptors                                      | 246            |
| 5-7 Signals and Software Tools                                        | 254            |
| SUMMARY                                                               | 265            |
| PROBLEMS                                                              | 266            |
| INTEGRATING PROBLEMS                                                  | 269            |
| <br><b>CHAPTER 6 • CAPACITANCE AND INDUCTANCE</b>                     | <br><b>271</b> |
| 6-1 The Capacitor                                                     | 272            |
| 6-2 The Inductor                                                      | 279            |
| 6-3 Dynamic OP AMP Circuits                                           | 286            |
| 6-4 Equivalent Capacitance and Inductance                             | 295            |
| SUMMARY                                                               | 298            |
| PROBLEMS                                                              | 299            |
| INTEGRATING PROBLEMS                                                  | 303            |
| <br><b>CHAPTER 7 • FIRST- AND SECOND-ORDER CIRCUITS</b>               | <br><b>305</b> |
| 7-1 $RC$ and $RL$ Circuits                                            | 306            |
| 7-2 First-Order Circuit Step Response                                 | 314            |
| 7-3 Initial and Final Conditions                                      | 323            |
| 7-4 First-Order Circuit Response to Exponential and Sinusoidal Inputs | 330            |
| 7-5 The Series $RLC$ Circuit                                          | 337            |
| 7-6 The Parallel $RLC$ Circuit                                        | 347            |
| 7-7 Second-Order Circuit Step Response                                | 353            |
| SUMMARY                                                               | 364            |

|                                                       |     |
|-------------------------------------------------------|-----|
| PROBLEMS                                              | 364 |
| INTEGRATING PROBLEMS                                  | 371 |
| <b>CHAPTER 8 • SINUSOIDAL STEADY-STATE RESPONSE</b>   | 375 |
| 8-1 Sinusoids and Phasors                             | 376 |
| 8-2 Phasor Circuit Analysis                           | 381 |
| 8-3 Basic Circuit Analysis with Phasors               | 386 |
| 8-4 Circuit Theorems with Phasors                     | 403 |
| 8-5 General Circuit Analysis with Phasors             | 413 |
| 8-6 Energy and Power                                  | 424 |
| SUMMARY                                               | 429 |
| PROBLEMS                                              | 430 |
| INTEGRATING PROBLEMS                                  | 436 |
| <b>CHAPTER 9 • LAPLACE TRANSFORMS</b>                 | 439 |
| 9-1 Signal Waveforms and Transforms                   | 440 |
| 9-2 Basic Properties and Pairs                        | 444 |
| 9-3 Pole-Zero Diagrams                                | 452 |
| 9-4 Inverse Laplace Transforms:<br>Classical Approach | 458 |
| 9-5 Inverse Laplace Transforms:<br>Software Approach  | 467 |
| 9-6 Circuit Response Using Laplace<br>Transforms      | 469 |
| 9-7 Initial Value and Final Value Properties          | 477 |
| SUMMARY                                               | 479 |
| PROBLEMS                                              | 480 |
| INTEGRATING PROBLEMS                                  | 484 |
| <b>CHAPTER 10 • s-DOMAIN CIRCUIT ANALYSIS</b>         | 485 |
| 10-1 Transformed Circuits                             | 486 |
| 10-2 Basic Circuit Analysis in the $s$ Domain         | 495 |
| 10-3 Circuit Theorems in the $s$ Domain               | 500 |
| 10-4 Node-Voltage Analysis in the $s$ Domain          | 508 |
| 10-5 Mesh-Current Analysis in the $s$ Domain          | 520 |
| 10-6 Summary of $s$ -Domain Circuit Analysis          | 526 |
| SUMMARY                                               | 531 |
| PROBLEMS                                              | 531 |
| INTEGRATING PROBLEMS                                  | 538 |
| <b>CHAPTER 11 • NETWORK FUNCTIONS</b>                 | 539 |
| 11-1 Definition of a Network Function                 | 540 |
| 11-2 Network Functions of One- and Two-Port Circuits  | 543 |

|                                                                |     |
|----------------------------------------------------------------|-----|
| 11-3 Network Functions and Impulse Response                    | 555 |
| 11-4 Network Functions and Step Response                       | 558 |
| 11-5 Network Functions and Sinusoidal<br>Steady-State Response | 564 |
| 11-6 Impulse Response and Convolution                          | 569 |
| 11-7 Network Function Design                                   | 575 |
| SUMMARY                                                        | 591 |
| PROBLEMS                                                       | 592 |
| INTEGRATING PROBLEMS                                           | 597 |
| <br>CHAPTER 12 • FREQUENCY RESPONSE                            | 599 |
| 12-1 Frequency-Response Descriptors                            | 600 |
| 12-2 Bode Diagrams                                             | 601 |
| 12-3 First-Order Low-Pass and High-Pass<br>Responses           | 604 |
| 12-4 Bandpass and Bandstop Responses                           | 617 |
| 12-5 The Frequency Response of <i>RLC</i> Circuits             | 625 |
| 12-6 Bode Diagrams with Real Poles and Zeros                   | 635 |
| 12-7 Bode Diagrams with Complex Poles and Zeros                | 646 |
| 12-8 Frequency Response and Step Response                      | 652 |
| SUMMARY                                                        | 658 |
| PROBLEMS                                                       | 658 |
| INTEGRATING PROBLEMS                                           | 665 |
| <br>CHAPTER 13 • FOURIER ANALYSIS                              | 667 |
| 13-1 Overview of Fourier Analysis                              | 668 |
| 13-2 Fourier Coefficients                                      | 669 |
| 13-3 Waveform Symmetries                                       | 678 |
| 13-4 Circuit Analysis Using the Fourier Series                 | 681 |
| 13-5 RMS Value and Average Power                               | 688 |
| 13-6 Fourier Transforms                                        | 691 |
| 13-7 Circuit Analysis Using Fourier Transforms                 | 706 |
| 13-8 Impulse Response and Convolution                          | 709 |
| 13-9 Parseval's Theorem                                        | 712 |
| SUMMARY                                                        | 720 |
| PROBLEMS                                                       | 720 |
| INTEGRATING PROBLEMS                                           | 726 |
| <br>CHAPTER 14 • ACTIVE FILTER DESIGN                          | 728 |
| 14-1 Active Filters                                            | 729 |
| 14-2 Second-Order Low-Pass and High-Pass Filters               | 730 |
| 14-3 Second-Order Bandpass and Bandstop Filters                | 740 |
| 14-4 Low-Pass Filter Design                                    | 746 |

|                                                            |         |
|------------------------------------------------------------|---------|
| 14-5 Low-Pass Filter Evaluation                            | 764     |
| 14-6 High-Pass Filter Design                               | 768     |
| 14-7 Bandpass and Bandstop Filter Design                   | 778     |
| SUMMARY                                                    | 782     |
| PROBLEMS                                                   | 783     |
| INTEGRATING PROBLEMS                                       | 787     |
| <br><b>CHAPTER 15 • MUTUAL INDUCTANCE AND TRANSFORMERS</b> | <br>789 |
| 15-1 Coupled Inductors                                     | 790     |
| 15-2 The Dot Convention                                    | 792     |
| 15-3 Energy Analysis                                       | 795     |
| 15-4 The Ideal Transformer                                 | 796     |
| 15-5 Linear Transformers                                   | 802     |
| 15-6 Transformer Equivalent Circuits                       | 807     |
| SUMMARY                                                    | 810     |
| PROBLEMS                                                   | 810     |
| INTEGRATING PROBLEMS                                       | 814     |
| <br><b>CHAPTER 16 • AC POWER SYSTEMS</b>                   | <br>815 |
| 16-1 Average and Reactive Power                            | 816     |
| 16-2 Complex Power                                         | 818     |
| 16-3 Single-Phase Circuit Analysis                         | 821     |
| 16-4 Single-Phase Power Flow                               | 825     |
| 16-5 Balanced Three-Phase Circuits                         | 830     |
| 16-6 Three-Phase Circuit Analysis                          | 836     |
| 16-7 Three-Phase Power Flow                                | 845     |
| SUMMARY                                                    | 849     |
| PROBLEMS                                                   | 850     |
| INTEGRATING PROBLEMS                                       | 855     |
| <br><b>CHAPTER 17 • TWO-PORT NETWORKS (ON WEB)</b>         | <br>W-1 |
| 17-1 Introduction                                          | W-2     |
| 17-2 Impedance Parameters                                  | W-3     |
| 17-3 Admittance Parameters                                 | W-5     |
| 17-4 Hybrid Parameters                                     | W-7     |
| 17-5 Transmission Parameters                               | W-9     |
| 17-6 Two-Port Conversions and Connections                  | W-12    |
| SUMMARY                                                    | W-15    |
| PROBLEMS                                                   | W-16    |
| INTEGRATING PROBLEMS                                       | W-18    |

|                                                  |      |
|--------------------------------------------------|------|
| APPENDIX A — COMPLEX NUMBERS                     | A-1  |
| APPENDIX B — COMPUTATIONAL TOOLS                 | A-5  |
| ANSWERS TO SELECTED PROBLEMS                     | A-9  |
| PHOTO CREDITS                                    | PC-1 |
| INDEX                                            | I-1  |
| WEB APPENDIX A — SOLUTION OF LINEAR EQUATIONS    | W-19 |
| WEB APPENDIX B — BUTTERWORTH AND CHEBYCHEV POLES | W-27 |