

ELECTRONICS

BASIC, ANALOG, AND DIGITAL

with PSpice®

μ_e

τ_F

N_D^+

N_A^-

NASSIR H. SABAH



CRC Press
Taylor & Francis Group

Contents

Preface.....	xxi
Introduction	xxv
Convention for Symbols.....	xxxiii
1. Basic Diode Circuits	1
Learning Objectives	1
1.1 Ideal and Practical Diodes	2
Ideal Diode	2
Ideal Si <i>pn</i> Junction Diode	2
Practical Diodes	3
Incremental Diode Resistance	4
1.2 Basic Analysis of Diode Circuits	5
Piecewise Linear Approximation	5
Bias Point	6
Small-Signal Model	6
1.3 Rectifier Circuits	10
Half-Wave Rectifier	10
Full-Wave Rectifier	11
Smoothing of Output	14
Capacitor-Input Filter	14
Approximate Analysis of Capacitor-Input Filter	16
1.4 Zener Voltage Regulator	24
Voltage-Current Characteristic	24
Analysis of Zener Regulator	25
Load Regulation and Line Regulation	28
1.5 Diode Voltage Limiters	32
Surge Protection	36
1.6 Diode-Capacitor Circuits	36
dc Restorer	36
Voltage Multiplication	41
Summary of Main Concepts and Results	42
Learning Outcomes	43
Supplementary Examples and Topics on Website	43
Problems and Exercises	44
2. Basic Principles of Semiconductors	55
Learning Objectives	55
2.1 Excerpts from Wave Mechanics	56
Some Basic Ideas	56
Schrödinger's Equation	58
Wave Packets	59
Free Atoms	64
Energy Band Structure	64
2.2 Electric Conduction in Semiconductors	66

	Electrons in a Periodic Potential	66
	Effective Mass	68
	Hole Conduction	69
	Density of Electron States	71
	Fermi–Dirac Distribution	73
2.3	Intrinsic and Extrinsic Semiconductors.....	74
	Crystal Structure.....	74
	Intrinsic Semiconductor.....	75
	Extrinsic Semiconductors	77
2.4	Electrochemical Potential	79
	Expression for Chemical Potential.....	79
	Expression for Electrochemical Potential.....	81
	Generalized Ohm’s Law.....	82
	State of Equilibrium	83
	Fermi Level and Electrochemical Potential	84
2.5	Carrier Concentrations in Semiconductors	85
	Carrier Generation and Recombination.....	87
	Intrinsic Semiconductor.....	88
	Position of Fermi Level	89
	<i>n</i> -Type Semiconductor.....	89
	<i>p</i> -Type Semiconductor.....	90
2.6	Carrier Mobility	94
	Variation with Dopant Concentration	94
	Variation with Temperature.....	95
2.7	Carrier Recombination	95
	Minority Carrier Lifetime.....	97
	Summary of Main Concepts and Results.....	98
	Learning Outcomes.....	99
	Supplementary Examples and Topics on Website.....	100
	Problems and Exercises.....	101
3.	<i>pn</i> Junction and Semiconductor Diodes.....	105
	Learning Objectives	105
3.1	The <i>pn</i> Junction at Equilibrium	106
	Junction Potential	106
	Depletion Approximation	107
3.2	The Biased <i>pn</i> Junction	112
	The <i>pn</i> Junction as a Rectifier.....	112
	Width of Depletion Region.....	113
	Charge Distributions and Currents under Bias	113
	Current–Voltage Relation.....	117
	Charge–Current Relation	118
	<i>pn</i> Junction Capacitances	118
	Temperature Effects	120
	Junction Breakdown.....	121
3.3	Semiconductor Photoelectric Devices.....	124
	Photoconductive Cell.....	124
	Photodiode	125

	Photocell	126
3.4	Light-Emitting Diodes	128
3.5	Tunnel Diode	131
3.6	Contacts between Dissimilar Materials	134
	Metal–Metal Contacts	135
	Metal–Semiconductor Contacts	136
	Schottky Diode	139
3.7	Heterojunction	139
	Summary of Main Concepts and Results	143
	Learning Outcomes	144
	Supplementary Examples and Topics on Website	144
	Problems and Exercises	145
4.	Semiconductor Fabrication	149
	Learning Objectives	149
4.1	Preparation of Silicon Wafer	150
	High-Purity Silicon	150
	Crystal Growth	150
	Wafer Production	151
	Oxidation	151
4.2	Patterning Processes	152
	Preparation of Masks	152
	Lithography	153
	Etching	156
4.3	Deposition Processes	157
	Ion Implantation	157
	Diffusion	157
	Chemical Vapor Deposition	158
	Metallization	158
	Clean Room Environment	159
4.4	Packaging	160
	Package Types	160
4.5	Fabrication of Simple Devices	161
	Resistors	161
	pn Junction Diodes	162
	Capacitors	163
4.6	CMOS Fabrication	163
	Transistor Isolation	163
	Transistor Formation	164
	Silicon-on-Insulator Technology	168
4.7	Fabrication of Bipolar Junction Transistors	169
	Basic BJT Structure	169
	Modified BJT Structures	170
	BiCMOS	171
4.8	Miscellaneous Topics	172
	SiGe Technology	172
	Crystal Defects	173
	Si–SiO ₂ Interface	174

Summary of Main Concepts and Results	175
Learning Outcomes.....	176
Supplementary Examples and Topics on Website.....	177
Problems and Exercises.....	177
5. Field-Effect Transistors	179
Learning Objectives	179
5.1 Amplifiers.....	180
Hypothetical Amplifying Device	181
5.2 Basic Operation of the MOSFET	183
Structure	183
Operation of Enhancement-Type MOSFETs	184
Current-Voltage Relations.....	187
<i>p</i> -Channel MOS Transistor	190
Small-Signal Operation.....	191
5.3 Secondary Effects in MOSFETs	196
Channel-Length Modulation	196
Transconductance.....	199
Overdrive Voltage.....	201
Temperature Effects	201
Breakdown	201
Body Effect	202
Capacitances.....	205
Unity-Gain Bandwidth	207
Short-Channel Effects	209
Carrier Velocity Saturation and Hot Carriers.....	210
Reduced Output Resistance and Threshold.....	211
Other Effects	211
Improved Performance.....	212
5.4 Depletion-Type MOSFETs	214
Diode Connection.....	217
5.5 Complementary MOSFETs	218
CMOS Amplifier.....	219
CMOS Transmission Gate.....	222
CMOS Inverter.....	225
5.6 Junction Field-Effect Transistor	225
Structure	225
Operation.....	226
Current-Voltage Relation.....	228
5.7 Metal-Semiconductor Field-Effect Transistor	232
Structure	233
Operation.....	233
High-Mobility Devices.....	234
Summary of Main Concepts and Results	235
Learning Outcomes.....	235
Supplementary Examples and Topics on CD.....	236
Problems and Exercises.....	236

6. Bipolar Junction Transistor	241
Learning Objectives	241
6.1 Basic Operation of the BJT	242
Common-Base dc Current Gains	245
Typical Structure	246
Common-Emitter Configuration.....	247
Small-Signal Current Gains	250
Small-Signal Equivalent Circuits.....	254
6.2 Secondary Effects in BJTs.....	256
Base-Width Modulation	256
Hybrid- π Equivalent Circuit	260
Variation of i_C with v_{be}	265
h -Parameter Equivalent Circuit.....	265
Temperature Effects	265
Breakdown	266
Punchthrough	268
BJT Capacitances	268
Unity-Gain Bandwidth	271
6.3 BJT Large-Signal Models.....	275
Ebers–Moll Model	275
Saturation Mode.....	278
The BJT as a Switch	281
Diode Connection.....	282
Regenerative Pair	282
Augmented Models	284
6.4 Heterojunction Bipolar Transistor	284
6.5 Noise in Semiconductors.....	286
6.6 Comparison of BJTs and FETs	287
Summary of Main Concepts.....	288
Learning Outcomes.....	288
Supplementary Examples and Topics on Website.....	289
Problems and Exercises.....	289
7. Two-Port Circuits, Amplifiers, and Feedback	295
Learning Objectives	295
7.1 Two-Port Circuits	296
Interpretation of Parameters.....	296
Equivalent Circuits.....	298
7.2 Ideal Amplifiers.....	298
7.3 Negative Feedback.....	300
Series–Shunt Feedback	301
Signal-Flow Diagrams	303
Series–Series Feedback	305
Shunt–Series Feedback	307
Shunt–Shunt Feedback.....	308
7.4 Ideal Operational Amplifier	310
Noninverting Configuration.....	311

Unity-Gain amplifier.....	313
Inverting Configuration	314
Integrator.....	317
Differentiator.....	318
Extraneous Signals	321
Gain-Bandwidth Product	322
Summary of Main Concepts and Results	325
Learning Outcomes.....	326
Supplementary Topics and Examples on Website.....	326
Problems and Exercises.....	326
8. Single-Stage Transistor Amplifiers	335
Learning Objectives	335
8.1 Transistor Biasing.....	336
Biasing of Discrete Transistors	336
Current Mirror.....	341
BJT Current Mirror.....	341
MOSFET Current Mirror.....	344
8.2 Basic Amplifier Configurations.....	346
General Considerations	346
Common-Emitter Amplifier.....	348
Common-Source Amplifier.....	350
Common-Drain Amplifier.....	350
Common-Collector Amplifier.....	353
Common-Source Amplifier with Source Resistor	356
Common-Emitter Amplifier with Emitter Resistor.....	358
Common-Gate Amplifier	361
Common-Base Amplifier.....	363
8.3 High-Frequency Response	368
Miller's Theorem	368
Poles and Zeros of Transfer Function	369
Common Emitter/Source Amplifier.....	370
Common Collector/Drain Amplifier.....	373
Common-Emitter/Source Amplifier with Feedback Resistor.....	375
Common-Base/Gate Amplifier	376
8.4 Composite Transistor Connections.....	379
Darlington Pair	379
Common Collector-Common Emitter Cascade	381
Cascode Amplifier.....	384
MOSFET Cascode.....	384
BJT Cascode.....	386
BiCMOS Cascode	389
8.5 Cascode Current Sources and Mirrors.....	391
Summary of Main Concepts and Results	392
Learning Outcomes.....	393
Supplementary Examples and Topics on Website.....	393
Problems and Exercises.....	394

9. Multistage and Feedback Amplifiers	405
Learning Objectives	405
9.1 Cascaded Amplifiers.....	406
dc Level Shifting.....	409
9.2 RC-Coupled Amplifiers.....	411
Common-Source Amplifier.....	411
Common-Emitter Amplifier.....	413
9.3 Feedback Amplifiers	416
Series–Shunt Feedback	417
Series–Series Feedback	424
Shunt–Series Feedback	428
Shunt–Shunt Feedback	433
9.4 Closed-Loop Stability	436
Stability from Bode Magnitude Plots.....	438
Frequency Compensation	441
Feedback Oscillators	445
Wien-Bridge Oscillator	445
High-Q Oscillator	446
9.5 Tuned Amplifiers	448
9.6 LC Oscillators.....	451
9.7 Crystal Oscillators.....	456
Summary of Main Concepts and Results	457
Learning Outcomes.....	458
Supplementary Examples and Topics on Website.....	458
Problems and Exercises.....	459
10. Differential and Operational Amplifiers	467
Learning Objectives	467
10.1 Differential Pair	468
Basic Operation.....	468
Transfer Characteristic.....	470
Small-Signal Differential Operation	471
High-Frequency Response	472
Small-Signal Common-Mode Response.....	472
High-Frequency Response	474
Input Bias Currents.....	476
Input Offset Voltage	476
Current-Mirror Load.....	478
MOSFET Differential Pair	483
10.2 Two-Stage CMOS Op Amp	486
Input-Offset Voltage	486
Voltage Gain and Output Swing	487
Common-Mode Response.....	488
Frequency Response	488
Slew Rate	491
10.3 Folded Cascode CMOS Op Amp.....	492
Common-Mode Input Range	492

	Output Voltage Swing.....	494
	Voltage Gain	494
	Frequency Response	495
	Slew Rate	495
10.4	CMOS Current and Voltage Biasing.....	498
	Self-Biasing.....	498
10.5	BJT Op Amps.....	501
	Input Resistance and Bias Current	502
	Input Offset Voltage	503
10.6	Some Basic Practical Op-Amp Circuits.....	507
	Inverting and Noninverting Op-amp Circuits.....	507
	Integrator	509
	Difference Amplifier	511
	Instrumentation Amplifier	514
10.7	Switched-Capacitor Circuits	516
10.8	Digital-Analog Conversion	519
	Summary of Main Concepts and Results.....	522
	Learning Outcomes.....	523
	Supplementary Examples and Topics on Website.....	523
	Problems and Exercises.....	524
11.	Power Amplifiers and Switches.....	531
	Learning Objectives	531
11.1	General Considerations	532
	Safe Operating Limits.....	532
	Thermal Resistance	533
	Thermal Stability	535
	Nonlinear Distortion.....	536
	Power-Conversion Efficiency	537
11.2	Class A Operation	539
	Transformer Coupling.....	542
	Emitter Follower.....	543
11.3	Class B Operation.....	545
11.4	Class AB Operation.....	546
11.5	Class C Operation	549
11.6	Power Operational Amplifiers	550
11.7	Power Switching.....	552
	Class D Amplifier.....	552
	Switched Regulated Supplies	553
	dc-to-ac Converters	556
11.8	Power Diodes.....	560
11.9	Power Transistors.....	563
	Bipolar Junction Transistors	563
	MOSFETs.....	567
	Insulated Gate Bipolar Transistors (IGBTs).....	569
11.10	Power Latches.....	572
	Thyristor	572
	Summary of Main Concepts and Results.....	577

Learning Outcomes.....	578
Supplementary Examples and Topics and on Website.....	578
Problems and Exercises.....	579
12. Basic Elements of Digital Circuits.....	587
Learning Objectives.....	587
12.1 Digital Signals and Processing.....	588
Digital Signals.....	588
Boolean Algebra.....	590
12.2 Logic Gates.....	592
Gate Types.....	592
CMOS Gate Examples.....	595
Gate Performance.....	596
12.3 Flip-Flops.....	602
Basic Latch.....	602
SR Latch.....	604
JK Flip-Flop.....	606
D Flip-Flop.....	608
12.4 Digital System Memories.....	611
Classification of Semiconductor Memories.....	612
Organization of RAM.....	613
12.5 Read/Write Memory.....	614
Static Memory Cell.....	614
Dynamic Memory Cell.....	616
Sense Amplifier and Precharge Circuit.....	617
Row Decoder.....	620
Column Decoder.....	622
12.6 Read Only Memory.....	623
Mask ROM.....	623
Programmable ROM.....	625
Erasable Programmable ROM.....	626
Flash ROM.....	627
12.7 Ferroelectric RAM.....	631
12.8 Metallic Interconnect.....	632
Capacitance.....	632
Resistance.....	632
Distributed Models.....	633
Summary of Main Concepts and Results.....	636
Learning Outcomes.....	637
Supplementary Examples and Topics on Website.....	637
Problems and Exercises.....	637
13. Digital Logic Circuit Families.....	647
Learning Objectives.....	647
13.1 CMOS.....	648
CMOS Inverter.....	648
Static Behavior.....	648
Noise Margins.....	651

Propagation Delay.....	653
Power Dissipation.....	655
CMOS Gates.....	657
NAND and NOR Gates.....	657
CMOS Gate Design.....	659
Effects of Sizing and Scaling.....	661
Low-Power CMOS.....	663
Summary.....	663
13.2 Pseudo NMOS.....	664
Static Operation.....	665
Dynamic Operation.....	667
13.3 Pass-Transistor Logic.....	668
13.4 Dynamic Logic.....	674
Basic Configuration.....	674
Limitations of Dynamic Logic.....	675
Domino Logic.....	676
Pipelined Single-Phase Clock Architecture.....	677
13.5 BiCMOS Logic.....	678
Basic Operation.....	678
Propagation Delay.....	680
BiCMOS Gates.....	680
13.6 Transistor-Transistor Logic.....	682
Basic TTL Inverter.....	682
Advanced Low-Power Schottky TTL.....	685
13.7 Emitter-Coupled Logic.....	686
Basic Circuit.....	686
ECL 100k.....	687
ECL Gates.....	691
Summary of Main Concepts and Results.....	693
Learning Outcomes.....	694
Supplementary Examples and Topics on Website.....	694
Problems and Exercises.....	694
Appendix A: Reference Material.....	703
Appendix B: Basic PSpice Models.....	705
References and Bibliography.....	709
Index.....	711