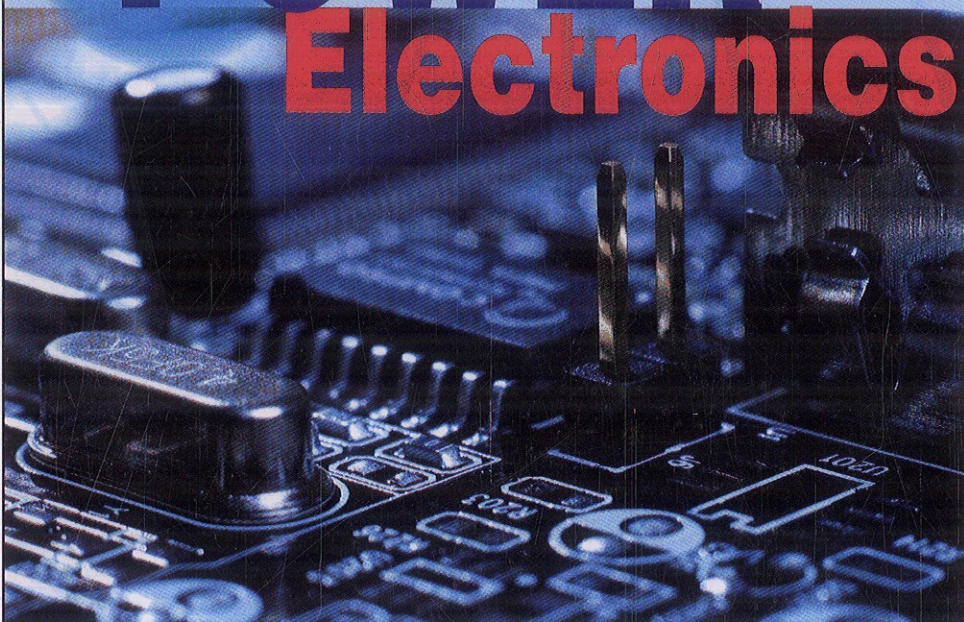


POWER **Electronics**



Daniel W. Hart

McGRAW-HILL INTERNATIONAL EDITION



Chapter 1

Introduction 1

- 1.1** Power Electronics 1
- 1.2** Converter Classification 1
- 1.3** Power Electronics Concepts 3
- 1.4** Electronic Switches 5
 - The Diode* 6
 - Thyristors* 7
 - Transistors* 8
- 1.5** Switch Selection 11
- 1.6** Spice, PSpice, and Capture 13
- 1.7** Switches in Pspice 14
 - The Voltage-Controlled Switch* 14
 - Transistors* 16
 - Diodes* 17
 - Thyristors (SCRs)* 18
 - Convergence Problems in PSpice* 18
- 1.8** Bibliography 19
- Problems 20

Chapter 2

Power Computations 21

- 2.1** Introduction 21
- 2.2** Power and Energy 21
 - Instantaneous Power* 21
 - Energy* 22
 - Average Power* 22
- 2.3** Inductors and Capacitors 25
- 2.4** Energy Recovery 27

- 2.5** Effective Values: RMS 34

- 2.6** Apparent Power and Power Factor 42

Apparent Power S 42

Power Factor 43

- 2.7** Power Computations for Sinusoidal AC Circuits 43

- 2.8** Power Computations for Nonsinusoidal Periodic Waveforms 44

Fourier Series 45

Average Power 46

Nonsinusoidal Source and

Linear Load 46

Sinusoidal Source and Nonlinear

Load 48

- 2.9** Power Computations Using PSpice 51

- 2.10** Summary 58

- 2.11** Bibliography 59
- Problems 59

Chapter 3

Half-Wave Rectifiers 65

- 3.1** Introduction 65

- 3.2** Resistive Load 65

Creating a DC Component

Using an Electronic Switch 65

- 3.3** Resistive-Inductive Load 67

- 3.4** PSpice Simulation 72

Using Simulation Software for

Numerical Computations 72

- 3.5 RL-Source Load 75**
 - Supplying Power to a DC Source from an AC Source 75*
- 3.6 Inductor-Source Load 79**
 - Using Inductance to Limit Current 79*
- 3.7 The Freewheeling Diode 81**
 - Creating a DC Current 81*
 - Reducing Load Current Harmonics 86*
- 3.8 Half-Wave Rectifier With a Capacitor Filter 88**
 - Creating a DC Voltage from an AC Source 88*
- 3.9 The Controlled Half-Wave Rectifier 94**
 - Resistive Load 94*
 - RL Load 96*
 - RL-Source Load 98*
- 3.10 PSpice Solutions For Controlled Rectifiers 100**
 - Modeling the SCR in PSpice 100*
- 3.11 Commutation 103**
 - The Effect of Source Inductance 103*
- 3.12 Summary 105**
- 3.13 Bibliography 106**
 - Problems 106
- Capacitance Output Filter 122*
- Voltage Doublers 125*
- LC Filtered Output 126*
- 4.3 Controlled Full-Wave Rectifiers 131**
 - Resistive Load 131*
 - RL Load, Discontinuous Current 133*
 - RL Load, Continuous Current 135*
 - PSpice Simulation of Controlled Full-Wave Rectifiers 139*
 - Controlled Rectifier with RL-Source Load 140*
 - Controlled Single-Phase Converter Operating as an Inverter 142*
- 4.4 Three-Phase Rectifiers 144**
- 4.5 Controlled Three-Phase Rectifiers 149**
 - Twelve-Pulse Rectifiers 151*
 - The Three-Phase Converter Operating as an Inverter 154*
- 4.6 DC Power Transmission 156**
- 4.7 Commutation: The Effect of Source Inductance 160**
 - Single-Phase Bridge Rectifier 160*
 - Three-Phase Rectifier 162*
- 4.8 Summary 163**
- 4.9 Bibliography 164**
 - Problems 164

Chapter 4

Full-Wave Rectifiers 111

- 4.1 Introduction 111**
- 4.2 Single-Phase Full-Wave Rectifiers 111**
 - The Bridge Rectifier 111*
 - The Center-Tapped Transformer Rectifier 114*
 - Resistive Load 115*
 - RL Load 115*
 - Source Harmonics 118*
 - PSpice Simulation 119*
 - RL-Source Load 120*

Chapter 5

AC Voltage Controllers 171

- 5.1 Introduction 171**
- 5.2 The Single-Phase AC Voltage Controller 171**
 - Basic Operation 171*
 - Single-Phase Controller with a Resistive Load 173*
 - Single-Phase Controller with an RL Load 177*
 - PSpice Simulation of Single-Phase AC Voltage Controllers 180*

- 5.3** Three-Phase Voltage Controllers 183
 - Y-Connected Resistive Load* 183
 - Y-Connected RL Load* 187
 - Delta-Connected Resistive Load* 189
- 5.4** Induction Motor Speed Control 191
- 5.5** Static VAR Control 191
- 5.6** Summary 192
- 5.7** Bibliography 193
 - Problems 193

Chapter 6

DC-DC Converters 196

- 6.1** Linear Voltage Regulators 196
- 6.2** A Basic Switching Converter 197
- 6.3** The Buck (Step-Down) Converter 198
 - Voltage and Current Relationships* 198
 - Output Voltage Ripple* 204
 - Capacitor Resistance—The Effect on Ripple Voltage* 206
 - Synchronous Rectification for the Buck Converter* 207
- 6.4** Design Considerations 207
- 6.5** The Boost Converter 211
 - Voltage and Current Relationships* 211
 - Output Voltage Ripple* 215
 - Inductor Resistance* 218
- 6.6** The Buck-Boost Converter 221
 - Voltage and Current Relationships* 221
 - Output Voltage Ripple* 225
- 6.7** The Ćuk Converter 226
- 6.8** The Single-Ended Primary Inductance Converter (SEPIC) 231
- 6.9** Interleaved Converters 237
- 6.10** Nonideal Switches and Converter Performance 239
 - Switch Voltage Drops* 239
 - Switching Losses* 240

- 6.11** Discontinuous-Current Operation 241
 - Buck Converter with Discontinuous Current* 241
 - Boost Converter with Discontinuous Current* 244
- 6.12** Switched-Capacitor Converters 247
 - The Step-Up Switched-Capacitor Converter* 247
 - The Inverting Switched-Capacitor Converter* 249
 - The Step-Down Switched-Capacitor Converter* 250
- 6.13** PSpice Simulation of DC-DC Converters 251
 - A Switched PSpice Model* 252
 - An Averaged Circuit Model* 254
- 6.14** Summary 259
- 6.15** Bibliography 259
 - Problems 260

Chapter 7

DC Power Supplies 265

- 7.1** Introduction 265
- 7.2** Transformer Models 265
- 7.3** The Flyback Converter 267
 - Continuous-Current Mode* 267
 - Discontinuous-Current Mode in the Flyback Converter* 275
 - Summary of Flyback Converter Operation* 277
- 7.4** The Forward Converter 277
 - Summary of Forward Converter Operation* 283
- 7.5** The Double-Ended (Two-Switch) Forward Converter 285
- 7.6** The Push-Pull Converter 287
 - Summary of Push-Pull Operation* 290
- 7.7** Full-Bridge and Half-Bridge DC-DC Converters 291

- 7.8 Current-Fed Converters 294
 - 7.9 Multiple Outputs 297
 - 7.10 Converter Selection 298
 - 7.11 Power Factor Correction 299
 - 7.12 PSpice Simulation of DC Power Supplies 301
 - 7.13 Power Supply Control 302
 - Control Loop Stability* 303
 - Small-Signal Analysis* 304
 - Switch Transfer Function* 305
 - Filter Transfer Function* 306
 - Pulse-Width Modulation Transfer Function* 307
 - Type 2 Error Amplifier with Compensation* 308
 - Design of a Type 2 Compensated Error Amplifier* 311
 - PSpice Simulation of Feedback Control* 315
 - Type 3 Error Amplifier with Compensation* 317
 - Design of a Type 3 Compensated Error Amplifier* 318
 - Manual Placement of Poles and Zeros in the Type 3 Amplifier* 323
 - 7.14 PWM Control Circuits 323
 - 7.15 The AC Line Filter 323
 - 7.16 The Complete DC Power Supply 325
 - 7.17 Bibliography 326
 - Problems 327
- Chapter 8**
- Inverters 331**
- 8.1 Introduction 331
 - 8.2 The Full-Bridge Converter 331
 - 8.3 The Square-Wave Inverter 333
 - 8.4 Fourier Series Analysis 337
 - 8.5 Total Harmonic Distortion 339
 - 8.6 PSpice Simulation of Square Wave Inverters 340
 - 8.7 Amplitude and Harmonic Control 342
 - 8.8 The Half-Bridge Inverter 346
 - 8.9 Multilevel Inverters 348
 - Multilevel Converters with Independent DC Sources* 349
 - Equalizing Average Source Power with Pattern Swapping* 353
 - Diode-Clamped Multilevel Inverters* 354
 - 8.10 Pulse-Width-Modulated Output 357
 - Bipolar Switching* 357
 - Unipolar Switching* 358
 - 8.11 PWM Definitions and Considerations 359
 - 8.12 PWM Harmonics 361
 - Bipolar Switching* 361
 - Unipolar Switching* 365
 - 8.13 Class D Audio Amplifiers 366
 - 8.14 Simulation of Pulse-Width-Modulated Inverters 367
 - Bipolar PWM* 367
 - Unipolar PWM* 370
 - 8.15 Three-Phase Inverters 373
 - The Six-Step Inverter* 373
 - PWM Three-Phase Inverters* 376
 - Multilevel Three-Phase Inverters* 378
 - 8.16 PSpice Simulation of Three-Phase Inverters 378
 - Six-Step Three-Phase Inverters* 378
 - PWM Three-Phase Inverters* 378
 - 8.17 Induction Motor Speed Control 379
 - 8.18 Summary 382
 - 8.19 Bibliography 383
 - Problems 383

Chapter 9**Resonant Converters 387**

- 9.1** Introduction 387
- 9.2** A Resonant Switch Converter:
Zero-Current Switching 387
 - Basic Operation* 387
 - Output Voltage* 392
- 9.3** A Resonant Switch Converter:
Zero-Voltage Switching 394
 - Basic Operation* 394
 - Output Voltage* 399
- 9.4** The Series Resonant Inverter 401
 - Switching Losses* 403
 - Amplitude Control* 404
- 9.5** The Series Resonant
DC-DC Converter 407
 - Basic Operation* 407
 - Operation for $\omega_s > \omega_o$* 407
 - Operation for $\omega_o/2 < \omega_s < \omega_o$* 413
 - Operation for $\omega_s < \omega_o/2$* 413
 - Variations on the Series Resonant DC-DC Converter* 414
- 9.6** The Parallel Resonant
DC-DC Converter 415
- 9.7** The Series-Parallel DC-DC
Converter 418
- 9.8** Resonant Converter Comparison 421
- 9.9** The Resonant DC Link Converter 422
- 9.10** Summary 426
- 9.11** Bibliography 426
 - Problems 427

Chapter 10**Drive Circuits, Snubber Circuits,
and Heat Sinks 431**

- 10.1** Introduction 431
- 10.2** MOSFET and IGBT Drive
Circuits 431
 - Low-Side Drivers* 431
 - High-Side Drivers* 433
- 10.3** Bipolar Transistor Drive
Circuits 437
- 10.4** Thyristor Drive Circuits 440
- 10.5** Transistor Snubber Circuits 441
- 10.6** Energy Recovery Snubber
Circuits 450
- 10.7** Thyristor Snubber Circuits 450
- 10.8** Heat Sinks and Thermal
Management 451
 - Steady-State Temperatures* 451
 - Time-Varying Temperatures* 454
- 10.9** Summary 457
- 10.10** Bibliography 457
 - Problems 458

**Appendix A Fourier Series for Some
Common Waveforms 461****Appendix B State-Space Averaging 467****Index 473**