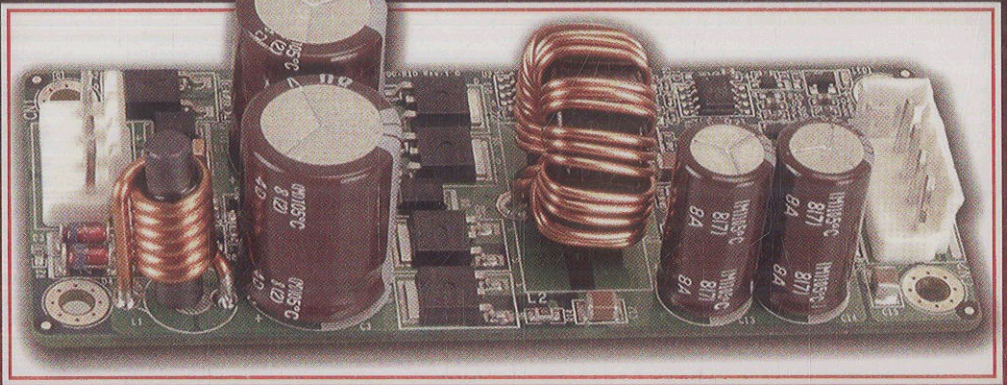


THIRD EDITION

POWER-SWITCHING CONVERTERS



SIMON ANG
ALEJANDRO OLIVA



CRC Press
Taylor & Francis Group

Contents

List of Figures	xiii
List of Tables	xxxix
Preface	xxxix
1 Introduction to Switching Converters	1
1.1 Introduction	1
1.1.1 Industry trends	1
1.2 Linear converter	3
1.2.1 Linear series-pass regulator	3
1.2.2 Linear shunt regulator	5
1.3 Switching converters	6
1.3.1 Basic switching converter with resistive load	7
1.3.2 Basic switching converter with RL load	9
1.4 Principles of steady-state converter analysis	12
1.4.1 Inductor volt-second balance	12
1.4.2 Capacitor charge balance	13
1.5 Problems	14
2 Basic Switching Converter Topologies	15
2.1 Introduction	15
2.2 Buck converter	16
2.2.1 Continuous mode	16
2.2.2 Discontinuous mode	21
2.3 Synchronous rectifier	28
2.4 Ripple steering	29
2.5 Boost converter	31
2.5.1 Continuous mode	32
2.5.2 Discontinuous mode	39
2.6 Buck-boost converter	44
2.6.1 Continuous mode	46
2.6.2 Discontinuous mode	49
2.7 Cuk converter	53
2.8 SEPIC converter	60
2.8.1 Continuous conduction mode	61
2.8.2 Design considerations	63

2.9	Zeta converter	64
2.10	Converter realization with nonideal components	66
2.10.1	Inductor model	67
2.10.2	Capacitor model	67
2.10.3	Semiconductor losses	69
2.10.4	Effect of semiconductor losses on the output voltage	70
2.11	Problems	72
3	Resonant Converters	75
3.1	Introduction	75
3.2	Parallel resonant circuit — A review	76
3.3	Series resonant circuit — A review	77
3.4	Classification of quasi-resonant switches	80
3.5	Zero-current-switching quasi-resonant buck converter	83
3.6	Zero-current-switching quasi-resonant boost converter	93
3.7	Zero-voltage-switching quasi-resonant buck converter	100
3.8	Zero-voltage-switching quasi-resonant boost converter	106
3.9	Series-loaded resonant converter	113
3.9.1	Discontinuous mode ($0 < f_s < 0.5f_n$)	114
3.9.2	Continuous mode ($f_s > f_n$ or above-resonant mode)	117
3.9.3	Continuous mode ($0.5f_n < f_s < f_n$ or below-resonant mode)	118
3.10	Parallel-loaded resonant converter	122
3.10.1	Discontinuous mode ($0 < f < 0.5f_n$)	123
3.10.2	Continuous mode ($f_s > f_2$ or above-resonant mode)	127
3.10.3	Continuous mode ($0.5f_n < f_s < f_n$ or below-resonant mode)	129
3.11	Problems	132
4	Isolated Switching Converters	135
4.1	Introduction	135
4.2	Forward converter	136
4.3	Two-switch forward converter	141
4.4	Push-pull converter	144
4.5	Half-bridge switching converter	148
4.6	Full-bridge switching converter	151
4.7	Flyback converter	153
4.8	Two-switch flyback converter	158
4.9	Dual active bridge converter	159
4.9.1	Power flow control	172
4.10	Zero-current-switching quasi-resonant half-bridge converter	175
4.11	Problems	181

5	Control Schemes of Switching Converters	183
5.1	Introduction	183
5.2	Pulse-width modulation	183
5.2.1	Voltage-mode PWM scheme	184
5.2.2	Current-mode PWM scheme	191
5.2.2.1	Instability for $D > 50\%$	191
5.2.2.2	Compensation with external ramp	193
5.3	Hysteresis control: switching current source	194
5.3.1	Steady-state analysis during t_{on}	196
5.4	Commercial integrated circuit controllers	199
5.4.1	Fixed-frequency voltage-mode SG3524 controller	199
5.4.2	Variable-frequency voltage-mode TL497 controller	202
5.4.3	Fixed-frequency current-mode UC3842 PWM controller	203
5.4.4	TinySwitch-II family of low power off-line switchers	208
5.5	Control schemes for resonant converters	211
5.5.1	Off-line controllers for resonant converters	213
5.5.2	L6598 operation	213
5.6	Problems	227
6	Continuous-Time Modeling of Switching Converters	229
6.1	Introduction	229
6.2	Switching converter analysis using classical control techniques	230
6.2.1	Basic linear model of the open-loop switching converter	230
6.2.2	PWM modulator model	231
6.2.3	Averaged switching converter models	237
6.2.4	Output filter model	241
6.3	Summary of small-signal models of switching converters	253
6.4	Linear model of the voltage regulator including external perturbances	258
6.4.1	Output impedance and stability	259
6.5	State-space representation of switching converters	260
6.5.1	Review of linear system analysis	260
6.5.2	State-space averaging	264
6.6	Switching converter transfer functions	285
6.6.1	Source-to-state transfer functions	285
6.7	Input EMI filters	289
6.7.1	Stability considerations	290
6.8	Problems	299
7	Analog Control of Switching Converters	301
7.1	Introduction	301
7.2	Review of negative feedback using classical-control techniques	301
7.2.1	Closed-loop gain	301
7.2.2	Stability analysis	302

7.2.3	Relative stability	302
7.3	Linear model of the closed-loop switching converter	304
7.3.1	Feedback network	304
7.3.2	Error amplifier compensation networks	304
7.3.3	PI compensation network	306
7.3.4	PID compensation network	309
7.3.5	Proportional control	314
7.4	Feedback compensation in a buck converter with output capacitor ESR	314
7.5	Feedback compensation in a buck converter with no output capacitor ESR	318
7.6	Complete state feedback	320
7.6.1	Design of a control system with complete state feedback	320
7.6.2	Pole selection	322
7.6.3	Feedback gains	322
7.7	Problems	327
8	Discrete-Time Modeling of Switching Converters	329
8.1	Introduction	329
8.2	Continuous-time systems	329
8.3	Direct discrete model	330
8.4	Linear direct discrete model	331
8.5	Continuous-time averaged state-space model	332
8.6	Averaged discrete-time model of the switching converter	335
8.7	Problems	338
9	Digital Control of Switching Converters	339
9.1	Introduction	339
9.2	Proportional controller	340
9.3	Digital redesign of a PID controller	340
9.4	Design of a discrete control system with complete state feedback	342
9.4.1	Pole selection	343
9.4.2	Feedback gains	344
9.4.3	Voltage mode control	344
9.4.4	Current mode control	347
9.5	Problems	351
10	Interleaved Converters	353
10.1	Introduction	353
10.2	Interleaved buck converter	353
10.2.1	State-space averaged model	354
10.3	Interleaved boost converter	356
10.3.1	State-space averaged model	358
10.4	Interleaved converter operation based on current mode	363

10.4.1	Ripple calculations	363
10.4.2	Number of converters	366
10.5	Power factor correction	366
10.6	Problems	369
11	Switched Capacitor Converters	371
11.1	Introduction	371
11.2	Unidirectional power flow SCC	371
11.2.1	Basic step-up converter	371
11.2.2	Basic step-down converter	372
11.2.3	Basic inverting converter	375
11.3	Alternative switched capacitor converter topologies	378
11.3.1	Step-down converter	378
11.3.2	Step-up converter	382
11.3.3	n-Stage step-down SCC	384
11.3.4	n-Stage step-up SCC	385
11.4	Bi-directional power flow SCC	386
11.4.1	Step-up step-down converter	387
11.4.2	Luo converter	390
11.5	Resonant converters	395
11.5.1	Zero-current switching	396
11.6	Losses on switched-capacitor power converters	398
11.7	Problems	401
12	Simulation of Switching Converters	403
12.1	Introduction	403
12.2	SPICE [®] circuit representation	403
12.2.1	PSPICE simulations using .CIR	405
12.2.2	PSPICE simulations using schematics entry	417
12.2.3	Small-signal analysis of switching converters	432
12.2.4	Creating capture symbols for PSPICE simulation	452
12.2.5	Solving convergence problems	452
12.3	Switching converter simulation using MATLAB [®]	457
12.3.1	Working with transfer functions	458
12.3.2	Working with matrices	461
12.4	Switching converter simulation using Simulink [®]	463
12.4.1	Transfer function example using Simulink [®]	463
12.4.2	State-space example using Simulink [®]	466
12.5	Problems	466
13	Applications of Switching Converters	469
13.1	Power factor correction	469
13.1.1	Introduction	469
13.1.2	Review of basic concepts	469
13.1.3	Principle of power factor correction	471

13.1.4	Self-power factor correction properties of switching converters	472
13.1.4.1	Buck converter	472
13.1.4.2	Boost converter	474
13.1.4.3	Buck-boost converter	474
13.1.4.4	Flyback converter	477
13.1.5	Control techniques for power factor correctors	477
13.1.5.1	Peak current mode control (PCM)	477
13.1.5.2	Average current mode control	479
13.1.5.3	Hysteresis control	479
13.1.5.4	Borderline or boundary control	481
13.1.5.5	Discontinuous current PWM control	482
13.1.6	Power factor correction circuits	484
13.2	Low noise DC-DC converters	487
13.2.1	Introduction	487
13.2.2	Techniques to reduce EMI	489
13.2.2.1	Capacitive coupling	489
13.2.2.2	Inductive coupling	489
13.2.2.3	Input filtering	489
13.2.2.4	Output Filtering	489
13.2.2.5	Slew rate limiting	490
13.3	Switching converters for solar cells	492
13.3.1	Introduction	492
13.3.2	Solar cell model	493
13.3.3	Maximum-power point tracking	495
13.3.4	Switching converters for solar cells	495
13.4	Switching converters for fuel cells	497
13.5	Switching converters for LED drivers	501
13.5.1	Buck-based LED drivers	502
13.5.2	Boost-based LED drivers	502
13.5.3	C _{uk} -based LED drivers	503
13.5.4	SEPIC-based LED drivers	504
13.5.5	LED drivers for AC input	504
14	Switching Converter Design Case Studies	505
14.1	Introduction	505
14.2	Voltage-mode discontinuous-conduction-mode buck converter design	506
14.2.1	Controller design	508
14.2.2	Small-signal model	511
14.2.3	Design of the compensation network and error amplifier	511
14.2.4	The closed-loop buck converter	516
14.2.5	Simulation results	517
14.2.6	Experimental results	517
14.3	Digital control of a voltage-mode synchronous buck converter	527

14.3.1	Circuit parameters	528
14.3.2	Closed-loop pole selection	528
14.3.3	Discrete-time model	530
14.3.4	Feedback gains	531
14.3.5	Control strategy	533
14.3.6	Analog model for PSPICE simulations	533
14.3.7	Simulation results	536
14.3.8	Sensitivity of the closed-loop poles	536
14.3.9	Experimental results	538
14.4	Digital control of a current-mode synchronous buck converter	540
14.4.1	Continuous-time state model	540
14.4.2	Obtaining the discrete-time model	541
14.4.3	Current-mode instability	542
14.4.4	Extended-state model for a tracking regulator	542
14.4.5	Feedback gains	543
14.4.6	Control strategy	545
14.4.7	Simulation results	546
14.4.8	Sensitivity of the closed-loop poles	546
14.4.9	Experimental results	546
14.4.10	DSP program	549
14.5	UC3842-based flyback design	556
14.5.1	Design specifications	557
14.5.2	Discontinuous conduction mode	557
14.5.3	Preliminary calculations	558
14.5.4	Open-loop simulations	559
14.5.5	Current-loop	561
14.5.6	Voltage loop	561
14.5.7	Small-signal model	565
14.5.8	Frequency compensation	566
14.5.9	EMI filter design	569
14.5.10	Printed circuit board design	573
14.5.11	Experimental results	575
14.6	TOPSwitch-based flyback design	576
14.6.1	Design specifications	576
14.6.2	Preliminary calculations	578
14.6.3	Experimental results	579
14.7	TinySwitch-based flyback design	581
14.7.1	Experimental results	581
14.8	Switching audio amplifier	585
14.8.1	Case study	589

Bibliography **599**

Index **613**