

# Contents

<b>1</b>	<b>ELEMENTS OF ELECTRIC DRIVE SYSTEMS</b>	<b>1</b>
1.1	Historical Background	2
1.2	Basic Components of an Electric Drive System	5
1.2.1	Mechanical Loads	6
1.2.2	Electric Motors	8
1.2.3	Power Sources	9
1.2.4	Converters	9
1.2.5	Controllers	10
<b>2</b>	<b>INTRODUCTION TO SOLID-STATE DEVICES</b>	<b>12</b>
2.1	Transistors	13
2.1.1	Bipolar Transistor	13
2.1.2	Field Effect Transistor (FET)	16
2.2	Thyristors	18
2.2.1	Four-Layer Diode	18
2.2.2	Silicon-Controlled Rectifier (SCR)	19
2.3	Other Power Devices	22
2.3.1	Darlington Transistor	22
2.3.2	Insulated Gate Bipolar Transistor (IGBT)	23
2.4	Ratings of Power Electronic Devices	24
2.5	$di/dt$ and $dv/dt$ Protection	26
	Chapter 2 Problems	30
<b>3</b>	<b>INTRODUCTION TO SOLID-STATE SWITCHING CIRCUITS</b>	<b>31</b>
3.1	Single-Phase, Half-Wave, ac/dc Conversion for Resistive Loads	31
3.1.1	Root-Mean-Squares	34
3.1.2	Electric Power	37
3.1.3	dc Power	40
3.1.4	Power Factor	41
3.2	Single-Phase, Full-Wave, ac/dc Conversion for Resistive Loads	43

3.3	Single-Phase, Half-Wave, ac/dc Conversion for Inductive Loads Without Freewheeling Diode	46
3.3.1	Average Voltage Across Inductance and Resistance	50
3.3.2	Average Power of Inductance	51
3.3.3	RMS voltage	52
3.4	Single-Phase, Half-Wave, ac/dc Conversion for Inductive Loads with Freewheeling Diode	53
3.5	Three-Phase, Half-Wave, ac/dc Conversion for Resistive Loads	58
3.6	Three-Phase, Half-Wave, ac/dc Conversion for Inductive Loads	61
3.7	Three-Phase, Full-Wave, ac/dc Conversion	63
3.8	dc/dc Conversion	69
3.9	dc/ac Conversion	73
3.9.1	Single-Phase, dc/ac Converter	73
3.9.2	Three-Phase, dc/ac Converter	74
3.9.3	Voltage, Frequency, and Sequence Control	81
3.9.4	Pulse-Width Modulation (PWM)	84
3.10	Energy Recovery Systems	87
3.10.1	Charging Operation	88
3.10.2	Discharging Operation	92
3.11	Three-Phase Energy Recovery Systems	95
3.12	Current Source Inverter	98
	Chapter 3 Problems	101

## **4 JOINT SPEED-TORQUE CHARACTERISTICS OF ELECTRIC MOTORS AND MECHANICAL LOADS 105**

4.1	Bidirectional Electric Drive Systems	106
4.2	Four-Quadrant Electric Drive Systems	108
	Chapter 4 Problems	111

## **5 SPEED-TORQUE CHARACTERISTICS OF ELECTRIC MOTORS 112**

5.1	dc Motors	112
5.1.1	Separately Excited Motors	115
5.1.2	Shunt Motors	120
5.1.3	Series Motors	120
5.1.4	Compound Motors	123
5.2	Induction Motors	126
5.2.1	Equivalent Circuit	130

5.2.2	Power Flow	134
5.2.3	Torque Characteristics	139
5.2.4	Starting Procedure	142
5.3	Synchronous Motors	144
5.3.1	Reactive Power	147
5.3.2	Power Flow	149
5.3.3	Torque Characteristics	151
5.3.4	Starting Procedure	151
5.4	Damage to Electric Machines	152
	Chapter 5 Problems	152

## **6 SPEED CONTROL OF DIRECT CURRENT MOTORS 156**

6.1	Speed Control of Shunt or Separately Excited Motors	156
6.1.1	Controlling Speed by Adding Resistance	157
6.1.2	Controlling Speed by Adjusting Armature Voltage	160
6.1.3	Controlling Speed by Adjusting Field Voltage	161
6.1.4	Solid-State Control	165
6.2	Speed Control of Series Motor	176
6.2.1	Controlling Speed by Adding Resistance to Armature Circuit	176
6.2.2	Controlling Speed by Adjusting Armature Voltage	178
6.2.3	Controlling Speed by Adjusting Field Current	178
	Chapter 6 Problems	182

## **7 SPEED CONTROL OF INDUCTION MOTORS 189**

7.1	Basic Principles of Speed Control	189
7.2	Controlling Speed Using Rotor Resistance	190
7.3	Rotor Voltage Injection	194
7.4	Slip Energy Recovery	200
7.4.1	Controlling Speed by the Slip Energy Recovery Method	202
7.4.2	Torque–Current Relationship	203
7.4.3	Efficiency	204
7.5	Controlling Speed Using Inductance	209
7.6	Controlling Speed by Adjusting the Stator Voltage	209
7.7	Controlling Speed by Adjusting the Supply Frequency	211
7.7.1	Effect of Excessively High Frequency	212
7.7.2	Effect of Excessively Low Frequency	216
7.8	Voltage/Frequency Control	217

7.9	Current Source Speed Control	220
7.9.1	Induction Motor with Constant Frequency CSI	223
7.9.2	Induction Motor with Adjustable Frequency CSI	225
	Chapter 7 Problems	227
<b>8</b>	<b>BRAKING OF ELECTRIC MOTORS</b>	<b>231</b>
8.1	Regenerative Braking	231
8.2	Dynamic Braking	233
8.3	Countercurrent Braking	235
	Chapter 8 Problems	235
<b>9</b>	<b>BRAKING OF dc MOTORS</b>	<b>236</b>
9.1	Regenerative Braking of dc Shunt Motors	236
9.2	Regenerative Braking of dc Series Motors	243
9.3	Dynamic Braking of dc Shunt Motors	244
9.4	Dynamic Braking of dc Series Motors	247
9.5	Countercurrent Braking of dc Shunt Motors	248
	9.5.1 Plugging	248
	9.5.2 Braking by Terminal Voltage Reversal (TVR)	253
9.6	Countercurrent Braking of dc Series Motors	263
	Chapter 9 Problems	266
<b>10</b>	<b>BRAKING OF INDUCTION MOTORS</b>	<b>269</b>
10.1	Regenerative Braking	269
10.2	Dynamic Braking	275
10.3	Countercurrent Braking	277
	Chapter 10 Problems	280
<b>11</b>	<b>DYNAMICS OF ELECTRIC DRIVE SYSTEMS</b>	<b>283</b>
11.1	Moment of Inertia	284
11.2	Basic Concept of Traveling Time	286
11.3	Gears and Belts	287
11.4	Traveling Time of dc Motors	290
11.5	Traveling Time of Induction Motors	295
	11.5.1 Unloaded Induction Motor	297
	11.5.2 Loaded Induction Motor	301
11.6	Traveling Time of Synchronous Motors	303
	Chapter 11 Problems	306
	<b>INDEX</b>	<b>309</b>