

Contents

Preface	xv
1 Introduction to Modern Network Theory	1
1.1 The Pole-Zero Concept	1
1.2 Synthesis of Filters from Polynomials	7
1.2.1 Synthesis by Expansion of Driving-Point Impedance	7
1.2.2 Synthesis for Unequal Terminations	9
1.2.3 Synthesis by Equating Coefficients	10
1.3 Active versus Passive Filters	11
1.3.1 Frequency Limitations	11
1.3.2 Size Considerations	12
1.3.3 Economics and Ease of Manufacture	12
1.3.4 Ease of Adjustment	12
References	12
2 Selecting the Response Characteristic	13
2.1 Frequency-Response Normalization	13
2.1.1 Frequency and Impedance Scaling	13
2.1.2 Low-Pass Normalization	17
2.1.3 High-Pass Normalization	18
2.1.4 Band-Pass Normalization	20
2.1.5 Band-Reject Normalization	28
2.2 Transient Response	33
2.2.1 The Effect of Nonuniform Time Delay	33
2.2.2 Step Response of Networks	36
2.2.3 Impulse Response	38
2.2.4 Estimating Transient Characteristics	38
2.3 Butterworth Maximally Flat Amplitude	47
2.4 Chebyshev Response	49
2.5 Bessel Maximally Flat Delay	56
2.6 Linear Phase with Equiripple Error	58
2.7 Transitional Filters	59
2.8 Synchronously Tuned Filters	64
2.9 Elliptic-Function Filters	71
2.9.1 Using Filter Solutions (Book Version) Software for Design of Elliptic Function Low-Pass Filters	80
2.9.2 Using the ELI 1.0 Program for the Design of Odd-Order Elliptic-Function Low-Pass Filters up to the 31st Order	81
2.10 Maximally Flat Delay With Chebyshev Stopband	81
2.11 Papoulis Optimum "L" Filter	82
References	83

3	Low-Pass Filter Design	85
3.1	LC Low-Pass Filters	85
3.1.1	All-Pole Filters	85
3.1.2	Elliptic-Function Filters	86
3.1.3	Effects of Dissipation	93
3.1.4	Using Predistorted Designs	95
3.2	Active Low-Pass Filters	99
3.2.1	All-Pole Filters	99
3.2.2	VCVS Uniform Capacitor Structure	109
3.2.3	The Low-Sensitivity Second-Order Section	110
3.2.4	Elliptic-Function VCVS Filters	112
3.2.5	State-Variable Low-Pass Filters	117
3.2.6	Generalized Impedance Converters	125
3.3	Minimal Phase-Shift Filters	132
	References	133
4	High-Pass Filter Design	135
4.1	LC High-Pass Filters	135
4.1.1	The Low-Pass to High-Pass Transformation	135
4.1.2	The T-to-Pi Capacitance Conversion	139
4.2	Active High-Pass Filters	141
4.2.1	The Low-Pass to High-Pass Transformation	141
4.2.2	All-Pole High-Pass Filters	141
4.2.3	Elliptic-Function High-Pass Filters	142
4.2.4	State-Variable High-Pass Filters	148
4.2.5	High-Pass Filters Using the GIC	157
4.2.6	Active Elliptic-Function High-Pass Filters Using the GIC	158
4.2.7	Constant-Delay High-Pass Filters	159
	References	162
5	Band-Pass Filters	163
5.1	LC Band-Pass Filters	163
5.1.1	Wideband Filters	163
5.1.2	Narrowband Filters	165
5.1.3	The Design of Parallel Tuned Circuits	173
5.1.4	The Design of Series Tuned Circuits	178
5.1.5	Synchronously Tuned Filters	180
5.1.6	Narrowband Coupled Resonators	181
5.1.7	Predistorted Band-Pass Filters	188
5.1.8	Elliptic-Function Band-Pass Filters	191
5.2	Active Band-Pass Filters	198
5.2.1	Wideband Filters	198
5.2.2	The Band-Pass Transformation of Low-Pass Poles and Zeros	199
5.2.3	Sensitivity in Active Band-Pass Circuits	206
5.2.4	All-Pole Band-Pass Configurations	207
5.2.5	Elliptic-Function Band-Pass Filters	224
	References	237

6	Band-Reject Filters	239
6.1	LC Band-Reject Filters	239
6.1.1	The Band-Reject Circuit Transformation	239
6.1.2	All-Pole Band-Reject Filters	240
6.1.3	Elliptic-Function Band-Reject Filters	244
6.1.4	Null Networks	252
6.2	Active Band-Reject Filters	257
6.2.1	Wideband Active Band-Reject Filters	257
6.2.2	Band-Reject Transformation of Low-Pass Poles	259
6.2.3	Narrowband Active Band-Reject Filters	265
6.2.4	Active Null Networks	272
	References	278
7	Networks for the Time Domain	279
7.1	All-Pass Transfer Functions	279
7.1.1	First-Order All-Pass Transfer Functions	279
7.1.2	Second-Order All-Pass Transfer Functions	281
7.2	Delay Equalizer Sections	283
7.2.1	LC All-Pass Structures	283
7.2.2	Active All-Pass Structures	287
7.3	Design of All-Pass Delay Lines	292
7.3.1	The Low-Pass to All-Pass Transformation	292
7.3.2	LC Delay Lines	293
7.3.3	Active Delay Lines	297
7.4	Delay Equalization of Filters	299
7.4.1	First-Order Equalizers	300
7.4.2	Second-Order Equalizers	303
7.5	Wideband 90° Phase-Shift Networks	307
7.6	Design of Passive Delay Lines with Repetitious Elements	313
7.6.1	An All-Pass Delay Line	313
7.6.2	Image Parameter Unsymmetrical Delay Line	315
	References	316
8	Refinements in LC Filter Design and the Use of Resistive Networks	317
8.1	Introduction	317
8.2	Tapped Inductors	317
8.3	Circuit Transformations	320
8.3.1	Norton's Capacitance Transformer	320
8.3.2	Narrowband Approximations	322
8.4	Designing with Parasitic Capacitance	325
8.5	Amplitude Equalization for Inadequate Q	328
8.6	Coil-Saving Elliptic-Function Band-Pass Filters	332
8.7	Filter Tuning Methods	336
8.8	Measurement Methods	337
8.8.1	Insertion Loss and Frequency Response	337
8.8.2	Input Impedance of Filter Networks	338
8.8.3	Time-Domain Characteristics	340

8.8.4	Group Delay	341
8.8.5	Measuring the Q of Inductors	343
8.9	Designing For Unequal Impedances	344
8.9.1	Exponentially Tapered Impedance Scaling	344
8.9.2	Minimum-Loss Resistive Pad for Impedance Matching	345
8.9.3	Design of Unsymmetrical Resistive T and π Attenuators for Impedance Matching	345
8.10	Symmetrical Attenuators	348
8.10.1	Symmetrical T and π Attenuators	348
8.11	Power Splitters	350
8.11.1	Resistive Power Splitters	350
8.11.2	A Magic- T Splitter	350
8.12	Introduction of Transmission Zeros to an Existing Design	352
	References	354
9	Component Selection for LC and Active Filters	355
9.1	Review of Basic Magnetic Principles	355
9.1.1	Units of Measurement	355
9.1.2	Saturation and DC Polarization	356
9.1.3	Inductor Losses	357
9.1.4	Effect of an Air Gap	357
9.2	Magnetic Materials and Physical Form Factors of Inductors	358
9.2.1	Magnetic Materials	358
9.2.2	Magnetic Coil Structures	360
9.2.3	Surface-Mount RF Inductors	360
9.3	Capacitor Selection	362
9.3.1	Properties of Dielectrics	362
9.3.2	Capacitor Construction	363
9.3.3	Selecting Capacitors for Filter Applications	366
9.4	Resistors	372
9.4.1	Fixed Resistors	373
9.4.2	Variable Resistors	375
9.4.3	Resistor Johnson (Thermal) Noise	377
	References	378
10	Normalized Filter Design Tables	379
11	Switched-Capacitor Filters	451
11.1	Introduction	451
11.2	The Theory of Switched-Capacitor Filters	451
11.2.1	The Switched Resistor	451
11.2.2	The Basic Integrator as a Building Block	452
11.2.3	The Limitations of Switched-Capacitor Filters	453
11.3	Universal Switched-Capacitor Second-Order Filters	454
11.3.1	Modes of Operation	455
11.3.2	Operating Mode Features	455
11.3.3	Using the MF10 and LMF100 Dual Universal Second-Order Filter	459

11.4	Types of Switched-Capacitor Filters	464
11.4.1	Universal	464
11.4.2	Microprocessor-Programmable Universal Switched-Capacitor Filters	464
11.4.3	Pin-Programmable Universal Switched-Capacitor Filters	465
11.4.4	Dedicated Switched-Capacitor Filters	465
11.5	The Switched-Capacitor Filter Selection Guide	465
	References	468
12	Adjustable and Fixed Delay and Amplitude Equalizers	469
12.1	The Need for Equalization	469
12.1.1	Delay and Amplitude Equalization	469
12.2	The Equalization Process	470
12.2.1	Amplitude Equalization	470
12.2.2	Delay Equalization	472
12.3	Pole-Zero Concept Applied to Amplitude and Delay Equalizers	473
12.4	Adjustable-Delay and Amplitude Equalizer Circuits	474
12.4.1	LC Delay Equalizers	474
12.4.2	LC Delay and Amplitude Equalizers	475
12.4.3	Active Delay and Amplitude Equalizers	477
	References	483
13	Voltage Feedback Operational Amplifiers	485
13.1	Review of Basic Op-Amp Theory	485
13.1.1	The Ideal Amplifier	485
13.1.2	Inverting Amplifier	486
13.1.3	Noninverting Amplifier	488
13.1.4	Differential Input Amplifier	489
13.1.5	Differential Input and Output Amplifier	490
13.2	Analysis of Nonideal Amplifiers	490
13.2.1	Noninverting Amplifier Analysis	490
13.2.2	Inverting Amplifier Analysis	491
13.2.3	Stability	492
13.2.4	Effects of Open-Loop Gain	494
13.3	Understanding Op-Amp Specifications	495
13.3.1	Bandwidth and Gain	495
13.3.2	Phase and Gain Margin	496
13.3.3	DC Offsets	496
13.3.4	Slew-Rate Limiting	497
13.3.5	Settling Time	497
13.3.6	Common-Mode Rejection Ratio (CMRR)	498
13.3.7	Output Voltage Swing	498
13.3.8	Noise	499
13.3.9	Total Harmonic Distortion (THD)	500
13.4	Power Supply Considerations	500

13.5	Operational Amplifier Selection	503
13.5.1	Op-Amp Types	503
13.5.2	Op-Amp Packaging	503
13.5.3	Survey of Popular Amplifiers	504
13.6	General Manufacturing Considerations	508
	References	508
14	Linear Amplifier Applications	509
14.1	Resistive Feedback Networks	509
14.1.1	Adding and Subtracting Signals	509
14.1.2	The Instrumentation Amplifier	512
14.1.3	AC Coupling of Amplifiers	514
14.1.4	Bootstrapping a Voltage Follower for high input impedance	516
14.1.5	T-Network in Inverting Amplifier Feedback Loop to Reduce Resistor Values	517
14.1.6	Bootstrapped Inverting Amplifier for High Input-Impedance	518
14.2	Current-to-Voltage and Voltage-to-Current Converters	519
14.2.1	Current-to-Voltage Converter	519
14.2.2	Voltage-to-Current Converter (Current Source)	520
14.2.3	The Howland Current Pump	521
14.2.4	Current-Mode Amplifiers	524
14.3	Bridge Amplifiers	524
	References	526
15	Nonlinear Circuits	527
15.1	Ideal Rectifiers and Their Applications	527
15.1.1	Half-Wave Precision Rectifier	527
15.1.2	Full-Wave Precision Rectifier	529
15.1.3	Peak Detector	531
15.1.4	Sample and Hold Circuit	532
15.2	Automatic Gain Control	534
15.3	Log and Antilog Circuits	538
15.4	Multipliers	541
15.4.1	The Gilbert Cell	542
15.4.2	Multiplier Parameters	543
15.4.3	Multiplier Math Functions	543
15.5	Modulators	544
	References	546
16	Waveform Shaping	547
16.1	Integrators and Differentiators	547
16.1.1	The Ideal Integrator	547
16.1.2	A Practical Integrator	549
16.1.3	Differentiators	549

16.2	Comparators	551
16.2.1	Basic Comparator	551
16.2.2	Window Comparator	554
16.2.3	Hysteresis	556
16.2.4	Limiters	557
16.2.5	Time-Delay Circuits Using Comparators	558
	References	562
17	Waveform Generation	563
17.1	Sine Wave Generators	563
17.1.1	Phase Shift Oscillators	563
17.1.2	The Wien Bridge Oscillator	566
17.1.3	Multiple-Feedback Band-Pass Oscillator	568
17.2	Generating Nonsinusoidal Waveforms	569
17.2.1	Square Wave Relaxation Oscillator	569
17.2.2	Triangular Wave Relaxation Oscillator	570
17.2.3	The 555 Timer	571
17.2.4	Hex Inverter RC Oscillators	575
	References	582
18	Current Feedback Amplifiers	583
18.1	Introduction to Current Feedback Amplifiers	583
18.2	Analysis and Applications of Current Feedback Amplifiers	584
18.2.1	Models of Current Feedback Amplifier	584
18.2.2	Stability	586
18.2.3	Slew Rate of CFB Op Amps	588
18.2.4	Implementing VFB Designs Using CFB Op Amps	589
	References	591
19	Large Signal Amplifiers	593
19.1	Class D Amplifiers for Audio	593
19.1.1	Half-Bridge Topology	593
19.1.2	Full-Bridge Topology	595
19.1.3	Class D Operation Without an Output Filter	595
19.1.4	Class D LC Filter Design	597
19.2	Crossover Networks	601
19.2.1	Component Selection	602
19.3	Transformer-Coupled Line Driver Configuration	603
19.3.1	Traditional Transformer-Coupled Line Driver	603
19.3.2	Differential Transformer-Coupled Line Driver	603
19.3.3	Active Output Impedance Line Driver	605
19.4	Thermal Management	607
	References	610

xiv Contents

Appendix A	Software Download and Errata	611
A.1	Software Download	611
A.2	Installing and Using "FILTER SOLUTIONS" (Book Version) Software for Design of Elliptic Function Low-Pass Filters	611
A.3	Installing and Using "ELI 1.0" Program for Design of Odd-Order Elliptic Function Low-Pass Filters up to 31st Order	612
A.4	FLTRFORM.XLS Spreadsheet of Formulas	612
A.5	Errata	612
	Index	613