

CONTENTS

CHAPTER 1 • INTRODUCTION	1
1-1 About This Book	2
1-2 Symbols and Units	3
1-3 Circuit Variables	5
1-4 Computational Software Introduction	10
SUMMARY	11
PROBLEMS	12
INTEGRATING PROBLEMS	14
CHAPTER 2 • BASIC CIRCUIT ANALYSIS	15
2-1 Element Constraints	16
2-2 Connection Constraints	21
2-3 Combined Constraints	28
2-4 Equivalent Circuits	36
2-5 Voltage and Current Division	44
2-6 Circuit Reduction	52
2-7 Computer-Aided Circuit Analysis	56
SUMMARY	60
PROBLEMS	61
INTEGRATING PROBLEMS	70
CHAPTER 3 • CIRCUIT ANALYSIS TECHNIQUES	73
3-1 Node-Voltage Analysis	74
3-2 Mesh-Current Analysis	92
3-3 Linearity Properties	100
3-4 Thévenin and Norton Equivalent Circuits	109
3-5 Maximum Signal Transfer	122
3-6 Interface Circuit Design	125
SUMMARY	138
PROBLEMS	139
INTEGRATING PROBLEMS	151

CHAPTER 4 • ACTIVE CIRCUITS	154
4-1 Linear Dependent Sources	155
4-2 Analysis of Circuits with Dependent Sources	156
4-3 The Operational Amplifier	177
4-4 OP AMP Circuit Analysis	184
4-5 OP AMP Circuit Design	201
4-6 OP AMP Circuit Applications	208
SUMMARY	226
PROBLEMS	226
APPLICATION PROBLEMS	234
INTEGRATING PROBLEMS	236
CHAPTER 5 • SIGNAL WAVEFORMS	239
5-1 Introduction	240
5-2 The Step Waveform	241
5-3 The Exponential Waveform	246
5-4 The Sinusoidal Waveform	251
5-5 Composite Waveforms	258
5-6 Waveform Partial Descriptors	266
SUMMARY	273
PROBLEMS	274
INTEGRATING PROBLEMS	278
CHAPTER 6 • CAPACITANCE AND INDUCTANCE	280
6-1 The Capacitor	281
6-2 The Inductor	287
6-3 Dynamic OP AMP Circuits	293
6-4 Equivalent Capacitance and Inductance	301
SUMMARY	305
PROBLEMS	305
INTEGRATING PROBLEMS	310
CHAPTER 7 • FIRST- AND SECOND-ORDER CIRCUITS	313
7-1 RC and RL Circuits	314
7-2 First-Order Circuit Step Response	324
7-3 Initial and Final Conditions	332
7-4 First-Order Circuit Response to Exponential and Sinusoidal Inputs	338
7-5 The Series RLC Circuit	345
7-6 The Parallel RLC Circuit	355
7-7 Second-Order Circuit Step Response	360
SUMMARY	367
PROBLEMS	368
INTEGRATING PROBLEMS	376

CHAPTER 8 • SINUSOIDAL STEADY-STATE RESPONSE	379
8-1 Sinusoids and Phasors	380
8-2 Phasor Circuit Analysis	385
8-3 Basic Phasor Circuit Analysis and Design	391
8-4 Circuit Theorems with Phasors	406
8-5 General Circuit Analysis with Phasors	419
8-6 Energy and Power	431
SUMMARY	436
PROBLEMS	437
INTEGRATING PROBLEMS	445
CHAPTER 9 • LAPLACE TRANSFORMS	447
9-1 Signal Waveforms and Transforms	448
9-2 Basic Properties and Pairs	451
9-3 Pole-Zero Diagrams	460
9-4 Inverse Laplace Transforms	463
9-5 Circuit Response Using Laplace Transforms	473
9-6 Initial and Final Value Properties	480
SUMMARY	483
PROBLEMS	483
INTEGRATING PROBLEMS	488
CHAPTER 10 • S-DOMAIN CIRCUIT ANALYSIS	490
10-1 Transformed Circuits	491
10-2 Basic Circuit Analysis in the s Domain	501
10-3 Circuit Theorems in the s Domain	506
10-4 Node-Voltage Analysis in the s Domain	516
10-5 Mesh-Current Analysis in the s Domain	525
10-6 Summary of s -Domain Circuit Analysis	531
SUMMARY	535
PROBLEMS	536
INTEGRATING PROBLEMS	543
CHAPTER 11 • NETWORK FUNCTIONS	545
11-1 Definition of a Network Function	546
11-2 Network Functions of One- and Two-Port Circuits	549
11-3 Network Functions and Impulse Response	561
11-4 Network Functions and Step Response	564
11-5 Network Functions and Sinusoidal Steady-State Response	568
11-6 Impulse Response and Convolution	575
11-7 Network Function Design	581

SUMMARY	597
PROBLEMS	597
INTEGRATING PROBLEMS	604
CHAPTER 12 • FREQUENCY RESPONSE	606
12-1 Frequency-Response Descriptors	607
12-2 Bode Diagrams	609
12-3 First-Order Low-Pass and High-Pass Responses	611
12-4 Bandpass and Bandstop Responses	625
12-5 The Frequency Response of <i>RLC</i> Circuits	631
12-6 Bode Diagrams with Real Poles and Zeros	640
12-7 Bode Diagrams with Complex Poles and Zeros	651
12-8 Frequency Response and Step Response	656
SUMMARY	662
PROBLEMS	662
INTEGRATING PROBLEMS	671
CHAPTER 13 • FOURIER ANALYSIS	673
13-1 Overview of Fourier Analysis	674
13-2 Fourier Coefficients	675
13-3 Waveform Symmetries	684
13-4 Circuit Analysis Using the Fourier Series	686
13-5 RMS Value and Average Power	694
13-6 Fourier Transforms	697
13-7 Circuit Analysis Using Fourier Transforms	712
13-8 Impulse Response and Convolution	715
13-9 Parseval's Theorem	718
SUMMARY	725
PROBLEMS	726
INTEGRATING PROBLEMS	733
CHAPTER 14 • ACTIVE FILTER DESIGN	735
14-1 Active Filters	736
14-2 Second-Order Low-Pass and High-Pass Filters	737
14-3 Second-Order Bandpass and Bandstop Filters	748
14-4 Low-Pass Filter Design	758
14-5 Low-Pass Filter Evaluation	776
14-6 High-Pass Filter Design	780
14-7 Bandpass and Bandstop Filter Design	791
SUMMARY	795
PROBLEMS	796
INTEGRATING PROBLEMS	800

CHAPTER 15 • MUTUAL INDUCTANCE AND TRANSFORMERS	803
15-1 Coupled Inductors	804
15-2 The Dot Convention	806
15-3 Energy Analysis	808
15-4 The Ideal Transformer	810
15-5 Linear Transformers	816
SUMMARY	823
PROBLEMS	823
INTEGRATING PROBLEMS	827
CHAPTER 16 • AC POWER SYSTEMS	828
16-1 Average and Reactive Power	829
16-2 Complex Power	831
16-3 Single-Phase Circuit Analysis	834
16-4 Single-Phase Power Flow	838
16-5 Balanced Three-Phase Circuits	843
16-6 Three-Phase Circuit Analysis	849
16-7 Three-Phase Power Flow	858
SUMMARY	861
PROBLEMS	862
INTEGRATING PROBLEMS	867
CHAPTER 17 • TWO-PORT NETWORKS	868
17-1 Introduction	869
17-2 Impedance Parameters	870
17-3 Admittance Parameters	872
17-4 Hybrid Parameters	874
17-5 Transmission Parameters	876
17-6 Two-Port Conversions and Connections	879
SUMMARY	885
PROBLEMS	885
INTEGRATING PROBLEMS	888
APPENDIX A — COMPLEX NUMBERS	889
ANSWERS TO SELECTED PROBLEMS	893
INDEX	917
WEB APPENDIX A — SOLUTION OF LINEAR EQUATIONS	
WEB APPENDIX B — BUTTERWORTH AND CHEBYCHEV POLES	
WEB APPENDIX C — COMPUTATIONAL TOOLS	
WEB APPENDIX D — SOLUTIONS TO EXERCISES	