

# Table of Contents

<b>1.</b>	<b>Introduction to Electronics</b>	
Thomas L. Floyd		<b>1</b>
<b>2.</b>	<b>Diodes and Applications</b>	
Thomas L. Floyd		<b>31</b>
<b>3.</b>	<b>Special-Purpose Diodes</b>	
Thomas L. Floyd		<b>117</b>
<b>4.</b>	<b>Bipolar Junction Transistors</b>	
Thomas L. Floyd		<b>181</b>
<b>5.</b>	<b>Transistor Bias Circuits</b>	
Thomas L. Floyd		<b>237</b>
<b>6.</b>	<b>BJT Amplifiers</b>	
Thomas L. Floyd		<b>283</b>
<b>7.</b>	<b>Power Amplifiers</b>	
Thomas L. Floyd		<b>353</b>
<b>8.</b>	<b>Field-Effect Transistors (FETs)</b>	
Thomas L. Floyd		<b>399</b>
<b>9.</b>	<b>FET Amplifiers and Switching Circuits</b>	
Thomas L. Floyd		<b>467</b>
<b>10.</b>	<b>Amplifier Frequency Response</b>	
Thomas L. Floyd		<b>523</b>
<b>11.</b>	<b>Thyristors</b>	
Thomas L. Floyd		<b>583</b>
<b>12.</b>	<b>The Operational Amplifier</b>	
Thomas L. Floyd		<b>623</b>
<b>13.</b>	<b>Basic Op-Amp Circuits</b>	
Thomas L. Floyd		<b>691</b>

<b>14. Special-Purpose Op-Amp Circuits</b>	<b>743</b>
Thomas L. Floyd	
<b>15. Active Filters</b>	<b>791</b>
Thomas L. Floyd	
<b>16. Oscillators</b>	<b>835</b>
Thomas L. Floyd	
<b>17. Voltage Regulators</b>	<b>883</b>
Thomas L. Floyd	
<b>Glossary</b>	<b>923</b>
Thomas L. Floyd	
<b>Index</b>	<b>931</b>