

Contents

Preface	xi
Acknowledgments	xiii
About the Author	xv
Contributors	xvii

1 Review of Fundamentals Related to DC Power Supply Design and Linear Regulators

1.1 Introduction	1-1
1.2 Simple Unregulated DC Power Supply and Estimating the Essential Component Values	1-2
1.3 Linear Regulators.....	1-3
1.4 Low-Dropout Regulators.....	1-18

2 Switching Power Supply Topologies and Design Fundamentals

2.1 Introduction	2-1
2.2 Why Switch Modes: An Overall Approach	2-2
2.3 Basic Switch-Mode Power Supply Topologies.....	2-3
2.4 Applications and Industry-Favorite Configurations	2-33
2.5 A Few Design Examples and Guidelines	2-39

3 Power Semiconductors

3.1 Introduction	3-1
3.2 Power Diodes and Thyristors.....	3-2
3.3 Gate Turn-Off Thyristors	3-18
3.4 Bipolar Power Transistors	3-20
3.5 Power MOSFETs	3-28
3.6 Insulated Gate Bipolar Transistor (IGBT)	3-45
3.7 MOS-Controlled Thyristor (MCT).....	3-50

4 Resonant Converters and Wireless Power Supplies

4.1 Introduction	4-1
4.2 Fundamentals of Resonant Converters.....	4-1
4.3 Resonant DC-DC Converters	4-5
4.4 Load Resonant Converters for Contactless Power Supplies	4-11

5	Control Loop Design of DC-to-DC Converters	
5.1	Introduction	5-1
5.2	Feedback Control and Frequency Response	5-1
5.3	Poles, Zeros, and S-Domain	5-2
5.4	Stability Using Bode Plots	5-3
5.5	Linear Regulators' Feedback and Loop Stability	5-4
5.6	Stability	5-11
5.7	Feedback Loop and Stability of Switch-Mode Power Supplies	5-19
5.8	Digital Control	5-27
5.9	Control Modes of Switch-Mode Converters	5-33
6	Power Management	
6.1	Introduction	6-1
6.2	Design Approaches and Specifications	6-1
6.3	Specifying DC Power Supply Requirements	6-13
6.4	Loading Considerations	6-18
6.5	Powering High-Power Processors and ASICs	6-20
7	Off-the-Line Switching Power Supplies	
7.1	Introduction	7-1
7.2	Building Blocks of a Typical Off-the-Line Switching Power Supply	7-1
7.3	Rectifier Section	7-2
7.4	Popular Transformer-Isolated Configurations for Off-the-Line Power Supplies and Industry Approaches	7-7
7.5	Magnetic Components	7-11
7.6	Output Blocks	7-18
7.7	Efficiency Improvements and Synchronous Rectification	7-21
7.8	EMI Reduction	7-25
7.9	Power Supply Protection	7-28
7.10	Age-Related Aspects	7-35
7.11	Testing of Power Supplies	7-36
8	Rechargeable Batteries and Their Management	
8.1	Introduction	8-1
8.2	Battery Terminology	8-2
8.3	Battery Technologies: An Overview	8-5
8.4	Lead-Acid Batteries	8-8
8.5	Nickel Cadmium (NiCd) Batteries	8-13
8.6	Nickel Metal Hydride Batteries	8-16
8.7	Lithium-Based Rechargeable Batteries	8-18
8.8	Reusable Alkaline Batteries	8-22
8.9	Zn-Air Batteries	8-24
8.10	Battery Management	8-25
8.11	Battery Communication and Related Standards	8-47
8.12	Battery Safety	8-49
8.13	Future	8-51

9	Protection of Systems from Surges and Transients	
9.1	Introduction	9-1
9.2	Types of Disturbances and Power Quality Issues.....	9-2
9.3	Principles of Surge Protection Techniques.....	9-9
9.4	Surge Protection Standards and Practices.....	9-16
9.5	Practical Design Considerations.....	9-26
Appendix A		AppendixA-1
Appendix B		AppendixB-1
Index		Index-1