

CONTENTS

Foreword	xiii
Preface	xv
1 Introduction to Wireless Circuit Design	1
1.1 Introduction / 1	
1.2 System Functions / 3	
1.3 The Radio Channel and Modulation Requirements / 5	
1.3.1 Introduction / 5	
1.3.2 Channel Impulse Response / 7	
1.3.3 Doppler Effect / 12	
1.3.4 Transfer Function / 13	
1.3.5 Time Response of Channel Impulse Response and Transfer Function / 14	
1.3.6 Lessons Learned / 16	
1.3.7 Wireless Signal Example: The TDMA System in GSM / 17	
1.3.8 From GSM to UMTS to LTE / 28	
1.4 About Bits, Symbols, and Waveforms / 29	
1.4.1 Introduction / 29	
1.4.2 Some Fundamentals of Digital Modulation Techniques / 37	
1.5 Analysis of Wireless Systems / 50	
1.5.1 Analog and Digital Receiver Designs / 50	
1.5.2 Transmitters / 57	
1.6 Building Blocks / 78	
1.7 System Specifications and Their Relationship to Circuit Design / 79	
1.7.1 System Noise and Noise Floor / 80	
1.7.2 System Amplitude and Phase Behavior / 89	
1.8 Testing / 108	
1.8.1 Introduction / 108	
1.8.2 Transmission and Reception Quality / 112	
1.8.3 Base Station Simulation / 113	
1.8.4 GSM / 122	
1.8.5 DECT / 122	
1.9 Converting C/N or SNR to E_B/N_0 / 123	
References / 124	
Further Reading / 125	

2 Models for Active Devices**127**

- 2.1 Diodes / 128
 - 2.1.1 Large-Signal Diode Model / 129
 - 2.1.2 Mixer and Detector Diodes / 133
 - 2.1.3 PIN Diodes / 141
 - 2.1.4 Tuning Diodes / 158
- 2.2 Bipolar Transistors / 203
 - 2.2.1 Transistor Structure Types / 203
 - 2.2.2 Large-Signal Behavior of Bipolar Transistors / 204
 - 2.2.3 Large-Signal Transistors in the Forward-Active Region / 218
 - 2.2.4 Improving RF Performance by Means of Heterostructures / 225
 - 2.2.5 Effects of Collector Voltage on Large-Signal Characteristics in the Forward-Active Region of BJTs / 226
 - 2.2.6 Effects of Collector Current and Voltage on Large-Signal Characteristics in the Forward-Active Region of HBTs / 229
 - 2.2.7 Saturation and Inverse Active Regions / 231
 - 2.2.8 Self-Heating / 236
 - 2.2.9 Small-Signal Models of Bipolar Transistors / 239
- 2.3 Field-Effect Transistors / 239
- 2.4 Large-Signal Behavior of JFETs / 248
 - 2.4.1 Small-Signal Behavior of JFETs / 251
 - 2.4.2 Large-Signal Behavior of MOSFETs / 256
 - 2.4.3 Small-Signal Model of the MOS Transistor in Saturation / 263
 - 2.4.4 Short-Channel Effects in FETs / 267
 - 2.4.5 Small-Signal Models of MOSFETs / 272
 - 2.4.6 III-V MESFETs and HEMTs / 289
 - 2.4.7 Small-Signal GaAs MESFET and HEMT Model / 298
- 2.5 Parameter Extraction of Active Devices / 324
 - 2.5.1 Introduction / 324
 - 2.5.2 Typical SPICE Parameters / 324
 - 2.5.3 Noise Modeling / 326
 - 2.5.4 Scalable Device Models / 334
 - 2.5.5 Generating a Databank for Parameter Extraction / 334
 - 2.5.6 Conclusions / 345
 - 2.5.7 Device Libraries / 347
 - 2.5.8 Physics-Based MESFET Modeling / 348
 - 2.5.9 Example: Improving the BFR193W Model / 351
- References / 355
- Further Reading / 357

3 Amplifier Design with BJTs and FETs**359**

- 3.1 Properties of Amplifiers / 359
 - 3.1.1 Introduction / 359
 - 3.1.2 Gain / 364
 - 3.1.3 Noise Figure (NF) / 369
 - 3.1.4 Linearity / 397
 - 3.1.5 AGC / 413
 - 3.1.6 Bias and Power Voltage and Current (Power Consumption) / 417

3.2	Amplifier Gain, Stability, and Matching / 423
3.2.1	Scattering Parameter Relationships / 423
3.2.2	Low-Noise Amplifiers / 429
3.2.3	High-Gain Amplifiers / 467
3.2.4	Low-Voltage Open-Collector Design / 476
3.3	Single-Stage Feedback Amplifiers / 484
3.3.1	Lossless or Noiseless Feedback / 489
3.3.2	Broadband Matching / 490
3.4	Two-Stage Amplifiers / 490
3.5	Amplifiers with Three or More Stages / 499
3.5.1	Stability of Multistage Amplifiers / 504
3.6	A Novel Approach to Voltage-Controlled Tuned Filters Including CAD Validation / 505
3.6.1	Diode Performance / 505
3.6.2	A VHF Example / 508
3.6.3	An HF/VHF Voltage-Controlled Filter / 508
3.6.4	Improving the VHF Filter / 513
3.6.5	Conclusion / 514
3.7	Differential Amplifiers / 514
3.8	Frequency Doublers / 518
3.9	Multistage Amplifiers with Automatic Gain Control (AGC) / 524
3.10	Biasing / 524
3.10.1	RF Biasing / 535
3.10.2	dc Biasing / 535
3.10.3	dc Biasing of IC-Type Amplifiers / 539
3.11	Push-Pull/Parallel Amplifiers / 539
3.12	Power Amplifiers / 542
3.12.1	Example 1: 7-W Class C BJT Amplifier for 1.6 GHz / 552
3.12.2	Example: A Highly Efficient 3.5 GHz Inverse Class-F GaN HEMT Power Amplifier / 565
3.12.3	Linear Amplifier Systems / 575
3.12.4	Impedance Matching Networks Applied to RF Power Transistors / 585
3.12.5	Example 2: Low-Noise Amplifier Using Distributed Elements / 606
3.12.6	Example 3: 1-W Amplifier Using the CLY15 / 612
3.12.7	Example 4: 90-W Push-Pull BJT Amplifier at 430 MHz / 617
3.12.8	Quasiparallel Transistors for Improved Linearity / 621
3.12.9	Distribution Amplifiers / 622
3.12.10	Stability Analysis of a Power Amplifier / 623
	References / 631
	Further Reading / 635

4 Mixer Design

637

4.1	Introduction / 637
4.2	Properties of Mixers / 640
4.2.1	Conversion Gain/Loss / 640
4.2.2	Noise Figure / 642

4.2.3	Linearity / 650
4.2.4	LO Drive Level / 652
4.2.5	Interport Isolation / 652
4.2.6	Port VSWR / 652
4.2.7	dc Offset / 654
4.2.8	dc Polarity / 654
4.2.9	Power Consumption / 654
4.3	Diode Mixers / 654
4.3.1	Single-Diode Mixer / 655
4.3.2	Single-Balanced Mixer / 664
4.3.3	Diode-Ring Mixer / 666
4.4	Transistor Mixers / 685
4.4.1	BJT Gilbert Cell / 686
4.4.2	BJT Gilbert Cell with Feedback / 689
4.4.3	FET Mixers / 697
4.4.4	MOSFET Gilbert Cell / 700
4.4.5	GaAsFET Single-Gate Switch—Resistive Mixer / 701
	References / 725
	Further Reading / 726

5 RF/Wireless Oscillators

727

5.1	Introduction of Frequency Control / 727
5.2	Background / 727
5.3	Oscillator Design / 728
5.3.1	Basics of Oscillators / 730
5.4	Oscillator Circuits / 744
5.4.1	Hartley / 744
5.4.2	Colpitts / 745
5.4.3	Clapp—Gouriet / 745
5.5	Design of RF Oscillators / 746
5.5.1	General Thoughts on Transistor Oscillators / 746
5.5.2	Two-Port Microwave/RF Oscillator Design / 749
5.5.3	Ceramic-Resonator Oscillators / 754
5.5.4	Using a Microstrip Inductor as the Oscillator Resonator / 757
5.5.5	Hartley Microstrip Resonator Oscillator / 763
5.5.6	Crystal Oscillators / 763
5.5.7	Voltage-Controlled Oscillators / 768
5.5.8	Diode-Tuned Resonant Circuits / 770
5.5.9	Practical Circuits / 775
5.6	Noise in Oscillators / 781
5.6.1	Linear Approach to the Calculation of Oscillator Phase Noise / 781
5.6.2	Phase-Noise Analysis Based on the Feedback Model / 789
5.6.3	AM-to-PM Conversion / 792
5.6.4	Numerically Optimized Oscillators / 800
5.7	Oscillators in Practice / 803
5.7.1	Oscillator Specifications / 803
5.7.2	More Practical Circuits / 808

5.8	Phase-Noise Improvements of Integrated RF and Millimeterwave Oscillators / 814
5.8.1	Abstract / 814
5.8.2	Review of Noise Analysis / 815
5.8.3	Workarounds / 818
5.8.4	Reduction of Flicker Noise / 819
5.8.5	Applications to Integrated Oscillators / 820
5.8.6	Summary / 826
	References / 826
	Interesting Patents / 828
	Further Reading / 828

6 Wireless Synthesizers 831

6.1	Introduction / 831
6.2	Phase-Locked Loops / 831
6.2.1	PLL Basics / 831
6.2.2	Phase-Frequency Comparators / 834
6.2.3	Filters for Phase Detectors Providing Voltage Output / 845
6.2.4	Charge-Pump-Based Phase-Locked Loops / 850
6.3	How to Do a Practical PLL Design Using CAD / 859
6.4	Fractional- <i>N</i> -Division PLL Synthesis / 864
6.4.1	The Fractional- <i>N</i> Principle / 864
6.4.2	Spur-Suppression Techniques / 866
6.5	Direct Digital Synthesis / 871
	References / 879
	Interesting Patents / 880
	Further Reading / 881

Index 883