

# Contents

*Preface*

xv

<b>1</b>	<b>Introduction</b>	<b>1</b>
1.1	Why Energy Conversion Electronics Circuits?	1
1.1.1	Applications in the Information and Telecommunication Industry	2
1.1.2	Applications in Renewable Energy Conversion	4
1.1.3	Future Energy Conversion – Fuel Cells	6
1.1.4	Electric Vehicles	6
1.1.5	Applications in Electronic Display Devices	8
1.1.6	Audio Amplifiers	9
1.1.7	Applications in Portable Electronic Devices	9
1.1.8	Applications in High Voltage Physics Experiments and Atomic Accelerators	10
1.1.9	Lighting Technology	11
1.1.10	Aerospace Applications	11
1.1.11	Power System Conditioning	12
1.1.12	Energy Recycling in Manufacturing Industry	12
1.1.13	Applications in Space Exploration	12
1.1.14	Defense Applications	14
1.1.15	Drives and High-Power Industrial Applications	15
1.1.16	Classification of Power Electronic Circuits	15
1.2	Basic Principles of Operation of a Power Electronics Circuit	17
1.3	Basic Components of the Power Circuit: Power Semiconductor Switches and Passive Reactive Elements	28
1.3.1	Uncontrollable Switches – Power Diodes	28
1.3.2	Semicontrollable Switches (Thyristors)	32
1.3.3	Controllable Switches	35
1.3.3.1	Bipolar Junction Transistor (BJT)	35
1.3.3.2	Power Metal Oxide Semiconductor Field-Effect Transistor (MOSFET)	38
1.3.3.3	Insulated Gate Bipolar Transistor (IGBT)	47
1.3.4	Gallium Nitride (GaN) Switch Technology	51
1.3.5	Energy Losses Associated with Power Switches	52
1.3.5.1	Switching Losses	52
1.3.5.2	Off-State Leakage Power Loss	54

1.3.5.3	Conduction Power Loss	56
1.3.5.4	Gate Drive Power Loss	56
1.3.5.5	Heat Sinks	56
1.3.5.6	Outline for Choosing a Transistor	57
1.3.6	Passive Reactive Elements	65
1.3.6.1	Capacitors	65
1.3.6.2	Inductors, Transformers, Coupled Inductors	72
1.3.7	Ultracapacitors	80
1.4	Basic Steady-State Analysis of Duty Cycle Controlled Converters with Constant Switching Frequency	81
1.4.1	Input-to-Output Voltage Ratio for Basic DC-DC Converters	81
1.4.2	Continuous and Discontinuous Conduction Operation Modes	85
1.4.3	Design of the Elements of the Basic Converters	85
1.4.4	Controller for Duty Cycle Control (PWM)	88
1.4.5	Conversion Efficiency, Hard-switching and Soft-switching	92
1.5	Introduction to Switched-Capacitor (SC) Converters	96
1.6	Frequency-Controlled Converters	101
1.6.1	Resonant Converters	101
1.6.2	Quasi-Resonant Converters (QRC)	110
1.7	Overview on AC-DC Rectifiers and DC-AC Inverters	119
1.7.1	Rectifiers	119
1.7.2	Inverters	132
1.8	Case Studies	140
1.8.1	Case Study 1	140
1.8.2	Case Study 2	146
1.8.3	Case Study 3	150
1.9	Highlights of the Chapter	154
	Problems	155
	Bibliography	157
<b>2</b>	<b>Modeling DC-DC Converters</b>	<b>161</b>
2.1	What is the Purpose of Modeling the Power Stage?	162
2.2	Average State-Space Equations, Small-Ripple Approximation (Time-Linearization)	164
2.3	DC Voltage Gain and AC Small-Signal Open-Loop Transfer Functions Based on Average State-Space Equations for Converters Operating in Continuous Conduction Mode	169
2.3.1	DC Voltage Gain and AC Open-Loop Line-to-Load Voltage Transfer Function	169
2.3.2	Duty Cycle-to-Output Voltage AC Transfer Function. Small-Signal Approximation	171
2.3.3	DC Gain and AC Small-Signal Open-Loop Transfer Functions of the Boost, Buck and Buck-Boost Converters Operating in CCM	173
2.3.3.1	Boost Converter	173
2.3.3.2	Buck Converter	182
2.3.3.3	Buck-Boost Converter	187
2.3.4*	Graphical Averaged Models of the Boost, Buck and Buck-Boost Converters Operating in CCM	191
2.3.4.1	Boost Converter	191

2.3.4.2	Buck Converter	203
2.3.4.3	Buck-Boost Converter	207
2.3.5*	Canonical Graphical Averaged Models of DC-DC Converters Operating in CCM	211
2.4	DC Voltage Gain and AC Small-Signal Open-Loop Transfer Functions Based on Average State-Space Equations for Converters Operating in Discontinuous Conduction Mode	217
2.4.1	Reduced-Order Averaged Models	217
2.4.1.1	Boost Converter	218
2.4.1.2	Buck-boost converter	226
2.4.1.3	Buck Converter	229
2.4.1.4*	An Alternative Way for Obtaining First-Order Average State-Space Equations for Converters Operating in DCM by Neglecting the Dynamics of the Inductor Current	235
2.4.2*	Full-Order Averaged Models	237
2.4.2.1	Average State-Space Equations Without Neglecting the Inductor Current Dynamics	237
2.4.2.2	Average State-Space Equations Without Neglecting the Inductor Current Dynamics and Without Neglecting the Parasitic Resistances in the Inductor Charging Process	239
2.4.2.3	Full-Order Small-Signal Transfer Functions for Converters Operating in DCM	241
2.5*	Average PWM Switch Model	253
2.5.1	Average PWM Switch Model for Converters Operating in Continuous Conduction Mode	253
2.5.2	Average PWM Switch Model for Converters Operating in Discontinuous Conduction Mode	263
2.5.2.1	DC Analysis of the Boost Converter in DCM	270
2.5.2.2	Small-Signal Analysis of the Boost Converter in DCM	271
2.5.2.3	DC Analysis of the Buck Converter in DCM	279
2.5.2.4	Small-Signal Analysis of the Buck Converter in DCM	280
2.5.2.5	DC Analysis of the Buck-Boost Converter in DCM	284
2.5.2.6	Small-Signal Analysis of the Buck-Boost Converter in DCM	285
2.6	Average Model of the Switches Resistances and Diode Forward Voltage. Average Model of the PWM	288
2.6.1	Average Model of the Switches DC Resistances and Diode Forward Voltage	288
2.6.2	Average Model of the PWM	291
2.7*	Average Resonant Switch Model for the DC and Small-Signal Analysis of QRC Converters	292
2.7.1	Average Model of the Zero-Current (ZC) Resonant Switch	293
2.7.2	Average Model of the Zero-Voltage (ZV) Resonant Switch	300
2.7.3	DC Analysis and Open-Loop Small-Signal Transfer Functions of ZCS Quasi-Resonant Converters	305
2.7.3.1	ZCS QR Buck Converter	305
2.7.3.2	ZCS QR Boost Converter	310
2.7.3.3	ZCS QR Buck-Boost Converter	318

2.7.4	DC Analysis and Open-Loop Small-Signal Transfer Functions of ZVS Quasi-Resonant Converters	325
2.7.4.1	ZVS QR Buck Converter	325
2.7.4.2	ZVS QR Boost Converter	331
2.7.4.3	ZVS QR Buck-Boost Converter	337
2.8	Simulation and Computer-Aided Design of Power Electronics Circuits	339
2.9	Case Study	355
2.10	Highlights of the Chapter	362
	Problems	365
	Bibliography	368
<b>3</b>	<b>Classical DC-DC PWM Hard-switching Converters</b>	<b>369</b>
3.1	Buck DC-DC PWM Hard-switching Converter	369
3.1.1	Influence of the DC Resistance of the Inductor	369
3.1.2	Boundary Control	375
3.1.3	Calculation of Losses in a Buck Converter Operating in CCM by Considering the Inductor Current Ripple and the ESR of the Capacitor	377
3.1.4	Design of a Buck Converter in CCM Operation	382
3.1.4.1	Design Example	385
3.1.5	Buck Converter with Input Filter	386
3.1.6	Review of the Steady-State Analysis of the Buck Converter in DCM Operation	390
3.1.7	Design of a Buck Converter in DCM Operation	395
3.1.7.1	Design Example	398
3.1.8*	Aspects of Dynamic Response of Buck Converter	399
3.2	Boost DC-DC PWM Hard-switching Converter	402
3.2.1	Boost Converter in Steady-State CCM Operation	402
3.2.1.1	Design Example	409
3.2.2	Boost Converter in Steady-State DCM Operation	410
3.2.2.1	Design Example	416
3.2.3*	Aspects of Dynamic Response of Boost Converter	417
3.3	Buck-Boost DC-DC PWM Hard-switching Converter	420
3.3.1	Buck-Boost Converter in Steady-State CCM Operation	421
3.3.1.1	Design Example Case Study	427
3.3.1.2	Four-Switch Noninverting Buck-Boost Converter	428
3.3.2	Buck-Boost Converter in Steady-State DCM Operation	429
3.3.3*	Aspects of Dynamic Response of Buck-Boost Converter	437
3.4	Ćuk (Boost-Buck) PWM Hard-switching Converter	437
3.4.1	Derivation and Switching Operation of the Ćuk Converter	438
3.4.2	Steady-State Analysis of Ćuk Converter in CCM Operation and its Design	438
3.4.3*	DC Voltage Gain and AC Small-Signal Characteristics of the Ćuk Converter in the Presence of Parasitic Resistances	447
3.4.4	Design Example and Commercially Available Ćuk Converters	455
3.4.4.1	Design of a Ćuk Converter Based on National Semiconductor LM2611 Current-Mode Controller	456

3.4.5*	Discontinuous Conduction Mode for the Ćuk Converter	456
3.4.6*	Ćuk Converter with Coupled Inductor	468
3.5	SEPIC PWM Hard-switching Converter	470
3.5.1	SEPIC Converter in CCM Operation	471
3.5.2	Steady-State Analysis of SEPIC Converter in CCM Operation	473
3.5.3*	Small-Signal Analysis of the SEPIC Converter in CCM Operation	479
3.5.4	Commercially Available SEPIC Converters: Case Studies	483
3.5.4.1	SEPIC Converter Based on National Semiconductor LM3478 Controller	483
3.5.4.2	SEPIC Converter Based on Unitrode (Texas Instruments) UCC3803 Controller	485
3.5.4.3	SEPIC Converter Based on Unitrode (Texas Instruments) UC2577 Controller for Automotive Applications	487
3.5.4.4	SEPIC Converter Based on Texas Instruments TPS61175 IC Controller	487
3.5.5*	SEPIC Converter in DCM Operation	489
3.5.5.1	Numerical Example	498
3.5.6*	AC Analysis of SEPIC Converter in DICM	500
3.5.7*	Isolated SEPIC Converter	503
3.6	Zeta (Inverse SEPIC) PWM Hard-switching Converter	503
3.6.1	Zeta Converter in CCM Operation	504
3.6.2	Steady-State Analysis of a Zeta Converter in CCM Operation	505
3.6.3*	Small-Signal Analysis of the Zeta Converter in CCM Operation	514
3.6.4	Design Example and Case Study	515
3.6.4.1	Zeta Converter Based on the Sipex SP6126 Controller	517
3.6.4.2	Zeta Converter Based on the Dual-Channel Synchronous Current-Mode Switching Controller ADP1877 from Analog Devices	519
3.6.4.3	Zeta Converter Based on the Texas Instruments TPS40200 Non-Synchronous Voltage-Mode Controller	520
3.6.5*	Zeta Converter in DCM Operation	520
3.6.5.1	Numerical Example	527
3.6.6*	Isolated Zeta Converter	529
3.7	Forward Converter	530
3.7.1	The Role of a High-Frequency Transformer in the Structure of DC-DC Converters	530
3.7.2	Derivation of Forward Converter	531
3.7.3	Operation of Forward Converter in CCM	534
3.7.3.1	First Switching Stage	534
3.7.3.2	Second Switching Stage	538
3.7.3.3	Third Switching Stage	542
3.7.3.4	Derivation of the Input-to-Output DC Voltage Conversion Ratio	543
3.7.3.5	Limit on the Maximum Duty Ratio	543
3.7.4	Operation of a Forward Converter in DCM and Design Considerations for CCM and DCM	545
3.7.5*	Multiple-Output Forward Converter	551
3.7.6*	Other Core Reset Strategies	551
3.7.6.1	Clamping Circuits for Core Reset	553

3.7.6.2	Operation of an Active Clamping Circuit Formed by a Switch and a Reset Capacitor	554
3.7.6.3	A Resonant Passive Clamping Circuit	559
3.7.6.4	Two-Transistor Forward Converter	563
3.7.7	Examples of Practical Designs: Case Studies	564
3.7.7.1	A Forward Converter with RCD Clamping Circuit	564
3.7.7.2	Forward Converter with a Reset Transformer Winding and Synchronous Rectification used in a Consumer Application for a USA Typical Input Voltage Range	564
3.7.7.3	Design of a Forward Converter using the MAX8541 Voltage-Mode Controller with Synchronous Rectifier	566
3.8*	Isolated Ćuk Converter	568
3.9	Flyback Converter	574
3.9.1	Derivation of the Flyback Converter	574
3.9.2	Operation of Flyback Converter in CCM and DCM	577
3.9.2.1	Analysis for CCM Operation	577
3.9.2.2	Particularities of Operation in DCM	583
3.9.3	Effects of the Coupled Inductor Leakage Inductance	587
3.9.3.1	Dissipative RCD Snubber Solution	589
3.9.3.2	Transformer Tertiary Winding Solution	593
3.9.3.3*	Two-Transistor Flyback Converter	593
3.9.3.4*	Flyback Converter with Active Clamping	597
3.9.4*	Small-Signal Model of the Flyback Converter	598
3.9.5	Designs of the Flyback Converter: Case Studies – Practical Considerations	600
3.9.5.1	Design of a Flyback Converter with Integrated Regulator Si9108, Vishai Siliconix	601
3.9.5.2	Flyback Converter for Battery-Powered CCDs (Charge Coupled Devices)	603
3.9.5.3	A Flyback Converter Designed for Telecommunication Industry (Unित्रode/Texas Instruments Application Note)	604
3.10	Push–Pull Converter	607
3.10.1	Push–Pull Converter of Buck Type (Voltage Driven)	607
3.10.2	CCM Operation of the Push–Pull Converter	608
3.10.3	Non-Idealities in the Push–Pull Converter	616
3.10.4	DCM Operation	619
3.10.5*	Push–Pull Converter of the Boost Type (Current Driven)	625
3.10.6	Design Example	631
3.11	Half-Bridge Converter	634
3.11.1	The Buck-Type Half-Bridge Topology	634
3.11.2	CCM Operation	636
3.11.3	Input-to-Output Voltage Conversion Ratio and Design of a Half-Bridge Converter in CCM Operation	645
3.11.4	Practical Aspects	647
3.11.5	DCM Operation	648
3.11.6*	Current-Driven Half-Bridge Converter	652
3.12	Full-Bridge Converter	657
3.12.1	Full-Bridge Topology	657

3.12.2	CCM Operation of the Buck-Type Full-Bridge Converter	660
3.12.3	Input-to-Output Voltage Conversion Ratio and Design of a Buck-Type Full-Bridge Converter in CCM Operation	672
3.12.4	Practical Aspects	676
3.12.5*	Other Transistor Control Schemes: Phase-Shift Control	676
3.12.6*	Current-Driven Full-Bridge Converter	680
3.13	Highlights of the Chapter	687
	Problems	696
	Bibliography	702
<b>4</b>	<b>Derived Structures of DC-DC Converters</b>	<b>705</b>
4.1	Current Doubler Rectifier (CDR) for Push–Pull, Half-Bridge and Full-Bridge Converters	705
4.1.1	Cyclical Operation of Current Doubler Rectifier	706
4.1.2	Voltage Conversion Ratio of Converters with CDR	711
4.1.3	Ripple Cancellation in the Output Current	711
4.1.4*	Other Structures of CDR	713
4.1.5	Penalties of CDR	719
4.1.6*	Current Tripler and Current Multiplier	719
4.2	Voltage Doubler and Voltage Multiplier Rectifier	721
4.2.1	Full-Wave Bridge Voltage Doubler	721
4.2.2	Greinacher Multiplier	723
4.2.3	Voltage Tripler and General Cockcroft–Walton Multiplier	727
4.2.4*	Voltage Doubler with One Capacitor	729
4.2.5	Fibonacci Voltage Multiplier	730
4.2.6	Voltage Dividers	735
4.2.7*	“Economy” Power Supply and the $4 \times 8$ Power Supply	736
4.3	Quadratic Converters	742
4.3.1	Quadratic Buck Converters	743
4.3.2*	Buck-Boost Quadratic Converters ( $D < 0.5$ )	746
4.4*	Two-Switch Buck-Boost Converter	748
4.4.1	Buck-Boost Converters Obtained by Interleaving a Boost and a Buck Switching Cell	749
4.4.2	Z-Source Buck-Boost Converter with Positive Output Voltage	753
4.5*	Switched-Capacitor/Switched-Inductor Integrated Basic Converters	757
4.5.1	Family of Converters Based on Switched-Capacitor/Switched-Inductor Structures	757
4.5.1.1	Switched-Capacitor/Switched-Inductor Building Blocks	757
4.5.1.2	Switched-Capacitor/Switched-Inductor Integrated Buck Converters	760
4.5.1.3	Switched-Capacitor/Switched-Inductor Integrated Boost Converters	767
4.5.1.4	Switched-Capacitor/Switched-Inductor Integrated Buck-Boost, Ćuk, SEPIC and Zeta Converters	770
4.5.2	KY Converter	776
4.5.2.1	First-Order KY Converter	776
4.5.2.2	Second-Order KY Converter	778
4.5.3	Watkins–Johnson Converter	782

4.6*	The Sheppard–Taylor Converter	783
4.6.1	CCM Operation	783
4.6.2	Discontinuous Conduction Mode Operation	785
4.6.3	Isolated Sheppard–Taylor Converter	791
4.7*	Converters with Low Voltage Stress on the Active Switches	793
4.7.1	Four-Switch Full-Bridge-Type Converter with $V_{in}/2$ Primary-Side Switches Voltage Stress	794
4.7.2	Converter with $V_{in}/3$ Voltage Stress on the Primary-Side Switches	797
4.7.3	Three-Level Boost Converter	797
4.8*	Tapped Inductor-Based Converters	805
4.8.1	Tapped Inductor Buck Converter and VRMs (Voltage Regulator Module)	805
4.8.1.1	Diode-To-Tap and Switch-To-Tap Buck Converters	805
4.8.1.2	Rail-To-Tap (Watkins–Johnson Type) Tapped Inductor Buck Converter For Automotive Applications	810
4.8.1.3	Voltage Regulator Module (VRM)	811
4.8.2	Tapped Inductor Boost Converter	812
4.9*	Current-Driven Dual-Bridge Converter with Center-Tapped Inductor	812
4.10	Highlights of the Chapter	824
	Problems	829
	Bibliography	830