

# CONTENTS

Preface	vii
---------	-----

## **PART I CIRCUITS FOR DC-TO-DC POWER CONVERSION**

<b>1</b>	<b>PWM Dc-to-Dc Power Conversion</b>	<b>3</b>
1.1	PWM Dc-to-Dc Power Conversion	4
1.1.1	Dc-to-Dc Power Conversion	4
1.1.2	PWM Technique	6
1.2	Dc-to-Dc Power Conversion System	7
1.3	Features and Issues of PWM Dc-to-Dc Converter	8
1.4	Chapter Highlights	11
	References	12
<b>2</b>	<b>Power Stage Components</b>	<b>13</b>
2.1	Semiconductor Switches	13
2.1.1	MOSFETs	14
2.1.2	Diodes	15
2.1.3	MOSFET-Diode Pair as SPDT Switch	16
2.2	Energy Storage and Transfer Devices	17
		<b>xiii</b>

2.2.1	Inductors	18
2.2.2	Capacitors	26
2.2.3	Transformers	31
2.3	Switching Circuits in Practice	39
2.3.1	Solenoid Drive Circuits	39
2.3.2	Capacitor Charging Circuit	45
2.4	Summary	50
	References	51
	Problems	52
<b>3</b>	<b>Buck Converter</b>	<b>71</b>
3.1	Ideal Step-Down Dc-to-Dc Power Conversion	72
3.2	Buck Converter: Step-Down Dc-to-Dc Converter	74
3.2.1	Evolution to Buck Converter	74
3.2.2	Frequency-Domain Analysis	75
3.3	Buck Converter in Start-Up Transient	78
3.3.1	Piecewise Linear Analysis	78
3.3.2	Start-up Response	78
3.4	Buck Converter in Steady State	80
3.4.1	Circuit Analysis Techniques	80
3.4.2	Steady-State Analysis	82
3.4.3	Estimation of Output Voltage Ripple	84
3.5	Buck Converter in Discontinuous Conduction Mode	89
3.5.1	Origin of Discontinuous Conduction Mode Operation	90
3.5.2	Conditions for DCM Operation	92
3.5.3	Steady-State Operation in DCM	94
3.6	Closed-Loop Control of Buck Converter	99
3.6.1	Closed-Loop Feedback Controller	99
3.6.2	Responses of Closed-Loop Controlled Buck Converter	103
3.7	Summary	109
	References	110
	Problems	110
<b>4</b>	<b>Dc-to-Dc Power Converter Circuits</b>	<b>123</b>
4.1	Boost Converter	124
4.1.1	Evolution to Boost Converter	124
4.1.2	Steady-State Analysis in CCM	126
4.1.3	Steady-State Analysis in DCM	130

4.1.4	Effects of Parasitic Resistance on Voltage Gain	132
4.2	Buck/Boost Converter	135
4.2.1	Evolution to Buck/Boost Converter	137
4.2.2	Steady-State Analysis in CCM	137
4.2.3	Steady-State Analysis in DCM	141
4.3	Structure and Voltage Gain of Three Basic Converters	143
4.4	Flyback Converter: Transformer-Isolated Buck/Boost Converter	145
4.4.1	Evolution to Flyback Converter	145
4.4.2	Steady-State Analysis in CCM	147
4.4.3	Steady-State Analysis in DCM	150
4.5	Bridge-Type Buck-Derived Isolated Dc-to-Dc Converters	153
4.5.1	Switch Network and Multi-Winding Transformer	154
4.5.2	Full-Bridge Converter	157
4.5.3	Half-Bridge Converter	163
4.5.4	Push-Pull Converter	163
4.6	Forward Converters	167
4.6.1	Basic Operational Principles	167
4.6.2	Tertiary-Winding Reset Forward Converter	172
4.6.3	Two-Switch Forward Converter	177
4.7	Summary	177
	References	180
	Problems	181

## **PART II MODELING, DYNAMICS, AND DESIGN OF PWM DC-TO-DC CONVERTERS**

<b>5</b>	<b>Modeling PWM Dc-to-Dc Converters</b>	<b>199</b>
5.1	Overview of PWM Converter Modeling	200
5.2	Averaging Power Stage Dynamics	202
5.2.1	State-Space Averaging	204
5.2.2	Circuit Averaging	210
5.2.3	Generalization of Circuit Averaging Technique	219
5.2.4	Circuit Averaging and State-Space Averaging	220
5.3	Linearizing Averaged Power Stage Dynamics	221
5.3.1	Linearization of Nonlinear Function and Small-Signal Model	221
5.3.2	Small-Signal Model for PWM Switch — PWM Switch Model	223
5.3.3	Small-Signal Model of Converter Power Stage	226

5.4	Frequency Response of Converter Power Stage	227
5.4.1	Sinusoidal Response of Power Stage	228
5.4.2	Frequency Response and s-Domain Small-Signal Model of Power Stage	230
5.5	Small-Signal Gain of PWM Block	232
5.6	Small-Signal Model for PWM Dc-to-Dc Converters	234
5.6.1	Voltage Feedback Circuit	234
5.6.2	Small-Signal Model for PWM Converters	236
5.7	Summary	238
	References	239
	Problems	239
<b>6</b>	<b>Power Stage Transfer Functions</b>	<b>245</b>
6.1	Bode Plot for Transfer Functions	245
6.1.1	Basic Definitions	246
6.1.2	Bode Plots for Multiplication Factors	248
6.1.3	Bode Plot Construction for Transfer Functions	257
6.1.4	Identification of Transfer Function from Bode Plot	262
6.2	Power Stage Transfer Functions of Buck Converter	264
6.2.1	Input-to-Output Transfer Function	265
6.2.2	Duty Ratio-to-Output Transfer Function	268
6.2.3	Load Current-to-Output Transfer Function	270
6.3	Power Stage Transfer Functions of Boost Converter	271
6.3.1	Input-to-Output Transfer Function	272
6.3.2	Duty Ratio-to-Output Transfer Function and RHP Zero	273
6.3.3	Load Current-to-Output Transfer Function	277
6.3.4	Physical Origin of RHP Zero	278
6.4	Power Stage Transfer Functions of Buck/Boost Converter	281
6.5	Empirical Methods for Small-Signal Analysis	283
6.6	Summary	286
	References	287
	Problems	289
<b>7</b>	<b>Dynamic Performance of PWM Dc-to-Dc Converters</b>	<b>297</b>
7.1	Stability	298
7.2	Frequency-Domain Performance Criteria	301
7.2.1	Loop Gain	301
7.2.2	Audio-Susceptibility	302

7.2.3	Output Impedance	303
7.3	Time-Domain Performance Criteria	304
7.3.1	Step Load Response	305
7.3.2	Step Input Response	306
7.4	Stability of Dc-to-Dc Converters	307
7.4.1	Stability of Linear Time-Invariant Systems	307
7.4.2	Small-Signal Stability of Dc-to-Dc Converters	307
7.5	Nyquist Criterion	308
7.6	Relative Stability: Gain Margin and Phase Margin	315
7.7	Summary	322
	References	323
	Problems	324
<b>8</b>	<b>Closed-Loop Performance and Feedback Compensation</b>	<b>331</b>
8.1	Asymptotic Analysis Method	332
8.1.1	Concept of Asymptotic Analysis Method	332
8.1.2	Examples of Asymptotic Analysis Method	334
8.2	Frequency-Domain Performance	339
8.2.1	Audio-Susceptibility	340
8.2.2	Output Impedance	343
8.3	Voltage Feedback Compensation and Loop Gain	344
8.3.1	Problems of Single Integrator	345
8.3.2	Voltage Feedback Compensation	347
8.4	Compensation Design and Closed-Loop Performance	349
8.4.1	Voltage Feedback Compensation and Loop Gain	349
8.4.2	Feedback Compensation Design Guidelines	352
8.4.3	Voltage Feedback Compensation and Closed-Loop Performance	353
8.4.4	Phase Margin and Closed-Loop Performance	367
8.4.5	Compensation Zeros and Speed of Transient Responses	372
8.4.6	Step Load Response	374
8.4.7	Non-Minimum Phase System Case: Boost and Buck/Boost Converters	379
8.5	Summary	383
	References	385
	Problems	385

<b>9</b>	<b>Practical Considerations in Modeling, Analysis, and Design of PWM Converters</b>	<b>407</b>
9.1	Generalization of PWM Converter Model	408
9.1.1	Converter Modeling with Parasitic Resistances	408
9.1.2	Modeling and Analysis of PWM Converters in DCM Operation	415
9.1.3	Modeling of Isolated PWM Converters	425
9.2	Design and Analysis of Dc-to-Dc Converters with Practical Source System	431
9.2.1	Audio-Susceptibility Analysis	432
9.2.2	Stability Analysis	434
9.2.3	Input Impedance of Regulated Dc-to-Dc Converter	441
9.2.4	Origin of Source-Impedance Induced Instability	446
9.2.5	Control Design with Source Impedance	447
9.2.6	Impacts of Source Impedance on Loop Gain and Output Impedance	448
9.3	Consideration for Non-Resistive Load	449
9.4	Summary	452
	References	453
	Problems	454

### **PART III CURRENT MODE CONTROL**

<b>10</b>	<b>Current Mode Control — Functional Basics and Classical Analysis</b>	<b>465</b>
10.1	Current Mode Control Basics	466
10.1.1	Evolution to Peak Current Mode Control	466
10.1.2	Benefits and Issues of Peak Current Mode Control	475
10.1.3	Average Current Mode Control and Charge Control	476
10.2	Classical Analysis and Control Design Procedures	479
10.2.1	Small-Signal Model for Peak Current Mode Control	480
10.2.2	Loop Gain Analysis	486
10.2.3	Stability Analysis	489
10.2.4	Voltage Feedback Compensation	492
10.2.5	Control Design Procedures	497
10.2.6	Analysis of Converter Dynamics in DCM	507
10.3	Closed-Loop Performance of Peak Current Mode Control	509
10.3.1	Audio-Susceptibility Analysis	511
10.3.2	Output Impedance Analysis	516

10.3.3	Step Load Response Analysis	520
10.4	Current Mode Control for Boost and Buck/Boost Converters	532
10.4.1	Stability Analysis and Control Design	532
10.4.2	Loop Gain Analysis	543
10.5	Summary	548
	References	550
	Problems	550
<b>11</b>	<b>Current Mode Control — Sampling Effects and New Control Design Procedures</b>	<b>559</b>
11.1	Sampling Effects of Current Mode Control	560
11.1.1	Origin and Consequence of Sampling Effects	561
11.1.2	Modeling Methodology for Sampling Effects	564
11.1.3	Feedforward Gains	564
11.1.4	Complete s-Domain Model for Current Mode Control	565
11.1.5	Two Prevalent s-Domain Models for Current Mode Control	565
11.2	Expressions for s-Domain Model for Current Mode Control	568
11.2.1	Modified Small-Signal Model	568
11.2.2	Modulator Gain $F_m^*$	570
11.2.3	$H_e(s)$ : s-Domain Representation of Sampling Effects	571
11.2.4	Feedforward Gains	580
11.3	New Control Design Procedures for Current Mode Control	584
11.3.1	New Power Stage Model	584
11.3.2	Control-to-Output Transfer Function with Current Loop Closed	586
11.3.3	Control Design Procedures	592
11.3.4	Correlation between New and Classical Design Procedures	606
11.4	Off-Line Flyback Converter with Optocoupler-Isolated Current Mode Control	612
11.4.1	Off-Line Power Supplies	612
11.4.2	Current Mode Control for Flyback Converter with Optocoupler-Isolated Feedback	613
11.5	Summary	628
	References	629
	Problems	629
	<b>Index</b>	<b>633</b>