
CONTENTS

PREFACE xi

CHAPTER 1 *INTRODUCTION* **1**

- 1.1 Introduction 1
- 1.2 Background 3
- 1.3 History of Power Switches and Power Converters 4
- 1.4 Applications of Power Electronics Converters 6
- 1.5 Summary 9
- References 9

CHAPTER 2 *POWER SWITCHES AND OVERVIEW OF BASIC POWER CONVERTERS* **10**

- 2.1 Introduction 10
- 2.2 Power Electronics Devices as Ideal Switches 11
 - 2.2.1 Static Characteristics 12
 - 2.2.2 Dynamic Characteristics 12
- 2.3 Main Real Power Semiconductor Devices 16
 - 2.3.1 Spontaneous Conduction/Spontaneous Blocking 17
 - 2.3.2 Controlled Conduction/Spontaneous Blocking Devices 18
 - 2.3.3 Controlled Conduction/Controlled Blocking Devices 19
 - 2.3.4 Spontaneous Conduction/Controlled Blocking Devices 22
 - 2.3.5 List of Inventors of the Major Power Switches 24
- 2.4 Basic Converters 25
 - 2.4.1 dc–dc Conversion 28
 - 2.4.2 dc–ac Conversion 33
 - 2.4.3 ac–dc Conversion 43
 - 2.4.4 ac–dc Conversion 49
- 2.5 Summary 50
- References 52

CHAPTER 3 *POWER ELECTRONICS CONVERTERS PROCESSING ac VOLTAGE AND POWER BLOCKS GEOMETRY* **56**

- 3.1 Introduction 56
- 3.2 Principles of Power Blocks Geometry (PBG) 58
- 3.3 Description of Power Blocks 62
- 3.4 Application of PBG in Multilevel Configurations 67
 - 3.4.1 Neutral-Point-Clamped Configuration 68

3.4.2	Cascade Configuration	72
3.4.3	Flying Capacitor Configuration	75
3.4.4	Other Multilevel Configurations	79
3.5	Application of PBG in ac–dc–ac Configurations	81
3.5.1	Three-Phase to Three-Phase Configurations	82
3.5.2	Single-Phase to Single-Phase Configurations	85
3.6	Summary	85
	References	87

CHAPTER 4 *NEUTRAL-POINT-CLAMPED CONFIGURATION***88**

4.1	Introduction	88
4.2	Three-Level Configuration	89
4.3	PWM Implementation (Half-Bridge Topology)	93
4.4	Full-Bridge Topologies	95
4.5	Three-Phase NPC Converter	98
4.6	Nonconventional Arrangements by Using Three-Level Legs	101
4.7	Unbalanced Capacitor Voltage	108
4.8	Four-Level Configuration	112
4.9	PWM Implementation (Four-Level Configuration)	115
4.10	Full-Bridge and Other Circuits (Four-Level Configuration)	118
4.11	Five-Level Configuration	119
4.12	Summary	124
	References	124

CHAPTER 5 *CASCADE CONFIGURATION***125**

5.1	Introduction	125
5.2	Single H-Bridge Converter	126
5.3	PWM Implementation of A Single H-Bridge Converter	129
5.4	Three-Phase Converter—One H-Bridge Converter Per Phase	140
5.5	Two H-Bridge Converters	144
5.6	PWM Implementation of Two Cascade H-Bridges	146
5.7	Three-Phase Converter—Two Cascade H-Bridges Per Phase	149
5.8	Two H-Bridge Converters (Seven- and Nine-Level Topologies)	162
5.9	Three H-Bridge Converters	164
5.10	Four H-Bridge Converters and Generalization	169
5.11	Summary	169
	References	170

CHAPTER 6 *FLYING-CAPACITOR CONFIGURATION***172**

6.1	Introduction	172
6.2	Three-Level Configuration	173
6.3	PWM Implementation (Half-Bridge Topology)	177
6.4	Flying Capacitor Voltage Control	179
6.5	Full-Bridge Topology	181
6.6	Three-Phase FC Converter	183
6.7	Nonconventional FC Converters with Three-Level Legs	186

6.8	Four-Level Configuration	189
6.9	Generalization	196
6.10	Summary	197
	References	198

CHAPTER 7 *OTHER MULTILEVEL CONFIGURATIONS*

199

7.1	Introduction	199
7.2	Nested Configuration	200
7.3	Topology with Magnetic Element at the Output	205
7.4	Active-Neutral-Point-Clamped Converters	211
7.5	More Multilevel Converters	214
7.6	Summary	218
	References	219

CHAPTER 8 *OPTIMIZED PWM APPROACH*

221

8.1	Introduction	221
8.2	Two-Leg Converter	222
	8.2.1 Model	222
	8.2.2 PWM Implementation	223
	8.2.3 Analog and Digital Implementation	228
	8.2.4 Influence of μ for PWM Implementation	231
8.3	Three-Leg Converter and Three-Phase Load	233
	8.3.1 Model	233
	8.3.2 PWM Implementation	235
	8.3.3 Analog and Digital Implementation	236
	8.3.4 Influence of μ for PWM Implementation in a Three-Leg Converter	236
	8.3.5 Influence of the Three-Phase Machine Connection over Inverter Variables	238
8.4	Space Vector Modulation (SVPWM)	243
8.5	Other Configurations with CPWM	247
	8.5.1 Three-Leg Converter—Two-Phase Machine	247
	8.5.2 Four-Leg Converter	249
8.6	Nonconventional Topologies with CPWM	252
	8.6.1 Inverter with Split-Wound Coupled Inductors	252
	8.6.2 Z-Source Converter	254
	8.6.3 Open-End Winding Motor Drive System	257
8.7	Summary	261
	References	261

CHAPTER 9 *CONTROL STRATEGIES FOR POWER CONVERTERS*

264

9.1	Introduction	264
9.2	Basic Control Principles	265
9.3	Hysteresis Control	271
	9.3.1 Application of the Hysteresis Control for dc Motor Drive	275
	9.3.2 Hysteresis Control for Regulating an ac Variable	278

- 9.4 Linear Control—dc Variable 279
 - 9.4.1 Proportional Controller: RL Load 279
 - 9.4.2 Proportional Controller: dc Motor Drive System 280
 - 9.4.3 Proportional-Integral Controller: RL Load 283
 - 9.4.4 Proportional-Integral Controller: dc Motor 285
 - 9.4.5 Proportional-Integral-Derivative Controller: dc Motor 286
- 9.5 Linear Control—ac Variable 288
- 9.6 Cascade Control Strategies 289
 - 9.6.1 Rectifier Circuit: Voltage-Current Control 289
 - 9.6.2 Motor Drive: Speed-Current Control 290
- 9.7 Summary 293
 - References 293

CHAPTER 10 *SINGLE-PHASE TO SINGLE-PHASE BACK-TO-BACK CONVERTER*

295

-
- 10.1 Introduction 295
 - 10.2 Full-Bridge Converter 296
 - 10.2.1 Model 296
 - 10.2.2 PWM Strategy 297
 - 10.2.3 Control Approach 298
 - 10.2.4 Power Analysis 299
 - 10.2.5 dc-link Capacitor Voltage 301
 - 10.2.6 Capacitor Bank Design 304
 - 10.3 Topology with Component Count Reduction 307
 - 10.3.1 Model 307
 - 10.3.2 PWM Strategy 308
 - 10.3.3 dc-link Voltage Requirement 309
 - 10.3.4 Half-Bridge Converter 310
 - 10.4 Topologies with Increased Number of Switches (Converters in Parallel) 310
 - 10.4.1 Model 311
 - 10.4.2 PWM Strategy 315
 - 10.4.3 Control Strategy 316
 - 10.5 Topologies with Increased Number of Switches (Converters in Series) 318
 - 10.6 Summary 321
 - References 321

CHAPTER 11 *THREE-PHASE TO THREE-PHASE AND OTHER BACK-TO-BACK CONVERTERS*

324

-
- 11.1 Introduction 324
 - 11.2 Full-Bridge Converter 325
 - 11.2.1 Model 325
 - 11.2.2 PWM Strategy 327
 - 11.2.3 Control Approach 328
 - 11.3 Topology with Component Count Reduction 330
 - 11.3.1 Model 330
 - 11.3.2 PWM Strategies 331
 - 11.3.3 dc-link Voltage Requirement 332
 - 11.3.4 Half-Bridge Converter 332

11.4	Topologies with Increased Number of Switches (Converters in Parallel)	332
11.4.1	Model	333
11.4.2	PWM	338
11.4.3	Control Strategies	339
11.5	Topologies with Increased Number of Switches (Converters in Series)	340
11.6	Other Back-To-Back Converters	340
11.7	Summary	344
	References	344