

CONTENTS

Preface	xiii
About the Companion Website	xv
1 Principles of Electric Power Conversion	1
1.1 What Is Power Electronics?	1
1.2 Generic Power Converter	3
1.3 Waveform Components and Figures of Merit	8
1.4 Phase Control and Square-Wave Mode	16
1.5 Pulse Width Modulation	22
1.6 Computation of Current Waveforms	30
1.6.1 Analytical Solution	30
1.6.2 Numerical Solution	35
1.6.3 Practical Example: Single-Phase Diode Rectifiers	38
Summary	43
Examples	43
Problems	50
Computer Assignments	53
Further Reading	56
2 Semiconductor Power Switches	57
2.1 General Properties of Semiconductor Power Switches	57
2.2 Power Diodes	59
2.3 Semi-Controlled Switches	63
2.3.1 SCRs	64
2.3.2 Triacs	67
2.4 Fully Controlled Switches	68
2.4.1 GTOs	68
2.4.2 IGCTs	69
2.4.3 Power BJTs	70
2.4.4 Power MOSFETs	74
2.4.5 IGBTs	75
2.5 Comparison of Semiconductor Power Switches	77
2.6 Power Modules	79
2.7 Wide Bandgap Devices	84

Summary	86
Further Reading	87

3 Supplementary Components and Systems **88**

3.1	What Are Supplementary Components and Systems?	88
3.2	Drivers	89
3.2.1	Drivers for SCRs, Triacs, and BCTs	89
3.2.2	Drivers for GTOs and IGCTs	90
3.2.3	Drivers for BJTs	91
3.2.4	Drivers for Power MOSFETs and IGBTs	94
3.3	Overcurrent Protection Schemes	96
3.4	Snubbers	98
3.4.1	Snubbers for Power Diodes, SCRs, and Triacs	101
3.4.2	Snubbers for GTOs and IGCTs	102
3.4.3	Snubbers for Transistors	103
3.4.4	Energy Recovery from Snubbers	104
3.5	Filters	106
3.6	Cooling	109
3.7	Control	111
	Summary	113
	Further Reading	114

4 AC-to-DC Converters **115**

4.1	Diode Rectifiers	115
4.1.1	Three-Pulse Diode Rectifier	115
4.1.2	Six-Pulse Diode Rectifier	117
4.2	Phase-Controlled Rectifiers	130
4.2.1	Phase-Controlled Six-Pulse Rectifier	130
4.2.2	Dual Converters	143
4.3	PWM Rectifiers	149
4.3.1	Impact of Input Filter	149
4.3.2	Principles of PWM	150
4.3.3	Current-Type PWM Rectifier	158
4.3.4	Voltage-Type PWM Rectifier	163
4.3.5	Vienna Rectifier	175
4.4	Device Selection for Rectifiers	178
4.5	Common Applications of Rectifiers	180
	Summary	184
	Examples	185
	Problems	191
	Computer Assignments	193
	Further Reading	195

5 AC-to-AC Converters 196

- 5.1 AC Voltage Controllers 196
 - 5.1.1 Phase-Controlled Single-Phase AC Voltage Controller 196
 - 5.1.2 Phase-Controlled Three-Phase AC Voltage Controllers 203
 - 5.1.3 PWM AC Voltage Controllers 211
- 5.2 Cycloconverters 215
- 5.3 Matrix Converters 220
 - 5.3.1 Classic Matrix Converters 220
 - 5.3.2 Sparse Matrix Converters 227
 - 5.3.3 Z-Source Matrix Converters 230
- 5.4 Device Selection for AC-to-AC Converters 234
- 5.5 Common Applications of AC-to-AC Converters 235
- Summary 236
- Examples 237
- Problems 241
- Computer Assignments 242
- Further Reading 243

6 DC-to-DC Converters 245

- 6.1 Static DC Switches 245
- 6.2 Step-Down Choppers 248
 - 6.2.1 First-Quadrant Chopper 250
 - 6.2.2 Second-Quadrant Chopper 254
 - 6.2.3 First-and-Second-Quadrant Chopper 256
 - 6.2.4 First-and-Fourth-Quadrant Chopper 258
 - 6.2.5 Four-Quadrant Chopper 260
- 6.3 Step-Up Chopper 262
- 6.4 Current Control in Choppers 265
- 6.5 Device Selection for Choppers 265
- 6.6 Common Applications of Choppers 267
- Summary 269
- Examples 269
- Problems 272
- Computer Assignments 274
- Further Reading 275

7 DC-to-AC Converters 276

- 7.1 Voltage-Source Inverters 276
 - 7.1.1 Single-Phase VSI 277
 - 7.1.2 Three-Phase VSI 286
 - 7.1.3 Voltage Control Techniques for PWM Inverters 295
 - 7.1.4 Current Control Techniques for VSIs 306

7.2	Current-Source Inverters	315
7.2.1	Three-Phase Square-Wave CSI	315
7.2.2	Three-Phase PWM CSI	319
7.3	Multilevel Inverters	322
7.3.1	Diode-Clamped Three-Level Inverter	324
7.3.2	Flying-Capacitor Three-Level Inverter	327
7.3.3	Cascaded H-Bridge Inverter	329
7.4	Soft-Switching Inverters	333
7.5	Device Selection for Inverters	341
7.6	Common Applications of Inverters	344
	Summary	352
	Examples	352
	Problems	359
	Computer Assignments	360
	Further Reading	362

8 Switching Power Supplies

364

8.1	Basic Types of Switching Power Supplies	364
8.2	Nonisolated Switched-Mode DC-to-DC Converters	365
8.2.1	Buck Converter	366
8.2.2	Boost Converter	369
8.2.3	Buck–Boost Converter	371
8.2.4	Ćuk Converter	374
8.2.5	SEPIC and Zeta Converters	378
8.2.6	Comparison of Nonisolated Switched-Mode DC-to-DC Converters	379
8.3	Isolated Switched-Mode DC-to-DC Converters	382
8.3.1	Single-Switch-Isolated DC-to-DC Converters	383
8.3.2	Multiple-Switch-Isolated DC-to-DC Converters	386
8.3.3	Comparison of Isolated Switched-Mode DC-to-DC Converters	389
8.4	Resonant DC-to-DC Converters	390
8.4.1	Quasi-Resonant Converters	391
8.4.2	Load-Resonant Converters	395
8.4.3	Comparison of Resonant DC-to-DC Converters	402
	Summary	402
	Examples	403
	Problems	406
	Computer Assignments	408
	Further Reading	410

9 Power Electronics and Clean Energy

411

9.1	Why Is Power Electronics Indispensable in Clean Energy Systems?	411
-----	---	-----

9.2	Solar and Wind Renewable Energy Systems	413
9.2.1	Solar Energy Systems	413
9.2.2	Wind Energy Systems	417
9.3	Fuel Cell Energy Systems	422
9.4	Electric Cars	424
9.5	Hybrid Cars	426
9.6	Power Electronics and Energy Conservation	430
	Summary	431
	Further Reading	432
Appendix A Spice Simulations		433
Appendix B Fourier Series		438
Appendix C Three-Phase Systems		442
Index		447