

Contents

Preface xvii

Author xix

Chapter 1 Mathematical Tools..... 1

1.1 Multiples and Submultiples..... 1

1.2 Periodic Waveforms..... 3

1.2.1 Sine Waves..... 9

1.2.2 Square Waves..... 9

1.2.3 Characterizations 10

1.2.3.1 Average Value 10

1.2.3.2 Root Mean Square Value 10

1.2.3.3 Descriptive Values..... 11

1.3 Fundamental Trigonometric Formulae 11

1.3.1 Pythagorean Identity..... 11

1.3.2 Addition and Subtraction 12

1.3.3 Werner Formulas 13

1.3.4 Duplication Formulas..... 13

1.3.5 Prosthaphaeresis Formulas..... 14

1.4 Complex Numbers..... 14

1.5 Phase Vector (or Phasor)..... 15

1.6 Laplace Transform 17

1.7 Taylor Series 18

1.8 Fourier Series and Integral 19

1.9 Modulation..... 21

1.10 Key Points, Jargon, and Terms 22

1.11 Exercises 23

Chapter 2 Physical and Electrical Background 29

2.1 Force, Work, Energy, Power..... 29

2.2 Heat and Temperature 32

2.2.1 Degree Celsius or Centigrade (°C) 32

2.2.2 Degree Fahrenheit (°F)..... 33

2.2.3 Kelvin (K) 33

2.3 Electric Charge..... 35

2.4 Coulomb Force 35

2.5 Electric Field 36

2.6 Electric Induction 38

2.7 Electric Current..... 39

2.8 Electric Voltage 41

2.9 Electron Mobility 43

2.10 Electric Energy and Power 43

2.11 Conventional Notations 45

Contents

2.12	Magnetic Field	45
2.12.1	Biot–Savart Law	46
2.12.2	Magnetic Properties of Matter	47
2.13	Magnetic Induction	48
2.14	Undulatory Phenomena	51
2.14.1	Electromagnetic Waves	51
2.14.1.1	Light	51
2.14.1.2	Electromagnetic Waves in a Medium	52
2.14.2	Mechanical Waves	53
2.15	Key Points, Jargon, and Terms	56
2.16	Exercises	57
Chapter 3	Nature of Matter	61
3.1	Atomic Model	61
3.1.1	Shells, Subshells, Orbitals	63
3.1.2	Spectroscopic Notation	66
3.1.3	Octet Rule	67
3.2	Lattice	68
3.3	Wave–Particle Duality	70
3.4	Electromagnetic Radiation	72
3.4.1	Photoelectric Effect	72
3.4.2	Production of Radiation	73
3.4.3	Radiation and Ionization	73
3.5	Energy Band Theory	76
3.6	Conductors	80
3.7	Insulators	81
3.8	Semiconductors	82
3.8.1	Intrinsic and Extrinsic Semiconductors	82
3.8.2	Commonly Used Semiconductors	82
3.8.2.1	Germanium	84
3.8.2.2	Silicon	84
3.8.2.3	Gallium Arsenide	87
3.8.2.4	Organic Semiconductors	88
3.8.2.5	Others	88
3.9	Electrical Resistance and Joule Heating	89
3.10	Temperature Coefficient	89
3.11	Key Points, Jargon, and Terms	90
Chapter 4	Two-Terminal Components	93
4.1	Definitions	93
4.2	Conventional Notations	95
4.3	Topology of Interconnections	95
4.3.1	Series Topology (Voltage Divider)	95
4.3.2	Parallel Topology (Current Divider)	95
4.3.3	Bridge Topology	96
4.3.4	Star and Triangle Topologies	96
4.4	Resistors	97

4.4.1	Resistance, Resistivity, Conductance, and Conductivity	97
4.4.2	Classification	99
4.4.3	Coding Scheme	100
4.4.4	Power Resistors	103
4.4.5	Trimmer and Potentiometer	104
4.4.6	SMD Resistors	104
4.4.7	Ohm's Law	105
4.4.8	Joule's Law	108
4.4.9	Real Power	108
4.4.10	Physical Meaning of the RMS Value	110
4.4.11	Resistors in Series	111
4.4.12	Resistors in Parallel	112
4.4.13	Resistor Bridge	113
4.4.14	Resistors in Star and Triangle Connections	113
4.4.15	Voltage Divider	115
4.4.16	Current Divider	116
4.5	Electrical Sources	116
4.5.1	Ideal Voltage Source	117
4.5.2	Ideal Current Source	118
4.5.3	Non-Ideal Voltage and Current Sources	118
4.6	Capacitors	119
4.6.1	Capacitance	119
4.6.2	Types of Capacitors	123
4.6.3	Capacitor Markings	124
4.6.3.1	Ceramic Capacitors	124
4.6.3.2	Polyester Capacitors	125
4.6.3.3	Electrolytic Capacitors	126
4.6.3.4	Color-Coding Scheme	126
4.6.3.5	SM Capacitors	126
4.6.4	Charge and Discharge of a Capacitor	127
4.6.5	Capacitors in Series	128
4.6.6	Capacitors in Parallel	129
4.6.7	Energy Stored in Capacitors	130
4.6.8	Reactive Power	131
4.7	Inductors	133
4.7.1	Inductance	133
4.7.2	Flux	134
4.7.3	Electromagnetic Induction	134
4.7.4	Self-Inductance	136
4.7.5	Types of Inductors	137
4.7.5.1	Solenoid	137
4.7.5.2	Coaxial	138
4.7.6	Inductors in Series	138
4.7.7	Inductors in Parallel	139
4.7.8	Energy Stored in Inductors	140
4.7.9	Reactive Power	140
4.8	Capacitor-Inductor Duality	141
4.9	Complex Power	142

Contents

4.10	Summary of Constitutive Relations	145
4.11	Key Points, Jargon, and Terms	145
4.12	Exercises	147
Chapter 5	Two-Port Networks.....	161
5.1	Definitions.....	161
5.2	Transformers	163
5.3	Dependent Sources	165
5.4	Models of Two-Port Networks.....	166
5.4.1	Classification.....	167
5.4.2	Equivalent Circuits	168
5.4.3	Examples of Conversion between Network Parameters.....	168
5.4.3.1	From (H) to (Z).....	168
5.4.3.2	From (Z) to (H).....	170
5.4.4	Conversion Table.....	171
5.4.5	Examples	172
5.5	Interconnections of Two-Port Networks.....	175
5.5.1	Series Connection	175
5.5.2	Parallel Connection	175
5.5.3	Series-Parallel and Parallel-Series Connections..	176
5.5.4	Cascade Connection	177
5.6	Key Points, Jargon, and Terms	178
5.7	Exercises	178
Chapter 6	Circuit Theorems	191
6.1	Definitions.....	191
6.1.1	Electric Circuit and Its Elements	191
6.1.2	Equivalent Networks.....	193
6.1.3	Node, Branch, Mesh.....	193
6.1.4	Ground and Floating Ground	194
6.1.5	Decibel	195
6.2	Kirchhoff's Laws.....	197
6.2.1	Kirchhoff's Current Law (KCL)	198
6.2.2	Kirchhoff's Voltage Law (KVL)	198
6.3	Thévenin's Theorem	199
6.4	Norton's Theorem.....	201
6.5	Superposition Theorem	202
6.6	Miller's Theorem.....	203
6.7	Miller's Dual Theorem.....	205
6.8	Substitution Theorem	206
6.9	Impedance Matching and Bridging	206
6.9.1	Introduction	206
6.9.2	Maximum Power Transfer Theorem	207
6.9.2.1	Resistive Impedances for Both Source and Load.....	207

Contents

6.9.2.2	Complex Impedance for Source and Resistive Impedance for Load.....	208
6.9.2.3	Complex Impedances for Both Source and Load.....	209
6.9.3	Maximum Voltage or Current Transfer.....	211
6.9.4	Efficiency	212
6.9.5	Matching Networks	213
6.10	Who Decides What	213
6.11	Key Points, Jargon, and Terms.....	214
6.12	Exercises	215
Chapter 7	Frequency Domain	223
7.1	Introduction	223
7.2	Resistance, Reactance, Impedance.....	224
7.2.1	Capacitive Reactance	225
7.2.2	Inductive Reactance	226
7.3	Electronic Filters	226
7.3.1	Low-Pass RC Filter	228
7.3.1.1	Amplitude Response	229
7.3.1.2	Phase Response.....	231
7.3.1.3	Group Delay Response	232
7.3.1.4	Considerations.....	233
7.3.2	High-Pass RC Filter	233
7.3.2.1	Amplitude Response	235
7.3.2.2	Phase Response.....	236
7.3.3	LC Filter	238
7.3.4	RLC Filter.....	240
7.3.5	Ideal Filters	244
7.4	Sources of Phase Shift	246
7.5	RC Integrator.....	247
7.6	Key Points, Jargon, and Terms.....	249
7.7	Exercises	249
Chapter 8	Semiconductor Components.....	253
8.1	Doping of Semiconductors	253
8.1.1	N-Type Silicon	255
8.1.2	P-Type Silicon.....	258
8.2	Charge Carriers.....	259
8.2.1	Electrons and Holes.....	259
8.2.2	Majority and Minority Carriers.....	260
8.2.3	Law of Mass Action.....	263
8.3	Current in Semiconductors.....	264
8.3.1	Drift Current.....	264
8.3.2	Diffusion Current.....	266
8.3.3	Total Current.....	268
8.3.4	Leakage Current.....	268

Contents

8.4	P-N Junction	268
8.4.1	Built-In Electric Field	269
8.4.2	Built-In Potential	271
8.5	Diode	272
8.5.1	The Bias	275
8.5.1.1	Forward Bias	275
8.5.1.2	Reverse Bias	276
8.5.2	I-V Characteristic and Threshold Voltage	277
8.5.3	The Resistance	279
8.5.3.1	Static Resistance	280
8.5.3.2	Dynamic Resistance	280
8.5.4	The Capacitance	281
8.5.4.1	Junction or Depletion Capacitance	281
8.5.4.2	Diffusion or Transit Time Capacitance	281
8.5.5	Zener	282
8.5.6	LED	283
8.6	BJT	286
8.6.1	Introduction	286
8.6.2	Working Principles	288
8.6.3	Forward-Active Mode	289
8.6.4	Cutoff Mode	293
8.6.5	Saturation Mode	293
8.6.6	Modes and Models	293
8.6.7	I-V Graph for C.B. Configuration	295
8.6.7.1	Input Characteristics (C.B.)	295
8.6.7.2	Output Characteristics (C.B.)	296
8.6.8	I-V Graph for C.E. Configuration	297
8.6.8.1	Input Characteristics (C.E.)	297
8.6.8.2	Output Characteristics (C.E.)	298
8.6.8.3	Early Effect	299
8.6.9	I-V Graph for C.C. Configuration	300
8.6.9.1	Input Characteristics (C.C.)	300
8.6.9.2	Output Characteristics (C.C.)	301
8.7	MOSFET	301
8.7.1	Field Effect Transistors	301
8.7.2	Working Principles	302
8.7.3	Ohmic Condition	304
8.7.4	Pinch-Off Condition	306
8.7.5	Saturation Condition	307
8.7.6	I-V Graph	307
8.7.7	Subthreshold Current	309
8.7.8	Types of MOSFETs	309
8.8	BJT versus MOSFET	310
8.9	Numbering and Coding Schemes	311
8.9.1	JEDEC	311
8.9.2	Pro Electron	312

Contents

	8.9.3	JIS	312
	8.9.4	Others.....	313
8.10		Key Points, Jargon, and Terms	314
8.11		Exercises	315
Chapter 9		Diode Circuits.....	319
9.1		Rectifiers.....	319
	9.1.1	Half-Wave Rectifier	319
	9.1.2	Filtered Half-Wave Rectifier	320
		9.1.2.1 Choice of Smoothing Capacitor	321
		9.1.2.2 Choice of Diode	322
		9.1.2.3 Observation on Harmonic Content	324
	9.1.3	Bridge Full-Wave Rectifier	325
	9.1.4	Filtered Full-Wave Rectifier.....	326
9.2		DC Power Supply	328
9.3		Voltage Doubler Circuits	330
9.4		Clamper Circuits	331
9.5		Clipper Circuits	332
9.6		Key Points, Jargon, and Terms	334
9.7		Exercises	334
Chapter 10		Amplifiers.....	339
10.1		Definitions and Classifications	339
10.2		Key Parameters	342
	10.2.1	Gain.....	342
	10.2.2	Impedances	342
	10.2.3	Efficiency	343
	10.2.4	Class.....	344
	10.2.5	Stability	347
	10.2.6	Bandwidth.....	347
	10.2.7	Slew Rate	351
	10.2.8	Distortion.....	351
	10.2.9	Noise	354
		10.2.9.1 Types	355
		10.2.9.2 Measures	357
10.3		Types of Amplifier	358
	10.3.1	Voltage Amplifier	358
	10.3.2	Current Amplifier.....	360
	10.3.3	Transresistance Amplifier	362
	10.3.4	Transconductance Amplifier	364
	10.3.5	Power Amplifier	367
10.4		Loading Effect and Driving Parameters	367
10.5		Key Points, Jargon, and Terms	368
10.6		Exercises	369

Chapter 11	Amplifiers: Basic BJT Configurations	371
11.1	Conventional Notations	371
11.2	Step-by-Step First Design	371
11.2.1	DC Bias Resistor	371
11.2.2	AC Source	373
11.2.3	DC Blocking Capacitors	373
11.2.4	AC Collector Resistor	374
11.3	BJT as a Signal Amplifier	375
11.3.1	BJT as a Two-Port Network	375
11.3.2	BJT Small Signal Model	375
11.3.2.1	Mathematical Meaning of the Hybrid Parameters	377
11.3.2.2	Physical Meaning of the Hybrid Parameters	378
11.3.3	DC and AC Current Gains	381
11.3.4	Typical H-Parameter Values	382
11.3.5	Hybrid Parameter Conversion	384
11.4	C.E. Configuration	385
11.4.1	DC Analysis	387
11.4.1.1	Fixed Bias	387
11.4.1.2	DC Load Line	388
11.4.1.3	DC Stability	389
11.4.1.4	Emitter Feedback Bias	390
11.4.1.5	Voltage Divider Bias	392
11.4.2	AC Analysis	395
11.4.2.1	AC Load Line	396
11.4.2.2	C.E.: Input Resistance	398
11.4.2.3	C.E.: Current Gain	400
11.4.2.4	C.E.: Voltage Gain	403
11.4.2.5	C.E.: Output Resistance	405
11.5	Swamped C.E.	406
11.5.1	DC Analysis	407
11.5.2	AC Analysis	407
11.5.2.1	Swamped C.E.: Current Gain	407
11.5.2.2	Swamped C.E.: Input Resistance	408
11.5.2.3	Swamped C.E.: Voltage Gain	410
11.5.2.4	Swamped C.E.: Output Resistance	413
11.6	C.C. Configuration (Emitter Follower)	413
11.6.1	DC Analysis	414
11.6.2	AC Analysis	415
11.6.2.1	C.C. (C.C. Hybrid Parameters): Input Resistance	416
11.6.2.2	C.C. (C.C. Hybrid Parameters): Current Gain	417
11.6.2.3	C.C. (C.C. Hybrid Parameters): Voltage Gain	418
11.6.2.4	C.C. (C.C. Hybrid Parameters): Output Resistance	419

Contents

11.6.3	AC Analysis (with C.E. Hybrid Parameters).....	420
11.6.3.1	C.C. (C.E. Hybrid Parameters): Current Gain.....	420
11.6.3.2	C.C. (C.E. Hybrid Parameters): Input Resistance.....	422
11.6.3.3	C.C. (C.E. Hybrid Parameters): Voltage Gain.....	423
11.6.3.4	C.C. (C.E. Hybrid Parameters): Output Resistance.....	424
11.7	C.B. Configuration.....	424
11.7.1	DC Analysis.....	425
11.7.2	AC Analysis.....	425
11.7.2.1	C.B.: Input Resistance.....	427
11.7.2.2	C.B.: Current Gain.....	428
11.7.2.3	C.B.: Voltage Gain.....	430
11.7.2.4	C.B.: Output Resistance.....	431
11.8	C.E., C.B., C.C. Comparisons.....	432
11.9	BJT Simplified Hybrid Model.....	434
11.10	Bias Stability.....	436
11.10.1	Fixed Bias.....	437
11.10.2	Collector Feedback Bias.....	438
11.10.3	Voltage Divider Bias.....	439
11.10.3.1	Stability versus I_{CBO}	440
11.10.3.2	Stability versus V_{BEQ}	441
11.10.3.3	Stability versus β	441
11.11	Key Points, Jargon, and Terms.....	443
11.12	Exercises.....	444
Chapter 12	Amplifiers: Basic MOSFET Configurations.....	453
12.1	MOSFET as a Signal Amplifier.....	453
12.1.1	Biasing Circuits.....	456
12.1.1.1	Drain Feedback Bias.....	456
12.1.1.2	Voltage Divider Bias.....	457
12.1.1.3	Source Feedback Bias.....	457
12.1.2	Small-Signal Model.....	458
12.2	C.S. Configuration.....	458
12.2.1	DC Analysis.....	459
12.2.2	AC Analysis.....	461
12.2.2.1	C.S.: Input Resistance.....	462
12.2.2.2	C.S.: Output Resistance.....	462
12.2.2.3	C.S.: Voltage Gain.....	463
12.3	C.D. Configuration (Source Follower).....	464
12.3.1	DC Analysis.....	464
12.3.2	AC Analysis.....	465
12.3.2.1	C.D.: Input Resistance.....	466
12.3.2.2	C.D.: Output Resistance.....	466
12.3.2.3	C.D.: Voltage Gain.....	468

12.4	C.G. Configuration.....	468
12.4.1	DC Analysis.....	468
12.4.2	AC Analysis.....	468
12.4.2.1	C.G.: Input Resistance.....	469
12.4.2.2	C.G.: Output Resistance.....	470
12.4.2.3	C.G.: Voltage and Current Gains.....	471
12.5	Comparisons among C.S., C.D., C.G.....	472
12.6	Bias Stability.....	472
12.7	MOSFET as a Switch.....	473
12.8	Key Points, Jargon, and Terms.....	474
12.9	Exercises.....	474
Chapter 13	Amplifiers: Variants.....	477
13.1	Increased Input Resistance.....	477
13.1.1	Darlington Pair.....	479
13.1.2	Current Source.....	482
13.1.3	Bootstrapping.....	484
13.2	Transformer-Coupled Load.....	485
13.3	Cascode Amplifier.....	490
13.4	Differential Amplifier.....	492
13.4.1	Introduction.....	492
13.4.2	Theory.....	492
13.4.3	Basic Emitter-Coupled Pair.....	495
13.5	Key Points, Jargon, and Terms.....	497
Chapter 14	Amplifiers: Cascading Stages.....	499
14.1	Coupling.....	500
14.1.1	RC, LC Coupling.....	501
14.1.2	Transformer Coupling.....	502
14.1.3	Impedance Coupling.....	503
14.1.4	Direct Coupling.....	503
14.2	DC Analysis.....	504
14.2.1	AC-Coupled Multistage Amplifiers.....	504
14.2.2	DC-Coupled Multistage Amplifiers.....	504
14.3	AC Analysis.....	505
14.3.1	Unilateral Stages.....	505
14.3.2	Non-Unilateral Stages.....	506
14.4	Double-Stage C.E.-C.E.....	507
14.4.1	AC Input Resistances.....	508
14.4.2	AC Current Gain.....	508
14.4.3	AC Voltage Gain.....	509
14.4.4	AC Output Resistance.....	510
14.5	Double-Stage C.E.-C.C.....	511
14.5.1	DC Analysis.....	511
14.5.2	AC Analysis.....	513
14.6	Double-Stage C.C.-C.E.....	514

Contents

14.7	Double-Stage C.S.–C.E	516
14.7.1	AC Input Resistance	517
14.7.2	AC Output Resistance	517
14.7.3	AC Voltage Gain	517
14.8	Bandwidth.....	517
14.9	Key Points, Jargon, and Terms	518
14.10	Exercises	518
Chapter 15	Some Applications.....	521
15.1	Audio Amplifier	521
15.2	FM Radio.....	523
15.2.1	Transmitter	523
15.2.2	Receiver	525
15.3	Battery Charger	525
15.3.1	USB-Powered Charger	525
15.3.2	AC Mains-Powered Charger	526
15.4	Early Heart Pacemaker	527
15.5	Other Transistor Applications	528
15.5.1	Liquid Level Indicator	529
15.5.2	Battery Voltage Monitor	529
15.5.3	Dark/Light Activated LED/Relay	530
15.5.4	Measure of Temperature.....	532
15.5.5	Simple Timer.....	532
15.5.6	Cyclic Beep Generator	532
Index		535