

Contents

Preface to the Second Edition	iv
About the Author	ix
1 Introduction to Analog Design	1
1.1 Why Analog?	1
1.1.1 Sensing and Processing Signals	1
1.1.2 When Digital Signals Become Analog	2
1.1.3 Analog Design Is in Great Demand	3
1.1.4 Analog Design Challenges	4
1.2 Why Integrated?	4
1.3 Why CMOS?	5
1.4 Why This Book?	5
1.5 Levels of Abstraction	5
2 Basic MOS Device Physics	7
2.1 General Considerations	7
2.1.1 MOSFET as a Switch	7
2.1.2 MOSFET Structure	8
2.1.3 MOS Symbols	9
2.2 MOS I/V Characteristics	10
2.2.1 Threshold Voltage	10
2.2.2 Derivation of I/V Characteristics	12
2.2.3 MOS Transconductance	19
2.3 Second-Order Effects	20
2.4 MOS Device Models	26
2.4.1 MOS Device Layout	26
2.4.2 MOS Device Capacitances	27
2.4.3 MOS Small-Signal Model	31
2.4.4 MOS SPICE models	34
2.4.5 NMOS Versus PMOS Devices	35
2.4.6 Long-Channel Versus Short-Channel Devices	35
2.5 Appendix A: FinFETs	36
2.6 Appendix B: Behavior of a MOS Device as a Capacitor	37

3	Single-Stage Amplifiers	45
3.1	Applications	45
3.2	General Considerations	45
3.3	Common-Source Stage	47
3.3.1	Common-Source Stage with Resistive Load	47
3.3.2	CS Stage with Diode-Connected Load	52
3.3.3	CS Stage with Current-Source Load	58
3.3.4	CS Stage with Active Load	59
3.3.5	CS Stage with Triode Load	60
3.3.6	CS Stage with Source Degeneration	61
3.4	Source Follower	68
3.5	Common-Gate Stage	75
3.6	Cascode Stage	82
3.6.1	Folded Cascode	90
3.7	Choice of Device Models	92
4	Differential Amplifiers	100
4.1	Single-Ended and Differential Operation	100
4.2	Basic Differential Pair	103
4.2.1	Qualitative Analysis	104
4.2.2	Quantitative Analysis	106
4.2.3	Degenerated Differential Pair	116
4.3	Common-Mode Response	118
4.4	Differential Pair with MOS Loads	123
4.5	Gilbert Cell	126
5	Current Mirrors and Biasing Techniques	134
5.1	Basic Current Mirrors	134
5.2	Cascode Current Mirrors	139
5.3	Active Current Mirrors	146
5.3.1	Large-Signal Analysis	149
5.3.2	Small-Signal Analysis	152
5.3.3	Common-Mode Properties	156
5.3.4	Other Properties of Five-Transistor OTA	159
5.4	Biasing Techniques	160
5.4.1	CS Biasing	161
5.4.2	CG Biasing	164
5.4.3	Source Follower Biasing	165
5.4.4	Differential Pair Biasing	166
6	Frequency Response of Amplifiers	173
6.1	General Considerations	173
6.1.1	Miller Effect	174
6.1.2	Association of Poles with Nodes	179
6.2	Common-Source Stage	180
6.3	Source Followers	188

6.4	Common-Gate Stage	193
6.5	Cascode Stage	196
6.6	Differential Pair	198
6.6.1	Differential Pair with Passive Loads	198
6.6.2	Differential Pair with Active Load	201
6.7	Gain-Bandwidth Trade-Offs	203
6.7.1	One-Pole Circuits	204
6.7.2	Multi-Pole Circuits	205
6.8	Appendix A: Extra Element Theorem	206
6.9	Appendix B: Zero-Value Time Constant Method	208
6.10	Appendix C: Dual of Miller's Theorem	212
7	Noise	219
7.1	Statistical Characteristics of Noise	219
7.1.1	Noise Spectrum	221
7.1.2	Amplitude Distribution	224
7.1.3	Correlated and Uncorrelated Sources	225
7.1.4	Signal-to-Noise Ratio	226
7.1.5	Noise Analysis Procedure	227
7.2	Types of Noise	228
7.2.1	Thermal Noise	228
7.2.2	Flicker Noise	234
7.3	Representation of Noise in Circuits	236
7.4	Noise in Single-Stage Amplifiers	243
7.4.1	Common-Source Stage	244
7.4.2	Common-Gate Stage	249
7.4.3	Source Followers	253
7.4.4	Cascode Stage	254
7.5	Noise in Current Mirrors	254
7.6	Noise in Differential Pairs	256
7.7	Noise-Power Trade-Off	263
7.8	Noise Bandwidth	264
7.9	Problem of Input Noise Integration	265
7.10	Appendix A: Problem of Noise Correlation	265
8	Feedback	274
8.1	General Considerations	274
8.1.1	Properties of Feedback Circuits	275
8.1.2	Types of Amplifiers	282
8.1.3	Sense and Return Mechanisms	284
8.2	Feedback Topologies	286
8.2.1	Voltage-Voltage Feedback	286
8.2.2	Current-Voltage Feedback	291
8.2.3	Voltage-Current Feedback	294
8.2.4	Current-Current Feedback	297
8.3	Effect of Feedback on Noise	298

8.4	Feedback Analysis Difficulties	299
8.5	Effect of Loading	303
8.5.1	Two-Port Network Models	303
8.5.2	Loading in Voltage-Voltage Feedback	304
8.5.3	Loading in Current-Voltage Feedback	308
8.5.4	Loading in Voltage-Current Feedback	310
8.5.5	Loading in Current-Current Feedback	313
8.5.6	Summary of Loading Effects	315
8.6	Bode's Analysis of Feedback Circuits	315
8.6.1	Observations	315
8.6.2	Interpretation of Coefficients	317
8.6.3	Bode's Analysis	320
8.6.4	Blackman's Impedance Theorem	325
8.7	Middlebrook's Method	331
8.8	Loop Gain Calculation Issues	332
8.8.1	Preliminary Concepts	332
8.8.2	Difficulties with Return Ratio	334
8.9	Alternative Interpretations of Bode's Method	336
9	Operational Amplifiers	344
9.1	General Considerations	344
9.1.1	Performance Parameters	344
9.2	One-Stage Op Amps	349
9.2.1	Basic Topologies	349
9.2.2	Design Procedure	353
9.2.3	Linear Scaling	354
9.2.4	Folded-Cascode Op Amps	355
9.2.5	Folded-Cascode Properties	358
9.2.6	Design Procedure	359
9.3	Two-Stage Op Amps	361
9.3.1	Design Procedure	363
9.4	Gain Boosting	364
9.4.1	Basic Idea	364
9.4.2	Circuit Implementation	368
9.4.3	Frequency Response	371
9.5	Comparison	373
9.6	Output Swing Calculations	373
9.7	Common-Mode Feedback	374
9.7.1	Basic Concepts	374
9.7.2	CM Sensing Techniques	377
9.7.3	CM Feedback Techniques	380
9.7.4	CMFB in Two-Stage Op Amps	386
9.8	Input Range Limitations	388
9.9	Slew Rate	390

9.10	High-Slew-Rate Op Amps	397
9.10.1	One-Stage Op Amps	397
9.10.2	Two-Stage Op Amps	399
9.11	Power Supply Rejection	400
9.12	Noise in Op Amps	402
10	Stability and Frequency Compensation	410
10.1	General Considerations	410
10.2	Multipole Systems	414
10.3	Phase Margin	416
10.4	Basic Frequency Compensation	420
10.5	Compensation of Two-Stage Op Amps	426
10.6	Slewing in Two-Stage Op Amps	433
10.7	Other Compensation Techniques	436
10.8	Nyquist's Stability Criterion	439
10.8.1	Motivation	439
10.8.2	Basic Concepts	440
10.8.3	Construction of Polar Plots	442
10.8.4	Cauchy's Principle	447
10.8.5	Nyquist's Method	447
10.8.6	Systems with Poles at Origin	450
10.8.7	Systems with Multiple 180° Crossings	454
11	Nanometer Design Studies	459
11.1	Transistor Design Considerations	459
11.2	Deep-Submicron Effects	460
11.3	Transconductance Scaling	463
11.4	Transistor Design	466
11.4.1	Design for Given I_D and $V_{DS,min}$	466
11.4.2	Design for Given g_m and I_D	469
11.4.3	Design for Given g_m and $V_{DS,min}$	470
11.4.4	Design for a Given g_m	471
11.4.5	Choice of Channel Length	472
11.5	Op Amp Design Examples	472
11.5.1	Telescopic Op Amp	473
11.5.2	Two-Stage Op Amp	487
11.6	High-Speed Amplifier	495
11.6.1	General Considerations	496
11.6.2	Op Amp Design	500
11.6.3	Closed-Loop Small-Signal Performance	501
11.6.4	Op Amp Scaling	502
11.6.5	Large-Signal Behavior	505
11.7	Summary	507

12 Bandgap References	509
12.1 General Considerations	509
12.2 Supply-Independent Biasing	509
12.3 Temperature-Independent References	513
12.3.1 Negative-TC Voltage	513
12.3.2 Positive-TC Voltage	514
12.3.3 Bandgap Reference	515
12.4 PTAT Current Generation	523
12.5 Constant- G_m Biasing	524
12.6 Speed and Noise Issues	525
12.7 Low-Voltage Bandgap References	529
12.8 Case Study	533
13 Introduction to Switched-Capacitor Circuits	539
13.1 General Considerations	539
13.2 Sampling Switches	543
13.2.1 MOSFETS as Switches	543
13.2.2 Speed Considerations	547
13.2.3 Precision Considerations	549
13.2.4 Charge Injection Cancellation	553
13.3 Switched-Capacitor Amplifiers	555
13.3.1 Unity-Gain Sampler/Buffer	555
13.3.2 Noninverting Amplifier	562
13.3.3 Precision Multiply-by-Two Circuit	567
13.4 Switched-Capacitor Integrator	568
13.5 Switched-Capacitor Common-Mode Feedback	571
14 Nonlinearity and Mismatch	576
14.1 Nonlinearity	576
14.1.1 General Considerations	576
14.1.2 Nonlinearity of Differential Circuits	579
14.1.3 Effect of Negative Feedback on Nonlinearity	581
14.1.4 Capacitor Nonlinearity	583
14.1.5 Nonlinearity in Sampling Circuits	584
14.1.6 Linearization Techniques	585
14.2 Mismatch	591
14.2.1 Effect of Mismatch	593
14.2.2 Offset Cancellation Techniques	598
14.2.3 Reduction of Noise by Offset Cancellation	602
14.2.4 Alternative Definition of CMRR	603
15 Oscillators	607
15.1 General Considerations	607
15.2 Ring Oscillators	609
15.3 LC Oscillators	618

15.3.1	Basic Concepts	618
15.3.2	Cross-Coupled Oscillator	621
15.3.3	Colpitts Oscillator	624
15.3.4	One-Port Oscillators	626
15.4	Voltage-Controlled Oscillators	630
15.4.1	Tuning in Ring Oscillators	633
15.4.2	Tuning in LC Oscillators	641
15.5	Mathematical Model of VCOs	644
16	Phase-Locked Loops	651
16.1	Simple PLL	651
16.1.1	Phase Detector	651
16.1.2	Basic PLL Topology	653
16.1.3	Dynamics of Simple PLL	660
16.2	Charge-Pump PLLs	666
16.2.1	Problem of Lock Acquisition	666
16.2.2	Phase/Frequency Detector	667
16.2.3	Charge Pump	669
16.2.4	Basic Charge-Pump PLL	671
16.3	Nonideal Effects in PLLs	677
16.3.1	PFD/CP Nonidealities	677
16.3.2	Jitter in PLLs	681
16.4	Delay-Locked Loops	683
16.5	Applications	685
16.5.1	Frequency Multiplication and Synthesis	685
16.5.2	Skew Reduction	687
16.5.3	Jitter Reduction	688
17	Short-Channel Effects and Device Models	691
17.1	Scaling Theory	691
17.2	Short-Channel Effects	695
17.2.1	Threshold Voltage Variation	695
17.2.2	Mobility Degradation with Vertical Field	697
17.2.3	Velocity Saturation	698
17.2.4	Hot Carrier Effects	700
17.2.5	Output Impedance Variation with Drain-Source Voltage	700
17.3	MOS Device Models	701
17.3.1	Level 1 Model	702
17.3.2	Level 2 Model	702
17.3.3	Level 3 Model	704
17.3.4	BSIM Series	706
17.3.5	Other Models	707
17.3.6	Charge and Capacitance Modeling	707
17.3.7	Temperature Dependence	708
17.4	Process Corners	708

18 CMOS Processing Technology	712
18.1 General Considerations	712
18.2 Wafer Processing	713
18.3 Photolithography	714
18.4 Oxidation	715
18.5 Ion Implantation	716
18.6 Deposition and Etching	718
18.7 Device Fabrication	718
18.7.1 Active Devices	718
18.7.2 Passive Devices	721
18.7.3 Interconnects	727
18.8 Latch-Up	730
19 Layout and Packaging	733
19.1 General Layout Considerations	733
19.1.1 Design Rules	734
19.1.2 Antenna Effect	736
19.2 Analog Layout Techniques	736
19.2.1 Multifinger Transistors	737
19.2.2 Symmetry	739
19.2.3 Shallow Trench Isolation Issues	743
19.2.4 Well Proximity Effects	744
19.2.5 Reference Distribution	744
19.2.6 Passive Devices	746
19.2.7 Interconnects	753
19.2.8 Pads and ESD Protection	757
19.3 Substrate Coupling	760
19.4 Packaging	764
Index	774