

Contents

Practical Applications of Electrical Engineering Principles 8

Preface 13

1

Introduction 21

- 1.1 Overview of Electrical Engineering 22
- 1.2 Circuits, Currents, and Voltages 26
- 1.3 Power and Energy 33
- 1.4 Kirchhoff's Current Law 36
- 1.5 Kirchhoff's Voltage Law 40
- 1.6 Introduction to Circuit Elements 43
- 1.7 Introduction to Circuits 51
- Summary 55
- Problems 56

2

Resistive Circuits 66

- 2.1 Resistances in Series and Parallel 67
- 2.2 Network Analysis by Using Series and Parallel Equivalents 71
- 2.3 Voltage-Divider and Current-Divider Circuits 75
- 2.4 Node-Voltage Analysis 80
- 2.5 Mesh-Current Analysis 100
- 2.6 Thévenin and Norton Equivalent Circuits 110
- 2.7 Superposition Principle 123
- 2.8 Wheatstone Bridge 127
- Summary 130
- Problems 131

3

Inductance and Capacitance 147

- 3.1 Capacitance 148
- 3.2 Capacitances in Series and Parallel 155

- 3.3 Physical Characteristics of Capacitors 158
- 3.4 Inductance 162
- 3.5 Inductances in Series and Parallel 167
- 3.6 Practical Inductors 169
- 3.7 Mutual Inductance 172
- 3.8 Symbolic Integration and Differentiation Using MATLAB 173
- Summary 177
- Problems 178

4

Transients 187

- 4.1 First-Order RC Circuits 188
- 4.2 DC Steady State 193
- 4.3 RL Circuits 195
- 4.4 RC and RL Circuits with General Sources 200
- 4.5 Second-Order Circuits 206
- 4.6 Transient Analysis Using the MATLAB Symbolic Toolbox 219
- Summary 225
- Problems 225

5

Steady-State Sinusoidal Analysis 235

- 5.1 Sinusoidal Currents and Voltages 236
- 5.2 Phasors 242
- 5.3 Complex Impedances 248
- 5.4 Circuit Analysis with Phasors and Complex Impedances 253
- 5.5 Power in AC Circuits 259
- 5.6 Thévenin and Norton Equivalent Circuits 272
- 5.7 Balanced Three-Phase Circuits 278
- 5.8 AC Analysis Using MATLAB 290
- Summary 294
- Problems 295

6 Electrical Engineering

Frequency Response, Bode Plots, and Resonance 307

- 6.1 Fourier Analysis, Filters, and Transfer Functions 308
- 6.2 First-Order Lowpass Filters 316
- 6.3 Decibels, the Cascade Connection, and Logarithmic Frequency Scales 321
- 6.4 Bode Plots 326
- 6.5 First-Order Highpass Filters 329
- 6.6 Series Resonance 333
- 6.7 Parallel Resonance 338
- 6.8 Ideal and Second-Order Filters 341
- 6.9 Bode Plots with MATLAB 348
- 6.10 Digital Signal Processing 351
 - Summary 360
 - Problems 361

7

Logic Circuits 375

- 7.1 Basic Logic Circuit Concepts 376
- 7.2 Representation of Numerical Data in Binary Form 379
- 7.3 Combinatorial Logic Circuits 387
- 7.4 Synthesis of Logic Circuits 395
- 7.5 Minimization of Logic Circuits 401
- 7.6 Sequential Logic Circuits 406
 - Summary 417
 - Problems 418

8

Computers, Microcontrollers and Computer-Based Instrumentation Systems 428

- 8.1 Computer Organization 429
- 8.2 Memory Types 432
- 8.3 Digital Process Control 434
- 8.4 Programming Model for the HCS12/9S12 Family 437
- 8.5 The Instruction Set and Addressing Modes for the CPU12 441
- 8.6 Assembly-Language Programming 450
- 8.7 Measurement Concepts and Sensors 455

- 8.8 Signal Conditioning 460

- 8.9 Analog-to-Digital Conversion 467
 - Summary 470
 - Problems 472

9

Diodes 479

- 9.1 Basic Diode Concepts 480
- 9.2 Load-Line Analysis of Diode Circuits 483
- 9.3 Zener-Diode Voltage-Regulator Circuits 486
- 9.4 Ideal-Diode Model 490
- 9.5 Piecewise-Linear Diode Models 492
- 9.6 Rectifier Circuits 495
- 9.7 Wave-Shaping Circuits 500
- 9.8 Linear Small-Signal Equivalent Circuits 505
 - Summary 511
 - Problems 511

10

Amplifiers: Specifications and External Characteristics 523

- 10.1 Basic Amplifier Concepts 524
- 10.2 Cascaded Amplifiers 529
- 10.3 Power Supplies and Efficiency 532
- 10.4 Additional Amplifier Models 535
- 10.5 Importance of Amplifier Impedances in Various Applications 538
- 10.6 Ideal Amplifiers 541
- 10.7 Frequency Response 542
- 10.8 Linear Waveform Distortion 547
- 10.9 Pulse Response 551
- 10.10 Transfer Characteristic and Nonlinear Distortion 554
- 10.11 Differential Amplifiers 556
- 10.12 Offset Voltage, Bias Current, and Offset Current 560
 - Summary 565
 - Problems 566

11

Field-Effect Transistors 577

- 11.1 NMOS and PMOS Transistors 578
- 11.2 Load-Line Analysis of a Simple NMOS Amplifier 586

- 11.3 Bias Circuits 588
- 11.4 Small-Signal Equivalent Circuits 592
- 11.5 Common-Source Amplifiers 596
- 11.6 Source Followers 600
- 11.7 CMOS Logic Gates 605
 - Summary 610
 - Problems 611

12

Bipolar Junction Transistors 619

- 12.1 Current and Voltage Relationships 620
- 12.2 Common-Emitter Characteristics 623
- 12.3 Load-Line Analysis of a Common-Emitter Amplifier 624
- 12.4 *pnp* Bipolar Junction Transistors 630
- 12.5 Large-Signal DC Circuit Models 632
- 12.6 Large-Signal DC Analysis of BJT Circuits 635
- 12.7 Small-Signal Equivalent Circuits 642
- 12.8 Common-Emitter Amplifiers 645
- 12.9 Emitter Followers 650
 - Summary 656
 - Problems 657

13

Operational Amplifiers 666

- 13.1 Ideal Operational Amplifiers 667
- 13.2 Inverting Amplifiers 668
- 13.3 Noninverting Amplifiers 675
- 13.4 Design of Simple Amplifiers 678
- 13.5 Op-Amp Imperfections in the Linear Range of Operation 683
- 13.6 Nonlinear Limitations 687
- 13.7 DC Imperfections 692
- 13.8 Differential and Instrumentation Amplifiers 696
- 13.9 Integrators and Differentiators 698
- 13.10 Active Filters 701
 - Summary 705
 - Problems 706

14

Magnetic Circuits and Transformers 718

- 14.1 Magnetic Fields 719
- 14.2 Magnetic Circuits 728

14.3 Inductance and Mutual

- Inductance 733
- 14.4 Magnetic Materials 737
- 14.5 Ideal Transformers 740
- 14.6 Real Transformers 748
 - Summary 753
 - Problems 753

15

DC Machines 764

- 15.1 Overview of Motors 765
- 15.2 Principles of DC Machines 774
- 15.3 Rotating DC Machines 779
- 15.4 Shunt-Connected and Separately Excited DC Motors 785
- 15.5 Series-Connected DC Motors 790
- 15.6 Speed Control of DC Motors 794
- 15.7 DC Generators 798
 - Summary 803
 - Problems 804

16

AC Machines 814

- 16.1 Three-Phase Induction Motors 815
- 16.2 Equivalent-Circuit and Performance Calculations for Induction Motors 823
- 16.3 Synchronous Machines 832
- 16.4 Single-Phase Motors 844
- 16.5 Stepper Motors and Brushless DC Motors 847
 - Summary 849
 - Problems 850

APPENDICES

A

Complex Numbers 856

- Summary 863
- Problems 863

B

Nominal Values and the Color Code for Resistors 865

C

The Fundamentals of Engineering Examination 867

D

Answers for the Practice Tests 868

E

On-Line Student Resources 877

Index 878