

TOLERANCE
ANALYSIS
OF ELECTRONIC
CIRCUITS

USING
Mathcad

Robert R. Boyd

Contents

INTRODUCTION	xi
---------------------------	-----------

PART 1

Root-Sum-Square and Extreme Value Analysis	1
---	----------

Mathcad Derivatives	1
---------------------------	---

Approximate Derivatives	3
-------------------------------	---

Extreme Value Analysis (EVA)	6
------------------------------------	---

EVA Summary	8
-------------------	---

Root-Sum-Square (RSS) Analysis.....	9
-------------------------------------	---

Mathcad Built-in Normal Distribution Functions.....	12
---	----

DC Differential Amplifier.....	20
--------------------------------	----

Asymmetric Tolerances	22
-----------------------------	----

General RSS/EVA Equation Sequence	27
---	----

Comparing Mathcad EVA with Spice.WCASE Analysis.....	28
--	----

Comparing Circuit Analysis Methods.....	33
---	----

More Complicated Circuits	34
---------------------------------	----

RTD A Matrix	36
--------------------	----

Mathcad EVA/RSS Analysis of an RTD Circuit	38
--	----

Tolerance Analysis of AC Circuits.....	41
--	----

Mathcad AC Analysis Method	42
----------------------------------	----

Tolerance Analysis of a Bandpass Filter.....	44
--	----

Spice Analysis.....	51
---------------------	----

Bandpass Filter with Asymmetric Tolerances.....	55
---	----

Low-Pass Filter	57
-----------------------	----

PART 2

Monte Carlo Analysis	63
-----------------------------------	-----------

Random Number Generator	64
-------------------------------	----

Mathcad's Random Number Generator	65
Gaussian Random Number Generator (RNG)	66
Converting to Random Tolerances	67
Monte Carlo Analysis—DC Differential Amplifier	70
MCA of RTD Circuit	75
MCA Bandpass Filter (BPF).....	79
Fast Monte Carlo Analysis (FMCA).....	87
FMCA—Bandpass Filter	88
MCA of BPF	90
Component Slopes	92
Sallen and Key BPF	97
Sallen and Key BPF—FMCA and EVA	103
MCA—Sallen and Key BPF	105
Why MCA Spikes Occur	106
Estimating Manufacturing Yield (MY)	108
BPF Manufacturing Yield Analysis.....	110

PART 3

Advanced Topics	115
Differential Amplifier, $V_o = 0$	115
EVA/RSS of Opamp Offsets	117
MCA of Opamp Offsets	119
Comparing Normal and Uniform Distributions	121
MCA of Opamp Offsets (Cont')	123
Tolerance Analysis of LM158 Opamp Stability/Phase Margin... ..	124
Tolerance Analysis of an A-to-D Circuit	130
Decimal to 8-Bit Binary Conversion	131
NS MF10 Switched Capacitor Filter—Mode 3 BPF.....	136
400-Hz Full-Wave Rectifier Circuit	139
Confidence Intervals for 3σ RSS	144
Confidence Intervals for the Mean.....	146
Large Circuit	147
Comparator Circuit	152

100-Hz Clock Generator	158
Complementary Feedback Amplifier.....	161
Iterative Transient Analysis	163
Half-Wave Rectifier Transient Analysis	166
Second Order Transient Analysis	168
Transient MCA of Bridged-T Circuit	173
Pulse Transformer-Frequency Response	175
Pulse Transformer-Transient Response	177
Spice Listing	184
APPENDIX	185
Derivation of the RSS Equation.....	185
Derivation of $\sqrt{3}$ Factor for Uniform Distribution Inputs	188
Asymmetric Gaussian Distribution	189
Ratio Algorithms.....	191
Bandpass Filter-Spice Comparison.....	195
MCA of BPF	196
Derivation of 400-Hz FWR DC Equation	198
REFERENCES	201