

High
Frequency
and
Microwave
Circuit
Design

Charles G. Nelson

Contents

Chapter 1	From Lumped to Distributed Parameters.....	1
1.1	Expected and Unexpected Results from the Network Analyzer	1
1.1.1	Interwire Capacitance in an Inductor	3
1.2	Distributed Parameters in Coaxial Lines.....	5
1.3	Equivalent Circuit for Coaxial Line.....	11
1.4	Characteristic Impedance on Coaxial Lines	13
1.5	Terminal Conditions — Reflection Coefficient	15
1.5.1	Generalized Reflection Coefficient	17
1.6	Mr. Smith's Invaluable Chart	19
1.7	Characteristic Impedance of Microstrip Lines.....	22
1.8	Two-Port High Frequency Models for Bipolar Transistors.....	25
1.9	Input and Output Impedances: General Case	28
1.10	Stability Circles for the Potentially Unstable Transistor.....	32
Chapter 2	Impedance Matching Techniques.....	37
2.1	Introduction	37
2.1.1	Matching Impedances Using Reactive L-Sections	37
2.1.2	Matching Lower Impedance to Higher Impedance.....	38
2.1.3	Matching a Real Load that has Greater Resistance than Source.....	39
2.2	Use of the Smith Chart in Lumped Impedance Matching	40
2.3	Impedance Matching with a Single Reactive Element	44
2.4	Stub Matching.....	46
2.5.1	Quarter-Wavelength Matching Sections.....	48
2.5.2	Matching with Other than Quarter-Wavelength.....	49
2.6	When and How to Unmatch Matched Lines	51
2.7	Designing Reactances for Waveguides	54
2.8	Location of Iris from Standing Wave Measurements.....	58
Chapter 3	Selective Circuits, Oscillators, and Receivers	61
3.1	LRC Series Resonance	61
3.2	Parallel Resonance	64
3.3	Receiver Requirements.....	66
3.4	Image Frequency and RF Amplifier Requirements.....	68
3.5	Piezoelectric Crystal Resonance.....	71

3.6	Principles of Sine-Wave Oscillators:	
	The Phase-Shift Oscillator.....	73
3.7	Colpitts and Hartley Configurations	74
3.8	Crystal-Controlled Oscillators	76
3.9	Voltage-Controlled Oscillators	77
Chapter 4	Modulation and Demodulation Circuitry	81
4.1	Some Fundamentals: Why Modulate?	81
4.2	How to Shift Frequency	82
4.3	Analog Multipliers, or "Mixers"	84
4.4	Synchronous Detection of Suppressed Carrier Signals	86
4.5	Single Sideband Suppressed Carrier	87
4.6	Amplitude Modulation as Double Sideband with Carrier	90
4.7	Modulation Efficiency	91
4.8	The Envelope Detector	92
4.9	Envelope Detection of SSB Using Injected Carrier.....	95
4.10	Direct vs. Indirect Means of Generating FM.....	96
4.11	Quick-and-Dirty FM Detection	99
4.12	Lower Distortion FM Detection	101
	4.12.1 Phase-Locked Loop.....	101
	4.13 Digital Means of Modulation	102
	4.13.1 Frequency Shift Keying	104
	4.13.2 Phase Shift Keying	105
4.14	Correlation Detection	105
4.15	Digital QAM	106
Chapter 5	Noise and Amplifier Noise Figure.....	109
5.1	Thermal Noise	109
	5.1.1 "Available" Noise Power	111
5.2	Amplifier Noise Figure and Excess Temperature.....	112
5.3	Noise Temperature and Noise Factor of Cascaded Amplifiers.....	113
	5.3.1 Noise Factor of an Attenuating Cable.....	115
5.4	Transistor Gain and Noise Circles	117
5.5	Narrowband Noise	120
5.6	Noise and Interference in FM Systems	125
5.7	Noise in Digital Systems	128
	5.7.1 Basic Properties of Gaussian Functions.....	128
	5.7.2 Determination of Logic Threshold Using Bayes Theorem	131
	5.7.3 Noise-Caused Bit Errors in Coherent Digital Systems.....	132
	5.7.4 Noise in Noncoherently Detected FSK	134

Chapter 6	Antennas and Antenna Systems	135
6.1	Fields from a Current Element.....	135
6.2	Radiated Power and Radiation Resistance.....	138
6.3	Directive Gain.....	140
6.4	Antenna Arrays for Increased Directive Gain	141
6.4.1	Actual Gain via Numerical Integration	145
6.5	Broadside Arrays.....	146
6.6	Antenna Aperture and Other Applications of Gain.....	147
6.7	The Communications Link Budget	149
Appendix A	Calculator Alternative to Smith Chart Calculations	151
A.1	Impedance Determination from Standing Wave Measurements	151
A.2	Series or Shunt Reactance Location and Value to Match Impedance.....	153
A.3	Short-Circuited "Stubs" for Impedance Matching.....	157
Index		159