

# Fundamentals of Linear Electronics Integrated and Discrete



2nd edition

Cox

Contents / v

Preface / ix

Section I Devices and Op-Amps / 1

Chapter 1 Introduction to Diodes / 3

- 1.1 Introduction to Diodes / 4
- 1.2 Inside the Diode / 6
- 1.3 Three Diode Models / 10
- 1.4 Computer Circuit Analysis / 16
- 1.5 MultiSIM Lab Exercise / 17

Chapter 2 Diode Circuits / 35

- 2.1 Rectifier Circuits / 35
- 2.2 Filtering Pulsating DC / 40
- 2.3 Block Diagram of a Complete Power Supply System / 42
- 2.4 Voltage Multipliers / 42
- 2.5 Clipper Circuits / 43
- 2.6 Clamper Circuits / 47
- 2.7 Diode Switching Circuits / 50
- 2.8 Diode Characteristics and Data Sheets / 51
- 2.9 Troubleshooting Diodes / 51
- Pre-Lab 2.1 Diode Rectifier Circuits / 55
- Lab 2.1 Diode Rectifier Circuits / 57
- Pre-Lab 2.2 Clipper and Clamper Circuits / 61
- Lab 2.2 Clipper and Clamper Circuits / 63

Chapter 3 Special Diodes / 77

- 3.1 Zener Diodes / 77
- 3.2 Zener Diode Applications / 78
- 3.3 Voltage Surge Protectors / 83
- 3.4 Varactor Diodes / 84
- 3.5 High Frequency Switching Diodes / 86
- 3.6 Light-Emitting Diodes (LEDs) / 88
- 3.7 Photodiodes / 91
- 3.8 Troubleshooting Special Diodes / 92
- Pre-Lab 3.1 Zener Diode Voltage Regulator Circuit / 95
- Lab 3.1 Zener Diode Voltage Regulator Circuit / 97
- Pre-Lab 3.2 LED Circuits / 99
- Lab 3.2 LED Circuits / 101

Chapter 4 The Bipolar Transistor / 113

- 4.1 Introduction to Transistors / 113
- 4.2 Inside the Transistor / 114
- 4.3 Transistor Switches / 118
- 4.4 Transistor Characteristics and Data Sheets / 122
- 4.5 The Transistor Amplifier / 123
- 4.6 Signal Analysis of the Base-Biased Amplifier / 127
- 4.7 Measuring Input and Output Impedance / 134
- 4.8 Transistor Output Characteristic Curves / 136

4.9	Troubleshooting Transistors / 139
Pre-Lab 4.1	Transistor Switch and Transistor Amplifier / 143
Lab 4.1	Transistor Switch and Transistor Amplifier / 145

## Chapter 5 Transistor Circuits / 161

5.1	Introduction / 161
5.2	Voltage Divider Biasing / 164
5.3	Signal Parameters in Voltage Divider Circuits / 166
5.4	Variations of Voltage Divider Biased Amplifiers / 170
5.5	Emitter Biased Amplifier / 175
5.6	Voltage-Mode Feedback Biased Amplifier / 177
5.7	Multistage RC Coupled Amplifiers / 178
5.8	Coupling and Bypass Capacitors / 179
5.9	Direct Coupled Amplifiers / 181
5.10	Troubleshooting Transistor Circuits / 183
Pre-Lab 5.1	Voltage Divider Biased Amplifiers / 185
Lab 5.1	Voltage Divider Biased Amplifiers / 187
Pre-Lab 5.2	Multistage Amplifier / 189
Lab 5.2	Multistage Amplifier / 191

## Chapter 6 Other Transistor Circuits / 203

6.1	Common-Collector Amplifiers / 203
6.2	Power and Current Gain / 207
6.3	Darlington Pairs / 209
6.4	Common-Collector Stage in the Multistage Amplifier / 211
6.5	Common-Base Amplifiers / 212
6.6	Comparison of Amplifier Configurations / 214
6.7	Current Sources / 215
6.8	Differential Amplifiers / 217
6.9	Troubleshooting Other Transistor Circuits / 220
Pre-Lab 6.1	Emitter Follower Buffer / 223
Lab 6.1	Emitter Follower Buffer / 225

## Chapter 7 Junction Field Effect Transistors / 239

7.1	Introduction to JFETs / 239
7.2	The JFET Versus the Bipolar Transistor / 241
7.3	JFET Characteristics / 241
7.4	Biasing the Common-Source JFET Amplifier / 246
7.5	JFET Signal Parameters / 252

7.6	Analyzing JFET Amplifier Circuits / 255
7.7	Common-Drain Amplifier / 259
7.8	N-Channel and P-Channel JFETs / 263
7.9	JFET Switching Circuits / 264
7.10	Troubleshooting JFET Circuits / 265
Pre-Lab 7.1	JFET Amplifiers / 267
Lab 7.1	JFET Amplifiers / 279

## Chapter 8 MOSFETs / 283

8.1	Introduction to MOSFETs / 283
8.2	D-MOSFET / 283
8.3	E-MOSFET / 286
8.4	Handling MOSFETs / 290
8.5	MOSFET Parameters / 291
8.6	MOSFET Applications / 292
8.7	Troubleshooting FET Circuits / 297
Pre-Lab 8.1	MOSFET Amplifier and Switching Circuits / 303
Lab 8.1	MOSFET Amplifier and Switching Circuits / 305

## Chapter 9 Basics of Operational Amplifiers / 317

9.1	Introduction to Op-Amps / 317
9.2	Voltage Follower / 319
9.3	Noninverting Amplifier / 320
9.4	Inside the Op-Amp and Negative Feedback / 322
9.5	The Inverting Amplifier / 325
9.6	Comparators / 326
9.7	Troubleshooting Op-Amp Circuits / 328
Pre-Lab 9.1	Basic Op-Amp Circuits / 329
Lab 9.1	Basic Op-Amp Circuits / 331

## Chapter 10 Op-Amp Limitations / 343

10.1	Input Bias Current / 343
10.2	Input Offset Current / 344
10.3	Input Offset Voltage / 345
10.4	Output Voltage Swing / 347
10.5	Output Short-Circuit Current / 348
10.6	Frequency Response / 349
10.7	Working with Logarithmic Scales / 356
10.8	Slew Rate (SR) / 359
10.9	Troubleshooting IC Op-Amp Circuits / 365
Pre-Lab 10.1	Op-Amp Limitations / 367
Lab 10.1	Op-Amp Limitations / 371

## Section II Subsystems / 391

### Chapter 11 Op-Amp Applications / 395

11.1	High Input Impedance Circuits / 395
11.2	Basic Arithmetic Circuits / 397

- 11.3 Mixers and Periodic Signals / 400
- 11.4 Integration / 402
- 11.5 Differentiation / 405
- 11.6 Single Supply Op-Amp Circuits / 407
- 11.7 Precision Rectifier Circuits / 408
- 11.8 Peak Detector / 410
- 11.9 Comparator Circuits / 411
- 11.10 Troubleshooting Op-Amp Applications / 417

Pre-Lab 11.1 Pulse-Activated Switching System / 419

Lab 11.1 Sound-Activated Switching System / 421

## Chapter 12 Filter Circuits / 439

- 12.1 Introduction to Filter Circuits / 439
  - 12.2 Passive RC Filter Circuits / 440
  - 12.3 Roll-Off / 443
  - 12.4 Bode Plot / 444
  - 12.5 First-Order Active Filters / 445
  - 12.6 Higher-Order Active Filters / 446
  - 12.7 Bandpass Filters / 448
  - 12.8 Bandstop Filters / 452
  - 12.9 State-Variable Filters / 453
  - 12.10 Switched Capacitor Filters / 454
  - 12.11 LC Tuned Amplifier / 455
  - 12.12 Crystal and Other Piezoelectric Filters / 457
  - 12.13 Troubleshooting Filter Circuits / 459
- Pre-Lab 12.1 Active RC Filters / 461
- Lab 12.1 Active RC Filters / 465

## Chapter 13 Sine Wave Oscillator Circuits / 483

- 13.1 Introduction to Basic Oscillator Theory / 483
  - 13.2 RC Sine Wave Oscillator Circuits / 484
  - 13.3 Oscillations in Amplifier Circuits / 488
  - 13.4 LC Oscillator Circuits / 489
  - 13.5 Crystal Oscillator Circuits / 491
  - 13.6 Troubleshooting Sine Wave Oscillator Circuits / 493
- Pre-Lab 13.1 Sine Wave Oscillators / 495
- Lab 13.1 Sine Wave Oscillators / 497

## Chapter 14 Nonsinusoidal Oscillators / 511

- 14.1 Introduction to Rectangular Wave Oscillators / 511
- 14.2 The 555 Astable Circuit / 512
- 14.3 The 555 as a Monostable Circuit / 516
- 14.4 Inverter Oscillators / 518
- 14.5 Scmitt Trigger RC Oscillators / 519

- 14.6 Crystal Controlled Oscillators / 521
  - 14.7 Triangular Wave Oscillators / 521
  - 14.8 Wave Shaping a Triangular Wave into a Sine Wave / 525
  - 14.9 Sawtooth Oscillators / 526
  - 14.10 Troubleshooting Oscillator Circuits / 528
- Pre-Lab 14.1 Periodic Waveform Oscillators / 529
- Lab 14.1 Periodic Waveform Oscillators / 533

## Chapter 15 Special ICs / 547

- 15.1 Differential Amplifiers / 547
  - 15.2 Instrumentation Amplifiers / 553
  - 15.3 Operational Transconductance Amplifiers (OTAs) / 555
  - 15.4 Optoisolators / 557
  - 15.5 Voltage Controlled Oscillators (VCOs) / 559
  - 15.6 Phase-Locked Loop (PLL) / 561
  - 15.7 PLL Applications / 564
  - 15.8 Troubleshooting ICs / 566
- Pre-Lab 15.1 Differential Amplifier and PLL Circuit / 567
- Lab 15.1 Differential Amplifier and PLL Circuit / 569

## Chapter 16 Power Circuits: Switching and Amplifying / 585

- 16.1 Introduction to Power Circuits / 585
  - 16.2 Power MOSFETs Versus Power Bipolar Transistors / 588
  - 16.3 Power Switching Circuits / 591
  - 16.4 Classes of Amplifiers / 593
  - 16.5 Class-C Power Amplifiers / 596
  - 16.6 Class-B Power Amplifiers / 596
  - 16.7 Integrated Power Amplifiers / 602
  - 16.8 Class-D Power Amplifiers / 603
  - 16.9 Heat Sinking Power Devices / 604
  - 16.10 Troubleshooting Power Circuits / 606
- Pre-Lab 16.1 Power Amplifiers / 607
- Lab 16.1 Power Amplifiers / 609

## Chapter 17 Thyristors / 623

- 17.1 Introduction to Thyristors / 623
- 17.2 Silicon-Controlled Rectifiers (SCRs) / 623
- 17.3 Triacs / 628
- 17.4 Gate-Turnoff SCR (GTO) / 629
- 17.5 Silicon-Controlled Switch (SCS) / 630
- 17.6 Shockley Diode / 630
- 17.7 Diacs / 631
- 17.8 Unijunction Transistors (UJTs) / 631
- 17.9 Programmable Unijunction Transistor (PUT) / 635
- 17.10 SCR Phase-Control Circuits / 636

- 17.11 Triac Phase-Control Circuits / 637
- 17.12 MOS-Gated Thyristors / 639
- 17.13 Troubleshooting Thyristor Circuits / 640
- Pre-Lab 17.1 SCR Phase Control / 641
- Lab 17.1 SCR Phase Control / 643
- Pre-Lab 17.2 Triac Phase Control / 647
- Lab 17.2 Triac Phase Control / 649

## Chapter 18 Power Supplies / 663

- 18.1 Introduction to Power Supplies / 663
- 18.2 Linear Versus Switching Power Supplies / 666
- 18.3 Linear Power Supplies / 669
- 18.4 IC Linear Regulators / 674
- 18.5 Switching Regulators / 678
- 18.6 IC Regulators / 685
- 18.7 Troubleshooting Power Supplies / 689
- Pre-Lab 18.1 Linear Regulated Power Supply / 691
- Lab 18.1 Linear Regulated Power Supply / 693
- Pre-Lab 18.2 Switching Regulators / 697
- Lab 18.2 Switching Regulators / 699

## Chapter 19 Data Conversion / 715

- 19.1 Introduction to Data Conversion Systems / 715
- 19.2 Relationship Between Analog and Digital Signals / 716
- 19.3 Resolution of Conversion Systems / 718
- 19.4 Digital-to-Analog Conversion / 720
- 19.5 Integrated DAC / 722
- 19.6 Digital Controlled Amplifier / 723
- 19.7 Analog-to-Digital Conversion / 724
- 19.8 Integrated ADC / 727
- 19.9 Sample-and-Hold Circuit / 728
- 19.10 Troubleshooting Conversion Systems / 729
- Pre-Lab 19.1 ADC and DAC / 731
- Lab 19.1 ADC and DAC / 733

## Chapter 20 Optoelectronics / 743

- 20.1 Introduction to Optoelectronics / 743

- 20.2 Cathode Ray Tubes (CRTs) / 743
- 20.3 Liquid-Crystal Displays (LCDs) / 748
- 20.4 LEDs / 750
- 20.5 Light Sensing Devices / 751
- 20.6 Photoactive Devices / 753
- 20.7 Optoisolators and Optical Sensors / 756
- 20.8 Lasers / 757
- 20.9 Laser Diodes / 759
- 20.10 Fiber Optics / 760
- Pre-Lab 20.1 Optical Sensors and Optoisolators / 767
- Lab 20.1 Optical Sensors and Optoisolators / 769

## Chapter 21 Transducers and Actuators / 781

- 21.1 Introduction to Transducers and Actuators / 781
- 21.2 Temperature Sensors / 782
- 21.3 Displacement Sensors / 790
- 21.4 Pressure Transducers / 794
- 21.5 Flow Transducers / 795
- 21.6 Acceleration Sensors / 796
- 21.7 Magnetic Sensors / 797
- 21.8 Sensor Signal Conditioning and Calibration / 801
- 21.9 Solenoids / 802
- 21.10 Relays / 803
- 21.11 Motors / 804
- 21.12 Speakers / 814
- Pre-Lab 21.1 Fan Control System / 815
- Lab 21.1 Fan Control System / 817

## Appendix A Components List / 833

## Appendix B Components Data / 837

## Appendix C Answers to Odd-Numbered Questions and Problems / 859

## Index / 875