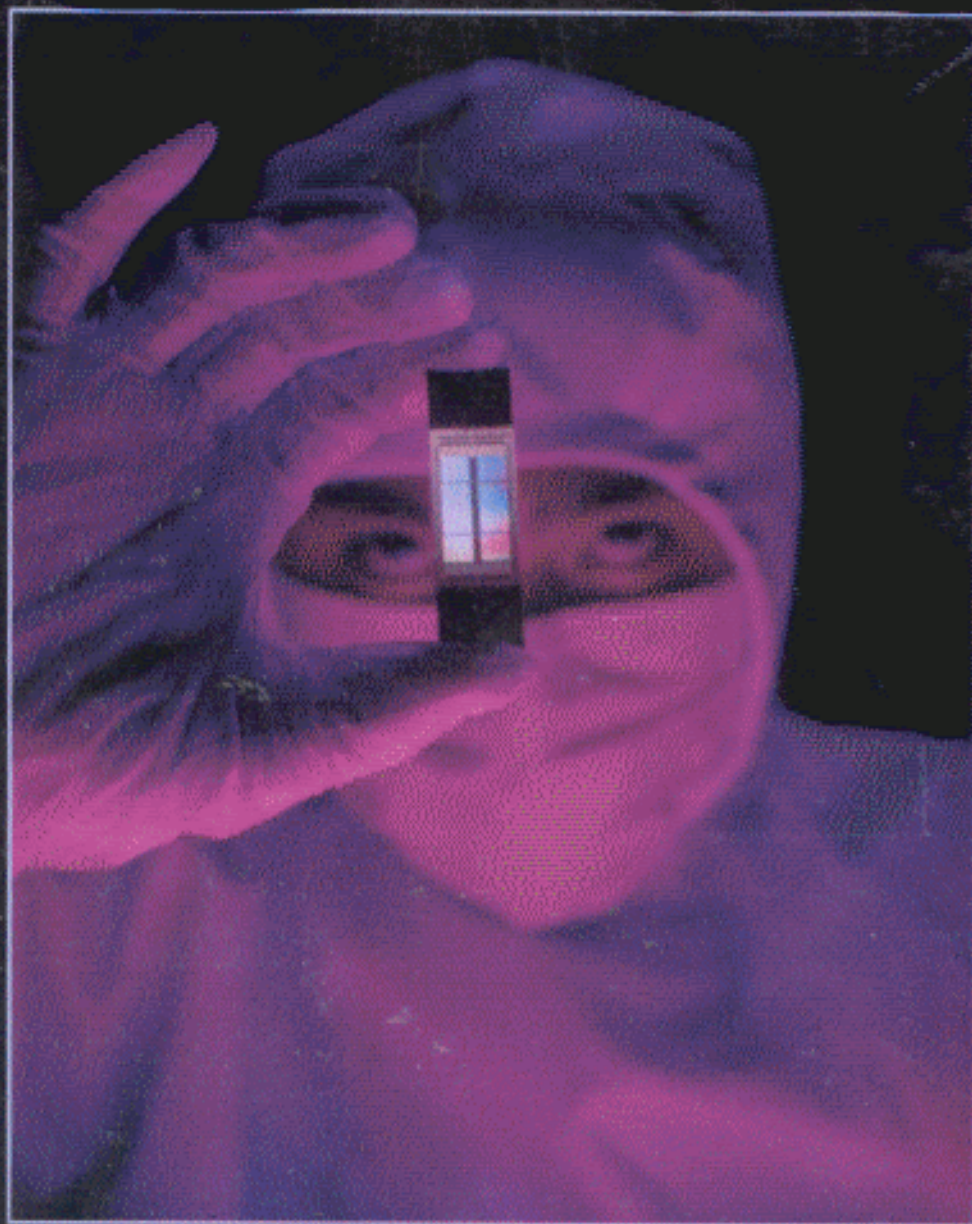


**J. DAVID IRWIN**

# *A Brief Introduction to Circuit Analysis*



**1...Basic Concepts ..... 1**

- 1.1 System of Units...2
  - 1.2 Basic Quantities...2
  - 1.3 Circuit Elements...7
  - Learning Check...11
  - Summary...11
  - Problems...11
- 

**2...Resistive Circuits ..... 14**

- 2.1 Ohm's Law...15
- 2.2 Kirchhoff's Laws...19
- 2.3 Single-Loop Circuits...25
- 2.4 Single-Node-Pair Circuits...30
- 2.5 Series and Parallel Resistor Combinations...35
- 2.6 Circuits with Series-Parallel Combinations of Resistors...38
- 2.7 Wye  $\iff$  Delta Transformations...41
- 2.8 Circuits with Dependent Sources...44
- Learning by Application...47
- Learning by Design...48
- Learning Check...50
- Summary...50
- Problems...51

### **3...Nodal and Loop Analysis Techniques ..... 65**

- 3.1 Nodal Analysis...66
  - 3.2 Loop Analysis...80
  - 3.3 Circuits with Operational Amplifiers...87
    - Learning by Application...97
    - Learning by Design...98
    - Learning Check...100
    - Summary...100
    - Problems...100
- 

### **4...Additional Analysis Techniques ..... 113**

- 4.1 Introduction...114
  - 4.2 Superposition...116
  - 4.3 Thévenin's and Norton's Theorems...120
  - 4.4 Maximum Power Transfer...131
  - 4.5 dc SPICE Analysis Using Schematic Capture...133
    - Learning by Application...144
    - Learning by Design...145
    - Learning Check...146
    - Summary...146
    - Problems...147
- 

### **5...Capacitance and Inductance ..... 159**

- 5.1 Capacitors...160
  - 5.2 Inductors...165
  - 5.3 Capacitor and Inductor Combinations...172
  - 5.4 RC Operational Amplifier Circuits...177
    - Learning by Application...179
    - Learning Check...182
    - Summary...182
    - Problems...182
- 

### **6...First- and Second-Order Transient Circuits ..... 192**

- 6.1 Introduction...193
- 6.2 First-Order Circuits...195
- 6.3 Second-Order Circuits...215
- 6.4 Transient PSpice Analysis Using Schematic Capture...227
  - Learning by Application...239

Learning by Design...	243
Learning Check...	245
Summary...	245
Problems...	246

---

## **7...AC Steady-State Analysis** ..... 258

7.1 Sinusoids...	259
7.2 Sinusoidal and Complex Forcing Functions...	263
7.3 Phasors...	266
7.4 Phasor Relationships for Circuit Elements...	268
7.5 Impedance and Admittance...	273
7.6 Phasor Diagrams...	279
7.7 Basic Analysis Using Kirchhoff's Laws...	282
7.8 Analysis Techniques...	284
7.9 AC PSPICE Analysis Using Schematic Capture...	294
Learning Check...	303
Summary...	303
Problems...	304

---

## **8...Variable-Frequency Network Performance** ..... 317

8.1 Variable Frequency-Response Analysis...	318
8.2 Sinusoidal Frequency Analysis...	328
8.3 Resonant Circuits...	340
8.4 Scaling...	360
8.5 Filter Networks...	362
Learning by Application...	379
Learning by Design...	382
Learning Check...	386
Summary...	386
Problems...	387

---

## **Appendix A Short Mathematics Primer for Basic Circuit Analysis** ..... 397

## **Index** ..... 419