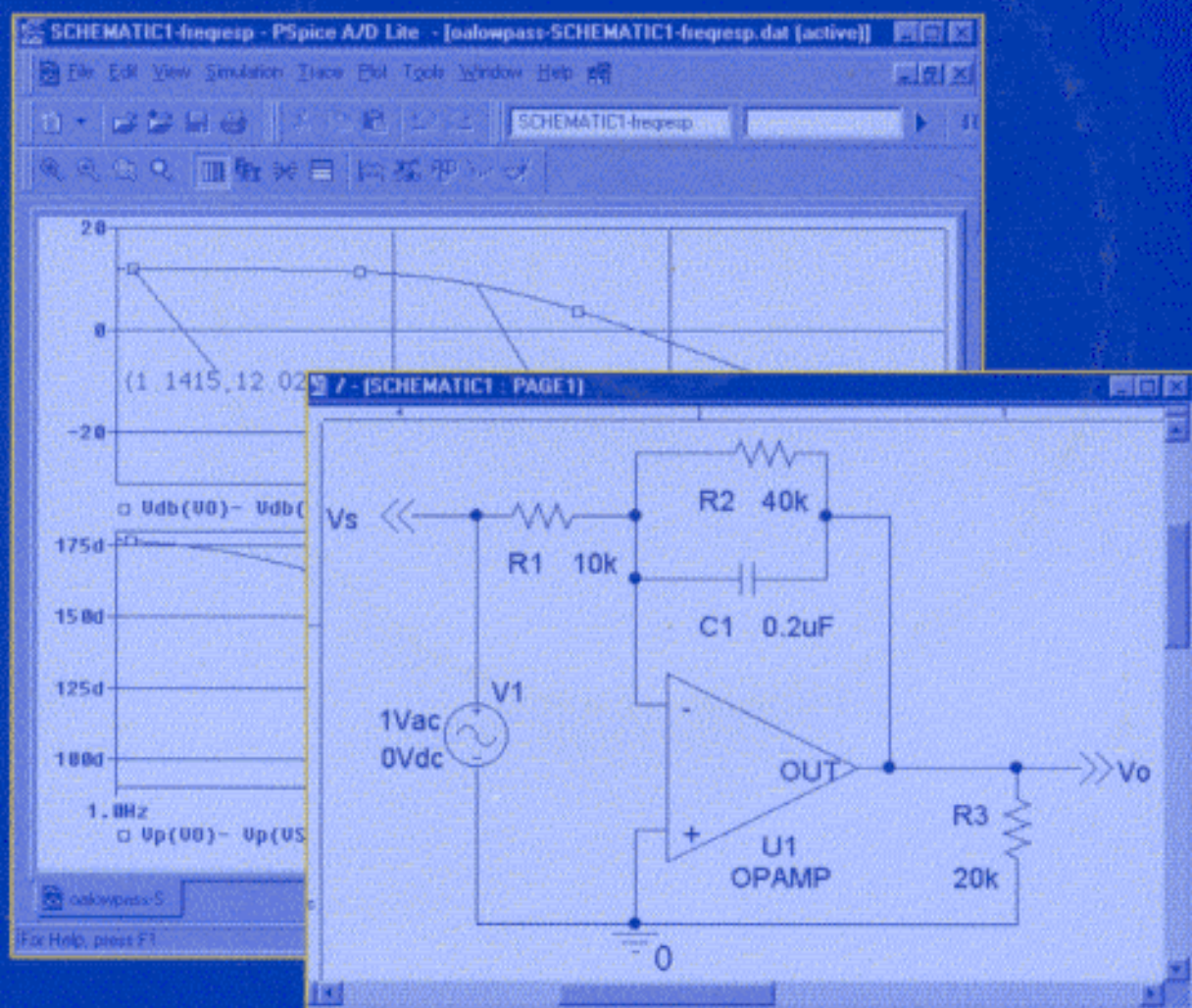


CD Included!
PSpice 9.2
Orcad Lite Edition

PSpice for Linear Circuits



James A. Svoboda

Contents

1. Getting Started with PSpice	1
1.1 Using PSpice	2
1.2 PSpice Notation	22
1.3 Summary	25
2. Analysis of DC Circuits	27
2.1 DC Circuits Containing Dependent Sources	28
2.2 Mesh and Node Equations	35
2.3 Comparing DC Circuits	43
2.4 Thevenin Equivalent Circuits	47
2.5 Capacitors and Inductors in DC Circuits	56
2.6 Summary	59
3. Variable DC Circuits	60
3.1 DC Sweep	61
3.2 Global Parameters	66
3.3 Summary	75
4. Time Domain Analysis	76
4.1 The Response of a RC Circuit to a Pulse Input	76
4.2 Switches	82
4.3 Piecewise Linear Inputs	86
4.4 AC Circuits in the Time Domain	91
4.5 Summary	97
5. Analysis of AC Circuits	98
5.1 AC Circuits	99
5.2 Coupled Coils	107
5.3 Ideal Transformers	112
5.4 Summary	116
6. Frequency Response	117
6.1 Frequency Response Plots	118
6.2 Summary	166
7. Fourier Series	137
Appendix	148