

**CMOS CURRENT  
AMPLIFIERS**

**Speed versus Nonlinearity**

**Kimmo Koli and Kari Halonen**

**Kluwer Academic Publishers**

# Contents

|          |  |           |
|----------|--|-----------|
| <b>1</b> | <b>Introduction to current-mode circuit techniques</b>         | <b>1</b>  |
| 1.1      | Development of integration technologies . . . . .              | 1         |
| 1.2      | Motivation for current-mode circuit design . . . . .           | 2         |
| 1.3      | Evolution of current-mode building blocks . . . . .            | 3         |
| 1.4      | Adjoint principle . . . . .                                    | 4         |
| 1.5      | Scope of this book . . . . .                                   | 6         |
| <b>2</b> | <b>Basic current amplifiers</b>                                | <b>11</b> |
| 2.1      | Current-mirror . . . . .                                       | 12        |
| 2.1.1    | Nonidealities due to the channel length modulation . . . . .   | 13        |
| 2.1.2    | Nonidealities due the $V_T$ mismatch . . . . .                 | 16        |
| 2.1.3    | High frequency nonidealities . . . . .                         | 18        |
|          | Linear effects . . . . .                                       | 18        |
|          | Nonlinearity in limited frequency ranges . . . . .             | 20        |
|          | Mirror as a feedback amplifier . . . . .                       | 22        |
| 2.1.4    | Distortion reduction methods . . . . .                         | 27        |
|          | Transconductance linearisation . . . . .                       | 27        |
|          | Nonlinear current reduction . . . . .                          | 28        |
|          | Nonlinear current cancellation . . . . .                       | 28        |
| 2.1.5    | Noise and dynamic range . . . . .                              | 31        |
| 2.1.6    | Other mirror topologies . . . . .                              | 33        |
|          | Accurate current-mirror topologies for large signal amplitudes | 33        |
|          | Resistively compensated mirror . . . . .                       | 35        |
| 2.2      | Current buffer . . . . .                                       | 38        |
| 2.2.1    | Linear nonidealities . . . . .                                 | 39        |
| 2.2.2    | Nonlinearity . . . . .   | 40        |
| 2.2.3    | Noise . . . . .  | 41        |
| 2.2.4    | Alternative topologies . . . . .                               | 41        |

|          |   |           |
|----------|---|-----------|
| <b>3</b> | <b>Open-loop current amplifiers</b>         | <b>45</b> |
| 3.1      | First generation current-conveyor CCI       | 45        |
| 3.1.1    | Linear nonidealities                        | 46        |
| 3.1.2    | Nonlinearity                                | 49        |
| 3.1.3    | Applications of the CCI                     | 49        |
| 3.1.4    | Push-pull CCI topologies                    | 50        |
| 3.1.5    | Low voltage CCI topologies                  | 54        |
| 3.2      | Second generation current-conveyor CCII     | 55        |
| 3.2.1    | Linear nonidealities                        | 57        |
| 3.2.2    | CCII macromodel                             | 59        |
| 3.2.3    | Applications of the CCII                    | 61        |
| 3.2.4    | Nonlinearity of the class-A CCII            | 67        |
| 3.2.5    | Alternative class-A CCII topologies         | 68        |
| 3.2.6    | Push-pull CCII topologies                   | 72        |
|          | Basic operation of a push-pull CCII+        | 72        |
|          | Basic operation of a push-pull CCII-        | 74        |
|          | X-terminal impedance                        | 75        |
|          | Current gain nonlinearity                   | 76        |
| 3.3      | Third generation current-conveyor CCIII     | 80        |
| <b>4</b> | <b>Current-mode feedback amplifiers</b>     | <b>85</b> |
| 4.1      | Current-feedback operational amplifier      | 85        |
| 4.1.1    | Closed loop bandwidth                       | 87        |
| 4.1.2    | Integrator implementations                  | 90        |
| 4.1.3    | Self-compensation of voltage followers      | 92        |
| 4.1.4    | Common-mode rejection                       | 93        |
| 4.1.5    | CMOS implementations                        | 95        |
| 4.2      | Operational floating conveyor               | 97        |
| 4.2.1    | Applications                                | 98        |
| 4.2.2    | Composite conveyors                         | 99        |
| 4.3      | Current-mode operational amplifiers         | 101       |
| 4.3.1    | Distortion                                  | 102       |
| 4.3.2    | Slew rate and full power bandwidth          | 104       |
| 4.3.3    | Alternative topologies                      | 105       |
| 4.4      | High-gain current-conveyor CCII $_{\infty}$ | 107       |
| 4.4.1    | Linear nonidealities                        | 108       |
| 4.4.2    | Applications                                | 110       |
| 4.4.3    | Distortion                                  | 113       |
| 4.4.4    | Design example                              | 115       |

|          |  |            |
|----------|--|------------|
| <b>5</b> | <b>System aspects of current-mode circuits</b>                             | <b>123</b> |
| 5.1      | Input voltage-to-current conversion . . . . .                              | 123        |
| 5.2      | Output current-to-voltage conversion . . . . .                             | 126        |
| 5.3      | Differential voltage input structures . . . . .                            | 129        |
| 5.3.1    | CMRR enhancement techniques . . . . .                                      | 130        |
|          | Common-mode bootstrapping . . . . .  | 131        |
|          | Output current subtraction . . . . .                                       | 131        |
|          | Composite conveyors . . . . .  | 135        |
| 5.4      | Differential current input structures . . . . .                            | 137        |
| 5.5      | Single-ended to differential conversion . . . . .                          | 138        |
| 5.6      | Noise in current-mode circuits . . . . .                                   | 141        |
| 5.6.1    | Class-A CMOS CCII+ . . . . .   | 141        |
| 5.6.2    | Other low-gain conveyor topologies . . . . .                               | 145        |
| 5.6.3    | High-gain current-conveyor . . . . .                                       | 145        |
| 5.6.4    | Other current-mode feedback amplifiers . . . . .                           | 148        |
| 5.6.5    | General notes on current amplifier noise . . . . .                         | 149        |
| <b>6</b> | <b>Current-mode continuous-time filters</b>                                | <b>153</b> |
| 6.1      | Integrator quality factor . . . . .  | 154        |
| 6.2      | Voltage-mode active-RC integrators . . . . .                               | 155        |
| 6.3      | OTA-based integrators . . . . .  | 157        |
| 6.3.1    | The effects of process variation and temperature drift . . . . .           | 158        |
| 6.3.2    | Transconductance linearity . . . . .                                       | 160        |
| 6.4      | Integrators with MOS-resistors . . . . .                                   | 162        |
| 6.5      | Current-conveyor based filters . . . . .                                   | 163        |
| 6.6      | Current-mirror based filter . . . . .                                      | 167        |
| 6.7      | High-gain current-conveyor based filters . . . . .                         | 172        |
| 6.8      | Multi-output current integrator with a linearised transconductor . . . . . | 176        |
| 6.8.1    | Linearization by drain current difference . . . . .                        | 177        |
| 6.8.2    | Linearisation by dynamic biasing . . . . .                                 | 181        |
| 6.9      | Design case: A 1 MHz current-mode low-pass filter . . . . .                | 183        |
| 6.9.1    | Filter building blocks . . . . .   | 183        |
|          | The transimpedance driver amplifier . . . . .                              | 184        |
|          | Multiple-output linearised transconductance element . . . . .              | 187        |
|          | Temperature drift compensation of the integrator time constant . . . . .   | 187        |
| 6.9.2    | The first filter realisation . . . . .                                     | 190        |
|          | Integrator Q-enhancement . . . . .   | 192        |
|          | Experimental results . . . . .   | 195        |
| 6.9.3    | The second test chip . . . . .   | 198        |

|          |  |            |
|----------|--|------------|
|          | Alternate driver implementation . . . . .  | 201        |
|          | Experimental results . . . . .   | 205        |
| 6.10     | Final remarks . . . . .  | 208        |
| <b>7</b> | <b>Current-mode logarithmic amplifiers</b>   | <b>213</b> |
| 7.1      | Diode-feedback logarithmic amplifiers . . . . .                                    | 214        |
| 7.1.1    | Voltage-mode operational amplifier based realizations . . . . .                    | 214        |
| 7.1.2    | Design case: CCII $\infty$ based logarithmic peak detector . . . . .               | 216        |
|          | BiCMOS implementation of a CCII $\infty$ . . . . .                                 | 217        |
|          | Logarithmic peak detector implementation . . . . .                                 | 217        |
|          | Post processing of the logarithmic output voltage . . . . .                        | 222        |
|          | Final remarks on the design . . . . .  | 229        |
| 7.2      | Pseudologarithmic amplifiers . . . . .   | 230        |
| 7.2.1    | Limiting CMOS voltage amplifiers . . . . .   | 231        |
| 7.2.2    | Limiting CMOS current amplifiers . . . . .   | 233        |
| 7.2.3    | Accuracy of the pseudologarithmic amplifier . . . . .                              | 235        |
| 7.2.4    | Amplitude detection in pseudologarithmic amplifiers . . . . .                      | 236        |
|          | CMOS rectifiers . . . . .  | 236        |
|          | CMOS squarers . . . . .  | 238        |
|          | CMOS peak detectors . . . . .  | 238        |
| 7.2.5    | Design case: A 2.5 V CMOS pseudologarithmic current amplifier . . . . .            | 242        |
|          | Limiting amplifier . . . . .   | 243        |
|          | Current reference . . . . .  | 245        |
|          | Current peak detector . . . . .  | 247        |
|          | Experimental results . . . . .   | 247        |
| 7.3      | Other approaches . . . . .   | 252        |
|          | Current peak detector with enhanced discharging time constant adjustment . . . . . | 252        |
|          | <b>Conclusions</b>   | <b>259</b> |
| <b>A</b> | <b>Basic distortion definitions</b>  | <b>261</b> |
| A.1      | Harmonic distortion . . . . .  | 261        |
| A.2      | Intermodulation distortion . . . . .   | 262        |
| A.3      | Distortion in feedback amplifiers . . . . .  | 263        |
| A.3.1    | Distortion in quasi-static feedback amplifiers . . . . .                           | 263        |
| A.3.2    | Distortion in dynamic feedback amplifiers . . . . .                                | 264        |

---

|          |   |            |
|----------|---|------------|
| <b>B</b> | <b>Distortion in push-pull current amplifiers</b>               | <b>269</b> |
| B.1      | Class-A operation . . . . .                                     | 269        |
| B.2      | Class-AB operation . . . . .                                    | 271        |
| <b>C</b> | <b>Distortion in CMOS operational amplifiers</b>                | <b>275</b> |
| C.1      | Miller-compensated unbuffered operational amplifier . . . . .   | 275        |
| C.2      | Folded cascode operational transconductance amplifier . . . . . | 279        |
| <b>D</b> | <b>Distortion in a dual current-mirror integrator</b>           | <b>283</b> |
| D.1      | Single-ended integrator . . . . .                               | 283        |
| D.2      | Differential integrator . . . . .                               | 286        |