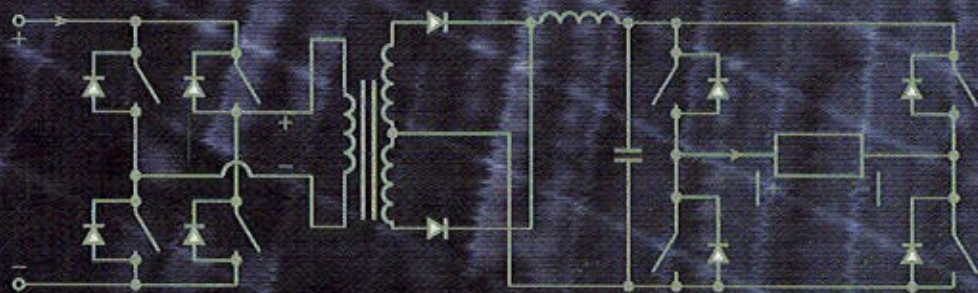


International Edition

POWER ELECTRONICS

CIRCUITS, DEVICES,
AND APPLICATIONS

THIRD EDITION



MUHAMMAD H. RASHID

Contents

Preface

xix

About the Author

xxiii

Chapter 1	Introduction	1
1.1	Applications of Power Electronics	1
1.1.1	History of Power Electronics	2
1.2	Power Semiconductor Devices	5
1.2.1	Power Diodes	5
1.2.2	Thyristors	6
1.2.3	Power Transistors	9
1.3	Control Characteristics of Power Devices	10
1.4	Characteristics and Specifications of Switches	16
1.4.1	Ideal Characteristics	16
1.4.2	Characteristics of Practical Devices	17
1.4.3	Switch Specifications	18
1.4.4	Device Choices	19
1.5	Types of Power Electronic Circuits	20
1.6	Design of Power Electronics Equipment	23
1.7	Determining the Root-Mean-Square Values of Waveforms	24
1.8	Peripheral Effects	24
1.9	Power Modules	26
1.10	Intelligent Modules	26
1.11	Power Electronics Journals and Conferences	28
	Summary	29
	References	29
	Review Questions	30
Chapter 2	Power Semiconductor Diodes and Circuits	31
2.1	Introduction	31
2.2	Semiconductor Basics	31
2.3	Diode Characteristics	33

2.4	Reverse Recovery Characteristics	35
2.5	Power Diode Types	38
2.5.1	General-Purpose Diodes	38
2.5.2	Fast-Recovery Diodes	38
2.5.3	Schottky Diodes	39
2.6	Silicon Carbide Diodes	39
2.7	Spice Diode Model	40
2.8	Series-Connected Diodes	42
2.9	Parallel-Connected Diodes	45
2.10	Diodes with RC and RL Loads	46
2.11	Diodes with LC and RLC Loads	49
2.12	Freewheeling Diodes	56
2.13	Recovery of Trapped Energy with a Diode	58
	Summary	62
	References	63
	Review Questions	63
	Problems	64
Chapter 3	Diode Rectifiers	68
3.1	Introduction	68
3.2	Single-Phase Half-Wave Rectifiers	68
3.3	Performance Parameters	69
3.4	Single-Phase Full-Wave Rectifiers	77
3.5	Single-Phase Full-Wave Rectifier with RL Load	82
3.6	Multiphase Star Rectifiers	87
3.7	Three-Phase Bridge Rectifiers	92
3.8	Three-Phase Bridge Rectifier with RL Load	95
3.9	Comparison of Diode Rectifiers	101
3.10	Rectifier Circuit Design	101
3.11	Output Voltage with LC Filter	112
3.12	Effects of Source and Load Inductances	116
	Summary	119
	References	119
	Review Questions	119
	Problems	120
Chapter 4	Power Transistors	122
4.1	Introduction	122
4.2	Bipolar Junction Transistors	123
4.2.1	Steady-State Characteristics	124
4.2.2	Switching Characteristics	128
4.2.3	Switching Limits	135
4.3	Power MOSFETs	137
4.3.1	Steady-State Characteristics	141
4.3.2	Switching Characteristics	142

4.4	COOLMOS	144
4.5	SITs	145
4.6	IGBTs	147
4.7	Series and Parallel Operation	150
4.8	di/dt and dv/dt Limitations	151
4.9	SPICE Models	155
	4.9.1 BJT SPICE Model	155
	4.9.2 MOSFET SPICE Model	155
	4.9.3 IGBT SPICE Model	158
4.10	Comparisons of Transistors	160
	Summary	160
	References	162
	Review Questions	163
	Problems	164
Chapter 5	DC–DC Converters	166
5.1	Introduction	166
5.2	Principle of Step-Down Operation	166
	5.2.1 Generation of Duty-Cycle	170
5.3	Step-Down Converter with RL Load	171
5.4	Principle of Step-Up Operation	176
5.5	Step-Up Converter with a Resistive Load	179
5.6	Performance Parameters	181
5.7	Converter Classification	182
5.8	Switching-Mode Regulators	186
	5.8.1 Buck Regulators	186
	5.8.2 Boost Regulators	190
	5.8.3 Buck–Boost Regulators	194
	5.8.4 Cúk Regulators	198
	5.8.5 Limitations of Single-Stage Conversion	204
5.9	Comparison of Regulators	205
5.10	Multioutput Boost Converter	206
5.11	Diode Rectifier-Fed Boost Converter	208
5.12	Chopper Circuit Design	211
5.13	State–Space Analysis of Regulators	217
	Summary	221
	References	221
	Review Questions	223
	Problems	224
Chapter 6	Pulse-Width-Modulated Inverters	226
6.1	Introduction	226
6.2	Principle of Operation	227
6.3	Performance Parameters	230
6.4	Single-Phase Bridge Inverters	232

6.5	Three-Phase Inverters	237
6.5.1	180-Degree Conduction	237
6.5.2	120-Degree Conduction	246
6.6	Voltage Control of Single-Phase Inverters	248
6.6.1	Single-Pulse-Width Modulation	248
6.6.2	Multiple-Pulse-Width Modulation	250
6.6.3	Sinusoidal Pulse-Width Modulation	253
6.6.4	Modified Sinusoidal Pulse-Width Modulation	257
6.6.5	Phase-Displacement Control	258
6.7	Advanced Modulation Techniques	260
6.8	Voltage Control of Three-Phase Inverters	264
6.8.1	Sinusoidal PWM	265
6.8.2	60-Degree PWM	268
6.8.3	Third-Harmonic PWM	268
6.8.4	Space Vector Modulation	271
6.8.5	Comparison of PWM Techniques	279
6.9	Harmonic Reductions	280
6.10	Current-Source Inverters	285
6.11	Variable DC-Link Inverter	288
6.12	Boost Inverter	289
6.13	Inverter Circuit Design	294
	Summary	299
	References	299
	Review Questions	300
	Problems	301

Chapter 7 Thyristors 304

7.1	Introduction	304
7.2	Thyristor Characteristics	304
7.3	Two-Transistor Model of Thyristor	307
7.4	Thyristor Turn-On	309
7.5	Thyristor Turn-Off	311
7.6	Thyristor Types	313
7.6.1	Phase-Controlled Thyristors	314
7.6.2	BCTs	314
7.6.3	Fast-Switching Thyristors	315
7.6.4	LASCs	316
7.6.5	Bidirectional Triode Thyristors	316
7.6.6	RCTs	317
7.6.7	GTOs	318
7.6.8	FET-CTHs	322
7.6.9	MTOs	323
7.6.10	ETOs	323
7.6.11	IGCTs	324
7.6.12	MCTs	325

7.6.13	SITHs	328
7.6.14	Comparisons of Thyristors	330
7.7	Series Operation of Thyristors	330
7.8	Parallel Operation of Thyristors	337
7.9	di/dt Protection	338
7.10	dv/dt Protection	339
7.11	SPICE Thyristor Model	341
7.11.1	Thyristor SPICE Model	341
7.11.2	GTO SPICE Model	343
7.11.3	MCT SPICE Model	345
7.11.4	SITH SPICE Model	345
	Summary	346
	References	347
	Review Questions	350
	Problems	350
Chapter 8	Resonant Pulse Inverters	352
8.1	Introduction	352
8.2	Series Resonant Inverters	353
8.2.1	Series Resonant Inverters with Unidirectional Switches	353
8.2.2	Series Resonant Inverters with Bidirectional Switches	361
8.3	Frequency Response of Series-Resonant Inverters	368
8.3.1	Frequency Response for Series Loaded	368
8.3.2	Frequency Response for Parallel Loaded	370
8.3.3	Frequency Response for Series-Parallel Loaded	372
8.4	Parallel Resonant Inverters	374
8.5	Voltage Control of Resonant Inverters	377
8.6	Class E Resonant Inverter	380
8.7	Class E Resonant Rectifier	383
8.8	Zero-Current-Switching Resonant Converters	388
8.8.1	L -Type ZCS Resonant Converter	389
8.8.2	M -Type ZCS Resonant Converter	391
8.9	Zero-Voltage-Switching Resonant Converters	393
8.10	Comparisons Between ZCS and ZVS Resonant Converters	396
8.11	Two-Quadrant ZVS Resonant Converters	396
8.12	Resonant DC-Link Inverters	399
	Summary	402
	References	403
	Review Questions	403
	Problems	404
Chapter 9	Multilevel Inverters	406
9.1	Introduction	406
9.2	Multilevel Concept	407

9.3	Types of Multilevel Inverters	408
9.4	Diode-Clamped Multilevel Inverter	409
	9.4.1 Principle of Operation	410
	9.4.2 Features of Diode-Clamped Inverter	411
	9.4.3 Improved Diode-Clamped Inverter	412
9.5	Flying-Capacitors Multilevel Inverter	414
	9.5.1 Principle of Operation	415
	9.5.2 Features of Flying-Capacitors Inverter	417
9.6	Cascaded Multilevel Inverter	417
	9.6.1 Principle of Operation	418
	9.6.2 Features of Cascaded Inverter	419
9.7	Applications	421
	9.7.1 Reactive Power Compensation	422
	9.7.2 Back-to-Back Intertie	423
	9.7.3 Adjustable Speed Drives	424
9.8	Switching Device Currents	424
9.9	DC-Link Capacitor Voltage Balancing	425
9.10	Features of Multilevel Inverters	427
9.11	Comparisons of Multilevel Converters	428
	Summary	428
	References	429
	Review Questions	430
	Problems	430

Chapter 10 Controlled Rectifiers 431

10.1	Introduction	431
10.2	Principle of Phase-Controlled Converter Operation	432
10.3	Single-Phase Full Converters	434
	10.3.1 Single-Phase Full Converter with RL Load	438
10.4	Single-Phase Dual Converters	440
10.5	Principle of Three-Phase Half-Wave Converters	443
10.6	Three-Phase Full Converters	447
	10.6.1 Three-Phase Full Converter with RL Load	451
10.7	Three-Phase Dual Converters	453
10.8	Power Factor Improvements	456
	10.8.1 Extinction Angle Control	456
	10.8.2 Symmetric Angle Control	457
	10.8.3 PWM Control	461
	10.8.4 Single-Phase Sinusoidal PWM	463
	10.8.5 Three-Phase PWM Rectifier	465
10.9	Single-Phase Semiconverters	467
	10.9.1 Single-Phase Semiconverter with RL Load	472
10.10	Three-Phase Semiconverters	474
	10.10.1 Three-Phase Semiconverters with RL Load	479
10.11	Single-Phase Series Converters	480
10.12	Twelve-Pulse Converters	485

10.13	Design of Converter Circuits	487
10.14	Effects of Load and Source Inductances	492
	Summary	494
	References	495
	Review Questions	496
	Problems	497

Chapter 11 AC Voltage Controllers 500

11.1	Introduction	500
11.2	Principle of On–Off Control	501
11.3	Principle of Phase Control	503
11.4	Single-Phase Bidirectional Controllers with Resistive Loads	506
11.5	Single-Phase Controllers with Inductive Loads	509
11.6	Three-Phase Full-Wave Controllers	514
11.7	Three-Phase Bidirectional Delta-Connected Controllers	518
11.8	Single-Phase Transformer Connection Changers	522
11.9	Cycloconverters	526
	11.9.1 Single-Phase Cycloconverters	527
	11.9.2 Three-Phase Cycloconverters	530
	11.9.3 Reduction of Output Harmonics	530
11.10	AC Voltage Controllers with PWM Control	534
11.11	Matrix Converter	536
11.12	Design of AC Voltage-Controller Circuits	537
11.13	Effects of Source and Load Inductances	545
	Summary	546
	References	547
	Review Questions	547
	Problems	548

Chapter 12 Static Switches 551

12.1	Introduction	551
12.2	Single-Phase AC Switches	551
12.3	Three-Phase AC Switches	554
12.4	Three-Phase Reversing Switches	554
12.5	AC Switches for Bus Transfer	556
12.6	DC Switches	557
12.7	Solid-State Relays	561
12.8	Microelectronic Relays	563
	12.8.1 Photovoltaic Relay	563
	12.8.2 Photovoltaic Isolators	565
12.9	Design of Static Switches	566
	Summary	567
	References	567
	Review Questions	568
	Problems	568

Chapter 13	Flexible AC Transmission Systems	570
13.1	Introduction	570
13.2	Principle of Power Transmission	571
13.3	Principle of Shunt Compensation	573
13.4	Shunt Compensators	575
13.4.1	Thyristor-Controlled Reactor	575
13.4.2	Thyristor-Switched Capacitor	577
13.4.3	Static VAR Compensator	580
13.4.4	Advanced Static VAR Compensator	581
13.5	Principle of Series Compensation	582
13.6	Series Compensators	585
13.6.1	Thyristor-Switched Series Capacitor	585
13.6.2	Thyristor-Controlled Series Capacitor	586
13.6.3	Forced-Commutation-Controlled Series Capacitor	587
13.6.4	Series Static VAR Compensator	589
13.6.5	Advanced SSVC	589
13.7	Principle of Phase-Angle Compensation	592
13.8	Phase-Angle Compensator	594
13.9	Unified Power Flow Controller	596
13.10	Comparisons of Compensators	597
	Summary	598
	References	598
	Review Questions	599
	Problems	599
Chapter 14	Power Supplies	601
14.1	Introduction	601
14.2	DC Power Supplies	602
14.2.1	Switched-Mode DC Power Supplies	602
14.2.2	Flyback Converter	602
14.2.3	Forward Converter	606
14.2.4	Push-Pull Converter	611
14.2.5	Half-Bridge Converter	613
14.2.6	Full-Bridge Converter	616
14.2.7	Resonant DC Power Supplies	619
14.2.8	Bidirectional Power Supplies	619
14.3	AC Power Supplies	621
14.3.1	Switched-Mode AC Power Supplies	623
14.3.2	Resonant AC Power Supplies	623
14.3.3	Bidirectional AC Power Supplies	624
14.4	Multistage Conversions	625
14.5	Control Circuits	626
14.6	Magnetic Design Considerations	630
14.6.1	Transformer Design	630
14.6.2	DC Inductor	634

14.6.3	Magnetic Saturation	635
	Summary	636
	References	636
	Review Questions	637
	Problems	637
Chapter 15	DC Drives	640
15.1	Introduction	640
15.2	Basic Characteristics of DC Motors	641
15.3	Operating Modes	645
15.4	Single-Phase Drives	648
15.4.1	Single-Phase Half-Wave-Converter Drives	649
15.4.2	Single-Phase Semiconverter Drives	650
15.4.3	Single-Phase Full-Converter Drives	651
15.4.4	Single-Phase Dual-Converter Drives	652
15.5	Three-Phase Drives	656
15.5.1	Three-Phase Half-Wave-Converter Drives	657
15.5.2	Three-Phase Semiconverter Drives	657
15.5.3	Three-Phase Full-Converter Drives	657
15.5.4	Three-Phase Dual-Converter Drives	658
15.6	DC–DC Converter Drives	662
15.6.1	Principle of Power Control	662
15.6.2	Principle of Regenerative Brake Control	664
15.6.3	Principle of Rheostatic Brake Control	667
15.6.4	Principle of Combined Regenerative and Rheostatic Brake Control	668
15.6.5	Two- and Four-Quadrant DC–DC Converter Drives	669
15.6.6	Multiphase DC–DC Converters	670
15.7	Closed-Loop Control of DC Drives	673
15.7.1	Open-Loop Transfer Function	673
15.7.2	Closed-Loop Transfer Function	678
15.7.3	Phase-Locked-Loop Control	684
15.7.4	Microcomputer Control of DC Drives	685
	Summary	687
	References	687
	Review Questions	688
	Problems	688
Chapter 16	AC Drives	692
16.1	Introduction	692
16.2	Induction Motor Drives	693
16.2.1	Performance Characteristics	694
16.2.2	Stator Voltage Control	701
16.2.3	Rotor Voltage Control	703
16.2.4	Frequency Control	711

16.2.5	Voltage and Frequency Control	713
16.2.6	Current Control	716
16.2.7	Voltage, Current, and Frequency Control	720
16.3	Closed-Loop Control of Induction Motors	721
16.4	Vector Controls	726
16.4.1	Basic Principle of Vector Control	727
16.4.2	Direct and Quadrature-Axis Transformation	728
16.4.3	Indirect Vector Control	734
16.4.4	Director Vector Control	736
16.5	Synchronous Motor Drives	738
16.5.1	Cylindrical Rotor Motors	738
16.5.2	Salient-Pole Motors	741
16.5.3	Reluctance Motors	743
16.5.4	Permanent-Magnet Motors	743
16.5.5	Switched Reluctance Motors	744
16.5.6	Closed-Loop Control of Synchronous Motors	745
16.5.7	Brushless DC and AC Motor Drives	747
16.6	Stepper Motor Control	749
16.6.1	Variable-Reluctance Stepper Motors	750
16.6.2	Permanent-Magnet Stepper Motors	753
	Summary	756
	References	756
	Review Questions	757
	Problems	758

Chapter 17 Gate Drive Circuits 761

17.1	Introduction	761
17.2	MOSFET Gate Drive	761
17.3	BJT Base Drive	763
17.4	Isolation of Gate and Base Drives	767
17.4.1	Pulse Transformers	769
17.4.2	Optocouplers	769
17.5	Thyristor Firing Circuits	770
17.6	Unijunction Transistor	772
17.7	Programmable Unijunction Transistor	775
17.8	Thyristor Converter Gating Circuits	777
17.9	Gate Drive ICs	777
17.9.1	Drive IC for Converters	781
17.9.2	High-Voltage IC for Motor Drives	784
	Summary	788
	References	789
	Review Questions	789
	Problems	790

Chapter 18	Protection of Devices and Circuits	791
18.1	Introduction	791
18.2	Cooling and Heat Sinks	791
18.3	Thermal Modeling of Power Switching Devices	797
18.3.1	Electrical Equivalent Thermal Model	798
18.3.2	Mathematical Thermal Equivalent Circuit	800
18.3.3	Coupling of Electrical and Thermal Components	801
18.4	Snubber Circuits	803
18.5	Reverse Recovery Transients	804
18.6	Supply- and Load-Side Transients	810
18.7	Voltage Protection by Selenium Diodes and Metal Oxide Varistors	813
18.8	Current Protections	815
18.8.1	Fusing	815
18.8.2	Fault Current with AC Source	822
18.8.3	Fault Current with DC Source	824
18.9	Electromagnetic Interference	827
18.9.1	Sources of EMI	828
18.9.2	Minimizing EMI Generation	828
18.9.3	EMI Shielding	829
18.9.4	EMI Standards	829
	Summary	830
	References	831
	Review Questions	831
	Problems	832
Appendix A	Three-Phase Circuits	835
Appendix B	Magnetic Circuits	839
Appendix C	Switching Functions of Converters	847
Appendix D	DC Transient Analysis	853
Appendix E	Fourier Analysis	857
Bibliography		860
Answers to Selected Problems		863
Index		871