

Electronic Devices

a design approach

Ali Aminian
Marian Kazimierczuk

CONTENTS

Chapter 1 Semiconductor Theory and the *P-N* Junction Diode

- 1.1 Introduction 1
- 1.2 A Brief Review of Atomic Theory 2
- 1.3 The *P-N* Junction 7
- 1.4 The *P-N* Junction Diode 12
 - Diode I-V Characteristics 12
 - Temperature Effects 14
 - The Diode Equation 15
 - DC and AC Resistances of the Diode 16
 - Basic Diode Circuits 20
 - Diode Switching Circuits 23
- 1.5 Zener Diode 24
- 1.6 Light-Emitting Diode 28
- 1.7 Summary 30
- 1.8 Device Specifications and Data Sheets 32
- Problems 38

Chapter 2 Diode Applications

- 2.1 Introduction 43
- 2.2 The Basic Power Supply 44
 - The Transformer 44
 - Half-Wave Rectifier 45
 - Full-Wave Rectifier 47
 - Filtering 53
 - Regulation 56
 - Regulated Power Supply 58
- 2.3 Summary 62
- Problems 63

Chapter 3 Bipolar Junction Transistors and DC Biasing the BJT Amplifier

- 3.1 Introduction 67
- 3.2 Basic Theory of BJT Operation 68
- 3.3 Common-Emitter Characteristics 71
- 3.4 Biasing the Common-Emitter Amplifier 76
 - The Base Bias 77
 - Emitter Bias 81
 - Voltage-Divider Bias 84
- 3.5 Biasing the Common-Collector Amplifier 88
- 3.6 Biasing the Common-Base Amplifier 89
- 3.7 DC Bias Analysis of the Cascode Amplifier 91
- 3.8 Reading the Transistor Data Sheets 93

3.9	DC Bias Design of BJT Amplifiers	94
3.10	The Transistor Switch	100
3.11	Summary	105
3.12	Device Specifications and Data Sheets	107
	Problems	116
Chapter 4	Transistor Modeling	
4.1	Introduction	121
4.2	The r -parameter Model	122
4.3	The Hybrid or h -parameter Model	131
	Problems	149
Chapter 5	Small-Signal Operation of the BJT Amplifier	
5.1	Introduction	155
5.2	The BJT Amplifier Fundamentals	157
5.3	Analysis of the BJT Amplifier	163
5.4	The Cascode Amplifier	183
5.5	Troubleshooting	187
5.6	Summary	191
	Problems	193
Chapter 6	Design of the Small-Signal BJT Amplifier	
6.1	Introduction	199
6.2	The AC Load Line and the Output Signal Swing	200
6.3	A Brief Introduction to Frequency Response	210
6.4	Design of the Common-Emitter Amplifier	212
6.5	Design of the Cascode Amplifier	219
6.6	Summary	224
	Problems	225
Chapter 7	Field-Effect Transistors	
7.1	Introduction	227
7.2	Junction Field-Effect Transistors (JFET)	228
	▪ JFET Structure and Characteristics	228
	▪ DC Biasing the JFET	235
	▪ Self-Bias	237
	▪ Voltage-Divider Bias	246
	▪ DC Bias Design of the JFET	254
7.3	Metal-Oxide Semiconductor FET (MOSFET)	261
	▪ Depletion MOSFET	261
	▪ Enhancement MOSFET	264
	▪ DC Biasing the Enhancement MOSFET	267
	▪ DC Bias Design of the MOSFET Amplifier	275
7.4	Summary	279

7.5	Device Specifications and Data Sheets	280
	Problems	284
Chapter 8	Small-Signal Operation of the FET Amplifier	
8.1	Introduction	289
8.2	Small-Signal Circuit Model of FET	290
8.3	Analysis of the Common-Source JFET Amplifier	294
8.4	Analysis of the Common-Drain JFET Amplifier	303
8.5	Analysis of the Enhancement MOSFET Amplifier	310
8.6	Analysis of the Common-Gate MOSFET Amplifier	323
8.7	Analysis of the FET Cascode Amplifier	327
8.8	Design of Small-Signal JFET and MOSFET Amplifiers	330
8.9	Summary	340
	Problems	343
Chapter 9	Frequency Response of BJT and FET Amplifiers	
9.1	Introduction	349
9.2	Frequency Response Fundamentals	349
9.3	Frequency Response of the CE BJT Amplifier	359
9.4	Frequency Response Plot of the CE BJT Amplifier	375
9.5	Frequency Response of the CB BJT Amplifier	377
9.6	Frequency Response of the BJT Cascode Amplifier	380
9.7	Frequency Response of the FET Amplifier	384
9.8	Frequency Response of the FET Cascode Amplifier	391
9.9	Summary	394
	Problems	396
Chapter 10	Current-Mirror Current Sources and Differential Amplifiers	
10.1	Introduction	401
10.2	Current-Mirror Current Sources	402
	▪ Basic Current Mirror	402
	▪ Wilson Current-Mirror	404
	▪ MOSFET Current-Mirror	408
10.3	Differential Amplifier	412
10.4	The Basic Differential Amplifier Circuit	415
10.5	Diff-Amp with Current-Mirror Current Source	424
	▪ Diff-Amp with Basic Current-Mirror	425
	▪ Diff-Amp with Wilson Current-Mirror	428
10.6	MOSFET Differential Amplifier	439
	▪ Diff-Amp with Basic MOSFET Current-Mirror	440
	▪ Diff-Amp with Cascode MOSFET Current-Mirror	444
10.7	Summary	446
	Problems	447

Chapter 11 Operational Amplifiers

11.1	Introduction	453	
11.2	Operational Amplifier	454	
11.3	Open-Loop Operation	456	
11.4	Closed-Loop Operation	464	
11.5	Basic Op-Amp Configurations	465	
	▪ Inverting Amplifier	465	
	▪ Non-Inverting Amplifier	471	
	▪ Unity-Gain Buffer	472	
	▪ Compensation Resistor	476	
11.6	Summing Amplifiers	479	
	▪ Inverting Summer	479	
	▪ Non-Inverting Summer	481	
11.7	Difference Amplifier	486	
	▪ Noise Suppression	488	
	▪ Instrumentation Amplifier	490	
11.8	Integrator and Differentiator	494	
11.9	Summary	504	
11.10	Device Specifications and Data Sheets	506	
	Problems	516	

Chapter 12 Negative Feedback, Op-Amp Characteristics

12.1	Introduction	523	
12.2	Negative Feedback	524	
	▪ Stability	524	
12.3	Basic Feedback Topologies	526	
	▪ Series-Shunt Feedback	526	
12.4	Op-Amp Characteristics	539	
	▪ DC Characteristics	539	
	▪ AC Characteristics	541	
12.5	Single-Supply Operation	545	
12.6	Summary	553	
12.7	Device Specifications and Data Sheets	554	
	Problems	561	

Chapter 13 Power Amplifiers and Output Stages

13.1	Introduction	565	
13.2	Classes of Operation	566	
13.3	Class A Power Amplifier	567	
13.4	Class B Push-Pull Power Amplifier	568	
13.5	Class AB Push-Pull Power Amplifier	577	
13.6	Heat Sinks and Thermal Considerations	585	
13.7	Summary	588	

Chapter 14 Active Filters

14.1	Introduction	595
14.2	Active Filters	596
14.3	First-Order Low-Pass Active Filter	596
14.4	First-Order High-Pass Active Filter	600
14.5	Design of the First-Order Active Filter	604
14.6	Second-Order Active Filters	608
	▪ Second-Order Low-Pass Active Filter	610
	▪ Second-Order High-Pass Active Filter	612
	▪ Sallen-Key Unity-Gain Active Filter	613
	▪ Sallen-Key Equal Component Active Filter	615
	▪ Design of the Second-Order Active Filter	619
14.7	Higher Order Active Filters	625
14.8	Band-Pass Active Filter	633
14.9	Band-Stop Active Filter	639
14.10	Summary	644
	Problems	645

Chapter 15 IC Regulators and Switching Power Supplies

15.1	Introduction	649
15.2	Integrated Circuit Regulators	650
15.3	Switching Power Supplies	658
	▪ Buck (Step-Down) DC-DC Converter	659
	▪ Boost (Step-Up) DC-DC Converter	669
	▪ Buck-Boost (Inverting Step-Down/Up) DC-DC Converter	678
15.4	Summary	688
15.5	Device Specifications and Data Sheets	689
	Problems	702

Chapter 16 Oscillators and Waveform Generators

16.1	Introduction	705
16.2	Oscillator Principles of Operation	706
16.3	RC Phase-Shift Oscillator	707
16.4	Wien-Bridge Oscillator	711
16.5	Colpitts Oscillator	715
16.6	Hartley Oscillator	717
16.7	Square-Wave Generator	720
16.8	The 555 Timer	722
16.9	Function Generator	726
	▪ Sine-Wave and Square-Wave Generation	726
	▪ Pulse and Ramp Generation	727
	▪ FSK Generation	729

16.10	Summary	730
	Problems	732

Chapter 17 Digital-to-Analog and Analog-to-Digital Conversion

17.1	Introduction	735
17.2	Digital-to-Analog Conversion	736
	▪ R-2R Ladder DAC	736
	▪ Binary-Weighted Resistor DAC	740
	▪ Monolithic Integrated Circuit DAC	742
17.3	Analog-to-Digital Conversion	743
	▪ Successive Approximation ADC	743
	▪ Monolithic Integrated Circuit ADC	744
	▪ Mixed Signal Design Example	746
17.4	Summary	749
	Problems	751

Chapter 18 Four-Layer Electronic Devices and Optoelectronic Devices

18.1	Introduction	753
18.2	Four-Layer Devices	754
	▪ Silicon Controlled Rectifier (SCR)	754
	▪ Silicon Controlled Switch (SCS)	757
	▪ DIACs and TRIACs	758
18.3	Optoelectronic Devices	763
	▪ Photoresistors	763
	▪ Photodiodes	764
	▪ Phototransistors	766
	▪ Optocouplers	766
18.4	Summary	768
18.5	Device Specifications and Data Sheets	770
	Problems	789