

SECOND EDITION

# Electronics and Circuit Analysis Using MATLAB®

JOHN OKYERE ATTIA



CRC PRESS

---

# **Contents**

---

<b>1</b>	<b>MATLAB Fundamentals .....</b>	<b>1</b>
1.1	MATLAB Basic Operations .....	1
1.2	Matrix Operations.....	3
1.3	Array Operations .....	7
1.4	Complex Numbers .....	9
1.5	The Colon Symbol (:) .....	11
1.6	M-Files .....	14
1.6.1	Script Files .....	15
1.6.2	Function Files.....	16
1.7	Mathematical Functions .....	19
	Bibliography .....	21
	Problems.....	21
<b>2</b>	<b>Plotting Functions.....</b>	<b>25</b>
2.1	Graph Functions .....	25
2.2	X-Y Plots and Annotations.....	25
2.3	Logarithmic and Polar Plots .....	30
2.4	Subplots and Screen Control .....	33
2.5	Other Plotting Functions .....	35
2.5.1	Bar Plots .....	35
2.5.2	Hist Function .....	36
2.5.3	Stem Plots .....	36
	Bibliography .....	38
	Problems.....	39
<b>3</b>	<b>Control Statements .....</b>	<b>43</b>
3.1	"For" Loops .....	43
3.2	"If" Statements .....	44
3.3	"While" Loops.....	52
3.4	Input/Output Commands .....	53
	Bibliography .....	58
	Problems.....	58
<b>4</b>	<b>DC Analysis.....</b>	<b>63</b>
4.1	Nodal Analysis.....	63
4.2	Loop Analysis.....	68
4.3	Maximum Power Transfer .....	77
4.3.1	MATLAB Diff and Find Functions.....	79

<b>Bibliography .....</b>	82
<b>Problems.....</b>	82
<b>5 Transient Analysis .....</b>	87
5.1 RC Network.....	87
5.2 RL Network .....	91
5.3 RLC Circuit.....	95
5.4 State Variable Approach .....	100
5.4.1 MATLAB Ode Functions .....	104
<b>Bibliography .....</b>	112
<b>Problems.....</b>	112
<b>6 AC Analysis and Network Functions.....</b>	117
6.1 Steady-State AC Power.....	117
6.1.1 MATLAB Functions quad and quad8 .....	119
6.2 Single- and Three-Phase AC Circuits .....	121
6.3 Network Characteristics .....	132
6.3.1 MATLAB Functions roots, residue, and polyval .....	133
6.4 Frequency Response.....	139
6.4.1 MATLAB Function freqs.....	140
<b>Bibliography .....</b>	145
<b>Problems.....</b>	146
<b>7 Two-Port Networks .....</b>	151
7.1 Two-Port Network Representations .....	151
7.1.1 z-Parameters.....	151
7.1.2 y-Parameters .....	153
7.1.3 h-Parameters .....	155
7.1.4 Transmission Parameters .....	157
7.2 Conversion of Two-Port Parameters .....	160
7.3 Interconnection of Two-Port Networks .....	163
7.4 Terminated Two-Port Networks.....	169
<b>Bibliography .....</b>	175
<b>Problems.....</b>	176
<b>8 Fourier Analysis .....</b>	183
8.1 Fourier Series.....	183
8.2 Average Power and Harmonic Distortion.....	193
8.3 Fourier Transforms .....	197
8.3.1 Properties of the Fourier Transform .....	197
8.4 Discrete and Fast Fourier Transforms .....	199
8.4.1 MATLAB Function fft.....	201
<b>Bibliography .....</b>	206
<b>Problems.....</b>	207

<b>9</b>	<b>Diodes .....</b>	<b>213</b>
9.1	Diode Characteristics .....	213
9.1.1	Forward-Biased Region.....	214
9.1.2	MATLAB Function polyfit.....	215
9.1.3	Temperature Effects .....	217
9.2	Analysis of Diode Circuits .....	218
9.3	Half-Wave Rectifier .....	224
9.3.1	MATLAB Function fzero.....	229
9.4	Full-Wave Rectification.....	231
9.5	Zener Diode Voltage Regulator Circuits.....	236
	Bibliography .....	241
	Problems .....	242
<b>10</b>	<b>Semiconductor Physics.....</b>	<b>247</b>
10.1	Intrinsic Semiconductors .....	247
10.1.1	Energy Bands .....	247
10.1.2	Mobile Carriers.....	248
10.2	Extrinsic Semiconductor .....	250
10.2.1	Electron and Hole Concentrations .....	250
10.2.2	Fermi Level.....	253
10.2.3	Current Density and Mobility.....	254
10.3	pn Junction: Contact Potential, Junction Current .....	259
10.3.1	Contact Potential .....	259
10.3.2	Junction Current.....	264
10.4	Depletion and Diffusion Capacitances.....	269
10.4.1	Depletion Capacitance.....	269
10.4.2	Diffusion Capacitance.....	274
10.5	Breakdown Voltages of pn Junctions .....	276
	References.....	280
	Problems .....	281
<b>11</b>	<b>Operational Amplifiers.....</b>	<b>285</b>
11.1	Properties of the Op Amp .....	285
11.2	Inverting Configuration.....	287
11.3	Noninverting Configuration .....	293
11.4	Effect of Finite Open-Loop Gain .....	297
11.5	Frequency Response of Op Amps .....	300
11.6	Slew Rate and Full-Power Bandwidth.....	304
11.7	Common-Mode Rejection.....	307
	Bibliography .....	311
	Problems .....	312
<b>12</b>	<b>Transistor Circuits.....</b>	<b>315</b>
12.1	Bipolar Junction Transistors .....	315
12.2	Biasing BJT Discrete Circuits .....	322

12.2.1	Self-Bias Circuit .....	322
12.2.2	Bias Stability.....	324
12.3	Integrated Circuit Biasing .....	329
12.3.1	Simple Current Mirror .....	330
12.3.2	Wilson Current Source .....	332
12.4	Frequency Response of Common-Emitter Amplifier .....	335
12.5	MOSFET Characteristics.....	340
12.6	Biassing of MOSFET Circuits .....	343
12.7	Frequency Response of Common-Source Amplifier.....	352
	Bibliography .....	357
	Problems.....	357
<b>13</b>	<b>Electronic Data Analysis .....</b>	<b>361</b>
13.1	Save, Load, and Textread Functions.....	361
13.1.1	Save and Load Functions.....	361
13.1.2	Textread Function.....	362
13.2	Statistical Analysis.....	366
13.3	Curve Fitting .....	369
13.4	Other Functions for Data Analysis .....	373
13.4.1	Integration Function (trapz) .....	373
	Bibliography .....	377
	Problems.....	378
<b>Index .....</b>		<b>383</b>