



POWER CONVERTER CIRCUITS

WILLIAM SHEPHERD
LI ZHANG

Contents

Preface

Nomenclature

vii

Part 1 AC to DC Converters (Rectifiers)

1. Switching and Semiconductor Switches	1
2. Single-Phase Uncontrolled Rectifier Circuits	13
3. Single-Phase Controlled Rectifier Circuits	52
4. Three-Phase, Half-Wave, Uncontrolled (Diode) Bridge Rectifier Circuits	96
5. Three-Phase Half-Wave Controlled Bridge Rectifier Circuits	136
6. Three-Phase Full-Wave Uncontrolled Bridge Rectifier Circuits	179
7. Three-Phase Full-Wave Controlled Bridge Rectifier Circuits with Passive Load Impedance	216
8. Rectifier Power Factor and Pulse-Width Modulation Controlled Rectifier Circuits	267

Part 2 DC to AC Converters (Inverters)

- | | |
|--|-----|
| 9. Three-Phase, Naturally Commutated, Controlled Bridge Rectifier-Inverter | 290 |
| 10. Three-Phase Step-Wave Inverter Circuits | 309 |
| 11. Three-Phase, Pulse-Width Modulation, Controlled Inverter Circuits | 340 |

Part 3 AC to AC Converters

- | | |
|--------------------------------------|-----|
| 12. Phase-Controlled Cycloconverters | 364 |
| 13. Envelope Cycloconverters | 397 |
| 14. Matrix Converters | 415 |

Part 4 DC to DC Converters

- | | |
|--|-----|
| 15. DC-DC Circuits Converter | 445 |
| 16. Switch-Mode Converter Power Supplies | 478 |

<i>Appendix: General Expressions for Fourier Series</i>	508
---	-----

<i>Answers to Problems</i>	510
----------------------------	-----

<i>References</i>	532
-------------------	-----

<i>Index</i>	535
--------------	-----