

Switching Power Supply Design & Optimization

- ✓ Thermal management techniques
- ✓ Key supply design equations and calculations
- ✓ Designing for PCBs
- ✓ Power supply design FAQ

Sanjaya Maniktala

Contents

Preface	x1
Acknowledgments	xv
About the Authors	xvii
Chapter 1. Overview of Switching Power	1
1.1 Introduction	1
1.2 The Voltsseconds Law	3
1.3 Basic Waveform Analysis	4
1.4 The r and K of the Current Waveform	7
1.5 Basic Design Procedure for Inductors	9
1.6 Calculating RMS Current for Capacitors	10
1.7 Topologies and Worst-Case Capacitor Currents	11
1.8 Worst-Case Input Voltage for a Power Supply	13
1.9 Using Too High an Inductance (small r)	15
1.10 The Flat-Top Approximation	16
1.11 Tolerance of Set Output Voltage	20
1.12 Preferred Resistor Values	23
1.13 Optimum Divider Selection	25
Chapter 2. DC-DC Converters and Their Configurations	31
2.1 Introduction	31
2.2 What Is Ground?	32
2.3 The N-switch and P-switch	33
2.4 The LSD Cell	34
2.5 Configurations of Switching Regulator Topologies	36
2.6 Basic Types of Switcher ICs	38
2.7 Flyback/Buck-Boost/Boost ICs Compared	40
2.8 Other Possible Applications of Buck and Buck-Boost ICs	42
2.9 Some Practical Cases	51
2.10 Differential Voltage Sensing	55
2.11 Some Topology Nuances	56
2.12 Composite Topologies	58

Chapter 3. Reference Equations and Graphs for Converter Design	61
3.1 The Defining Difference between the Topologies	61
3.2 Definition of Current Ripple Ratio	61
3.3 Graphical Tools for Inductor Selection	62
3.4 The Design Equations Table	66
Chapter 4. Discontinuous Conduction Mode Equations	69
4.1 Introduction	69
4.2 How DCM Equations Are Calculated	71
4.3 The Duty Cycle Equations	75
Chapter 5. Front-End of Off-Line Power Supplies	77
5.1 Conventional Front-End Design	77
5.1.1 Input voltage shape	77
5.1.2 The Input current shape	84
5.2 Front-End with PFC	87
5.2.1 Regulatory issues	87
5.2.2 Boost PFC	89
5.2.3 Capacitor selection	92
5.2.4 Synchronizing the PFC and PWM stages	95
5.2.5 Synchronization over a wide input range	98
5.2.6 Calculating the high- and low-frequency rms components	100
5.2.7 Sequencing, protection, and some related observations	101
5.2.8 Core losses in the PFC choke	106
Chapter 6. Isolated Topologies for Off-Line Applications	109
6.1 The Forward Converter	109
6.1.1 Introduction and overview	109
6.2 The Flyback Topology	114
6.2.1 Introduction	114
6.2.2 The integrated power switch	114
6.2.3 The equivalent buck-boost models	115
6.2.4 A worked example	121
6.2.5 Dealing with multi-output converters	121
6.2.6 The primary-side leakage term	123
6.2.7 The secondary-side leakage term	125
6.2.8 Optimization and analysis	129
6.2.9 Dissipation estimates and efficiency	140
6.2.10 Practical flyback designs using 600-V switches	144
6.2.11 Diode rating for higher V_{OR}	145
6.2.12 Pulse-skipping and required preload	145
6.2.13 Overload protection	149
Chapter 7. Concepts in Magnetics	153
7.1 Basic Magnetic Concepts and Definitions (MKS Units)	153
7.2 The Inductor Equation	154
7.3 The Voltage-Independent Equation	155
7.4 The Voltage-Dependent Equation	157

7.5 Units in Magnetics	161
7.6 The Magnetomotive Force (mmf) Equation	163
7.7 Effective Area and Effective Length	165
7.8 The Effect of the Air Gap	166
7.9 The Gap Factor z	168
7.10 The Origin and Significance of z	169
7.11 Relating B to H	171
7.12 E-cores	171
7.13 Energy Storage Considerations	172
First study: ampere-turns constant, ($N = \text{constant}$)	174
Second study: B constant, ($N \propto z$)	174
Third study: L constant, ($N \propto z^{1/2}$)	175
7.14 How an Air Gap Helps	176
7.15 Understanding L	178
7.16 Difference between an Inductor and (Flyback) Transformer	180
7.17 Transformers	181
7.18 Fringing Flux Correction	185
7.19 Worked Example	188
Chapter 8. Tapped-Inductor Topologies	191
8.1 The Tapped-Inductor Buck	191
8.2 Other Tapped-Inductor Stages and Duty Cycle	196
Chapter 9. Selecting Inductors for DC-DC Converters	199
9.1 Introduction	199
9.2 Specifying the Current Ripple Ratio r	202
9.3 Mapping the Inductor	203
9.4 Voltseconds	204
9.5 Choosing r and L	205
9.6 B in Terms of Current	208
9.7 A Feel for Core Loss Optimization by Understanding Variations	210
Varying the volume of the core	210
Varying the frequency	212
9.8 A Walk-Through Example	214
9.9 Choosing an Inductor	215
9.10 Evaluating the Inductor in Our Application	216
Chapter 10. Flyback Transformer Design	223
10.1 Design Equations	223
10.2 Worked Example (Part 1)	226
10.3 Some Finer Points of Optimization	230
10.4 Rule of Thumb for Quick Selection of Flyback Transformer Cores	231
10.5 Worked Example (Part 2)	232
10.6 Circular mils (cmils)	234
10.7 Current Carrying Capacity of Wires	235
10.8 Skin Depth	237

10.9 A Feel for Wire Gauges	242
10.10 Diameter of Coated Wire	244
10.11 SWG Comparison	245
Chapter 11. Forward Converter Magnetics Design	249
11.1 Introduction	249
11.2 The Transformer and Choke Compared	249
11.3 Introducing the Proximity Effect	253
11.4 More about Skin Depth	254
11.5 Dowell's Equations	256
11.6 The Equivalent Foil Transformation	263
11.7 Some Useful Equations for Quick Selection of Forward Converter Cores	265
11.8 Stacking Wires and Bundles	268
11.9 Core Loss Calculations	269
Chapter 12. PCBs and Layout	273
12.1 Introduction	273
12.2 Trace Analysis	273
12.3 Miscellaneous Points to Note	276
12.4 Routing the Feedback Trace	279
12.5 The Ground Plane	280
12.6 Some Manufacturing Issues	282
12.7 PCB Vendors and Gerber Files	285
Chapter 13. Thermal Management	287
13.1 Introduction	287
13.2 Thermal Measurements and Efficiency Estimates	288
13.3 The Equations of Natural Convection	290
13.4 Historical Definitions	291
13.5 Available Equations	292
13.6 Manipulating the Equations	294
13.7 Comparing the Two Standard Equations	295
13.8 h from Thermodynamic Theory	296
13.9 Working with the Tables of the Standard Equations	297
13.10 PCBs for Heatsinking	301
13.11 Natural Convection at an Altitude	303
13.12 Forced Air Cooling	303
13.13 Radiative Heat Transfer	305
13.14 Miscellaneous Issues	306
Chapter 14. Stabilizing Current Mode Converters	309
14.1 Background	309
14.2 Why Slope Compensation?	312
14.3 Generalized Rule for Avoiding Subharmonic Instability	316

Chapter 15. Practical EMI Filter Design	319
15.1 The CISPR 22 Standard	319
15.2 The LISN	320
15.3 Fourier Series	321
15.4 The Trapezoid	322
15.5 Practical DM Filter Design	323
15.6 Practical CM Filter Design	326
Chapter 16. Things to Try	331
16.1 Introduction	331
16.2 Synchronizing two 3844 ICs	331
16.3 A Self-Oscillating Low-Cost Standby/Auxiliary Power Supply	332
16.4 An Adapter with Battery Charging Function	334
16.5 Paralleling Bridge Rectifiers	335
16.6 Self-Contained Inrush Protection Circuit	335
16.7 Cheap Power Good Signal	336
16.8 An Overcurrent Protection Circuit	336
16.9 Another Overcurrent Protection Circuit	337
16.10 Adding Overtemperature Protection to the 384x Series	337
16.11 Turn-On Snubber for PFC	338
16.12 A Unique Active Inrush Protection Circuit	339
16.13 Floating Drive from a 384x Controller	340
16.14 Floating Buck Topology	340
16.15 Symmetrical Boost Topology	341
16.16 A Slave Converter	342
16.17 A Boost Preregulator with a Regulated Auxiliary Output	343
Chapter 17. Reliability, Testing, and Safety Issues	345
17.1 Introduction	345
17.2 Reliability Definitions	345
17.3 Chi-Square Distribution	347
17.4 Chargeable Failures	349
17.5 Warranty Costs	350
17.6 Calculating Reliability	351
17.7 Testing and Qualifying Power Supplies	352
HAST/HALT, HASS, and ESS	352
17.8 Safety Issues	354
17.9 Calculating Working Voltage	357
17.10 Estimating Capacitor Life	361
17.11 Safety Restrictions on the Total Y-Capacitance	369
17.12 Safety and the 5-cent Zener	370
Appendix. Components and FAQ	373
References	387
Index	389