



# POWER-SWITCHING CONVERTERS

*Second Edition*

SIMON ANG  
ALEJANDRO OLIVA

# Contents

<i>Preface to the Second Edition</i>	<i>ix</i>
<b>1. Introduction to Switching Converters</b>	<b>1</b>
1.1 Introduction	1
1.2 Industry Trends	2
1.3 Linear Converter	3
1.3.1 Linear Series-Pass Regulator	3
1.3.2 Linear Shunt Regulator	5
1.4 Switching Converters	7
1.4.1 Basic Switching Converter with Resistive Load	8
1.4.2 Basic Switching Converter with $R_L$ Load	11
1.5 Principles of Steady-State Converter Analysis	13
1.5.1 Inductor Volt-Second Balance	13
1.5.2 Capacitor Charge Balance	14
Problems	15
References	16
<b>2. Basic Switching Converter Topologies</b>	<b>17</b>
2.1 Introduction	17
2.2 Buck Converter	18
2.2.1 Continuous Mode	19

2.2.2	Discontinuous Mode	24
2.3	Synchronous Rectifier	31
2.4	Boost Converter	32
2.4.1	Continuous Mode	33
2.4.2	Discontinuous Mode	38
2.5	Buck-Boost Converter	42
2.5.1	Continuous Mode	45
2.5.2	Discontinuous Mode	49
2.6	Cûk Converter	52
	Mode 1 ( $0 < t \leq t_{on}$ )	53
	Mode 2 ( $t_{on} \leq t < T$ )	55
2.7	Converter Realization with Nonideal Components	61
2.7.1	Inductor Model	61
2.7.2	Semiconductor Losses	62
2.7.3	Capacitor Model	63
	Problems	64
	References	66
<b>3.</b>	<b>Resonant Converters</b>	<b>69</b>
3.1	Introduction	69
3.2	Parallel Resonant Circuit — A Review	71
3.3	Series Resonant Circuit — A Review	72
3.4	Classification of Quasi-Resonant Switches	73
3.5	Zero-Current-Switching Quasi-Resonant Buck Converter	77
	Mode 1 ( $0 < t \leq t_1$ )	78
	Mode 2 ( $t_1 < t \leq t_2$ )	79
	Mode 3 ( $t_2 < t \leq t_3$ )	83
	Mode 4 ( $t_3 < t \leq T_s$ )	83
3.6	Zero-Current-Switching Quasi-Resonant Boost Converter	87
	Mode 1 ( $0 < t \leq t_1$ )	88
	Mode 2 ( $t_1 < t \leq t_2$ )	89
	Mode 3 ( $t_2 < t \leq t_3$ )	91
	Mode 4 ( $t_3 < t \leq T_s$ )	92
3.7	Zero-Voltage-Switching Quasi-Resonant Buck Converter	94
	Mode 1 ( $0 < t \leq t_1$ )	95
	Mode 2 ( $t_1 < t \leq t_2$ )	96
	Mode 3 ( $t_2 < t \leq t_3$ )	98
	Mode 4 ( $t_3 < t \leq T_s$ )	98
3.8	Zero-Voltage-Switching Quasi-Resonant Boost Converter	101
	Mode 1 ( $0 < t \leq t_1$ )	101
	Mode 2 ( $t_1 < t \leq t_2$ )	102

	Mode 3 ( $t_2 < t \leq t_3$ )	104
	Mode 4 ( $t_3 < t \leq T_s$ )	105
3.9	Series-Loaded Resonant Converter	107
3.9.1	Discontinuous Mode ( $0 < f < 0.5f_n$ )	108
3.9.2	Continuous Mode ( $f_s > f_n$ or Above-Resonant Mode)	110
3.9.3	Continuous Mode ( $0.5f_n < f < f_n$ or Below-Resonant Mode)	113
3.10	Parallel-Loaded Resonant Converter	116
3.10.1	Discontinuous Mode ( $0 < f < 0.5f_n$ )	117
3.10.2	Continuous Mode ( $f_s > f_2$ or Above-Resonant Mode)	121
3.10.3	Continuous Mode ( $0.5f_n < f_s < f_n$ or Below-Resonant Mode)	123
	Problems	126
	References	128
<b>4.</b>	<b>Transformerized Switching Converters</b>	<b>129</b>
4.1	Introduction	129
4.2	Forward Converter	130
	Mode 1 ( $0 < t \leq t_1$ )	131
	Mode 2 ( $t_{on} < t \leq T_s$ )	132
4.3	Push-Pull Converter	136
4.4	Half-Bridge Switching Converter	140
4.5	Full-Bridge Switching Converter	143
4.6	Flyback Converter	145
4.7	Zero-Current-Switching Quasi-Resonant Half-Bridge Converter	151
	Mode 1 ( $0 < t \leq t_1$ )	152
	Mode 2 ( $t_1 < t \leq t_2$ )	153
	Mode 3 ( $t_2 < t \leq t_3$ )	154
	Mode 4 ( $t_3 < t \leq T_s/2$ )	155
	Problems	158
	References	159
<b>5.</b>	<b>Control Schemes of Switching Converters</b>	<b>161</b>
5.1	Introduction	161
5.2	Pulse-Width Modulation	162
5.2.1	Voltage-Mode PWM Scheme	162
5.2.2	Current-Mode PWM Scheme	169
	5.2.2.1 Instability for $D > 50\%$	171
	5.2.2.2 Compensation with External Ramp	172

5.3	Hysteresis Control: Switching Current Source	172
5.3.1	Steady-State Analysis During $t_{on}$	175
5.4	Commercial Integrated Circuit Controllers	177
5.4.1	Fixed-Frequency Voltage-Mode SG3524 Controller	177
5.4.2	Variable-Frequency Voltage-Mode TL497 Controller	180
5.4.3	Fixed-Frequency Current-Mode UC3842 PWM Controller	181
5.4.4	TinySwitch-II Family of Low Power Off-Line Switchers	185
5.5	Control Schemes for Resonant Converters	187
5.5.1	Off-Line Controllers for Resonant Converters	190
5.5.1.1	L6598 Operation	190
	Problems	195
	References	196
<b>6.</b>	<b>Dynamic Analysis of Switching Converters</b>	<b>199</b>
6.1	Introduction	199
6.2	Continuous-Time Linear Models	201
6.2.1	Switching Converter Analysis Using Classical Control Techniques	201
6.2.1.1	Basic Linear Model of the Open-Loop Switching Converter	201
6.2.1.2	PWM Modulator Model	202
6.2.1.3	Averaged Switching Converter Models	207
6.2.1.4	Switch Losses	210
6.2.1.5	Switch Delay	210
6.2.1.6	Output Filter Model	211
6.2.2	Summary of Small-Signal Models of Switching Converters	221
6.2.3	Review of Negative Feedback Using Classical-Control Techniques	221
6.2.3.1	Closed-Loop Gain	221
6.2.3.2	Stability Analysis	225
6.2.3.3	Linear Model of the Closed-Loop Switching Converter	227
6.2.4	Feedback Compensation in a Buck Converter with Output Capacitor ESR	236
6.2.5	Feedback Compensation in a Buck Converter with no Output Capacitor ESR	240

6.2.6	Linear Model of the Voltage Regulator Including External Perturbances	242
6.2.7	Output Impedance and Stability	243
6.2.8	State-Space Representation of Switching Converters	245
6.2.8.1	Review of Linear System Analysis	245
6.2.9	State-Space Averaging	247
6.2.9.1	State-Space Averaged Model for an Ideal Buck Converter	248
6.2.9.2	State-Space Averaged Model for the Discontinuous-Mode Buck Converter	255
6.2.9.3	State-Space Averaged Model for a Buck Converter with a Capacitor ESR	263
6.2.9.4	State-Space Averaged Model for an Ideal Boost Converter	268
6.2.10	Switching Converter Transfer Functions	276
6.2.10.1	Source-to-State Transfer Functions	276
6.2.10.2	Open-Loop Transfer Functions	281
6.2.10.3	Loop Compensations in Buck Converter	283
6.2.11	Complete State Feedback	286
6.2.11.1	Design of a Control System with Complete State Feedback	286
6.2.11.2	Pole Selection	288
6.2.11.3	Feedback Gains	288
6.2.12	Input EMI Filters	292
6.2.12.1	Stability Considerations	293
6.3	Discrete-Time Models	302
6.3.1	Introduction	302
6.3.2	Continuous-Time and Discrete-Time Domains	302
6.3.3	Continuous-Time State-Space Model	303
6.3.4	Discrete-Time Model of the Switching Converter	306
6.3.5	Design of a Discrete Control System with Complete State Feedback	308
6.3.5.1	Pole Selection	309
6.3.5.2	Feedback Gains	309
6.3.6	Voltage Mode Control	309
6.3.6.1	Extended-State Model for a Tracking Regulator	311
6.3.7	Current Mode Control	312
6.3.7.1	Extended-State Model for a Tracking Regulator	314
	Problems	315
	References	318

<b>7. Interleaved Converters</b>	<b>321</b>
7.1 Introduction	321
7.2 Interleaved Buck Converter	322
7.2.1 State-Space Averaged Model	324
7.3 Interleaved Boost Converter	326
7.3.1 State-Space Averaged Model	326
7.4 Interleaved Converter Operation Based on Current-Mode	331
7.4.1 Ripple Calculations	332
7.4.2 Number of Converters	334
7.5 Power Factor Correction	334
Problems	338
References	338
<b>8. Switched Capacitor Converters</b>	<b>341</b>
8.1 Introduction	341
8.2 Unidirectional Power Flow SCC	342
8.2.1 Basic Step-Up Converter	342
8.2.2 Basic Step-Down Converter	344
8.2.3 Basic Inverting Converter	345
8.3 Alternative Switched Capacitor Converter Topologies	347
8.3.1 Step-Down Converter	348
8.4 State-Space Averaging Model	350
8.4.1 Step-Up Converter	352
8.4.2 $n$ -Stage Step-Down SCC	353
8.4.3 $n$ -Stage Step-Up SCC	355
8.5 Bi-Directional Power Flow SCC	356
8.5.1 Step-Up Step-Down Converter	356
8.5.1.1 Step-Down Operation	357
8.5.1.2 Step-Up Operation	358
8.5.2 Luo Converter	359
8.6 Resonant Converters	365
8.6.1 Zero-Current Switching	365
8.6.1.1 Condition of Zero-Current Switching	368
8.7 Losses on Switched-Capacitor Power Converters	369
Problems	370
References	371

<b>9. Simulation of Switching Converters</b>	<b>373</b>
9.1 Introduction	373
9.2 PSpice Circuit Representation	374
9.3 PSpice Simulations Using .CIR	375
9.3.1 An Ideal Open-Loop Buck Converter	375
9.3.2 Buck Converter with an Ideal Switch	381
9.4 PSpice Simulations Using Schematics Entry	386
9.4.1 Boost Converter	387
9.4.2 PSpice Simulations Using Behavioral Modeling	388
9.4.2.1 Control System Parts	389
9.4.2.2 PSpice-Equivalent Parts	389
9.4.3 Examples of ABM Blocks Use	392
9.4.4 PSpice Simulations Using Control Blocks	397
9.4.4.1 Voltage-Mode PWM Boost Converter	399
9.4.5 PSpice Simulations Using Vendor Models	402
9.5 Small-Signal Analysis of Switching Converters	403
9.5.1 Open-Loop Transfer Function	407
9.5.2 Input Impedance	409
9.5.3 Output Impedance	409
9.5.4 Small-Signal Transient Analysis	409
9.5.5 Measuring the Loop Gain	411
9.5.6 Frequency Compensation	412
9.5.6.1 PID Compensation	413
9.5.6.2 PI Compensation	418
9.6 Creating Capture Symbols for PSpice Simulation	422
9.7 Solving Convergence Problems	422
9.7.1 DC Analysis Error Messages	423
9.7.2 Transient Analysis Error Messages	423
9.7.3 Solutions to Convergence Problems	424
9.7.4 Bias Point (DC) Convergence	424
9.7.5 Checking Circuit Topology and Connectivity	424
9.7.5.1 Setting up the Options for the Analog Simulation	425
9.7.6 Transient Convergence	426
9.7.6.1 Circuit Topology and Connectivity	426
9.7.6.2 PSpice Options	427
9.8 Switching Converter Simulation Using MATLAB	428
9.8.1 Working with Transfer Functions	428
9.8.2 Working with Matrices	431
9.9 Switching Converter Simulation Using Simulink	433
9.9.1 Transfer Function Example Using Simulink	434
9.9.2 State-Space Example Using Simulink	436



Problems	436
References	437
<b>10. Switching Converter Design: Case Studies</b>	<b>439</b>
10.1 Introduction	439
10.2 Voltage-Mode Discontinuous-Conduction-Mode Buck Converter Design	441
10.2.1 Controller Design	442
10.2.2 Small-Signal Model	443
10.2.3 Design of the Compensation Network and Error Amplifier	446
10.2.3.1 MATLAB Program to Calculate the Compensation Network	448
10.2.4 The Closed-Loop Buck Converter	452
10.2.5 Simulation Results	452
10.2.6 Experimental Results	452
10.2.6.1 Open-Loop Experimental Data	454
10.2.6.2 Open-Loop Load Regulation	454
10.2.6.3 Bode Plot of the Loop Gain	455
10.2.6.4 Closed-Loop Experimental Results	456
10.2.6.5 Closed-Loop Line and the Load Regulations	457
10.3 Digital Control of a Voltage-Mode Synchronous Buck Converter	460
10.3.1 Circuit Parameters	461
10.3.2 Closed-Loop Pole Selection	462
10.3.3 Discrete-Time Model	463
10.3.4 Feedback Gains	465
10.3.5 Control Strategy	466
10.3.6 Analog Model for PSpice Simulations	467
10.3.7 Simulation Results	470
10.3.8 Sensitivity of the Closed-Loop Poles Due to Load Variations	470
10.3.9 Experimental Results	472
10.4 Digital Control of a Current-Mode Synchronous Buck Converter	473
10.4.1 Continuous-Time State Model	474
10.4.2 Obtaining the Discrete-Time Model	475
10.4.3 Current-Mode Instability	476
10.4.4 Extended-State Model for a Tracking Regulator	476

10.4.5	Feedback Gains	477
	10.4.5.1 MATLAB Design File	477
10.4.6	Control Strategy	479
10.4.7	Simulation Results	479
10.4.8	Sensitivity of the Closed-Loop Poles Due to Load Variations	481
10.4.9	Experimental Results	481
10.4.10	DSP Program	482
10.5	UC3842-Based Flyback Design	489
	10.5.1 Design Specifications	490
	10.5.2 Discontinuous Conduction Mode	490
	10.5.3 Preliminary Calculations	492
	10.5.4 Open-Loop Simulations	493
	10.5.5 Current Loop	494
	10.5.6 Voltage Loop	494
	10.5.6.1 Current-Sensing Resistor and Filtering	495
	10.5.6.2 Dissipative Snubber	496
	10.5.6.3 The Error Amplifier	496
	10.5.6.4 The Bias Circuit	497
	10.5.7 Small Signal Model	498
	10.5.8 Frequency Compensation	499
	10.5.8.1 Closed-Loop Simulations	500
	10.5.9 EMI Filter Design	502
	10.5.10 Printed Circuit Board Design	504
	10.5.11 Experimental Results	506
10.6	TopSwitch-Based Flyback Design	508
	10.6.1 Design Specifications	509
	10.6.2 Preliminary Calculations	509
	10.6.3 Experimental Results	510
	10.6.3.1 Line Regulation	513
	10.6.3.2 Load Regulation	513
10.7	TinySwitch-Based Flyback Design	513
	10.7.1 Experimental Results	514
	10.7.1.1 Waveforms	514
	10.7.1.2 Line Regulation	516
	10.7.1.3 Load Regulation	516
10.8	Switching Audio Amplifier	516
	10.8.1 Case Study	521
	10.8.1.1 The Output Stage	522

10.8.1.2	The Error Amplifier	523
10.8.1.3	PWM Modulator	523
10.8.1.4	The Feedback Loop	526
10.8.1.5	Evaluation	526
References		532
<i>Index</i>		533