

**INTERNATIONAL EDITION**



**CD-ROMs INCLUDED**

# **ELECTRICAL ENGINEERING**

***PRINCIPLES AND APPLICATIONS***

**THIRD EDITION**

**ALLAN R. HAMBLEY**



# Contents

---

Practical Applications of  
Electrical Engineering Principles iv

Contents v

Preface ix

## **PART ONE** Circuits 1

### **1**

#### **Introduction 2**

- 1.1 Overview of Electrical Engineering 3
- 1.2 Circuits, Currents, and Voltages 8
- 1.3 Power and Energy 15
- 1.4 Kirchhoff's Current Law 19
- 1.5 Kirchhoff's Voltage Law 22
- 1.6 Introduction to Circuit Elements 24
- 1.7 Introduction to Circuits 34
- Summary 37
- Problems 39

### **2**

#### **Resistive Circuits 45**

- 2.1 Resistances in Series and Parallel 46
- 2.2 Network Analysis by Using Series and Parallel Equivalents 50
- 2.3 Voltage-Divider and Current-Divider Circuits 54
- 2.4 Node-Voltage Analysis 59
- 2.5 Mesh-Current Analysis 74
- 2.6 Thévenin and Norton Equivalent Circuits 82
- 2.7 Superposition Principle 95
- 2.8 Wheatstone Bridge 98
- Summary 101
- Problems 102

### **3**

#### **Inductance and Capacitance 114**

- 3.1 Capacitance 115
- 3.2 Capacitances in Series and Parallel 124
- 3.3 Physical Characteristics of Capacitors 125
- 3.4 Inductance 129
- 3.5 Inductances in Series and Parallel 135
- 3.6 Practical Inductors 136
- 3.7 Mutual Inductance 138
- Summary 140
- Problems 141

### **4**

#### **Transients 148**

- 4.1 First-Order *RC* Circuits 149
- 4.2 DC Steady State 153
- 4.3 *RL* Circuits 155
- 4.4 *RC* and *RL* Circuits with General Sources 160
- 4.5 Second-Order Circuits 167
- Summary 181
- Problems 182

### **5**

#### **Steady-State Sinusoidal Analysis 189**

- 5.1 Sinusoidal Currents and Voltages 190
- 5.2 Phasors 195
- 5.3 Complex Impedances 201
- 5.4 Circuit Analysis with Phasors and Complex Impedances 206
- 5.5 Power in AC Circuits 212
- 5.6 Thévenin and Norton Equivalent Circuits 225

- 5.7 Balanced Three-Phase Circuits 231
  - Summary 243
  - Problems 245

## 6

### Frequency Response, Bode Plots, and Resonance 254

- 6.1 Fourier Analysis, Filters, and Transfer Functions 255
- 6.2 First-Order Lowpass Filters 263
- 6.3 Decibels, the Cascade Connection, and Logarithmic Frequency Scales 269
- 6.4 Bode Plots 274
- 6.5 First-Order Highpass Filters 277
- 6.6 Series Resonance 285
- 6.7 Parallel Resonance 291
- 6.8 Ideal and Second-Order Filters 294
- 6.9 Digital Signal Processing 300
  - Summary 311
  - Problems 312

## PART TWO Digital Systems 323

## 7

### Logic Circuits 324

- 7.1 Basic Logic Circuit Concepts 325
- 7.2 Representation of Numerical Data in Binary Form 328
- 7.3 Combinatorial Logic Circuits 336
- 7.4 Synthesis of Logic Circuits 345
- 7.5 Minimization of Logic Circuits 352
- 7.6 Sequential Logic Circuits 355
  - Conclusions 367
  - Summary 367
  - Problems 368

## 8

### Microcomputers 374

- 8.1 Computer Organization 375
- 8.2 Memory Types 378
- 8.3 Digital Process Control 381
- 8.4 The Motorola 68HC11/12 384

- 8.5 The Instruction Set and Addressing Modes for the 68HC11 390
- 8.6 Assembly-Language Programming 399
  - Summary 404
  - Problems 405

## 9

### Computer-Based Instrumentation Systems 408

- 9.1 Measurement Concepts and Sensors 409
- 9.2 Signal Conditioning 414
- 9.3 Analog-to-Digital Conversion 422
- 9.4 LabVIEW 425
  - Summary 437
  - Problems 438

## PART THREE Electronics 441

## 10

### Diodes 442

- 10.1 Basic Diode Concepts 443
- 10.2 Load-Line Analysis of Diode Circuits 447
- 10.3 Zener-Diode Voltage-Regulator Circuits 449
- 10.4 Ideal-Diode Model 454
- 10.5 Piecewise-Linear Diode Models 456
- 10.6 Rectifier Circuits 460
- 10.7 Wave-Shaping Circuits 464
- 10.8 Linear Small-Signal Equivalent Circuits 471
  - Summary 477
  - Problems 478

## 11

### Amplifiers: Specifications and External Characteristics 487

- 11.1 Basic Amplifier Concepts 488
- 11.2 Cascaded Amplifiers 494
- 11.3 Power Supplies and Efficiency 497
- 11.4 Additional Amplifier Models 500

- 11.5 Importance of Amplifier Impedances in Various Applications 504
- 11.6 Ideal Amplifiers 506
- 11.7 Frequency Response 508
- 11.8 Linear Waveform Distortion 513
- 11.9 Pulse Response 517
- 11.10 Transfer Characteristic and Nonlinear Distortion 521
- 11.11 Differential Amplifiers 524
- 11.12 Offset Voltage, Bias Current, and Offset Current 528
  - Summary 533
  - Problems 534

## 12

### Field-Effect Transistors 544

- 12.1 NMOS and PMOS Transistors 545
- 12.2 Load-Line Analysis of a Simple NMOS Amplifier 553
- 12.3 Bias Circuits 556
- 12.4 Small-Signal Equivalent Circuits 559
- 12.5 Common-Source Amplifiers 564
- 12.6 Source Followers 568
- 12.7 CMOS Logic Gates 573
  - Summary 577
  - Problems 577

## 13

### Bipolar Junction Transistors 584

- 13.1 Current and Voltage Relationships 585
- 13.2 Common-Emitter Characteristics 588
- 13.3 Load-Line Analysis of a Common-Emitter Amplifier 590
- 13.4 *pnp* Bipolar Junction Transistors 597
- 13.5 Large-Signal DC Circuit Models 599
- 13.6 Large-Signal DC Analysis of BJT Circuits 602
- 13.7 Small-Signal Equivalent Circuits 609
- 13.8 Common-Emitter Amplifiers 613
- 13.9 Emitter Followers 618
  - Summary 624
  - Problems 624

## 14

### Operational Amplifiers 632

- 14.1 Ideal Operational Amplifiers 633
- 14.2 Inverting Amplifiers 635
- 14.3 Noninverting Amplifiers 642
- 14.4 Design of Simple Amplifiers 645
- 14.5 Op-Amp Imperfections in the Linear Range of Operation 651
- 14.6 Nonlinear Limitations 655
- 14.7 DC Imperfections 660
- 14.8 Differential and Instrumentation Amplifiers 665
- 14.9 Integrators and Differentiators 667
- 14.10 Active Filters 670
  - Summary 675
  - Problems 676

## PART FOUR Electromechanics 687

## 15

### Magnetic Circuits and Transformers 688

- 15.1 Magnetic Fields 689
- 15.2 Magnetic Circuits 699
- 15.3 Inductance and Mutual Inductance 705
- 15.4 Magnetic Materials 709
- 15.5 Ideal Transformers 712
- 15.6 Real Transformers 721
  - Summary 725
  - Problems 726

## 16

### DC Machines 735

- 16.1 Overview of Motors 736
- 16.2 Principles of DC Machines 745
- 16.3 Rotating DC Machines 751
- 16.4 Shunt-Connected and Separately Excited DC Motors 758
- 16.5 Series-Connected DC Motors 763
- 16.6 Speed Control of DC Motors 767
- 16.7 DC Generators 773

Summary 778

Problems 779

## 17

### AC Machines 787

17.1 Three-Phase Induction Motors 788

17.2 Equivalent-Circuit and Performance  
Calculations for Induction Motors 796

17.3 Synchronous Machines 806

17.4 Single-Phase Motors 819

17.5 Stepper Motors and Brushless DC  
Motors 823

Summary 825

Problems 825

## A

### Complex Numbers 831

Summary 839

Problems 839

## B

Nominal Values and the Color Code  
for Resistors 840

## C

The Fundamentals  
of Engineering Examination 842

## D

Computer-Aided Circuit  
Analysis 848

D.1 Analysis of DC Circuits 848

D.2 Transient Analysis 857

D.3 Frequency Response 861

D.4 Other Examples 864

## E

Software Installation 867

Index 869