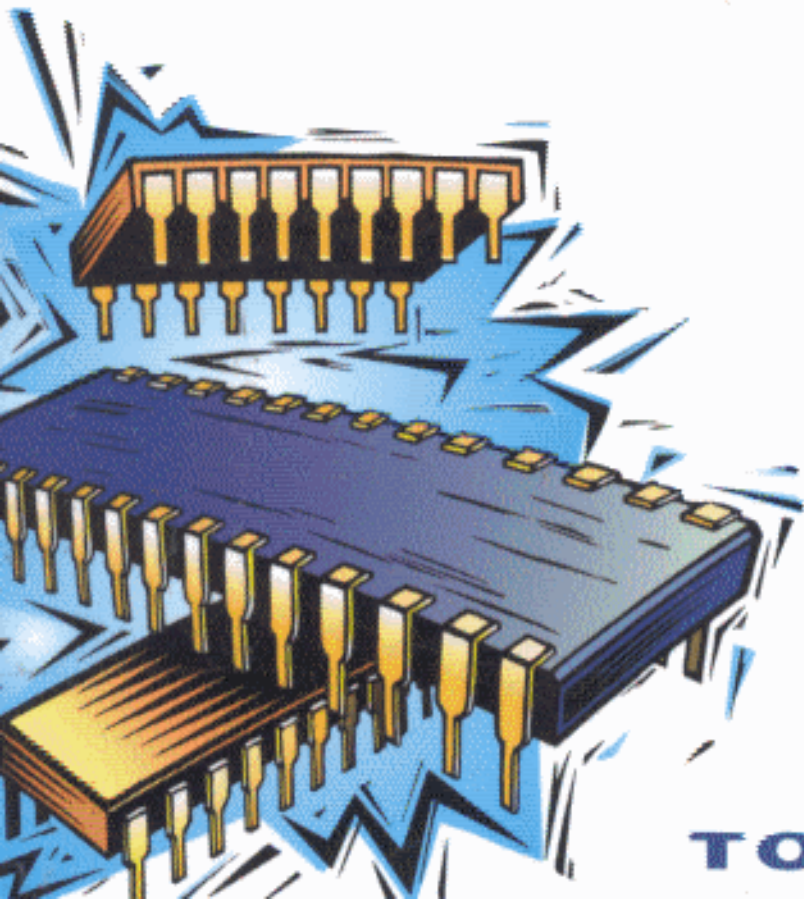




PROGRAMMING AND CUSTOMIZING THE HC11 MICROCONTROLLER

HC11 Data Sheets
available online @
[www.books.mcgraw-hill.com/
engineering/update-zone.html](http://www.books.mcgraw-hill.com/engineering/update-zone.html)



**Includes 10
complete projects**

**Tips and techniques
to interface the
68HC11 to a wide
range of external
devices**

**CD includes
software tools
and source code
for developing
68HC11
applications**

TOM FOX

CONTENTS

Acknowledgments xi

Introduction	1
What Are Microcontrollers? 3	
What Are Embedded Controllers? 3	
Chapter 1 What Is a Computer?	5
Solderless Breadboards 6	
Power Sources 9	
An Updated Version of a Circa 1965 Hobbyist Computer 11	
The Architecture of a Simple Computer 18	
Chapter 2 Introducing the HC11 and Breadboarding: A Simple HC11 Computer Circuit	23
A Quick Look at the MC68HC11AIP 23	
Tips on Breadboarding This Experimenter Circuit 24	
What the Circuit Is All About 27	
How Does the HC11 Know What to Do? 30	
What's Inside an HC11 31	
Port A—One of the HC11's Access Lanes to the Real World 32	
What Makes the LED Blink 33	
Chapter 3 Getting to Know the HC11	37
The Registers 37	
Memory Addressing 40	
Memory Locations 40	
Machine Language 43	
A Quick Look into Assembly Language 47	
Chapter 4 The Mag-11 Single-Board Computer	51
Why Mag-11? 52	
A Quick Look at Mag-11 and Its Features 52	
Mag-11's Construction 56	
Having Trouble with Mag-11? 64	
About Mag-11's Circuit 64	
A Simplified Look at Mag-11's Built-in "Outside World" Interface 70	
Using M11DIAG2 Firmware 71	
Adding Even More Reliability—The Clock Monitor Reset 79	
More About the Stop Instruction 80	
HC11's Input Capture System—Using Mag-11's Binary Thermometer 81	

Chapter 5 The SCI and Mag-11

91

- The Basics of Asynchronous Serial Communication 92
- Real-Life Nuts-and-Bolts Connection from MAG-11 to a PC 92
- A Look Inside HC11's Own SCI 94
- Reading SCI Data 97
- Transmitting SCI Data 99
- Connecting to MAG-11's Serial Interface 100
- A Look at M11DIAG2's Communication Program 101
- The BUFFALO Monitor 106
- Physically Connecting Mag-11 to Your Computer 107
- Using the BUFFALO Monitor 107
- Using the BUFFALO Line Assembler/Disassembler 109
- Flash Data LEDs with a Program Entered into EEPROM
with BUFFALO's ASM Line Assembler 110
- Running Programs from the BUFFALO Monitor 112
- Experiments Using Mag-11 and BUFFALO's Line Assembler 113
- The HC11's A/D Converter 119
- Advantages of an HC11-Based Photometer 130

Chapter 6 Programming and Customizing the HC11 Microcontroller

133

- How the Squarewave Generator Program Works 134
- Creating a Squarewave Using the Output Compare Interrupt 136
- Using the Interrupts 139
- Mag-11's Musical Talents 141
- A Brief Look at Advanced I/O Pin Control 145
- The Timer's Other Life 145
- Having More Fun with the RTI 151
- Introducing the Pulse Accumulator 152
- What Is the Computer Operating Properly (COP) Watchdog System? 154

Chapter 7 Programming and Customizing the HC11 Microcontroller: HC11's SPI Interface

157

- Master vs. Slave 158
- Using HC11's SPI to Add Another Output Port to Mag-11 158
- A Look at the 74HC595 161
- HC11's SPI-Related Signal Pins 162
- HC11's SPI-Related Registers 163
- CPOL and CPHA 166
- Using the HC11's SPI to Input Data 176
- The Circuit 179
- The Mystery of the Wrong CPOL and CPHA Bits 181

Chapter 8 The AS11 Cross-Assembler

185

- From an Idea to a Program 186
- How AS11 Expects Its Line of Source Code to Look 193
- Don't Sweat About AS11 Format Rules 195

AS11 Instructions	196
AS11 Directives	196
Read the File AS11.TXT on the CD-ROM	202
A Sampling of HC11 Instructions	202
Condition Code Register	207
Additional HC11 Instructions	211
Subroutines and Subroutine-Related Instructions	217
Motorola's MC11 Instruction Set Details	220
Talking Frankly About the Location of Internal RAM and Registers	223
Experiment a Bit More with DAYALERT	224

Chapter 9 Introducing a Simpler, Cheaper Way **227**

Running Programs from the HC11's EEPROM	228
Tale of the "Invisible" Address Bus	230
Programming MC68HC11AIP EEPROMs Using Mag-11 and .S19 Files	234
The Origins of MagPro-11	237
A Look at MagPro-11	238
Programming HC11s	243
Programming HC811s	244

Chapter 10 Construction and Use of MagTroll-11 **249**

About MagTroll-11	249
Using the HC11's Internal EEPROM	257
Using the HC811's Internal EEPROM	258
Another Look at HCx11's All-Important Interrupt Vectors	258
Tips on Setting Bits in a Register or Other Memory Location	263
Tips When Using the MC68HC811E2FN in MagTroll-11	264
Tips When Using the Standard MC68HC11A1FN in MagTroll-11	265
Using MagTroll-11 in an Expanded Multiplex System	266
Using the EEPROM to Store the MagTroll-11's Program	266
Jumping to EEPROM by Sending a NUL	269

Chapter 11 An MCU-Based Solid-State Wind Vane **271**

The Solid-State Wind Vane	271
Sensor Assembly's Physical Description	273
Note on Power Supplies for MagTroll-11	295

Chapter 12 A "Voodoo-Designed" Wind Vane **303**

A Solid-State Wind Vane with Only Four Sensors	304
Calibration	315
Location for Sensor Assembly for both Four- and Eight-Sensor Wind Vanes	315
Using MagTroll-11 in Other Designs	320

Chapter 13 68HC11A1's Sisters, Brothers, and Cousins **323**

The HC11—A Really Hot MCU	323
---------------------------	-----

Appendix A. Binary and Hexadecimal Numbers: A Different Way of Looking at Them **331**

Appendix B. Programming EPROMS **341**

Appendix C. Sources for Printed Circuit Boards, Kits, and Parts	347
Appendix D. Parts Lists	355
Appendix E. Dynamite Hints on Making PC Boards	365
Appendix F. Handling Static-Sensitive Parts	369
Appendix G. HC11-Related Internet Resources	371
Appendix H. Data Sheets and All	375