- 100" calculations and worked solutions
- Solutions to every problem you'll meet
- · From McGraw-Hill and EC&M Books

## EC&M's Electrical Calculations Handbook

JOHN M. PASCHAL, JR.



## **Contents**

ΤK

151

P37

2000

## B 042308

Preface xI List of Problems xill

Chapter 1. Basic Electrical Working Definitions and Concepts	1
Voltage as Potential Difference	1
Current	3
Resistance	4
Direct-Current (dc) Voltage Sources	4
Direct and Alternating Current	
dc Voltage	6
Current Flow in a Resistive Circuit	15
Current Flow in a Series Resistive Circuit	16
Voltage Division in a Series Circuit	18
Power Rating of a Resistor	18
ac Voltage	23
ac Circuits with Resistance	23
ac Phase Angle and Power	26
Current and Power in a Single-Phase ac Circuit	33
Current and Power in a Three-Phase ac Circuit	33
Inductive Reactance	42
Capacitive Reactance	46
Impedance	52
Chapter 2. Three-Phase Systems	55
Wys-Connected Systems	58
Delta-Connected Systems	60

Chapter 3. Mathematics for Electrical Calculations, Power Factor Correction, and Harmonics	69
Changing Vectors from Rectangular to Polar Form and	
Back Again	<b>169</b>
Adding Vectors	70
Multiplying or Dividing Vectors	74
Solving for Current and Power Factor in an ac Circuit Containing Only inductive Reactance	75
Solving for Current and Power Factor in an ac Circuit Containing Both inductive Reactance and Resistance in	
Series with One Another	77
Solving for Current and Power Factor In an ac Circuit	•
Containing Two Parallel Branches That Both Have Inductive	
Reactance and Resistance in Series with One Another	77
Solving for Current and Power Factor in an ac Circuit Containing Parallel Branches, One of Which Has Inductive Reactance and Resistance in Series with One Another and	
the Other of Which Has a Capacitive Reactance	79
Electrical Power in Common ac Circuits	79
Power Factor Correction to Normal Limits	87
Real Power (Kilowatts), Apparent Power (Kilovoltamperes), Demand, and the Electrical Utility Bill	90
Power Factor Correction System Design In an Electrical Power System Containing No Harmonics	93
Power Factor Correction System Design in an Electrical Power System Containing Harmonics	104
Calculating the Paraliel Harmonic Resonance of an Electrical Power System Containing Capacitors	107
Resulting Values of Adding Harmonic Currents or Voltages	108
Acceptable Levels of Harmonic Current and Voltage	110
The Harmonic Current-Flow Model	111
Effects of Harmonic Current on Transformers	114
Effects of Harmonic Voltage on Motors	116
Harmonic Current Flow through Transformers	116
Harmonic Filters	117
Harmonics Symptoms, Causes, and Remedies	122
Chapter 4. Conductors	125
Conductors, Conductor Resistance, Conductor and Cable Impedance, and Voltage Drop	125
Calculating the One-Way Resistance of a Wire	12!
Calculating the impedance of a Cable	133
Calculating the impedance of a Cable	140

Contents	vil
Calculating do Resistance in a Bus Bar	143
Calculating Heat Loss in a Conductor	143
Wires and Cables	143
Determining Wire Size Given insulation Type, Circuit Breaker	
Clearing Time, and Short Circuit Current	160
Selecting the Proper insulation for an Environment	161
Aluminum Conductors	170
Conductor and Cable Selection	170
Chapter 5. Short-Circuit Calculations	179
Sources of Short-Circuit Current	182
The Ability of the Electrical Utility System to Produce	
Short-Circuit Current	183
Short-Circuit Contributions of On-Site Generators	184
Short-Circuit Contributions of Motors	185
Let-Through Values of Transformers	187
Let-Through Values of Reactors	188
Let-Through Power Values of Cables	189
Sample Short-Circuit Calculation	190
Chapter 6. Generator Sizing Calculations	195
Sizing a Gas-Turbine Generator Set for a Known Kilowatt Load	196
Sizing a Reciprocating Engine-Driven Generator Set for a Known Kliowatt Load	198
· · · · · · · · · · · · · · · · · · ·	200
Sizing of Generator Feeder Conductors	200
Chapter 7. Grounding	205
The Functions of Grounding	205
Calculating the Resistance to Remote Earth of Ground Rods	208
Grounding-Electrode Conductors	211
Equipment-Grounding Conductors	211
Methods of Grounding Systems	215
Obtaining the System Grounding Point	217
Chapter 8. Lighting	221
The Lumen Method	221
The Point-by-Point Method	223
Indoor Lighting	229
Lighting Rules of Thumb	245

## viil Contents

Chapter 9. Transformers	251
Three-Phase Transformers	255
Overcurrent Protection of Transformers	255 265
Buck-Boost Autotransformers	,205 275
Chapter 10. Motors	285
Selecting Motor Characteristics	
Calculating Motor Running Current	286
Calculating Motor Branch-Circuit Overcurrent Protection	295
and Wire Size	296
Chapter 11. Raceways	311
Raceway Types and Their Characteristics	311
Chapter 12. Overcurrent Devices	319
Overcurrent Devices: Fuses and Circuit Breakers	319
Fuses	321
Circuit Breakers	323
Medium-Voltage and Special-Purpose Circuit Breakers and Relay Controllers	325
Chapter 13. Circuits for Special Loads	335
Designing Circuits for Various Electrical Loads	335
Designing an Electrical System for a Commercial Building	339
Designing an Electrical System for an Industrial Facility	349
Chapter 14. Electrical Design and Layout Calculations	357
Straight-Through Pull Box in a Conduit System	357
Angle Pull Box in a Conduit System	358
Working Space Surrounding Electrical Equipment	358
Minimum Centerline-to-Centerline Dimensions of Knockouts to Provide for Locknut Clearance	364
Chapter 15. Electrical Cost Estimating	371
Electrical Takeoff and Personnel-Hour Cost Estimating	371
Factoring of Labor Units	397
Estimate of Project Expense	409

	Contents	Kİ
Engineering Economics Calculations Considering the Value of Money	Time	411
Chapter 16. Conversion Calculations		425
Temperature Conversion Calculations		425
Frequently Used Conversion Calculations		425
Multiple Conversion Calculations		425