
SENSORS AND SIGNAL CONDITIONING

Second Edition



Ramon Pallàs-Areny / John G. Webster

CONTENTS

Preface

xi

1 Introduction to Sensor-Based Measurement Systems

1

- 1.1 General Concepts and Terminology, 1
 - 1.1.1 Measurement systems, 1
 - 1.1.2 Transducers, sensors and actuators, 2
 - 1.1.3 Signal conditioning and display, 4
 - 1.1.4 Interfaces, data domains, and conversion, 4
- 1.2 Sensor Classification, 6
- 1.3 General Input-Output Configuration, 7
 - 1.3.1 Interfering and modifying inputs, 7
 - 1.3.2 Compensation techniques, 11
- 1.4 Static Characteristics of Measurement Systems, 12
 - 1.4.1 Accuracy, precision, and sensitivity, 13
 - 1.4.2 Other characteristics: Linearity and resolution, 15
 - 1.4.3 Systematic errors, 17
 - 1.4.4 Random errors, 18
- 1.5 Dynamic Characteristics, 21
 - 1.5.1 Zero-order measurement systems, 22
 - 1.5.2 First-order measurement systems, 23
 - 1.5.3 Second-order measurement systems, 26
- 1.6 Other Sensor Characteristics, 31
 - 1.6.1 Input characteristics: Impedance, 33
 - 1.6.2 Reliability, 34
- 1.7 Primary Sensors, 36

1.7.1	Temperature sensors: Bimetals,	37
1.7.2	Pressure sensors,	38
1.7.3	Flow velocity and flow-rate sensors,	41
1.7.4	Level sensors,	48
1.7.5	Force and torque sensors,	50
1.7.6	Acceleration and inclination sensors,	51
1.7.7	Velocity sensors,	52
1.8	Materials for Sensors,	54
1.8.1	Conductors, semiconductors, and dielectrics,	57
1.8.2	Magnetic materials,	59
1.9	Microsensor Technology,	62
1.9.1	Thick-film technology,	63
1.9.2	Thin-film technology,	64
1.9.3	Micromachining technologies,	65
1.10	Problems,	68
	References,	70
2	Resistive Sensors	73
2.1	Potentiometers,	73
2.2	Strain Gages,	80
2.2.1	Fundamentals: Piezoresistive effect,	80
2.2.2	Types and applications,	85
2.3	Resistive Temperature Detectors (RTDs),	88
2.4	Thermistors,	94
2.4.1	Models,	94
2.4.2	Thermistors types and applications,	102
2.4.3	Linearization,	106
2.5	Magnetoresistors,	109
2.6	Light-Dependent Resistors (LDRs),	114
2.7	Resistive Hygrometers,	119
2.8	Resistive Gas Sensors,	121
2.9	Liquid Conductivity Sensors,	126
2.10	Problems,	129
	References,	131
3	Signal Conditioning for Resistive Sensors	133
3.1	Measurement of Resistance,	133
3.2	Voltage Dividers,	139
3.2.1	Potentiometers,	141
3.2.2	Application to thermistors,	146
3.2.3	Dynamic measurements,	147
3.2.4	Amplifiers for voltage dividers,	149
3.3	Wheatstone Bridge: Balance Measurements,	152
3.4	Wheatstone Bridge: Deflection Measurements,	154

3.4.1	Sensitivity and linearity, 154	
3.4.2	Analog linearization of resistive sensor bridges, 158	
3.4.3	Sensor bridge calibration and balance, 158	
3.4.4	Difference and average measurements and compensation, 159	
3.4.5	Power supply of Wheatstone bridges, 165	
3.4.6	Detection methods for Wheatstone bridges, 168	
3.5	Differential and Instrumentation Amplifiers, 170	
3.5.1	Differential amplifiers, 170	
3.5.2	Instrumentation amplifier based on two op amps, 177	
3.5.3	Instrumentation amplifiers based on three op amps, 179	
3.6	Interference, 184	
3.6.1	Interference types and reduction, 184	
3.6.2	Signal circuit grounding, 188	
3.6.3	Shield grounding, 190	
3.6.4	Isolation amplifiers, 193	
3.7	Problems, 198	
	References, 205	
4	Reactance Variation and Electromagnetic Sensors	207
4.1	Capacitive Sensors, 207	
4.1.1	Variable capacitor, 207	
4.1.2	Differential capacitor, 216	
4.2	Inductive Sensors, 220	
4.2.1	Variable reluctance sensors, 220	
4.2.2	Eddy current sensors, 225	
4.2.3	Linear variable differential transformers (LVDTs), 229	
4.2.4	Variable transformers: Synchros, resolvers, and Inductosyn, 238	
4.2.5	Magnetoelastic and magnetostrictive sensors, 250	
4.2.6	Wiegand and pulse-wire sensors, 254	
4.2.7	Saturation-core (flux-gate) sensors, 256	
4.2.8	Superconducting quantum interference devices (SQUIDs), 258	
4.3	Electromagnetic Sensors, 260	
4.3.1	Sensors based on Faraday's law, 260	
4.3.2	Hall effect sensors, 267	
4.4	Problems, 272	
	References, 274	
5	Signal Conditioning for Reactance Variation Sensors	277
5.1	Problems and Alternatives, 277	
5.2	ac Bridges, 281	

5.2.1	Sensitivity and linearity, 281	
5.2.2	Capacitive bridge analog linearization, 285	
5.2.3	ac amplifiers and power supply decoupling, 286	
5.2.4	Electrostatic shields and driven shields, 292	
5.2.5	ac/dc signal converters, 294	
5.3	Carrier Amplifiers and Coherent Detection, 299	
5.3.1	Fundamentals and structure of carrier amplifiers, 299	
5.3.2	Phase-sensitive detectors, 306	
5.3.3	Application to LVDTs, 311	
5.4	Specific Signal Conditioners for Capacitive Sensors, 313	
5.5	Resolver-to-Digital and Digital-to-Resolver Converters, 316	
5.5.1	Synchro-to-resolver converters, 317	
5.5.2	Digital-to-resolver converters, 319	
5.5.3	Resolver-to-digital converters, 321	
5.6	Problems, 322	
	References, 326	
6	Self-Generating Sensors	329
6.1	Thermoelectric Sensors: Thermocouples, 329	
6.1.1	Reversible thermoelectric effects, 329	
6.1.2	Common thermocouples, 334	
6.1.3	Practical thermocouple laws, 339	
6.1.4	Cold junction compensation in thermocouple circuits, 341	
6.2	Piezoelectric Sensors, 345	
6.2.1	The piezoelectric effect, 345	
6.2.2	Piezoelectric materials, 348	
6.2.3	Applications, 350	
6.3	Pyroelectric Sensors, 357	
6.3.1	The pyroelectric effect, 357	
6.3.2	Pyroelectric materials, 359	
6.3.3	Radiation laws: Planck, Wien, and Stefan-Boltzmann, 360	
6.3.4	Applications, 362	
6.4	Photovoltaic Sensors, 363	
6.4.1	The photovoltaic effect, 363	
6.4.2	Materials and applications, 365	
6.5	Electrochemical Sensors, 366	
6.6	Problems, 369	
	References, 373	
7	Signal Conditioning for Self-Generating Sensors	375
7.1	Chopper and Low-Drift Amplifiers, 376	
7.1.1	Offset and drifts in op amps, 376	
7.1.2	Chopper amplifiers, 383	

- 7.1.3 Autozero amplifiers, 384
- 7.1.4 Composite amplifiers, 386
- 7.1.5 Offset and drifts in instrumentation amplifiers, 387
- 7.2 Electrometer and Transimpedance Amplifiers, 388
 - 7.2.1 Transimpedance amplifiers, 391
 - 7.2.2 Current measurement by integration, 394
 - 7.2.3 Cautions in designing electrometer circuits, 395
- 7.3 Charge Amplifiers, 397
- 7.4 Noise in Amplifiers, 403
 - 7.4.1 Noise fundamentals, 403
 - 7.4.2 Noise in op amps, 407
 - 7.4.3 Noise in transimpedance amplifiers, 416
 - 7.4.4 Noise in charge amplifiers, 418
 - 7.4.5 Noise in instrumentation amplifiers, 419
- 7.5 Noise and Drift in Resistors, 421
 - 7.5.1 Drift in fixed resistors, 421
 - 7.5.2 Drift in adjustable resistors (potentiometers), 424
 - 7.5.3 Noise in resistors, 425
- 7.6 Problems, 427
 - References, 432

8 Digital and Intelligent Sensors

433

- 8.1 Position Encoders, 433
 - 8.1.1 Incremental position encoders, 434
 - 8.1.2 Absolute position encoders, 441
- 8.2 Resonant Sensors, 445
 - 8.2.1 Sensors based on quartz resonators, 447
 - 8.2.2 SAW sensors, 451
 - 8.2.3 Vibrating wire strain gages, 453
 - 8.2.4 Vibrating cylinder sensors, 455
 - 8.2.5 Digital flowmeters, 456
- 8.3 Variable Oscillators, 458
 - 8.3.1 Sinusoidal oscillators, 459
 - 8.3.2 Relaxation oscillators, 460
 - 8.3.3 Variable CMOS oscillators, 463
 - 8.3.4 Linearity in variable oscillators, 465
- 8.4 Conversion to Frequency, Period, or Time Duration, 467
 - 8.4.1 Voltage-to-frequency conversion, 468
 - 8.4.2 Direct quantity-to-frequency conversion, 470
 - 8.4.3 Direct quantity-to-time duration conversion, 474
- 8.5 Direct Sensor-Microcontroller Interfacing, 476
 - 8.5.1 Frequency measurement, 476
 - 8.5.2 Period and time-interval measurement, 478
 - 8.5.3 Calculations and compensations, 482

- 8.5.4 Velocity measurement. Digital tachometers, 484
- 8.6 Communication Systems for Sensors, 486
 - 8.6.1 Current telemetry: 4 to 20 mA loop, 487
 - 8.6.2 Simultaneous analog and digital communication, 489
 - 8.6.3 Sensor buses: Fieldbus, 490
- 8.7 Intelligent Sensors, 492
- 8.8 Problems, 494
 - References, 498

9 Other Sensing Methods

501

- 9.1 Sensors Based on Semiconductor Junctions, 501
 - 9.1.1 Thermometers based on semiconductor junctions, 502
 - 9.1.2 Magnetodiodes and magnetotransistors, 508
 - 9.1.3 Photodiodes, 509
 - 9.1.4 Position-sensitive detectors (PSDs), 518
 - 9.1.5 Phototransistors, 519
 - 9.1.6 Semiconductor-junction nuclear radiation detectors, 521
- 9.2 Sensors Based on MOSFET Transistors, 522
- 9.3 Charge-Coupled and CMOS Image Sensors, 525
 - 9.3.1 Fundamentals, 525
 - 9.3.2 Types of CCD and CMOS imaging sensors and applications, 529
- 9.4 Fiber-Optic Sensors, 533
 - 9.4.1 Fiber-optic basics, 533
 - 9.4.2 Fiber-optic sensor technologies and applications, 535
- 9.5 Ultrasonic-Based Sensors, 538
 - 9.5.1 Fundamentals of ultrasonic-based sensors, 539
 - 9.5.2 Ultrasonic-based sensing methods and applications, 541
- 9.6 Biosensors, 544
- 9.7 Problems, 546
 - References, 550

Appendix: Solutions to the Problems

553

Index

571