

ADVANCED
MICROELECTRONICS

M. Makimoto
S. Yamashita

Microwave Resonators and Filters for Wireless Communi- cation

Theory, Design
and Application



Springer

Contents

1. Introduction	1
1.1 The History of Filters in Telecommunication	1
1.2 Filters for Wireless Communication	3
1.3 Classification of Resonators and Filters for Wireless Communication	5
1.4 Transmission-Line Resonators and Stepped Impedance Resonator (SIR)	7
2. Basic Structure and Characteristics of SIR	11
2.1 Basic Structure of SIR	11
2.2 Resonance Conditions and Resonator Electrical Length	12
2.3 Spurious Resonance Frequencies	16
2.4 Derivation of an Equivalent Circuit of SIR	16
3. Quarter-Wavelength-Type SIR	19
3.1 Analysis of $\lambda_g/4$ -Type Coaxial SIR	20
3.1.1 Impedance Ratio R_Z	20
3.1.2 Effects of Discontinuity	21
3.1.3 Unloaded-Q of Coaxial SIR	24
3.2 Bandpass Filters Using Coaxial SIR	30
3.2.1 Synthesis Method of SIR-BPF Using Capacitive Coupling	30
3.2.2 Design Examples and Performances	32
3.3 Double Coaxial SIR (DC-SIR)	39
3.3.1 Advantages of DC-SIR	39
3.3.2 Resonance Condition and Unloaded-Q	39
3.3.3 400 MHz-Band High-Power Antenna Duplexer	41
3.4 Dielectric Coaxial SIR	45
3.4.1 Dielectric Materials and Features of Dielectric Resonators	45
3.4.2 Basic Structure and Characteristics of Dielectric Coaxial Resonator	47
3.4.3 Design Example of Antenna Duplexer for Portable Radio Telephone	50
3.4.4 Dielectric DC-SIR	53
3.4.5 Dielectric Monoblock SIR-BPF	58

1. 3.5 Stripline SIR.....	60
3.5.1 Basic Structures and Features.....	60
3.5.2 Coupling Between Resonators.....	61
3.5.3 Stripline SIR-BPF.....	62
4. Half-Wavelength-Type SIR.....	65
4.1 Stripline $\lambda_g/2$ Type SIR.....	66
4.1.1 Basic Characteristics.....	66
4.1.2 Equivalent Expressions for Parallel Coupled-Lines Using Inverter.....	67
4.1.3 Synthesis of Stripline Parallel-Coupled SIR-BPF.....	71
4.1.4 Filter Design Examples.....	74
4.2 Internally Coupled SIR.....	84
4.2.1 Basic Structures and Resonance Condition.....	84
4.2.2 Equivalent Circuits at Resonance.....	89
4.2.3 Filter Design Examples.....	91
4.2.4 Application to Oscillator and Mixer Circuits.....	101
5. One-Wavelength-Type SIR.....	107
5.1 Orthogonal Resonance Modes in the Ring Resonator.....	107
5.2 Application of λ_g -Type SIR as Four-Port Devices.....	109
5.3 Application of λ_g -Type SIR as Two-Port Devices.....	112
5.3.1 Coupling Means for Orthogonal Resonant Modes.....	112
5.3.2 Analysis of Coupling Between Orthogonal Resonant Modes.....	115
5.3.3 Application to Filters.....	119
6. Expanded Concept and Technological Trends in SIR.....	127
6.1 SIR Composed of Composite Materials.....	127
6.1.1 Combination of Magnetic and Dielectric Materials.....	127
6.1.2 Coaxial SIR Partially Loaded with Dielectric Material.....	128
6.2 Multistep SIR and Tapered-Line Resonators.....	131
6.3 Folded-Line SIR.....	139
6.4 Technological Trends of SIR in the Future.....	145
Appendix. Analysis of Resonator Properties Using General-Purpose Microwave Simulator.....	149
A.1 Design Parameters of Direct-Coupled Resonator BPF.....	149
A.2 Filter Design by Experimental Method.....	150
A.3 Determination of Q and k Using General Purpose Microwave Simulator.....	151
A.3.1 Determination of Q	151
A.3.2 Determination of Coupling Coefficient.....	154
References.....	157
Index.....	161