



THIRD EDITION

ELECTRIC MACHINERY AND TRANSFORMERS

**BHAG S. GURU
HÜSEYİN R. HIZIROĞLU**

Contents

Preface	xiii
Acknowledgments	xvii

1

Review of Electric Circuit Theory **1**

1.1	Introduction	2
1.2	Direct-Current Circuit Analysis	3
1.3	Alternating-Current Circuit Analysis	7
1.4	Three-Phase Circuits	20
1.5	Power and Impedance Measurements	29
	Summary	52
	Review Questions	53
	Problems	55

2

Review of Basic Laws of Electromagnetism **63**

2.1	Introduction	64
2.2	Maxwell's Equations	64
2.3	Magnetic Materials and Their Properties	75
2.4	Magnetic Circuits	83
2.5	Self and Mutual Inductances	97
2.6	Magnetically Coupled Coils	104
2.7	Magnetic Losses	109
2.8	Permanent Magnets	115

Summary	122
Review Questions	124
Problems	126

3

Principles of Electromechanical Energy Conversion 138

3.1	Introduction	139
3.2	Electric Field as a Medium	140
3.3	Magnetic Field as a Medium	146
3.4	A Coil in a Uniform Magnetic Field	156
3.5	A Coil in a Time-Varying Magnetic Field	170
3.6	Synchronous Motor	181
3.7	Reluctance Motor	182
3.8	Electromagnetic Relays	186
	Summary	190
	Review Questions	193
	Problems	194

4

Transformers 202

4.1	Introduction	203
4.2	Construction of a Transformer	204
4.3	An Ideal Transformer	205
4.4	A Nonideal Transformer	213
4.5	Voltage Regulation	225
4.6	Maximum Efficiency Criterion	228
4.7	Determination of Transformer Parameters	232
4.8	Per-Unit Computations	239
4.9	The Autotransformer	244
4.10	Three-Phase Transformers	253
4.11	The Constant-Current Transformer	268
4.12	Instrument Transformers	270
	Summary	273
	Review Questions	276
	Problems	277

5

Direct-Current Generators

284

5.1	Introduction	285
5.2	Mechanical Construction	285
5.3	Armature Windings	289
5.4	Induced emf Equation	299
5.5	Developed Torque	303
5.6	Magnetization Characteristic of a DC Machine	305
5.7	Theory of Commutation	307
5.8	Armature Reaction	310
5.9	Types of DC Generators	314
5.10	Voltage Regulation	315
5.11	Losses in DC Machines	316
5.12	A Separately Excited DC Generator	319
5.13	A Shunt Generator	323
5.14	A Series Generator	330
5.15	Compound Generators	332
5.16	Maximum Efficiency Criterion	338
	Summary	341
	Review Questions	342
	Problems	344

6

Direct-Current Motors

351

6.1	Introduction	352
6.2	Operation of a DC Motor	352
6.3	Speed Regulation	356
6.4	Losses in a DC Motor	356
6.5	A Series Motor	356
6.6	A Shunt Motor	362
6.7	The Compound Motor	368
6.8	Methods of Speed Control	372
6.9	The Ward-Leonard System	379
6.10	Torque Measurements	382
6.11	Braking or Reversing DC Motors	386

Summary	392
Review Questions	393
Problems	395

7

Synchronous Generators 402

7.1	Introduction	403
7.2	Construction of a Synchronous Machine	404
7.3	Armature Windings	405
7.4	Pitch Factor	409
7.5	Distribution Factor	412
7.6	Winding Connections	414
7.7	Induced emf Equation	418
7.8	The Equivalent Circuit	422
7.9	Power Relationships	429
7.10	Synchronous Generator Tests	434
7.11	The External Characteristic	440
7.12	Salient-Pole Synchronous Generator	445
7.13	Parallel Operation of Synchronous Generators	452
	Summary	460
	Review Questions	463
	Problems	464

8

Synchronous Motors 470

8.1	Introduction	471
8.2	Construction and Operation of a Synchronous Motor	471
8.3	Equivalent Circuit of a Synchronous Motor	475
8.4	Power Expressions	482
8.5	Exact Condition for Maximum Power	489
8.6	Effect of Excitation	493
8.7	Power Factor Correction	498
	Summary	501
	Review Questions	502
	Problems	504

9

Polyphase Induction Motors

508

9.1	Introduction	509
9.2	Construction	509
9.3	Principle of Operation	511
9.4	Development of an Equivalent Circuit	514
9.5	An Approximate Equivalent Circuit	523
9.6	Maximum Power Criterion	526
9.7	Maximum Torque Criterion	528
9.8	Maximum Efficiency Criterion	533
9.9	Some Important Conclusions	533
9.10	Equivalent Circuit Parameters	536
9.11	Starting of Induction Motors	542
9.12	Rotor Impedance Transformation	547
9.13	Speed Control of Induction Motors	550
9.14	Types of Induction Motors	554
	Summary	555
	Review Questions	560
	Problems	561

10

Single-Phase Motors

565

10.1	Introduction	566
10.2	Single-Phase Induction Motor	566
10.3	Analysis of a Single-Phase Induction Motor	572
10.4	Types of Single-Phase Induction Motors	578
10.5	Analysis of a Single-Phase Motor Using Both Windings	583
10.6	Testing Single-Phase Motors	592
10.7	Shaded-Pole Motor	598
10.8	Universal Motor	602
	Summary	607
	Review Questions	608
	Problems	609

11	Dynamics of Electric Machines	614
11.1	Introduction	615
11.2	DC Machine Dynamics	616
11.3	Synchronous Generator Dynamics	640
	Summary	653
	Review Questions	654
	Problems	655
12	Special-Purpose Electric Machines	658
12.1	Introduction	659
12.2	Permanent-Magnet Motors	659
12.3	Step Motors	666
12.4	Switched-Reluctance Motors	673
12.5	Brushless DC Motors	675
12.6	Hysteresis Motors	676
12.7	Linear Induction Motors	678
	Summary	684
	Review Questions	685
	Problems	685
A	System of Units	687
B	The Laplace Transform	690
	Bibliography	692
	Index	693