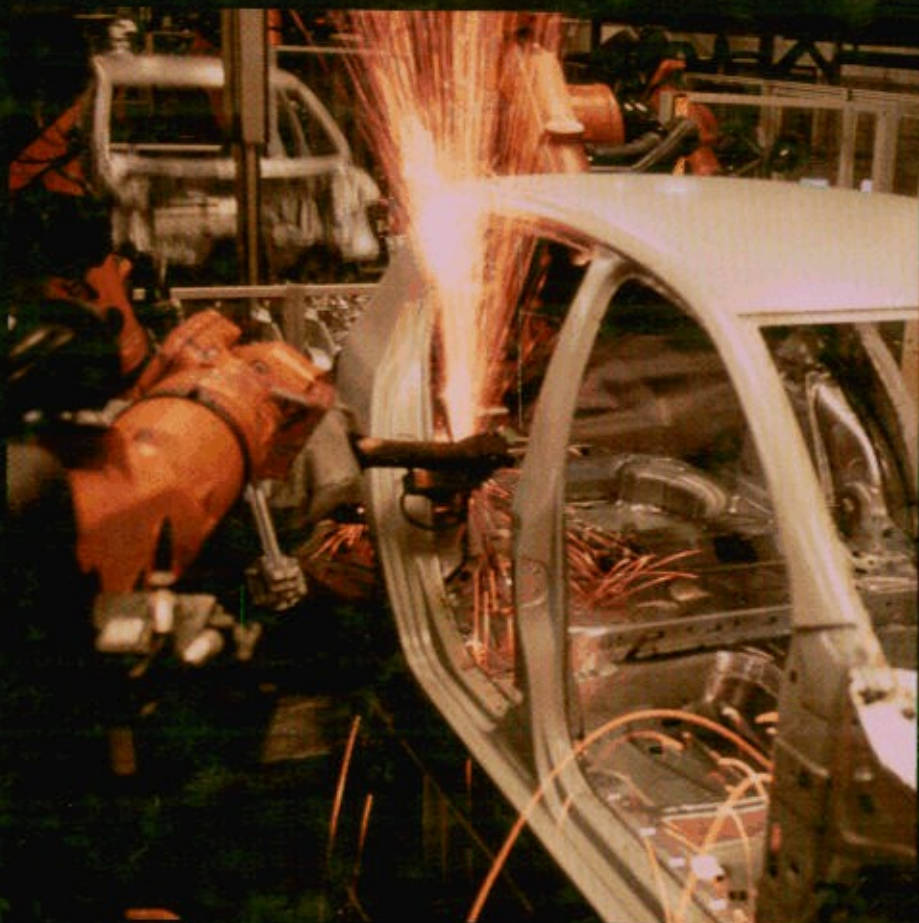


PROGRAMMABLE LOGIC CONTROLLERS



JAMES A. REHG
GLENN J. SARTORI



Contents

Part 1 Programmable Logic Controllers—Fundamental Concepts 1

Goal	1
Objectives	1
Career Insight	1

Chapter 1 Introduction to Programmable Logic Controllers 3

1-1	Goals and Objectives	3
1-2	The PLC Industry Today	3
1-2-1	PLC Definitions	4
1-2-2	PC versus PLC	5
1-3	Relay Ladder Logic	6
1-3-1	Electromagnetic Relay	6
1-3-2	Relay Control Systems	8
1-4	PLC System and Components	11
1-4-1	Backplane	13
1-4-2	Processor and Power Supply	13
1-4-3	Programming Device	13
1-4-4	Input and Output Interface	13
1-4-5	Special Communications Modules and Network Connections	16
1-4-6	PLC Special-Purpose Modules	20
1-5	PLC Types	20
1-5-1	Rack/Slot Address Based	20
1-5-2	Tag Based PLCs	22
1-5-3	Soft PLCs or PC-Based Control	22
1-6	PLC Ladder Logic Programming	22
1-6-1	PLC Solution	22
1-6-2	Ladder Logic Operation	24
1-6-3	An Alternate Solution	25
1-6-4	PLC Advantages	25
1-7	Electrical and PLC Safety	28
1-7-1	Electrical Shock—How the Body Reacts	28
1-7-2	The Nature of Electrical Shock	29
1-7-3	Safe Electrical Practices	31
1-7-4	Response to Shock Victims	32
1-8	Web Sites for PLC Manufacturers	32
	Problems	34

Chapter 2 Input Devices and Output Actuators 35

2-1	Goals and Objectives	35
2-2	Manually Operated Industrial Switches	35
2-2-1	Toggle Switches	36
2-2-2	Push Button Switches	38
2-2-3	Selector Switches	40
2-3	Mechanically Operated Industrial Switches	41
2-3-1	Limit Switches	41
2-3-2	Flow Switches	42
2-3-3	Level Switches	42

2-3-4	Pressure Switches	44
2-3-5	Temperature Switches	45
2-3-6	Control Diagrams	45
2-4	Industrial Sensors	48
2-4-1	Proximity Sensors	49
2-4-2	Photoelectric Sensors	51
2-5	Interfacing Input Field Devices	60
2-5-1	Powering Input Field Devices	61
2-5-2	Input Wiring	61
2-5-3	Current Sinking and Current Sourcing Devices	62
2-6	Electromagnetic Output Actuators	63
2-6-1	Solenoid-Controlled Devices	63
2-6-2	Control Relays	66
2-6-3	Latching Relays	69
2-6-4	Contactors	69
2-6-5	Motor Starters	69
2-7	Visual and Audio Output Devices	71
2-7-1	Pilot Lamps	71
2-7-2	Horns and Alarms	71
2-8	Interfacing Output Field Devices	72
2-8-1	Powering Output Field Devices	72
2-8-2	Output Wiring	73
2-8-3	Current Sinking and Current Sourcing Devices	73
2-9	Troubleshooting Input and Output Devices	74
2-9-1	Troubleshooting Switches	75
2-9-2	Troubleshooting Relays	75
2-9-3	Troubleshooting Proximity Sensors	76
2-9-4	Troubleshooting Photoelectric Sensors	76
	Problems	78

Chapter 3 Introduction to PLC Programming 79

3-1	Goals and Objectives	80
3-2	Number Systems	80
3-2-1	Number System Basics	80
3-2-2	Binary System	81
3-2-3	Octal Number System	82
3-3	Bits, Bytes, Words, And Memory	84
3-4	PLC Memory and Register Structure	85
3-4-1	Allen-Bradley Memory Organization	85
3-4-2	Allen-Bradley PLC 5 Memory Organization	86
3-4-3	Allen-Bradley SLC 500 Memory Organization	87
3-4-4	Allen-Bradley Logix System Memory Organization	89
3-5	Input and Output Addressing	93
3-5-1	PLC 5 Rack/Group-Based Addressing	93
3-5-2	SLC 500 Rack/Slot-Based Addressing	96
3-5-3	Other Vendors' Rack/Slot PLC Addressing	101
3-5-4	Tag-Based Addressing	101
3-6	Internal Control Relay Bit Addressing	105
3-6-1	PLC 5 and SLC 500 Binary Bit Addressing	106
3-6-2	ControlLogix Binary Bit Addressing	107
3-6-3	Retentive and Non-retentive Memory	109
3-7	Status Data Addressing	110
3-7-1	PLC 5 and SLC 500 Status Data Addressing	110
3-7-2	Logix System Status	110
3-8	Allen-Bradley Input Instructions and Output Coils	111
3-8-1	Examine if Closed and Examine if Open Instructions	112
3-8-2	Output Energize, Output Latch, and Output Unlatch Instructions	115

3-9	Inputs, Outputs, and Scan Time	118
3-9-1	Scan Time	118
3-9-2	Linking Inputs and Outputs	119
3-9-3	Process Tank Application	120
3-10	PLC Program Design and Relay Ladder Logic Conversion	123
3-10-1	Examine if Closed and Examine if Open Selection	124
3-10-2	Multiple Inputs	126
3-10-3	Multiple Outputs	128
3-10-4	Empirical Program Design	129
3-10-5	Converting Relay Logic to PLC Solutions	134
3-11	Troubleshooting Ladder Logic Control Systems	137
3-11-1	System Troubleshooting Tools	137
3-11-2	Troubleshooting Sequence	141
3-11-3	Troubleshooting Input and Output Modules	142
	General Problems	145
	PLC 5 Problems	146
	SLC 500 Problems	146
	Controllogix Problems	146
	Challenge Problems	147

Chapter 4 Programming Timers 149

4-1	Goals and Objectives	149
4-2	Mechanical Timing Relays	149
4-2-1	Timed Contacts	150
4-2-2	Instantaneous Contacts	151
4-2-3	Timing Relay Operation	152
4-2-4	Selecting Timing Relays	153
4-3	Electronic Timing Relays	153
4-4	PLC Timer Instructions	154
4-5	Allen-Bradley Timer Instructions	154
4-5-1	Allen-Bradley Timer Symbol and Parameters	154
4-5-2	Allen-Bradley Timer Bits	157
4-5-3	Allen-Bradley TON, TOF, and RTO Instructions	157
4-6	Allen-Bradley Timer Parameter and Bit Addressing	161
4-6-1	PLC 5 and SLC 500 Timer Memory Map	161
4-6-2	ControlLogix Timer Addressing	163
4-6-3	Timer Contacts versus PLC Instructions	163
4-7	Programming Allen-Bradley TON and TOF Timer Ladder Logic	163
4-7-1	Standard Ladder Logic for Allen-Bradley TON Timers	164
4-7-2	Standard Ladder Logic for Allen-Bradley TOF Timers	166
4-7-3	Allen-Bradley TON and TOF Timer Applications	166
4-8	Allen-Bradley Retentive Timers	172
4-8-1	Reset Instruction for RTO Timer and Other Allen-Bradley Instructions	173
4-9	Cascaded Timers	176
4-10	Empirical Design Process with PLC Timers	176
4-10-1	Adding Timers to the Process	176
4-11	Conversion of Relay Logic Timer Ladders to PLC Logic	184
4-12	Troubleshooting Ladder Rungs with Timers	184
4-12-1	Troubleshooting Timer Ladder Logic	186
4-12-2	Temporary End Instruction	186
4-13	Location of the Instructions	187
	General Problems	188

PLC 5 Problems	189
SLC 500 Problems	189
Controllogix Problems	189
Challenge Problems	190

Chapter 5 Programming Counters 191

5-1	Goals and Objectives	191
5-2	Mechanical and Electronic Counters	191
5-3	Introduction to Allen-Bradley Counters	192
5-3-1	Counter Output Bits	193
5-4	Allen-Bradley Counter and Reset Instructions	195
5-4-1	PLC 5 and SLC 500 Counter and Reset Addressing	195
5-4-2	Logix Counter Instructions	198
5-4-3	Standard Ladder Logic for Counters	200
5-4-4	Allen-Bradley Up Counters	203
5-4-5	Allen-Bradley Down Counters	209
5-4-6	Allen-Bradley Up/Down Counters	209
5-4-7	Allen-Bradley One-Shot Instructions	210
5-5	Cascaded Counters	214
5-6	Empirical Design Process with PLC Counters	214
5-6-1	Adding Counters to the Process	215
5-7	Conversion of Relay Logic Counter Ladders to PLC Logic	219
5-8	Troubleshooting Counter Ladder Logic	220
5-8-1	Suspend Instruction	220
5-8-2	Process Speed versus Scan Time	220
5-9	Location of the Instructions	221
	General Problems	223
	PLC 5 Problems	224
	SLC 500 Problems	224
	Controllogix Problems	225
	Challenge Problems	225

Chapter 6 Arithmetic and Move Instructions 227

6-1	Goals and Objectives	227
6-2	Binary Arithmetic	227
6-3	Signed Binary Numbers	229
6-4	Allen-Bradley Arithmetic Instructions	231
6-4-1	Structure for Arithmetic Instructions	232
6-5	Operation of Allen-Bradley Arithmetic and Move Instructions	232
6-5-1	Addition Instruction	234
6-5-2	Subtraction Instruction	235
6-5-3	Multiplication Instruction	235
6-5-4	Division Instruction	235
6-5-5	Square Root Instruction	237
6-5-6	Move Instructions	239
6-6	Standard Ladder Logic for Allen-Bradley Math and Move Instructions	240
6-7	Empirical Design Process with Math and Move Instructions	248
6-7-1	Adding Math and Move Instructions to the Process	248
6-8	Troubleshooting Math and Move Ladder Logic	253
6-8-1	SLC 500 Test Modes	253
6-9	Location of the Instructions	255
	General Problems	257

PLC 5 Problems	257
SLC 500 Problems	258
Controllogix Problems	258
Challenge Problems	228

Chapter 7 Conversion and Comparison Instructions 261

7-1	Goals and Objectives	261
7-2	Binary Coded Decimal System	261
7-2-1	Allen-Bradley BCD Instructions and Standard Ladder Logic	263
7-3	Hexadecimal System	271
7-4	Comparison Instruction Structure	271
7-5	Allen-Bradly Comparison Instructions	273
7-5-1	Standard Ladder Logic for EQU, NEQ, LES, and GRT Comparison Instructions	273
7-5-2	Standard Ladder Logic for LEQ, GEQ, MEQ, and LIM Comparison Instructions	274
7-5-3	Standard Ladder Logic for Multiple Instructions and Hysteresis	276
7-6	Empirical Design Process with BCD Conversion and Comparison Instructions	280
7-6-1	Adding BCD Conversion Instructions to the Process	280
7-6-2	Adding Comparison Instructions to the Process	280
7-6-3	Process Tank Design	281
7-6-4	Pneumatic Robot Design	287
7-7	Troubleshooting BCD Conversion and Comparison Ladder Logic	289
7-7-1	Troubleshooting with the Module Indicators	290
7-8	Location of the Instructions	292
	General Problems	295
	PLC 5 Problems	296
	SLC 500 Problems	296
	Challenge Problems	297
	Controllogix Problems	297

Chapter 8 Program Control Instructions 299

8-1	Goals and Objectives	299
8-2	Program Control Instructions	299
8-3	Allen-Bradley Program Control Instructions	300
8-3-1	Master Control Reset Instructions	300
8-3-2	Jump and Label Zone Control Instructions	303
8-3-3	Subroutine Instructions	306
8-3-4	PLC 5 and SLC 500 Subroutine Instructions	307
8-3-5	PLC 5 and ControlLogix Options for Subroutine Instructions	315
8-4	Allen-Bradley Immediate Input and Output Instructions	321
8-4-1	PLC 5 Immediate Input and Output Instructions	322
8-4-2	SLC 500 Immediate Input and Output Instructions	322
8-4-3	ControlLogix Immediate Output Instruction	324
8-5	Empirical Design Process with Program Control Instructions	325
8-5-1	Adding Program Control Instructions to the Process	325
8-6	Troubleshooting Program Control Instructions in Ladder Logic	327

8-7	Location of the Instructions -	327
	General Problems	329
	PLC 5 Problems	331
	SLC 500 Problems	331
	ControlLogix Problems	332
	Challenge Problems	332
Chapter 9	Indirect and Indexed Addressing	333
9-1	Goals and Objectives	333
9-2	Allen-Bradley Addressing Modes	333
	9-2-1 Direct Addressing	334
	9-2-2 Indirect Addressing	334
	9-2-3 Indexed Addressing	335
	9-2-4 Indexed Indirect Addressing	335
	9-2-5 PLC 5, SLC 500, and Logix Systems Syntax	335
9-3	Empirical Design Process with Indirect and Indexed Addressing	340
	9-3-1 Adding Indirect and Indexed Addressing to the Process	340
9-4	Troubleshooting Indirect and Indexed Addressing in Ladder Logic	343
	General Problems	346
	PLC 5 Problems	346
	SLC 500 Problems	346
	Controllogix Problems	346
	Challenge Problems	347
PART 2	Advanced PLC Instructions and Applications Goals	349
	Goal	349
	Career Insights	350
	Data Handling Instructions and Shift Registers	351
Chapter 10	Data Handling Instructions and Shift Register	351
10-1	Goals and Objectives	351
10-2	Data Handling	352
	10-2-1 Bit Patterns in Words	352
	10-2-2 Word Patterns in Files	352
10-3	Allen-Bradley Data Transfer And Manipulation Instructions	353
	10-3-1 AND, OR, and XOR Instructions	353
	10-3-2 File-Arithmetic-Logic (FAL) Instruction	355
	10-3-3 Shift Registers	359
	10-3-4 First In, First Out (FIFO) Function	367
	10-3-5 Last In, First Out (LIFO) Function	371
	10-3-6 Copy and Fill Instructions	373
10-4	Empirical Design Process with Bit and Word Operation Instructions	377
10-5	Troubleshooting Data Handling Instructions and Shift Registers in Ladder Logic	380
10-6	Location of the Instructions	382
	Challenge Problems	384
	PLC 5 Problems	383
	SLC 500 Problems	384
	Controllogix Problems	384
	General Problems	383

Chapter 11 PLC Sequencer Functions 385

11-1	Goals and Objectives	385
11-2	Electromechanical Sequencing	385
11-3	Basic PLC Sequencer Function	387
11-4	Allen-Bradley Sequencer Instructions	387
11-4-1	PLC 5 and SLC 500 SQO and SQC Sequencer Instruction Structure	388
11-4-2	PLC 5 and SLC 500 SQO Instruction Operation	389
11-4-3	ControlLogix SQO Sequencer Instruction	390
11-4-4	PLC 5 and ControlLogix Sequencer Input (SQL) Instruction	397
11-4-5	Sequencer Compare (SQC) Instruction	405
11-4-6	Sequencer Load (SQL) Instruction	406
11-5	Cascading Sequencers	408
11-6	Empirical Design Process with Sequencer Instructions	408
11-6-1	Adding Sequential Instructions to the Process	409
11-7	Troubleshooting Sequencer Instructions	410
11-8	Location of the Instructions	410
	General Problems	412
	PLC 5 Problems	413
	SLC 500 Problems	413
	ControlLogix Problems	413
	Challenge Problems	413

Chapter 12 Analog Sensors and Control Systems 415

12-1	Goals and Objectives	415
12-2	Analog Sensors	415
12-2-1	Temperature Sensors	416
12-2-2	Pressure Sensors	419
12-2-3	Flow Sensors	421
12-2-4	Position Sensors	430
12-2-5	Vision Systems	431
12-2-6	Troubleshooting Analog Sensors	438
12-3	Analog Modules and Field Devices Interfacing	441
12-3-1	Analog Input and Output Data	442
12-3-2	PLC 5, SLC 500, and Logix Options	443
12-4	Closed-Loop Control Systems	443
12-4-1	Direct-Acting and Reverse-Acting Controllers	443
12-4-2	Analysis of Closed-Loop Systems	445
12-4-3	Load Change—Process Disturbance	447
12-5	Attributes of an Effective Control System	448
12-5-1	Transient Response	448
12-5-2	Response to Change	448
12-5-3	Controller Response and Damping	450
12-5-4	Transient Response Options	451
12-5-5	Steady-State Response	451
12-5-6	Understanding Steady-State Error	452
12-5-7	Correction for Steady-State Error	456
12-5-8	Controller Gain Side Effects	459
12-5-9	Steady-State Error Correction with Bias	460
12-5-10	Stability	461
12-6	Troubleshooting the Proportional Gain Controller Problems	463

Chapter 13	PLC Standard IEC 61131-3 Function Block Diagrams	467
13-1	Goals and Objectives	467
13-2	PLC Standards	467
13-2-1	IEC 61131-3 Standard Languages	468
13-3	Function Block Diagram (FBD)	469
13-3-1	Signal Flow Types, Execution Order, and Data Latching	471
13-3-2	Feedback Loops	473
13-3-3	Function Block Diagram Program Development Sequence	474
13-3-4	Allen-Bradley RSLogix 5000 FBD Programming	475
13-4	Empirical Design With Function Block Diagrams	477
13-4-1	Standard Function Block Control Solutions	477
13-5	Sites for Allen-Bradley Products and Demo Software	487
	Controllogix Problems	492
Chapter 14	Intermittent and Continuous Process Control	493
14-1	Goals And Objectives	493
14-2	Process Control	493
14-3	Intermittent Controllers	494
14-3-1	On-Off Control	494
14-3-2	Two-Position Control	496
14-3-3	Floating Control	499
14-4	Continuous Controllers	500
14-4-1	Proportional Control	501
14-4-2	Proportional Integral (PI) Control	504
14-4-3	Proportional Derivative (PD) Control	507
14-4-4	Proportional Integral and Derivative (PID) Control	511
14-4-5	Fuzzy Control	511
14-5	DIGITAL CONTROL	515
14-5-1	Digital Sample and Hold	515
14-5-2	Proportional Control Mode	516
14-5-3	Integral Control Mode	517
14-5-4	Derivative Control Mode	519
14-6	Scaling In Process Control	520
14-7	Manual Control Mode and Bumpless Transfer	521
14-8	Location of the Instructions	521
	Controllogix Problems	523
Chapter 15	PLC Standard IEC 61131-3 Structured Text Language	525
15-1	Goals and Objectives	525
15-2	Overview of IEC 61131-3 Text Languages	525
15-3	Allen-Bradley IEC 61131 Structured Text Implementation	526
15-4	Structure Text Programming	526
15-4-1	Assignment Statements	526
15-4-2	Expressions	527
15-4-3	Operators and Functions	527
15-4-4	Relational Operators	528
15-4-5	Logical Operators and Bitwise Operators	528
15-4-6	Constructs	530
15-5	Empirical Design with Structured Text	535
15-5-1	Standard Structured Text Control Solutions	535
15-5-2	Discrete and Process Implementation	537
	Problems	541

Chapter 16	PLC Standard IEC 61131-3 Sequential Function Chart	543
16-1	Goals and Objectives	543
16-2	IEC 61131-3 Standard Languages	543
16-3	Sequential Function Chart (SFC)	544
16-3-1	Standard SFC Sequences	544
16-3-2	SFC Sequences	545
16-3-3	SFC Step Programming	546
16-4	Sites for Allen-Bradley Products and Demo Software	557
	Controllogix Problems	558
Chapter 17	Industrial Networks and Distributive Control	559
17-1	Goals and Objectives	559
17-2	PLC Network Architecture	559
17-3	Ethernet	561
17-3-1	Ethernet Operation	561
17-3-2	Ethernet Industry Protocol	561
17-4	Controlnet	562
17-4-1	ControlNet Operation	562
17-4-2	ControlNet Features	562
17-5	Devicenet	563
17-5-1	DeviceNet Operation	563
17-5-2	DeviceNet Features	564
17-6	Special Network Interfaces	565
17-6-1	SERCOS Interfaces	565
17-6-2	Smart I/O Interfaces	565
17-6-3	Remote I/O Interfaces	565
17-6-4	Serial Communication Interfaces	566
17-6-5	Wireless Interfaces	567
17-6-6	Human-Machine Interfaces	568
17-7	Network Applications	569
17-7-1	Profibus Network	569
17-7-2	Data Highway Networks	570
17-7-3	Modbus Network	570
17-8	Troubleshooting Network Systems	572
17-9	Distributive Control	573
17-10	Distributed I/O	574
17-10-1	In-cabinet I/O	574
17-10-2	On-machine I/O	575
17-11	Selecting and Designing Networks	575
17-12	Web Sites for Industrial Networks	578
	Problems	579