

# **Protective Relaying**

## Principles and Applications

Third Edition



J. Lewis Blackburn  
Thomas J. Domin



CRC Press  
Taylor & Francis Group

# Table of Contents

## Chapter 1

Introduction and General Philosophies .....	1
1.1    Introduction and Definitions .....	1
1.2    Typical Protective Relays and Relay Systems.....	5
1.3    Typical Power Circuit Breakers .....	6
1.4    Nomenclature and Device Numbers .....	12
1.5    Typical Relay and Circuit Breaker Connections .....	16
1.6    Basic Objectives of System Protection .....	17
1.6.1    Reliability.....	19
1.6.2    Selectivity.....	20
1.6.3    Speed .....	20
1.6.4    Simplicity .....	21
1.6.5    Economics .....	22
1.6.6    General Summary .....	22
1.7    Factors Affecting the Protection System .....	22
1.7.1    Economics .....	22
1.7.2    Personality Factor .....	23
1.7.3    Location of Disconnecting and Input Devices.....	23
1.7.4    Available Fault Indicators .....	23
1.8    Classification of Relays.....	24
1.8.1    Protective Relays .....	24
1.8.2    Regulating Relays .....	24
1.8.3    Reclosing, Synchronism Check, and Synchronizing Relays .....	24
1.8.4    Monitoring Relays .....	25
1.8.5    Auxiliary Relays .....	25
1.8.6    Other Relay Classifications .....	25
1.9    Protective Relay Performance .....	25
1.9.1    Correct Operation .....	26
1.9.2    Incorrect Operation .....	26
1.9.3    No Conclusion .....	26
1.10    Principles of Relay Application .....	27
1.11    Information for Application .....	29
1.11.1    System Configuration .....	29
1.11.2    Impedance and Connection of the Power Equipment, System Frequency, System Voltage, and System Phase Sequence .....	29

1.11.3	Existing Protection and Problems .....	30
1.11.4	Operating Procedures and Practices .....	30
1.11.5	Importance of the System Equipment Being Protected.....	30
1.11.6	System Fault Study .....	30
1.11.7	Maximum Loads and System Swing Limits .....	30
1.11.8	Current and Voltage Transformer Locations, Connections, and Ratios .....	31
1.11.9	Future Expansion .....	31
1.12	Structural Changes within the Electric Power Industry .....	31
1.13	Reliability and Protection Standards .....	33
	Bibliography .....	34

## **Chapter 2**

	Fundamental Units: Per Unit and Percent Values .....	37
2.1	Introduction.....	37
2.2	Per Unit and Percent Definitions .....	37
2.3	Advantages of Per Unit and Percent .....	38
2.4	General Relations between Circuit Quantities.....	39
2.5	Base Quantities .....	40
2.6	Per Unit and Percent Impedance Relations .....	41
2.7	Per Unit and Percent Impedances of Transformer Units.....	43
2.7.1	Transformer Bank Example.....	44
2.8	Per Unit and Percent Impedances of Generators .....	45
2.9	Per Unit and Percent Impedances of Overhead Lines.....	46
2.10	Changing Per Unit (Percent) Quantities to Different Bases.....	47
2.10.1	Example: Base Conversion with Equation 2.34 .....	48
2.10.2	Example: Base Conversion Requiring Equation 2.33 .....	48
	Bibliography .....	50

## **Chapter 3**

	Phasors and Polarity .....	51
3.1	Introduction.....	51
3.2	Phasors .....	51
3.2.1	Phasor Representation.....	51
3.2.2	Phasor Diagrams for Sinusoidal Quantities .....	53
3.2.3	Combining Phasors .....	53
3.2.4	Phasor Diagrams Require a Circuit Diagram.....	54
3.2.5	Nomenclature for Current and Voltage.....	54
3.2.5.1	Current and Flux.....	54
3.2.5.2	Voltage .....	56
3.2.6	Phasor Diagram.....	56
3.3	Circuit and Phasor Diagrams for a Balanced Three-Phase Power System .....	57

3.4	Phasor and Phase Rotation .....	59
3.5	Polarity.....	59
3.5.1	Transformer Polarity.....	59
3.5.2	Relay Polarity .....	62
3.6	Application of Polarity for Phase-Fault Directional Sensing .....	64
3.6.1	$90^\circ$ - $60^\circ$ Connection for Phase-Fault Protection.....	66
3.7	Directional Sensing for Ground Faults: Voltage Polarization.....	68
3.8	Directional Sensing for Ground Faults: Current Polarization .....	69
3.9	Other Directional-Sensing Connections.....	71
3.10	Application Aspects of Directional Relaying .....	71
3.11	Summary .....	73

## Chapter 4

	Symmetrical Components: A Review .....	75
4.1	Introduction and Background .....	75
4.2	Positive-Sequence Set.....	76
4.3	Nomenclature Convenience.....	77
4.4	Negative-Sequence Set.....	77
4.5	Zero-Sequence Set .....	78
4.6	General Equations.....	78
4.7	Sequence Independence.....	79
4.8	Positive-Sequence Sources .....	80
4.9	Sequence Networks .....	83
4.9.1	Positive-Sequence Network.....	83
4.9.2	Negative-Sequence Network .....	85
4.9.3	Zero-Sequence Network .....	87
4.9.4	Sequence Network Reduction .....	89
4.10	Shunt Unbalance Sequence Network Interconnections .....	90
4.10.1	Fault Impedance.....	91
4.10.2	Substation and Tower-Footing Impedance.....	91
4.10.3	Sequence Interconnections for Three-Phase Faults .....	92
4.10.4	Sequence Interconnections for Single-Phase-to-Ground Faults .....	92
4.10.5	Sequence Interconnections for Phase-to-Phase Faults .....	93
4.10.6	Sequence Interconnections for Double-Phase-to-Ground Faults .....	95
4.10.7	Other Sequence Interconnections for Shunt System Conditions.....	96
4.11	Example: Fault Calculations on a Typical System Shown in Figure 4.16 .....	96
4.11.1	Three-Phase Fault at Bus G.....	99
4.11.2	Single-Phase-to-Ground Fault at Bus G.....	99
4.12	Example: Fault Calculation for Autotransformers.....	100
4.12.1	Single-Phase-to-Ground Fault at H Calculation .....	102

4.13	Example: Open-Phase Conductor .....	104
4.14	Example: Open Phase Falling to Ground on One Side .....	106
4.15	Series and Simultaneous Unbalances .....	107
4.16	Overview .....	108
4.16.1	Voltage and Current Phasors for Shunt Faults.....	109
4.16.2	System Voltage Profiles during Faults.....	111
4.16.3	Unbalanced Currents in the Unfaulted Phases for Phase-to-Ground Faults in Loop Systems .....	113
4.16.4	Voltage and Current Fault Phasors for All Combinations of the Different Faults.....	114
4.17	Summary .....	117
	Bibliography .....	118
Appendix 4.1	Short-Circuit MVA and Equivalent Impedance.....	119
Appendix 4.2	Impedance and Sequence Connections for Transformer Banks.....	121
Appendix 4.3	Sequence Phase Shifts through Wye–Delta Transformer Banks .....	128

## **Chapter 5**

	Relay Input Sources.....	131
5.1	Introduction.....	131
5.2	Equivalent Circuits of Current and Voltage Transformers.....	132
5.3	Current Transformers for Protection Applications .....	135
5.4	Current Transformer Performance on a Symmetrical AC Component .....	136
5.4.1	Performance by Classic Analysis .....	137
5.4.2	Performance by CT Characteristic Curves.....	138
5.4.3	Performance by ANSI/IEEE Standard Accuracy Classes .....	138
5.4.4	IEC Standard Accuracy Classes .....	142
5.5	Secondary Burdens during Faults .....	142
5.6	CT Selection and Performance Evaluation for Phase Faults .....	144
5.6.1	CT Ratio Selection for Phase-Connected Equipment.....	144
5.6.2	Select the Relay Tap for the Phase-Overcurrent Relays .....	144
5.6.3	Determine the Total Connected Secondary Load (Burden) in Ohms.....	144
5.6.4	Determine the CT Performance Using the ANSI/IEEE Standard .....	145
5.6.4.1	When Using a Class T CT .....	145
5.6.4.2	When Using a Class C CT and Performance by the ANSI/IEEE Standard .....	146
5.6.4.3	When Using a Class C CT and Performance with the CT Excitation Curves.....	147

5.7	Performance Evaluation for Ground Relays .....	147
5.8	Effect of Unenergized CTs on Performance.....	148
5.9	Flux Summation Current Transformer.....	150
5.10	Current Transformer Performance on the DC Component .....	151
5.11	Summary: Current Transformer Performance Evaluation.....	153
5.11.1	Saturation on Symmetrical AC Current Input Resulting from the CT Characteristics and the Secondary Load .....	153
5.11.2	Saturation by the DC Offset of the Primary AC Current .....	153
5.12	Current Transformer Residual Flux and Subsidence Transients .....	155
5.13	Auxiliary Current Transformers in CT Secondary Circuits .....	157
5.14	Voltage Transformers for Protective Applications .....	157
5.15	Optical Sensors .....	159
	Bibliography .....	160

## **Chapter 6**

	Protection Fundamentals and Basic Design Principles .....	163
6.1	Introduction.....	163
6.2	Differential Principle .....	163
6.3	Overcurrent-Distance Protection and the Basic Protection Problem .....	166
6.3.1	Time Solution .....	168
6.3.2	Communication Solution .....	168
6.4	Backup Protection: Remote vs. Local.....	168
6.5	Basic Design Principles .....	169
6.5.1	Time-Overcurrent Relays.....	170
6.5.2	Instantaneous Current-Voltage Relays .....	173
6.5.3	Directional-Sensing Power Relays .....	175
6.5.4	Polar Unit.....	175
6.5.5	Phase Distance Relays .....	176
6.5.5.1	Balanced Beam Type: Impedance Characteristic .....	176
6.5.6	R-X Diagram.....	178
6.5.7	MHO Characteristic .....	178
6.5.8	Single-Phase MHO Units .....	181
6.5.9	Polyphase MHO Units .....	182
6.5.9.1	Three-Phase Fault Units .....	182
6.5.9.2	Phase-to-Phase Fault Units.....	183
6.5.10	Other MHO Units .....	185
6.5.11	Reactance Units .....	186
6.6	Ground Distance Relays .....	186

6.7	Solid-State Microprocessor Relays .....	188
6.8	Summary .....	190
	Bibliography .....	190

## **Chapter 7**

	System-Grounding Principles.....	191
7.1	Introduction.....	191
7.2	Ungrounded Systems .....	191
7.3	Transient Overvoltages.....	195
7.4	Grounded-Detection Methods for Ungrounded Systems.....	197
7.4.1	Three-Voltage Transformers.....	197
7.4.2	Single-Voltage Transformers.....	198
7.5	High-Impedance-Grounding Systems .....	200
7.5.1	Resonant Grounding .....	201
7.5.2	High-Resistance Grounding.....	202
7.5.3	Example: Typical High-Resistance Neutral Grounding .....	204
7.5.4	Example: Typical High-Resistance Grounding with Three Distribution Transformers.....	208
7.6	System Grounding for Mine or Other Hazardous-Type Applications.....	211
7.7	Low-Impedance Grounding.....	213
7.7.1	Example: Typical Low-Resistance Neutral Reactor Grounding .....	214
7.7.2	Example: Typical Low-Resistance Neutral Resistance Grounding .....	216
7.8	Solid (Effective) Grounding .....	216
7.8.1	Example: Solid Grounding .....	217
7.8.2	Ground Detection on Solid-Grounded Systems .....	218
7.9	Ferroresonance in Three-Phase Power Systems .....	219
7.9.1	General Summary for Ferroresonance for Distribution Systems .....	223
7.9.2	Ferroresonance at High Voltages .....	223
7.10	Safety Grounding .....	224
7.11	Grounding Summary and Recommendations .....	226
	Bibliography .....	227

## **Chapter 8**

	Generator Protection/Intertie Protection for Distributed Generation .....	229
8.1	Introduction.....	229
8.1.1	Historical Perspectives.....	229
8.1.2	Bulk Power Generators.....	231
8.1.3	Distributed Generators .....	232
8.1.4	Potential Problems .....	233

8.2	Generator Connections and Overview of Typical Protection.....	234
8.3	Stator Phase-Fault Protection for All Size Generators .....	236
8.3.1	Differential Protection (87) for Small kVA (MVA) Generators .....	237
8.3.2	Multi-CT Differential Protection (87) for All Size Generators .....	237
8.3.3	High-Impedance Voltage Differential Protection for Generators .....	240
8.3.4	Direct-Connected Generator Current Differential Example .....	241
8.3.5	Phase Protection for Small Generators That Do Not Use Differentials .....	242
8.3.6	Unit Generator Current Differential (87) Example for Phase Protection.....	243
8.4	Unit Transformer Phase-Fault Differential Protection (87TG) .....	245
8.5	Phase-Fault Backup Protection (51 V) or (21) .....	246
8.5.1	Voltage-Controlled or Voltage-Restrain Time-Overcurrent (51 V) Backup Protection.....	246
8.5.2	Phase-Distance (21) Backup Protection .....	247
8.6	Negative-Sequence Current Backup Protection.....	247
8.7	Stator Ground-Fault Protection .....	248
8.7.1	Ground-Fault Protection for Single Medium or Small Wye-Connected Generators .....	249
8.7.2	Ground-Fault Protection of Multiple Medium or Small Wye- or Delta-Connected Generators .....	250
8.7.3	Ground-Fault Protection for Ungrounded Generators .....	251
8.7.4	Ground-Fault Protection for Very Small, Solidly Grounded Generators .....	251
8.7.5	Ground-Fault Protection for Unit-Connected Generators Using High-Impedance Neutral Grounding .....	251
8.7.6	Added Protection for 100% Generator Ground Protection with High-Resistance Grounding.....	253
8.7.7	High-Voltage Ground-Fault Coupling Can Produce $V_0$ in High-Impedance-Grounding Systems .....	255
8.7.8	Ground-Fault Protection for Multidirect-Connected Generators Using High-Resistance Grounding .....	255
8.8	Multiple Generator Units Connected Directly to a Transformer: Grounding and Protection.....	256
8.9	Field Ground Protection (64) .....	258
8.10	Generator Off-Line Protection .....	258
8.11	Reduced or Lost Excitation Protection (40) .....	259
8.11.1	Loss of Excitation Protection with Distance (21) Relays.....	259
8.11.2	Loss of Excitation Protection with a Var-Type Relay.....	263

8.12	Generator Protection for System Disturbances and Operational Hazards .....	263
8.12.1	Loss of Prime-Mover: Generator Motoring (32) .....	264
8.12.2	Overexcitation: Volts per Hertz Protection (24) .....	264
8.12.3	Inadvertent Energization: Nonsynchronized Connection (67) .....	265
8.12.4	Breaker Pole Flashover (61).....	265
8.12.5	Thermal Overload (49).....	266
8.12.6	Off-Frequency Operation.....	266
8.12.7	Overvoltage.....	267
8.12.8	Loss of Synchronism: Out-of-Step .....	268
8.12.9	Subsynchronous Oscillations.....	268
8.13	Loss of Voltage Transformer Signal .....	269
8.14	Generator Breaker Failure .....	270
8.15	Excitation System Protection and Limiters .....	271
8.15.1	Field Grounds.....	271
8.15.2	Field Overexcitation .....	272
8.15.3	Field Underexcitation .....	273
8.15.4	Practical Considerations .....	273
8.16	Synchronous Condenser Protection.....	273
8.17	Generator-Tripping Systems.....	274
8.18	Station Auxiliary Service System .....	274
8.19	Distributed Generator Intertie Protection.....	275
8.19.1	Power Quality Protection.....	276
8.19.2	Power System Fault Protection .....	281
8.19.3	System Protection for Faults on Distributed Generator Facilities.....	283
8.19.4	Other Intertie Protection Considerations .....	283
8.19.5	Induction Generators.....	284
8.19.6	Practical Considerations of Distributed Generation.....	284
8.20	Protection Summary .....	285
	Bibliography .....	287

## **Chapter 9**

	Transformer, Reactor, and Shunt Capacitor Protection.....	289
9.1	Transformers .....	289
9.2	Factors Affecting Differential Protection .....	292
9.3	False Differential Current.....	292
9.3.1	Magnetization Inrush .....	292
9.3.2	Overexcitation .....	295
9.3.3	Current Transformer Saturation.....	296
9.4	Transformer Differential Relay Characteristics .....	296
9.5	Application and Connection of Transformer Differential Relays.....	298

9.6	Example: Differential Protection Connections for a Two-Winding Wye–Delta Transformer Bank.....	299
9.6.1	First Step: Phasing .....	300
9.6.2	Second Step: CT Ratio and Tap Selections .....	301
9.7	Load Tap-Changing Transformers .....	303
9.8	Example: Differential Protection Connections for Multiwinding Transformer Bank.....	303
9.9	Application of Auxiliaries for Current Balancing .....	307
9.10	Paralleling CTs in Differential Circuits .....	307
9.11	Special Connections for Transformer Differential Relays.....	309
9.12	Differential Protection for Three-Phase Banks of Single-Phase Transformer Units .....	311
9.13	Ground (Zero-Sequence) Differential Protection for Transformers .....	311
9.14	Equipment for Transfer Trip Systems.....	313
9.14.1	Fault Switch .....	314
9.14.2	Communication Channel .....	314
9.14.3	Limited Fault-Interruption Device .....	315
9.15	Mechanical Fault-Detection for Transformers.....	315
9.15.1	Gas Detection.....	315
9.15.2	Sudden Pressure .....	315
9.16	Grounding Transformer Protection .....	316
9.17	Ground Differential Protection with Directional Relays .....	318
9.18	Protection of Regulating Transformers .....	321
9.19	Transformer Overcurrent Protection .....	324
9.20	Transformer Overload-Through-Fault-Withstand Standards.....	325
9.21	Examples: Transformer Overcurrent Protection .....	330
9.21.1	An Industrial Plant or Similar Facility Served by a 2500 kVA, 12 kV: 480 V Transformer with 5.75% Impedance .....	330
9.21.2	A Distribution or Similar Facility Served by a 7500 kVA, 115: 12 kV Transformer with 7.8% Impedance .....	333
9.21.3	A Substation Served by a 12/16/20 MVA, 115: 12.5 kV Transformer with 10% Impedance .....	336
9.22	Transformer Thermal Protection.....	337
9.23	Oversupply on Transformers.....	338
9.24	Summary: Typical Protection for Transformers .....	338
9.24.1	Individual Transformer Units .....	338
9.24.2	Parallel Transformer Units .....	339

9.24.3	Redundancy Requirements for Bulk Power Transformers .....	343
9.25	Reactors .....	344
9.25.1	Types of Reactors .....	344
9.25.2	General Application of Shunt Reactors.....	345
9.25.3	Reactor Protection.....	345
9.26	Capacitors .....	346
9.27	Power System Reactive Requirements.....	346
9.28	Shunt Capacitor Applications.....	347
9.29	Capacitor Bank Designs .....	348
9.30	Distribution Capacitor Bank Protection .....	349
9.31	Designs and Limitations of Large Capacitor Banks.....	351
9.32	Protection of Large Capacitor Banks.....	354
9.33	Series Capacitor Bank Protection.....	359
9.34	Capacitor Bank Protection Application Issues .....	361
	Bibliography .....	361

## **Chapter 10**

	Bus Protection.....	363
10.1	Introduction: Typical Bus Arrangements.....	363
10.2	Single Breaker-Single Bus.....	364
10.3	Single Buses Connected with Bus Ties .....	365
10.4	Main and Transfer Buses with Single Breakers .....	366
10.5	Single Breaker–Double Bus .....	370
10.6	Double Breaker–Double Bus.....	371
10.7	Ring Bus .....	371
10.8	Breaker-and-Half Bus .....	371
10.9	Transformer–Bus Combination .....	372
10.10	General Summary of Buses .....	372
10.11	Differential Protection for Buses .....	372
10.11.1	Multirestraint Current Differential .....	376
10.11.2	High-Impedance Voltage Differential .....	376
10.11.3	Air-Core Transformer Differential .....	378
10.11.4	Moderate High-Impedance Differential .....	379
10.12	Other Bus Differential Systems .....	379
10.12.1	Time–Overcurrent Differential.....	380
10.12.2	Directional Comparison Differential .....	380
10.12.3	Partial Differential .....	380
10.12.4	Short Time Delay Scheme—Instantaneous Blocking .....	382
10.13	Ground-Fault Bus .....	383
10.14	Protection Summary .....	383
10.15	Bus Protection—Practical Considerations .....	383
	Bibliography .....	384

## **Chapter 11**

Motor Protection.....	385
11.1    Introduction.....	385
11.2    Potential Motor Hazards.....	385
11.3    Motor Characteristics Involved in Protection .....	386
11.4    Induction Motor Equivalent Circuit .....	388
11.5    General Motor Protection.....	389
11.6    Phase-Fault Protection.....	389
11.7    Differential Protection.....	392
11.8    Ground-Fault Protection .....	393
11.9    Thermal and Locked-Rotor Protection .....	395
11.10    Locked-Rotor Protection for Large Motors (21) .....	397
11.11    System Unbalance and Motors.....	398
11.12    Unbalance and Phase Rotation Protection .....	403
11.13    Undervoltage Protection .....	405
11.14    Bus Transfer and Reclosing .....	405
11.15    Repetitive Starts and Jogging Protection .....	406
11.16    Multifunction Microprocessor Motor Protection Units .....	406
11.17    Synchronous Motor Protection.....	407
11.18    Summary: Typical Protection for Motors .....	409
11.19    Practical Considerations of Motor Protection.....	409
Bibliography .....	409

## **Chapter 12**

Line Protection .....	411
12.1    Classifications of Lines and Feeders.....	411
12.2    Line Classifications for Protection.....	414
12.2.1    Distribution Lines .....	415
12.2.2    Transmission and Subtransmission Lines .....	416
12.3    Techniques and Equipment for Line Protection .....	417
12.3.1    Fuses.....	418
12.3.2    Automatic Circuit Reclosers.....	418
12.3.3    Sectionalizers .....	419
12.3.4    Coordinating Time Interval .....	419
12.4    Coordination Fundamentals and General Setting Criteria.....	421
12.4.1    Phase Time–Overcurrent Relay Setting .....	421
12.4.2    Ground Time–Overcurrent Relay Setting .....	422
12.4.3    Phase and Ground Instantaneous Overcurrent Relay Setting.....	422
12.5    Distribution Feeder, Radial Line Protection, and Coordination .....	423
12.6    Example: Coordination for a Typical Distribution Feeder.....	426
12.6.1    Practical Distribution Coordination Considerations .....	430

12.7	Distributed Generators and Other Sources Connected to Distribution Lines.....	431
12.8	Example: Coordination for a Loop System .....	432
12.9	Instantaneous Trip Application for a Loop System.....	438
12.10	Short-Line Applications .....	440
12.11	Network and Spot Network Systems .....	441
12.12	Distance Protection for Phase Faults .....	441
12.13	Distance Relay Applications for Tapped and Multiterminal Lines .....	444
12.14	Voltage Sources for Distance Relays.....	447
12.15	Distance Relay Applications in Systems Protected by Inverse-Time–Overcurrent Relays .....	447
12.16	Ground-Fault Protection for Lines .....	448
12.17	Distance Protection for Ground Faults and Direction Overcurrent Comparisons .....	448
12.18	Fault Resistance and Relaying .....	450
12.19	Directional Sensing for Ground–Overcurrent Relays.....	452
12.20	Polarizing Problems with Autotransformers.....	453
12.21	Voltage Polarization Limitations .....	456
12.22	Dual Polarization for Ground Relaying .....	457
12.23	Ground Directional Sensing with Negative Sequence.....	457
12.24	Mutual Coupling and Ground Relaying.....	458
12.25	Ground Distance Relaying with Mutual Induction.....	465
12.26	Long EHV Series-Compensated Line Protection .....	465
12.27	Backup: Remote, Local, and Breaker Failure.....	467
12.28	Summary: Typical Protection for Lines.....	470
12.29	Practical Considerations of Line Protection .....	471
	Bibliography .....	472

## **Chapter 13**

	Pilot Protection .....	475
13.1	Introduction.....	475
13.2	Pilot System Classifications .....	475
13.3	Protection Channel Classifications.....	476
13.4	Directional Comparison Blocking Pilot Systems .....	477
13.5	Directional Comparison Unblocking Pilot System.....	480
13.5.1	Normal-Operating Condition (No Faults) .....	480
13.5.2	Channel Failure.....	480
13.5.3	External Fault on Bus G or in the System to the Left.....	482
13.5.4	Internal Faults in the Protected Zone .....	482

13.6	Directional Comparison Overreaching Transfer Trip Pilot Systems .....	482
13.6.1	External Fault on Bus G or in the System to the Left...	484
13.6.2	Internal Faults in the Protected Zone .....	484
13.7	Directional Comparison Underreaching Transfer Trip Pilot Systems .....	484
13.7.1	Zone Acceleration.....	485
13.8	Phase Comparison: Pilot Wire Relaying–Wire-Line Channels.....	487
13.9	Phase Comparison: Audio Tone or Fiber-Optic Channels .....	489
13.9.1	External Fault on Bus H or in the System to the Right .....	491
13.9.2	Internal Faults in the Protected Zone .....	491
13.10	Segregated Phase Comparison Pilot Systems .....	492
13.11	Single-Pole–Selective-Pole Pilot Systems.....	492
13.12	Directional Wave Comparison Systems.....	494
13.13	Digital Current Differential .....	494
13.14	Pilot Scheme Enhancements .....	494
13.14.1	Transient Blocking.....	494
13.14.2	Weak Infeed Logic .....	495
13.14.3	“Breaker Open” Keying.....	495
13.15	Transfer Trip Systems .....	496
13.16	Communication Channels for Protection .....	496
13.16.1	Power-Line Carrier: On–Off or Frequency-Shift,.....	497
13.16.2	Pilot Wires: Audio Tone Transmission.....	498
13.16.3	Pilot Wires: 50 or 60 Hz Transmission.....	499
13.16.4	Digital Channels .....	499
13.17	Summary and General Evaluation of Pilot Systems.....	501
13.18	Pilot Relaying—Operating Experiences .....	502
	Bibliography .....	504
	Appendix 13.1 Protection of Wire-Line Pilot Circuits .....	506

## **Chapter 14**

	Stability, Reclosing, Load Shedding, and Trip Circuit Design.....	511
14.1	Introduction.....	511
14.2	Electric Power and Power Transmission .....	511
14.3	Steady-State Operation and Stability .....	512
14.4	Transient Operation and Stability .....	512
14.5	System Swings and Protection .....	516
14.6	Out-of-Step Detection by Distance Relays .....	520
14.7	Automatic Line Reclosing.....	524
14.8	Distribution Feeder Reclosing.....	525
14.9	Subtransmission and Transmission-Line Reclosing .....	526

14.10	Reclosing on Lines with Transformers or Reactors .....	528
14.11	Automatic Synchronizing .....	528
14.12	Frequency Relaying for Load Shedding—Load Saving.....	528
14.13	Underfrequency Load Shedding Design .....	531
	14.13.1 Underfrequency Load Shedding Criteria .....	531
	14.13.2 Underfrequency Load Shedding Scheme Architecture..	532
	14.13.3 Underfrequency Control Scheme Design.....	533
14.14	Performance of Underfrequency Load Shedding Schemes .....	535
14.15	Frequency Relaying for Industrial Systems .....	536
14.16	Voltage Collapse.....	536
14.17	Voltage Collapse Mitigating Techniques.....	537
14.18	Protection and Control Trip Circuits.....	538
14.19	Substation DC Systems .....	539
14.20	Trip Circuit Devices .....	540
	14.20.1 Auxiliary Relays .....	541
	14.20.2 Targeting and Seal-In Devices .....	541
	14.20.3 Switches and Diodes.....	542
	14.20.4 Trip Coils .....	543
14.21	Trip Circuit Design.....	543
14.22	Trip Circuit Monitoring and Alarms .....	544
14.23	Special Protection Schemes.....	546
14.24	Practical Considerations—Special Protection Schemes .....	548
	Bibliography .....	548

## **Chapter 15**

	Microprocessor Applications and Substation Automation .....	549
15.1	Introduction.....	549
15.2	Microprocessor-Based Relay Designs.....	550
15.3	Programable Logic Controllers .....	551
15.4	Application of Microprocessor Relays.....	552
15.5	Programming of Microprocessor Relaying .....	553
	15.5.1 Boolean Algebra .....	553
	15.5.2 Control Equation Elements.....	559
	15.5.3 Binary Elements.....	559
	15.5.4 Analog Quantities .....	559
	15.5.5 Math Operators .....	559
	15.5.6 Settings.....	559
15.6	Attributes of Microprocessor-Based Relays .....	560
15.7	Protection Enhancements .....	561
	15.7.1 Distribution Protection Systems .....	561
	15.7.2 Transmission Protection Systems .....	563
15.8	Multifunctional Capability .....	564

15.9	Wiring Simplification .....	565
15.10	Event Reports .....	566
15.10.1	Types of Event Reports .....	566
15.11	Commissioning and Periodic Testing .....	567
15.12	Setting Specifications and Documentation .....	569
15.13	Fault Location.....	570
15.14	Power System Automation.....	573
15.15	Practical Observations—Microprocessor Relay Application .....	576
	Bibliography .....	577
	<b>Problems .....</b>	<b>579</b>
	<b>Index.....</b>	<b>609</b>