

Second Edition

Distribution System Modeling and Analysis

William H. Kersting



CRC Press
Taylor & Francis Group

Table of Contents

1	Introduction to Distribution Systems	1
1.1	The Distribution System.....	2
1.2	Distribution Substations	2
1.3	Radial Feeders.....	5
1.4	Distribution Feeder Map	6
1.5	Distribution Feeder Electrical Characteristics.....	8
1.6	Summary	9
2	The Nature of Loads.....	11
2.1	Definitions.....	11
2.2	Individual Customer Load.....	13
2.2.1	Demand.....	13
2.2.2	Maximum Demand.....	13
2.2.3	Average Demand.....	14
2.2.4	Load Factor.....	14
2.3	Distribution Transformer Loading.....	15
2.3.1	Diversified Demand.....	16
2.3.2	Maximum Diversified Demand	17
2.3.3	Load Duration Curve	18
2.3.4	Maximum Noncoincident Demand	18
2.3.5	Diversity Factor (DF)	19
2.3.6	Demand Factor	19
2.3.7	Utilization Factor.....	20
2.3.8	Load Diversity	21
2.4	Feeder Load	21
2.4.1	Load Allocation	21
2.4.1.1	Application of DFs	22
2.4.1.2	Load Survey.....	22
2.4.1.3	Transformer Load Management.....	26
2.4.1.4	Metered Feeder Maximum Demand	26
2.4.1.5	What Method to Use?	28
2.4.2	Voltage Drop Calculations Using Allocated Loads	28
2.4.2.1	Application of DFs	28
2.4.2.2	Load Allocation Based upon Transformer Ratings	32
2.5	Summary	34

3 Approximate Method of Analysis.....	41
3.1 Voltage Drop.....	41
3.2 Line Impedance.....	43
3.3 K Factors	45
3.3.1 K_{drop} Factor	45
3.3.2 K_{rise} Factor	48
3.4 Uniformly Distributed Loads	49
3.4.1 Voltage Drop	49
3.4.2 Power Loss	52
3.4.3 The Exact Lumped Load Model.....	54
3.5 Lumping Loads in Geometric Configurations.....	57
3.5.1 The Rectangle.....	57
3.5.2 The Triangle	62
3.5.3 The Trapezoid	68
3.6 Summary	73
References.....	73
4 Series Impedance of Overhead and Underground Lines.....	79
4.1 Series Impedance of Overhead Lines.....	79
4.1.1 Transposed Three-Phase Lines.....	80
4.1.2 Untransposed Distribution Lines	81
4.1.3 Carson's Equations	84
4.1.4 Modified Carson's Equations.....	85
4.1.5 Primitive Impedance Matrix for Overhead Lines	88
4.1.6 Phase Impedance Matrix for Overhead Lines.....	89
4.1.7 Sequence Impedances.....	92
4.2 Series Impedance of Underground Lines.....	102
4.2.1 Concentric Neutral Cable	103
4.2.2 Tape Shielded Cables.....	109
4.2.3 Parallel Underground Distribution Lines	113
4.3 Summary	117
References.....	118
5 Shunt Admittance of Overhead and Underground Lines.....	125
5.1 General Voltage Drop Equation	126
5.2 Overhead Lines	127
5.2.1 The Shunt Admittance of Overhead Parallel Lines.....	131
5.3 Concentric Neutral Cable Underground Lines	134
5.4 Tape-Shielded Cable Underground Lines	138
5.5 Sequence Admittance	140
5.6 The Shunt Admittance of Parallel Underground Lines	141
5.7 Summary	142
References.....	143

6 Distribution System Line Models	145
6.1 Exact Line Segment Model	145
6.2 The Modified Line Model	152
6.2.1 The Three-Wire Delta Line	153
6.2.2 The Computation of Neutral and Ground Currents.....	154
6.3 The Approximate Line Segment Model.....	157
6.4 The General Matrices for Parallel Lines	162
6.4.1 Physically Parallel Lines	166
6.4.2 Electrically Parallel Lines.....	172
6.5 Summary	178
References.....	178
7 Voltage Regulation.....	185
7.1 Standard Voltage Ratings	185
7.2 Two-Winding Transformer Theory	187
7.3 Two-Winding Autotransformer.....	191
7.3.1 Autotransformer Ratings	196
7.3.2 Per-Unit Impedance	198
7.4 Step-Voltage Regulators.....	202
7.4.1 Single-Phase Step-Voltage Regulators	204
7.4.1.1 Type A Step-Voltage Regulator.....	204
7.4.1.2 Type B Step-Voltage Regulator	204
7.4.1.3 Generalized Constants	208
7.4.1.4 The Line Drop Compensator	209
7.4.2 Three-Phase Step-Voltage Regulators	215
7.4.2.1 Wye Connected Regulators.....	215
7.4.2.2 Closed Delta Connected Regulators.....	221
7.4.2.3 Open Delta Connected Regulators	224
7.5 Summary	234
References.....	235
8 Three-Phase Transformer Models	241
8.1 Introduction	241
8.2 Generalized Matrices	242
8.3 The Delta-Grounded Wye Step-Down Connection	243
8.3.1 Voltages	244
8.3.2 Currents	248
8.4 The Ungrounded Wye-Delta Step-Down Connection.....	254
8.5 The Grounded Wye-Grounded Wye Connection.....	264
8.6 The Delta-Delta Connection.....	266
8.7 Open Wye—Open Delta	278

8.8	Thevenin Equivalent Circuit.....	284
8.9	Summary	287
9	Load Models	293
9.1	Wye Connected Loads	293
9.1.1	Constant Real and Reactive Power Loads	294
9.1.2	Constant Impedance Loads	294
9.1.3	Constant Current Loads.....	295
9.1.4	Combination Loads.....	295
9.2	Delta Connected Loads.....	298
9.2.1	Constant Real and Reactive Power Loads	299
9.2.2	Constant Impedance Loads	299
9.2.3	Constant Current Loads.....	300
9.2.4	Combination Loads.....	300
9.2.5	Line Currents Serving a Delta Connected Load.....	300
9.3	Two-Phase and Single-Phase Loads	300
9.4	Shunt Capacitors.....	300
9.3.1	Wye Connected Capacitor Bank.....	301
9.3.2	Delta Connected Capacitor Bank	301
9.5	The Three-Phase Induction Machine.....	302
9.5.1	The Induction Machine Model	303
9.5.2	The Equivalent T Circuit.....	308
9.5.3	Computation of Slip	315
9.5.4	Induction Generator.....	318
9.6	Summary	319
	References.....	319

10	Distribution Feeder Analysis	323
10.1	Power-Flow Analysis	323
10.1.1	The Ladder Iterative Technique.....	324
10.1.1.1	Linear Network.....	324
10.1.1.2	Nonlinear Network	325
10.1.2	General Feeder.....	328
10.1.3	The Unbalanced Three-Phase Distribution Feeder.....	330
10.1.3.1	Series Components	330
10.1.3.2	Shunt Components	332
10.1.4	Applying the Ladder Iterative Technique.....	333
10.1.5	Let Us Put It All Together.....	334
10.1.6	Load Allocation	343
10.1.7	Summary of Power-Flow Studies.....	343
10.2	Short-Circuit Studies	344
10.2.1	General Theory	344
10.2.2	Specific Short Circuits.....	348

10.3 Summary	353
References.....	353
11 Center-Tapped Transformers and Secondaries.....	357
11.1 Center-Tapped Single-Phase Transformer Model	358
11.1.1 Matrix Equations	359
11.1.2 Center-Tapped Transformer Serving Loads through a Triplex Secondary	365
11.2 Ungrounded Wye-Delta Transformer Bank with a Center-Tapped Transformer	370
11.2.1 Backward Sweep Equations	370
11.2.2 Forward Sweep Equations.....	375
11.3 Leading Open Wye–Open Delta Transformer Connection	382
11.4 Lagging Open Wye–Open Delta Connection	385
11.5 Four-Wire Secondary.....	388
11.6 Putting It All Together	392
11.6.1 Computation of Line-to-Neutral Transformer Voltages	393
11.7 Summary	404
Reference	404
Appendix A	407
Appendix B	411
Index	413