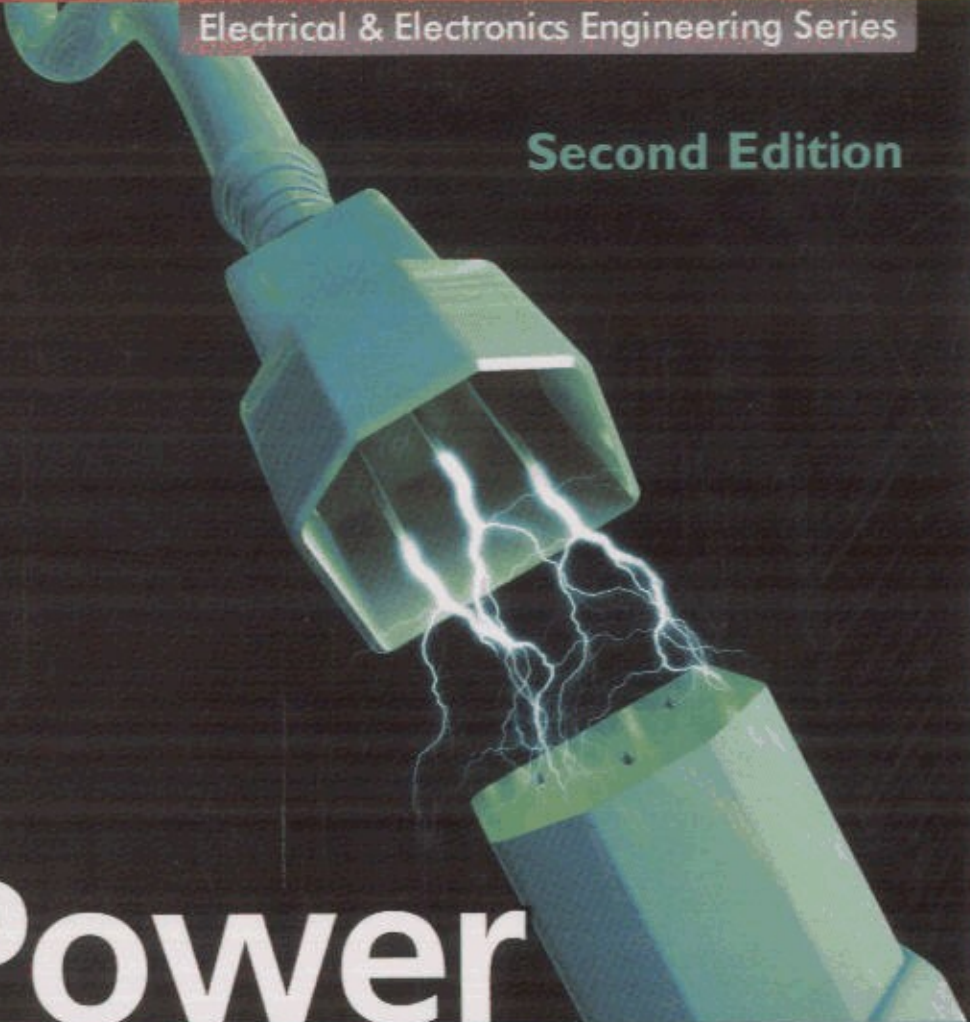


The McGraw-Hill Companies

Electrical & Electronics Engineering Series

Second Edition



Power Electronics



M D Singh
K B Khanchandani

Contents

<i>Preface to the Second Edition</i>	xv
<i>Preface to the First Edition</i>	xix
<i>Acknowledgements</i>	xxi

1. POWER ELECTRONIC SYSTEMS: AN OVERVIEW 1

1.1	Introduction	1
1.2	History of Power Electronics Development	2
1.3	Power Electronic Systems	2
1.4	Power Semiconductor Devices	4
1.5	Power Electronic Converters	11
1.6	Power Electronic Applications	12
1.7	Computer Simulation of Power Electronic Circuits	14
	<i>Review Questions</i>	15
	<i>References</i>	16

2. THYRISTOR: PRINCIPLES AND CHARACTERISTICS 17

2.1	Introduction	17
2.2	Principle of Operation of SCR	18
2.3	Static Anode-Cathode Characteristics of SCR	19
2.4	The Two-transistor Model of SCR (Two Transistor Analogy)	23
2.5	Thyristor Construction	25
2.6	Gate Characteristics of SCR	27
2.7	Turn-on Methods of a Thyristor	33
2.8	Dynamic Turn-on Switching Characteristics	35
2.9	Turn-off Mechanism (Turn-off Characteristic)	37
2.10	Turn-off Methods	38
2.11	Thyristor Ratings	55
2.12	Measurement of Thyristor Parameters	63
2.13	Comparison between Transistors and Thyristors	65
	<i>Review Questions</i>	66
	<i>Problems</i>	67
	<i>References</i>	69

3. GATE TRIGGERING CIRCUITS**70**

- 3.1 Introduction 70
- 3.2 Firing of Thyristors 71
- 3.3 Pulse Transformers 76
- 3.4 Optical Isolators (Optoisolators) 78
- 3.5 Gate Trigger Circuits 81
- 3.6 Unijunction Transistor 87
- 3.7 The Programmable Unijunction Transistor (PUT) 100
- 3.8 Phase Control using Pedestal-And-Ramp Triggering 106
- 3.9 Microprocessor Interfacing to Power Thyristor 108
- Review Questions 110*
- Problems 111*
- References 113*

4. SERIES AND PARALLEL OPERATION OF THYRISTORS**114**

- 4.1 Introduction 114
- 4.2 Series Operations of Thyristors 115
- 4.3 Need for Equalising Network 115
- 4.4 Equalising Network Design 118
- 4.5 Triggering of Series Connected Thyristors 121
- 4.6 Parallel Operation of Thyristors 124
- 4.7 Methods for Ensuring Proper Current Sharing 126
- 4.8 Triggering of Thyristors in Parallel 129
- 4.9 String Efficiency 130
- 4.10 Derating 131
- Review Questions 133*
- Problems 133*
- References 134*

5. POWER SEMICONDUCTOR DEVICES**135**

- 5.1 Introduction 135
- 5.2 Historical Perspective 137
- 5.3 Power Semiconductor Devices 139
- 5.4 Phase Controlled Thyristors 141
- 5.5 Inverter-Grade Thyristors 141
- 5.6 Asymmetrical Thyristor (ASCR) 142
- 5.7 Reverse Conducting Thyristor (RCT) 144
- 5.8 Bidirectional Diode Thyristor (Diac) 145
- 5.9 Bidirectional Triode Thyristor (TRIAC) 146
- 5.10 Silicon Unilateral Switch (SUS) 156
- 5.11 Silicon Bilateral Switch (SBS) 156
- 5.12 Silicon Controlled Switch (SCS) 156
- 5.13 Light-Activated Silicon-Controlled Rectifiers (LASCR) 158

5.14	Power MOSFETs	159
5.15	Insulated Gate Bipolar Transistors (IGBTs)	187
5.16	Gate Turn-off Thyristors (GTOs or Latching Transistors)	212
5.17	Static Induction Devices	222
5.18	MOS Controlled Thyristor (MCT)	224
5.19	Integrated Gate-Commutated Thyristor (IGCT)	231
5.20	MOS Turn-off Thyristor (MTO)	235
5.21	Emitter Turn-Off Thyristor (ETO)	236
5.22	Power Integrated Circuit (PICs)	244
5.23	Comparison of Power Devices	247
5.24	Silicon Carbide Devices	250
	<i>Review Questions</i>	250
	<i>Problems</i>	254
	<i>References</i>	256

6. PHASE CONTROLLED CONVERTERS

258

6.1	Introduction	258
6.2	Control Techniques	259
6.3	Single Phase Half-Wave Controlled Rectifier	263
6.4	Single-Phase Full-Wave Controlled Rectifier (Two-quadrant Converters)	273
6.5	Single-Phase Half Controlled Bridge-Rectifier	291
6.6	Performance Factors of Line-commutated Converters	302
6.7	The Performance Measures of Two-pulse Converters	303
6.8	Three-Phase Controlled Converters	307
6.9	Three-Pulse Converters (M_3 Connection)	308
6.10	Six-Pulse Converters	323
6.11	Three-Phase Fully Controlled Bridge Converter	329
6.12	Three-Phase Half Controlled Bridge Converter (Three-Phase Semiconverters)	346
6.13	The External Performance Measures of Six-Pulse Converters	359
6.14	The Effect of Input Source Impedance	361
6.15	Performance of Converter Circuits with Battery Load (Or Effect of Load Inductance)	378
6.16	Selection of Converter Circuits	380
6.17	Power Factor Improvement	380
6.18	Microprocessor-Based Firing Scheme for Three-Phase Fully-Controlled Bridge Converter	395
	<i>Review Questions</i>	402
	<i>Problems</i>	407
	<i>References</i>	411

7. DUAL CONVERTERS	412
7.1 Introduction	412
7.2 Principle of Dual Converter (Ideal Dual Converter)	415
7.3 Practical Dual Converter	416
7.4 Dual Converter without Circulating Current Operation	417
7.5 Dual Converter with Circulating Current Operation	421
7.6 Dual-Mode Dual Converter	426
7.7 Comparison between Non-Circulating Current Mode and Circulating Current Mode	428
7.8 Microprocessor Based-Firing Scheme for a Dual Converter	429
<i>Review Questions</i>	432
<i>Problems</i>	433
<i>References</i>	433
8. CHOPPERS	434
8.1 Introduction	434
8.2 Basic Chopper Classification	436
8.3 Basic Chopper Operation	437
8.4 Control Strategies	444
8.5 Chopper Configuration	447
8.6 Thyristor Chopper Circuits	481
8.7 Jones Chopper	496
8.8 Morgan Chopper	502
8.9 A.C. Choppers	504
8.10 Source Filter	505
8.11 Multiphase Chopper	508
8.12 Flyback Converters [Switching Regulators]	510
<i>Review Questions</i>	530
<i>Problems</i>	532
<i>References</i>	534
9. INVERTERS	535
9.1 Introduction	535
9.2 Classification of Inverters	537
9.3 Single-Phase Half-Bridge Voltage-Source Inverters	538
9.4 Single-Phase Full-Bridge Inverters	545
9.5 Performance Parameters of Inverters	551
9.6 Voltage Control of Single-Phase Inverters	554
9.7 Pulse-Width Modulated (PWM) Inverters	565
9.8 Three-Phase Inverters	574
9.9 Voltage Control of Three-Phase Inverters	593
9.10 Thyristor-Based Inverters	593

9.11	Series Inverters (Series Resonant Inverters)	594
9.12	Self-Commutated Inverters	606
9.13	Parallel Inverter	609
9.14	The Single-Phase SCR Bridge Inverter	615
9.15	Current Source Inverters	643
9.16	Performance Comparisons of PWM, AVI and CSI	651
9.17	Harmonic Reduction	653
9.18	Harmonic Filters	657
	<i>Review Questions</i>	664
	<i>Problems</i>	667
	<i>References</i>	669

10. CYCLOCONVERTERS

670

10.1	Introduction	670
10.2	The Basic Principle of Operation	671
10.3	Single-phase to Single-phase Cycloconverter	673
10.4	Three-phase Half-wave Cycloconverters	680
10.5	Cycloconverter Circuits for Three-Phase Output	686
10.6	Output Voltage Equation	686
10.7	Control Circuit	689
10.8	Comparison between Cycloconverter and D.C. Link Converter	697
10.9	Load-Commutated Cycloconverter	698
	<i>Review Questions</i>	701
	<i>Problems</i>	702
	<i>References</i>	703

11. A.C. REGULATORS

704

11.1	Introduction	704
11.2	Single-Phase A.C. Regulators	705
11.3	Sequence Control of A.C. Regulators	723
11.4	Three-phase A.C. Regulators	729
11.5	A.C. Regulators to Feed Transformers	740
	<i>Review Questions</i>	742
	<i>Problems</i>	744
	<i>References</i>	745

12. RESONANT CONVERTERS

746

12.1	Introduction	746
12.2	Basic Resonance Circuit Concepts	747
12.3	Classification of Resonant Converters	752
12.4	Load Resonant Converters (Self-Commutating Converters)	753
12.5	Parallel Resonant Inverters	767

- 12.6 Class-E Resonant Inverters 768
- 12.7 Class-E Resonant Rectifier 770
- 12.8 Resonant-Switch Converters 772
- 12.9 ZVS Three-Level PWM-Converter 787
- 12.10 Resonant DC Link Inverters 793

Review Questions 795

Problems 796

References 797

13. PROTECTION AND COOLING OF POWER SWITCHING DEVICES 798

- 13.1 Introduction 798
- 13.2 Overvoltage Conditions 799
- 13.3 Overvoltage Protection 803
- 13.4 Practical Overvoltage Protection in Naturally-Commutated Circuits 815
- 13.5 Overvoltage Protection in Forced-Commutated Circuits 816
- 13.6 Overcurrent Fault Conditions 816
- 13.7 Overcurrent Protection 821
- 13.8 Gate Protection 827
- 13.9 Heat Sinks 833
- 13.10 Thyristor Mounting Techniques 838
- 13.11 SCR Reliability 839

Review Questions 843

Problems 844

References 845

14. CONTROL OF D.C. DRIVES 846

- 14.1 Introduction 846
- 14.2 Basic Machine Equations 847
- 14.3 Schemes for D.C. Motor Speed Control 849
- 14.4 Single-Phase Separately Excited Drives 851
- 14.5 Braking Operation of Rectifier Controlled Separately Excited Motor 870
- 14.6 Single-Phase Series D.C. Motor Drives 871
- 14.7 Three-Phase Separately Excited Drives 879
- 14.8 D.C. Chopper Drives 888
- 14.9 Phase-Locked Loop (PLL) Control of D.C. Drives 893
- 14.10 Microcomputer Control of D.C. Drives 895

Review Questions 898

Problems 899

References 902

15. CONTROL OF A.C. DRIVES**903**

- 15.1 Introduction 903
- 15.2 Basic Principle of Operation 905
- 15.3 Speed Control of Induction Motors 912
- 15.4 Stator Voltage Control 913
- 15.5 Variable Frequency Control 917
- 15.6 Rotor Resistance Control 942
- 15.7 Slip Power Recovery Scheme 949
- 15.8 Synchronous Motor Drives 959
- 15.9 The Drive Selection 978
- Review Questions 981*
- Problems 983*
- References 985*

16. POWER ELECTRONIC APPLICATIONS**987**

- 16.1 Introduction 987
- 16.2 Uninterruptible Power Supply 988
- 16.3 Switched Mode Power Supplies (SMPS) 998
- 16.4 High Voltage D.C. Transmission 1024
- 16.5 Static VAR Compensators 1029
- 16.6 RF Heating 1031
- 16.7 Switch-Mode Welding 1041
- 16.8 Electronic Lamp Ballast 1042
- 16.9 Battery Charger 1042
- 16.10 Emergency Lighting System 1044
- 16.11 Static Circuit Breaker 1045
- 16.12 Time-Delay Circuit 1047
- 16.13 Flasher Circuits 1047
- 16.14 Integral Cycle Triggering (Or Burst Firing) 1049
- Review Questions 1051*
- Problems 1053*
- References 1053*

APPENDIX A : Simulation Tools for Power Electronic Circuits**1054****APPENDIX B : High Voltage Gate Driver ICs (HVICs), Power
Modules and Intelligent Power Modules****1060****INDEX****1065**