

NEW AGE

REVISED SECOND EDITION

Control of Machines



S K Bhattacharya • Brijinder Singh



NEW AGE INTERNATIONAL PUBLISHERS

Contents

Preface

vii

1	INTRODUCTION TO CONTROL OF MACHINES	1
1.1	General Idea of Controls	1
1.2	Disadvantages of Manual Control	2
1.3	Introduction to Magnetic Control	2
1.4	Advantages of Magnetic Control	4
1.5	Semi-automatic and Automatic Control of Modern Machinery	5
1.6	Development of Control Circuit	6
1.6.1	Development of Two-wire and Three-wire Control	6
1.6.2	Remote Control Operation of a Motor	8
1.6.3	Interlocking of Drives	9
2	CONTROL CIRCUIT COMPONENTS	11
2.1	Introduction	11
2.2	Fuses, Switches and Fuse Switch Units	12
2.3	Moulded Case Circuit Breaker and Miniature Circuit Breaker (MCCB & MCB)	14
2.4	Contactors	16
2.4.1	Solenoid Type Contactor	16
2.4.2	Clapper Type Contactor	17
2.4.3	Lock-out Type Contactor	19
2.4.4	Inductive Accelerating Contactors	20
2.5	Contactor Ratings	21
2.6	Relays	22
2.6.1	Voltage Relays	23
2.6.2	D.C. Series Current Relay	24
2.6.3	Frequency Responsive Relay	25
2.6.4	Latching Relays	26
2.7	Overload Relays	28
2.7.1	Bimetallic Thermal Overload Relay	28
2.7.2	Ratchet Type Eutectic Alloy Relay	30
2.7.3	Magnetic Dash Pot Oil Filled Relay	30
2.8	Time Delay Relays (Timers)	32
2.8.1	Thermal Timer	33

2.8.2	Pneumatic Timer	33
2.8.3	Motor Driven Timers	35
2.8.4	Electronic Timer	36
2.9	Phase Failure Relay (Single Phasing Preventer)	37
2.10	Push Button Switches	39
2.11	Selector Switches	40
2.12	Drum Switches	42
2.13	Limit Switches	42
2.13.1	A Simple Limit Switch	43
2.13.2	Rotary Cam Type Limit Switches	45
2.13.3	Heavy Duty Limit Switches	45
2.13.4	Speed Actuating Sensing Switches	46
2.14	Solenoid Valves	46
2.15	Pressure Switches	48
2.16	Pressure Transducer	50
2.17	Temperature Switches (Thermostats)	51
2.18	Float Switch	52
2.19	Control Transformer	54
2.20	Symbols for Various Components	55
2.21	Control Diagrams	56

3 STARTERS FOR 3-PHASE SQUIRREL CAGE MOTOR 63

3.1	Introduction	63
3.1.1	Motor Current at Start and During Acceleration	64
3.1.2	No-load Speed and Final Speed of Motor	65
3.1.3	Starting of Motor	66
3.2	Primary Resistor Type Starters	67
3.2.1	Manual Primary Resistor Type Starter	67
3.2.2	Semi-automatic Stepless Resistance Starter	69
3.2.3	Automatic Primary Resistor Type Starter	70
3.3	Increment Resistance Starter	71
3.4	Line-reactor Reduced Voltage Starter	73
3.5	Auto-Transformer Reduced Voltage Starters	75
3.5.1	Manual Auto-transformer Starter	76
3.5.2	Automatic Auto-transformer Starter (Open Circuit Transition)	77
3.5.3	Auto-transformer Voltage Starter (Closed Circuit Transition)	79
3.6	Part Winding Motor Starter	82
3.6.1	Two Step Starting	83
3.6.2	Three Step Starting	84
3.7	Star-Delta Starter	85
3.7.1	Manual Star-delta Starter	87
3.7.2	Push-button Operated Manual Star-delta Starter	88
3.7.3	Semi-automatic Star-delta Starter	89

3.7.4	Automatic Star-delta Starter (Open Circuit Transition)	91
3.7.5	Automatic Star-delta Starter (Closed Circuit Transition)	92
3.8	Starters for Multi-Speed Motors	95
3.8.1	Starter for Two-speed, Two Winding (Separate Winding) Motor	97
3.8.2	Two Speed One Winding (Consequent Pole) Motor Starter	99
3.9	Reversing the Direction of Rotation of Induction Motors	102
3.10	Plug Stopping of Motor	103
3.11	Dynamic Braking	104
4	STARTERS FOR WOUND ROTOR INDUCTION MOTORS	109
4.1	Introduction	109
4.2	Motor Acceleration	111
4.3	Manual Face Plate Starter	113
4.4	Manual Starter Using Master Controllers	115
4.5	Automatic Control of Acceleration	116
4.5.1	Definite Time Limit Starter	116
4.5.2	Current Limit Acceleration Starter	120
4.5.3	Secondary Frequency Acceleration Starter	121
5	STARTERS FOR DIRECT CURRENT MOTORS	124
5.1	Types of DC Motors and their Applications	124
5.1.1	Shunt Motor	124
5.1.2	Series Motor	124
5.1.3	Compound Motor	125
5.2	Principles of DC Motor Acceleration	125
5.3	Manual Starters for DC Motors	129
5.3.1	Two-point Starter	129
5.3.2	Three-point Starter	129
5.3.3	Four-point Starter	130
5.4	Types of Starters for Automatic Acceleration	131
5.4.1	Direct-on-line Starter	132
5.4.2	Current Limit Acceleration Starters	133
5.4.3	Definite Timer Acceleration Starters	137
5.5	Reversing of DC Motors	140
5.6	Jogging Operation of Motor	143
5.7	Dynamic Breaking of Motor	144
5.8	Plugging Circuit for DC Motor	146
6	CONTROL OF SINGLE PHASE MOTORS	149
6.1	Types of Single Phase Motors	149
6.2	Universal Series Motors	150
6.2.1	Reversing Direction of Rotation of Universal Motor	150
6.2.2	Speed Control of Universal Motor	152

6.3	Shaded Pole Motor	153
6.4	Split Phase Motors	155
6.4.1	Standard Split Phase Motors	155
6.4.2	Capacitor Type Split Phase Motors	157
6.4.3	Starters for Capacitor Type Split Phase Motors	157
6.4.4	Starter for Two Value Capacitor Type Split-phase Motors	158
6.4.5	Starter for a Two Value Capacitor Motor Using a Current Relay and an Auto Transformer	159
6.4.6	Dynamic Breaking of Split Phase Motors	160
6.4.7	Plug Reversing of Capacitor Start Motors	160
6.4.8	Speed Control of Split Phase Motors	161
6.4.9	Speed Control of Permanent Split Capacitor Motors	162
7	CONTROL OF SYNCHRONOUS MOTORS	165
7.1	Construction and Operation of a Synchronous Motor	165
7.2	Manual Push Button Synchronising Starter	166
7.3	Timed Semi-automatic Synchronising	167
7.4	Automatic Starter Using Polarised Field Frequency Relay	167
8	PROTECTION OF MOTORS	171
8.1	Protection of AC Motors	171
8.2	Co-Ordination of Fuse, Overload Relay and Contactor/Circuit Breaker Operating Characteristics	171
8.3	Overload, Short Circuit, and Over-temperature Protection	172
8.3.1	Overload and Short Circuit Protection	172
8.3.2	Over Temperature Protection	175
8.3.3	Under Voltage Protection	176
8.3.4	Phase Failure and Phase Reversal Protection	177
8.4	Protection of DC Motors	178
8.4.1	Field Failure Protection Circuit for DC Shunt Motors	178
8.4.2	Field Acceleration Protection Circuit	179
8.4.3	Field Deceleration Protection Circuit	181
9	INDUSTRIAL CONTROL CIRCUITS	184
9.1	Introduction	184
9.2	Planer Machine	184
9.3	Skip Hoist Control	187
9.4	Automatic Control for a Water Pump	189
9.5	Lifting Magnet	191
9.6	Control of Electrical Oven	193
9.7	Overhead Crane	196
9.8	Battery Trolley	202
9.9	Battery Operated Truck	205

9.10	Air Compressor	208
9.11	Walking Beam	212
9.12	Conveyor System	217
9.13	Elevator	222
10	TROUBLESHOOTING IN CONTROL CIRCUITS	231
10.1	Introduction	231
10.2	Trouble Spots	232
10.2.1	Fuses	232
10.2.2	Loose Connections	232
10.2.3	Faulty Contacts	233
10.2.4	Incorrect Wire Marking	234
10.2.5	Combination Problems	234
10.2.6	Low Voltage	235
10.2.7	Grounding	235
10.2.8	Momentary Faults	236
10.2.9	Poor Maintenance	237
10.3	General Procedure for Troubleshooting	237
11	STATIC CONTROL OF MACHINES	242
11.1	Introduction	242
11.2	Advantages of Static Control Over Magnetic Relay Control	243
11.3	Disadvantages of Static Control Over Magnetic Relay Control	244
11.4	Explanation of Different Gates	245
11.4.1	AND Gate	245
11.4.2	OR Gate	246
11.4.3	NOT Gate or Inverter	248
11.4.4	NOR Gate	248
11.4.5	NAND Gate	249
11.4.6	Exclusive OR Gate	249
11.5	Solid State Timer	250
11.6	Memory Elements (Off-return Type)	251
11.6.1	Clocked RS Flip-Flop	253
11.6.2	JK Flip-Flop	253
11.7	Retentive Memory Element	254
11.8	Development of Logic Circuits	255
11.9	Input Devices for Solid State Logic	259
11.9.1	Capacitive Switch Filters	259
11.9.2	Bounce Eliminators	260
11.9.3	Signal Converters	261
11.10	Output Devices for Solid State Logic	263
11.11	Solenoid Valve Operated Cylinder Piston Assembly	264
11.12	Control of Three Stage Air Conditioning System	265

11.13	Speed Control of Wound Rotor Induction Motor	267
11.14	Control of Planer Machine	269
11.15	Control of Three Conveyors	272
11.16	Shift Register	274
11.17	Conveyor System Using a Shift Register	275
11.18	Counter	277
11.19	Decoder	278
11.20	Loading of Castings into Annealing Furnace Using Decade Counter and Decoder	279
11.21	Mono Shot	281
11.22	Clock	282
11.23	Automatic Filling of Silos Using a Clock and a Mono Shot	283
11.24	Down Counter	285
11.25	Encoder	286
11.26	Product Dispersion Conveyor System Using a Down-counter, an Encoder, a Mono Shot and a Timer	287
12	PROGRAMMABLE LOGIC CONTROLLER	291
12.1	Introduction	291
12.2	Input/Output Section	294
12.2.1	Fixed I/O	294
12.2.2	Modular I/O	295
12.3	Discrete Input Modules	296
12.3.1	AC Discrete Input Module	297
12.3.2	DC Discrete Input Module	298
12.4	Discrete Output Modules	299
12.4.1	AC Output Module	299
12.4.2	DC Output Modules	301
12.4.3	Rating of Output Modules	301
12.5	Analog I/O Modules	302
12.6	Safety Circuit	303
12.7	Processor Unit	303
12.7.1	Internal Self Diagnostic System	307
12.7.2	Memory Types	307
12.7.3	Input Image Table	308
12.7.4	Output Image Table	308
12.7.5	User Program Memory	309
12.7.6	Variable Data Memory	309
12.8	Programming Device	310
12.8.1	Dedicated Desktop Programmers	310
12.8.2	Hand-held Programmers	311
12.8.3	Computer Programmers	311
12.8.4	Advantages of Using Personal Computers for Programming	312

12.8.5	Disadvantages of Using Personal Computer for Programming a PLC	313
12.9	Fundamental PLC Programming	313
12.9.1	Introduction	313
12.9.2	Physical Components Versus Program Components	315
12.9.3	Examine ON Instruction	316
12.9.4	Examine OFF Instruction	317
12.9.5	Internal Relay Instruction	317
12.9.6	Latching Instruction	317
12.9.7	Output Instruction	318
12.9.8	Programming Stop Push-buttons	318
12.9.9	Logical Holding Instructions Versus Discrete Holding Contacts	320
12.9.10	Overload Contacts	320
12.9.11	Master Control Relay Instruction	321
12.9.12	Branch Open and Branch Close Instructions	323
12.9.13	Timer Instruction	325
12.9.14	Counter Instruction	327
12.9.15	Sequencer Instruction	329
12.9.16	Basic Operation of Time Driven Output Sequencer Instruction	331
12.10	A Simple Programming Example	332
12.10.1	Sand Mixing Machine	332
12.10.2	Relay Ladder Logic Diagram	332
12.10.3	Ladder Logic Program on PLC for Sand Mixing Machine	334
12.10.4	Explanation for the Ladder Program	334
	<i>References and Suggestions for Further Study</i>	338